

APRIL 5, 1979

A CAHNERS PUBLICATION

EDN

EXCLUSIVELY FOR DESIGNERS AND DESIGN MANAGERS IN ELECTRONICS


A.
Find switcher efficiency
without a wattmeter

Top-octave generators
make your products sing

Why all the fuss
about PASCAL?

Rec'd June 4th

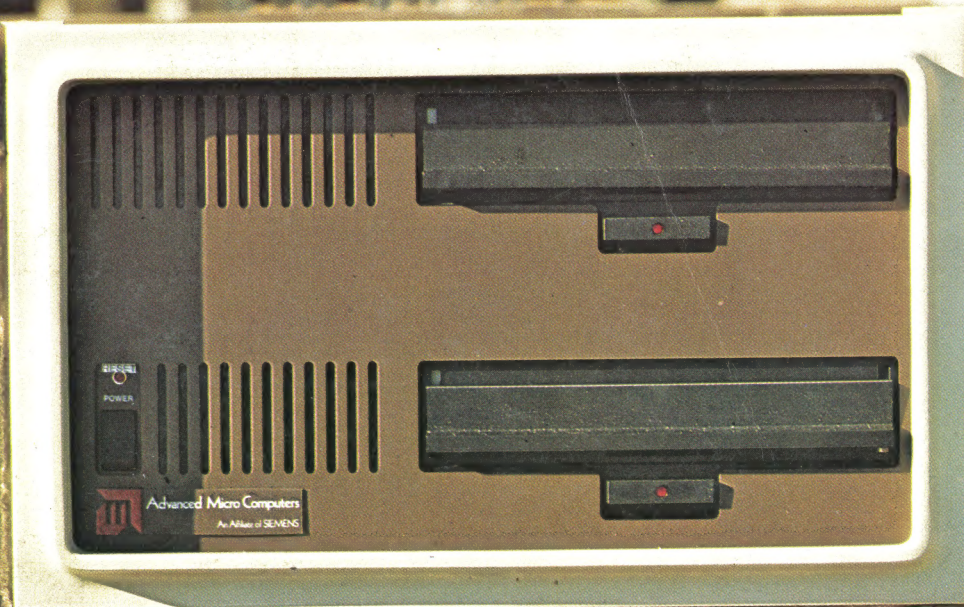μ C development systems
buttress the product-design process



Around the corner or off the beaten path, we'll get answers for you fast.

You don't have to live on Main Street to get express service from Hollingsworth. We're a service-oriented company. And that means fast attention to your problems, whatever they are and wherever you are.


When you give us a problem, it starts a lot of

Hollingsworth people galloping. Start with your Hollingsworth man for immediate answers. And for more help, use the assistance of Hollingsworth's applications engineers. They're waiting for your call.

Fast service is one reason Hollingsworth is growing at a faster rate than any other terminal manufacturer. But it's not the only reason. High-quality, attractive pricing, delivery when you need it, and a complete line of terminals and matched tools are others.

No horsing around!

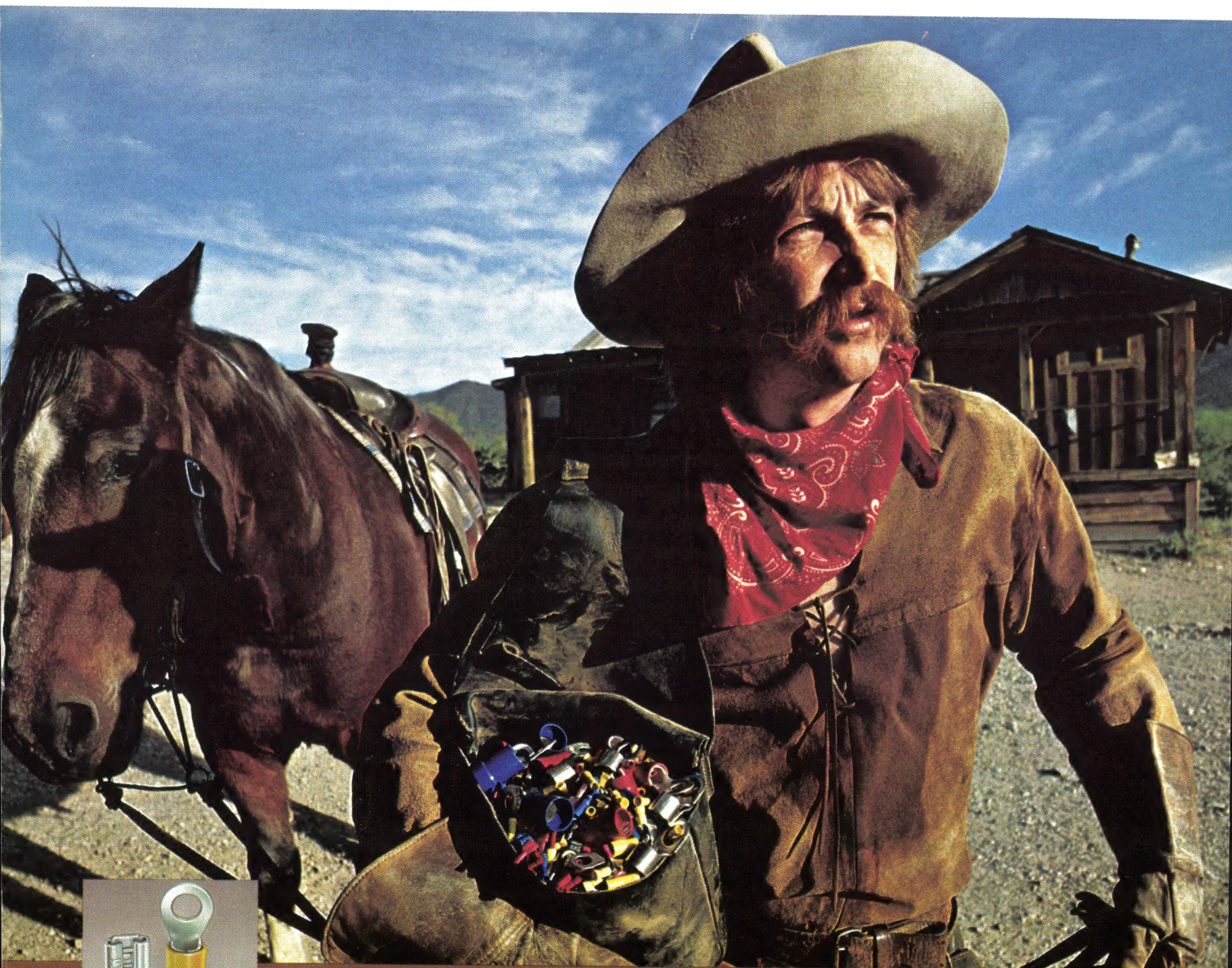Test us by calling your Hollingsworth man with your problem now. He's listed in the Yellow Pages. Or write for our new terminal and connector catalog. Hollingsworth Solderless Terminal Company, 85 Benjamin Franklin Highway, Pottstown, PA 19464.



HOLLINGSWORTH®

Atlanta • Boston • Chicago • Cleveland • Dallas • Ft. Lauderdale • Los Angeles • Philadelphia • San Francisco • Seattle • London • Sao Paulo • Toronto

For more information, Circle No 1

Never available until now. . .

Ultra-low distortion MIXERS

High-level (+17 dBm LO)

**Guaranteed -55 dB
two-tone third-order
intermodulation spec**
(below IF output)

Test conditions

RF 1 = 200 MHz, RF 2 = 202 MHz at 0 dBm
LO = 180 MHz at +17 dBm

Special Features:

- Wide bandwidth
50 kHz — 1000 MHz
- 1 dB compression point +15 dBm
- Low insertion loss 6 dB
- High isolation,
greater than 45 dB
- 3 connector versions,
2 pin versions

NOW. . . improve your systems
intermod spec by as much as 10 dB
guaranteed. . . specify Mini-Circuits'
state-of-the-art ultra-low distortion
Double-Balanced Mixers. Prices start at
an unbelievable low \$19.95. . .
with off-the-shelf delivery.

For complete specifications,
performance curves and application
information, refer to 78-79 MicroWaves'
Product Data Directory (pgs 161-352)
or EEM (pgs 2890-3058).



\$19.95

MODEL TAK-1H (5-24)

Model No.	Freq. (MHz)	Conv. loss (dB max.)	Signal level (dBm min.)	Con- nections	Size (w x l x ht.) (in.)	Price (Qty.)
TFM-1H	2 — 500	8.5	+14	4 pins	0.21 x 0.5 x 0.25	\$23.95 (5-24)
TFM-2H	5 — 1000	10	+14	4 pins	0.21 x 0.5 x 0.25	\$31.95 (5-24)
TFM-3H	0.1 — 250	8.5	+13	4 pins	0.21 x 0.5 x 0.25	\$23.95 (5-24)
TAK-1H	2 — 500	8.5	+14	8 pins	0.4 x 0.8 x 0.25	\$19.95 (5-24)
TAK-1WH	5 — 750	9.0	+14	8 pins	0.4 x 0.8 x 0.25	\$23.95 (5-24)
TAK-3H	0.05 — 300	8.5	+13	8 pins	0.4 x 0.8 x 0.25	\$21.95 (5-24)
ZAD-1SH	2 — 500	8.5	+14	BNC, TNC	1.15 x 2.25 x 1.40	\$40.95 (4-24)
ZAD-1WSH	5 — 750	9.0	+14	BNC, TNC	1.15 x 2.25 x 1.40	\$44.95 (4-24)
ZAD-3SH	0.05 — 300	8.5	+13	BNC, TNC	1.15 x 2.25 x 1.40	\$42.95 (4-24)
ZLW-1SH	2 — 500	8.5	+14	SMA	0.88 x 1.50 x 1.15	\$50.95 (4-24)
ZLW-1WSH	5 — 750	9.0	+14	SMA	0.88 x 1.50 x 1.15	\$54.95 (4-24)
ZLW-3SH	0.05 — 300	8.5	+13	SMA	0.88 x 1.50 x 1.15	\$52.95 (4-24)
ZFM-1H	2 — 500	8.5	+14	BNC, TNC SMA, N	1.25 x 1.25 x 0.75	\$53.95 (1-24)
ZFM-2H	5 — 1000	10	+14	BNC, TNC SMA, N	1.25 x 1.25 x 0.75	\$61.95 (1-24)
ZFM-3H	0.05 — 300	8.5	+13	BNC, TNC SMA, N	1.25 x 1.25 x 0.75	\$54.95 (1-24)

Impedance: 50 ohms, Isolation: 30 dB min.,
BNC standard, TNC on request. Type N and SMA \$5.00 additional

2625 East 14th Street Brooklyn, New York 11235 (212) 769-0200
Domestic and International Telex 125460 International Telex 620156

International Representatives: □ AFRICA: Alitra (PTY) Ltd., P.O. Box 9813, Johannesburg 2000, South Africa. □ AUSTRALIA: General Electronic Service, 99 Alexander St., New South Wales, Australia 2065. □ EASTERN CANADA: B.D. Hummel, 2224 Maynard Ave., Utica, NY 13502. □ ENGLAND: Dale Electronics Ltd., Dale House, Wharf Road, Frimley Green, Camberley Surrey, United Kingdom. □ FRANCE: S.C.I.E.-D.I.M.E.S., 31 Rue George-Sand, 91120 Palaiseau, France. □ GERMANY, AUSTRIA, SWITZERLAND, DENMARK: Industrial Electronics GmbH, 6000 Frankfurt Main, Klüberstrasse 14, West Germany. □ INDIA: Gaekwar Enterprises, Kamal Mahal, 17 M.L. Dahanukar Marg, Bombay 400 026, India. □ ISRAEL: Vectronics Ltd., 69 Gordon St., Tel-Aviv, Israel. □ JAPAN: Densho Kaisha, Ltd., Eguchi Building 8-1 1-Chome, Hamamatsucho Minato-Ku, Tokyo, Japan. □ NETHERLANDS, LUXEMBOURG, BELGIUM: B.V. Technische Handelsonderneming, COIMEX, P.O. Box 19, 8050 AA Hattem, Holland. □ NORWAY: Datamatikk As, Postboks 111, BRYN, Oslo 6, Osøngsveien 62, Norway. □ SINGAPORE & MALAYSIA: Electronics Trading Co. (PTE) Ltd, Suites C13, C22 & C23 (1st Floor), President Hotel Shopping Complex, 181 Kitchen Road, Singapore-8, Republic of Singapore. □ SWEDEN: Integrerad Elektronik AB, Box 43 S-182 51, Djursholm, Sweden.

U.S. Distributors: □ NORTHERN CALIFORNIA: Pen Stock, 105 Fremont Ave., Los Altos, CA 94022, Tel: (415) 948-6533. □ SOUTHERN CALIFORNIA, ARIZONA: Crown Electronics, 11440 Collins St., N. Hollywood, CA 91601, Tel: (213) 877-3550. □ METROPOLITAN NEW YORK, NORTHERN NEW JERSEY, WESTCHESTER COUNTY: Microwave Distributors, 61 Mall Drive, Commack, NY 11725, Tel: (516) 543-4771.

World's largest manufacturer of Double-Balanced Mixers



Mini-Circuits


A Division of Scientific Components Corp

For more information, Circle No 2

Guaranteed Compatible!


S-100 Bus OEM Boards

From SD Systems at reasonable prices

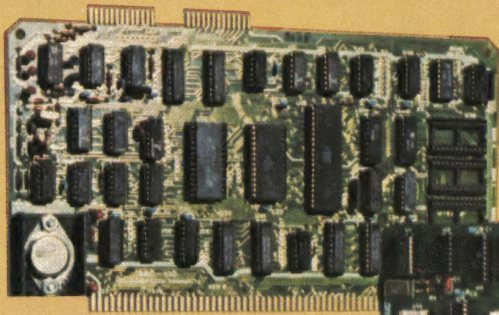


Single Board Computer (SBC-100)

Video Display Board (VDB-8024)

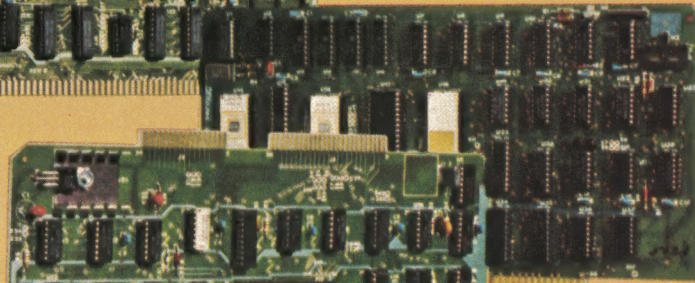

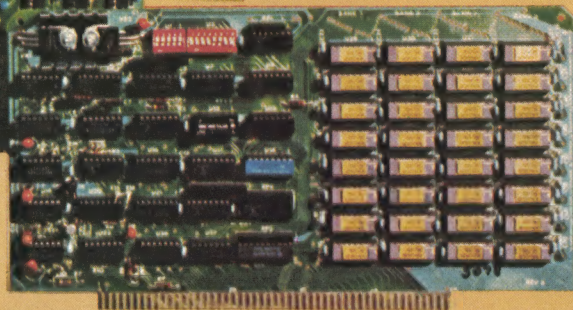Flexible Disk Drive Controller (Versafloppy)



64K Random Access Memory (ExpandoRAM)

ASSEMBLED TESTED AND FULLY BURNED IN


The search is over for the convenience of S-100 Bus Computer boards that are really compatible and dependable. State-of-the-Art engineering, outstanding flexibility, rapid delivery, and low costs make the SD Systems computer boards the best OEM buy. The **SBC-100 Single Board Computer** is based on the Z80 microprocessor. Up to 8K of 2716 PROM, Serial RS-232 Port, Parallel Input/Output Ports, Software programmable baud rate generator, Four channel counter/timer, and 1K of RAM, all on-board. **VDB-8024 Video Display Board** features an on-board Z80 microprocessor for maximum flexibility in video control. 80 characters by 24 lines, displayed with high resolution on a 7x10 dot matrix. On-board Keyboard power and interface, 2K memory and a glitch-free display by use of I/O mapped interface make this board the most superior board on the market.




The **ExpandoRAM** is available in 16, 32, 48, or 64K versions using 4116 RAMs. The population can be increased in the field at a future point if requirements change. Featuring Switch selectable boundaries, Bank Selectable Write Protect and using less than 5 watts, the ExpandoRAM is more reliable memory for the money than any other OEM board. **Versafloppy, Flexible Disk Drive Controller** with IBM 3740 soft sector-ed format compatibility controls up to four single or double sided disk drives either mini or standard size. **Full Line Software** includes Editor, Z80 Assembler, Linker, C-Basic, Complete Business Packages, System Diagnostic and Control Software and Disk Operating System. **PROM Programming Software and Hardware** also available. Circle the reader service number for full Technical Data. . . or call toll free to our Customer Service Department: 800-527-3460.

EDN

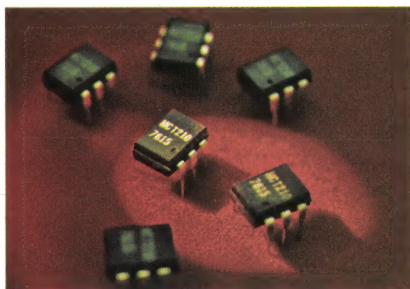APRIL 5, 1979 • VOLUME 24, NUMBER 7 • EXCLUSIVELY FOR DESIGNERS AND DESIGN MANAGERS IN ELECTRONICS



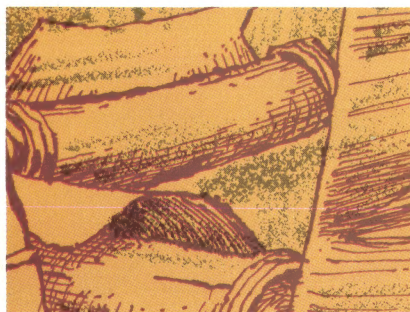Optoisolators find use in a variety of new applications (pg 48).



The PASCAL language offers designers a host of opportunities—and some dilemmas (pg 78).



On the cover: A μ C development system is the cornerstone of effective system design (pg 62). (Photo courtesy Advanced Micro Computers)

DESIGN FEATURES

SPECIAL REPORT

μ C development systems62

No two development systems are alike, but no two development tasks are, either. The ideal system remains flexible.

Top-octave generators make beautiful music71

Add musical sounds with top-octave generators— μ P-controllable chips providing in-tune, multiple-frequency outputs.

SPECIAL REPORT: PASCAL78

PASCAL has now become the darling of commercial computer makers and users. Why this enthusiasm? What can it do for you?

Measure switcher efficiency without a wattmeter87

Although switching power supplies draw pulsed ac currents, you don't need a wattmeter to measure their efficiency.

Synchronous static CMOS RAMs increase μ C performance ..93

It's a challenge to design a RAM array with synchronous memories, but many μ Cs can benefit from their use.

Learn the peculiarities of low-end- μ C architectures99

The odd architectures and instruction sets of low-end, calculator-based 1-chip μ Cs can be very cost effective.

DESIGN IDEAS111

Conversion circuit handles binary or BCD . . . Comparator detects frequency . . . Op amp provides linear current source . . . Single chip converts BCD to binary . . . Flip flop provides long delay.

TECHNOLOGY NEWS

New production means will spur solar-cell use37

Switching-power-supply improvements will dominate Powercon 6 . . . 64-pin-chip packaging developers offer an alternative to JEDEC standard . . . Versatile optoisolators, couplers move into new applications.

NEW PRODUCTS

Feature Products119

Electronic load handles 300A, features no-guess digital readout.

Computer-System Subassemblies 121 Computers & Peripherals 124

Instrumentation & Power Sources 129 Components & Packaging 132

ICs & Semiconductors144

DEPARTMENTS

Signals and Noise16

Books18

Leadtime Index25

The Editor's Column31

Editorial Staff32

μ Computerist Corner 51

Literature149

Business Staff155

Career Opportunities156


Advertisers Index161

News and Notes162



EDN (USPS 074-090) is published semimonthly (except monthly in July and December) by Cahners Publishing Company, Division of Reed Holdings, Inc. 221 Columbus Avenue, Boston, MA 02116. Norman L. Cahners, Chairman; Saul Goldweitz, President; William M. Platt, Vice President/Division Manager. Controlled Circulation paid at Pontiac, IL 61764 and Oakland, CA 94623. Postmaster: Send Form 3579 to EDN, 270 St Paul St, Denver, CO 80206. Advertising and editorial offices: 221 Columbus Ave, Boston, MA 02116. Phone (617) 536-7780. Subscription offices: 270 St Paul St, Denver, CO 80206. Phone (303) 388-4511. EDN is circulated without charge to those qualified. Subscription to others in the continental US: \$2/copy (special issues may vary), \$25/year; international subscriptions: \$40/year (\$30/year in Canada), with air mail delivery available at additional cost. Send requests for qualification forms and/or change of address to subscription office.

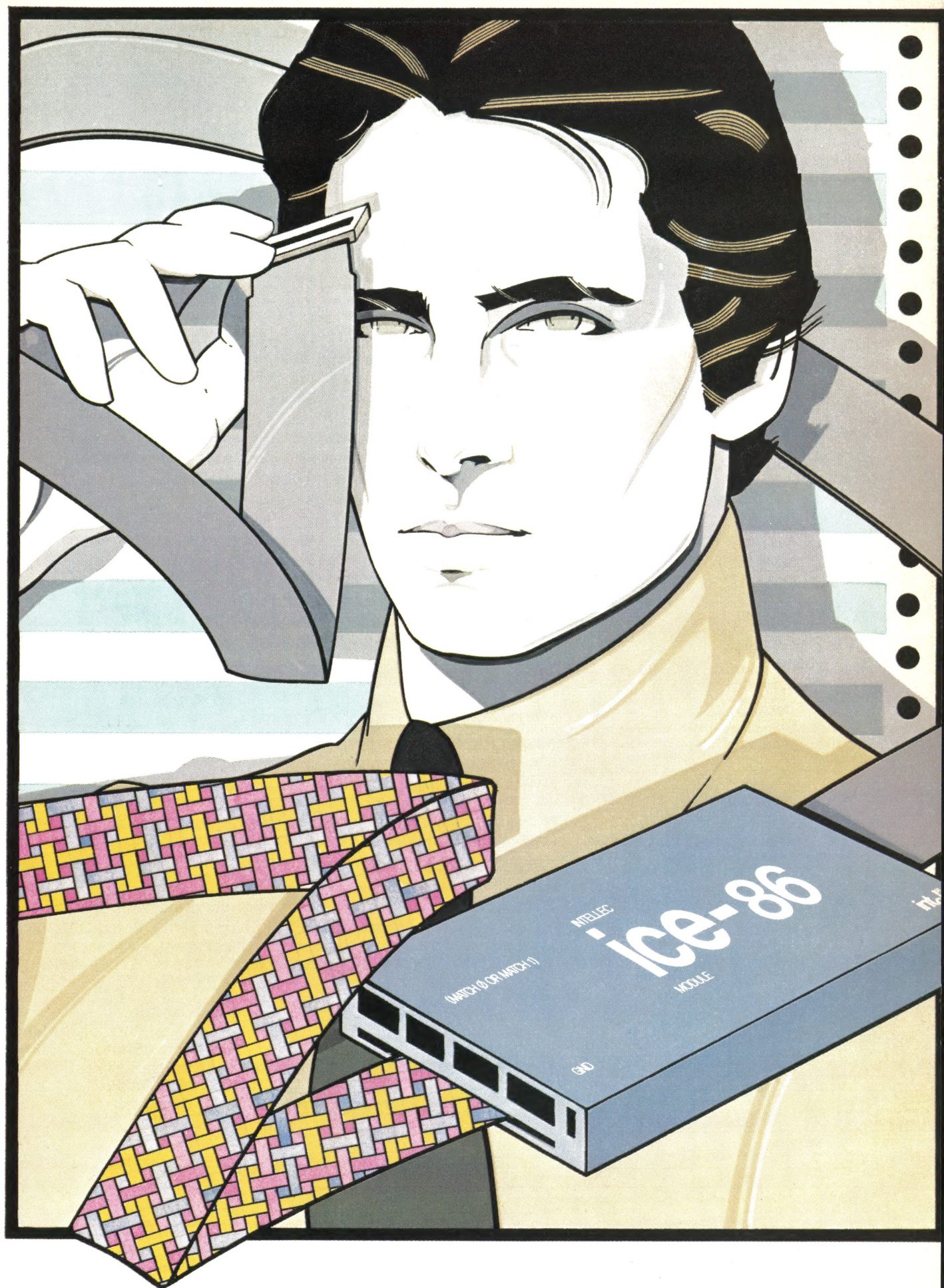©1979 by Cahners Publishing Company, Division of Reed Holdings, Inc. All rights reserved.



Sixth Sense for 8086 Users.

Intel delivers ICE-86™ emulator, the designer's direct diagnostic connection to 8086 system development.

Intel's new 8086 sets the standard for 16-bit microcomputers. It delivers the Architecture of the Future today, high-level languages for programming and the Intellec® development system for unsurpassed support.

Now that support moves even further out in front. Introducing the ICE-86 module. Experienced microcomputer designers have learned that having a development system with in-circuit emulation — ICE — is like having a vital sixth sense. Only ICE emulation provides designers with the real insight in actual system operation absolutely necessary for cost effective, efficient product development. Now Intel delivers that sixth sense for 8086 users.

ICE-86™ puts the future in your hands

The 8086's early availability provides the opportunity to get your new products to market a year or more ahead of your competitors who wait for follow-on 16-bit microprocessors. Only Intel delivers the future today.

The Intellec development system with in-circuit emulation enables you to seize that opportunity. You can actually begin software development and debugging in an 8086 environment before any prototype hardware exists. Or you can use the ICE-86 module to begin simultaneous hardware and software development and integration while your system is little more than an 8086 cpu and system clock.

The ICE-86 cable plugs into your system cpu socket to provide emulation of system operation, up to the full megabyte of memory the 8086 can address.

Communicate in English, or symbolic references.

The ICE-86 emulator is actually a complex breakpoint and logic trace system supporting the most advanced symbolic debugging techniques. English-like statements or symbolic references entered at the Intellec keyboard eliminate the need to search memory maps, keep track of address changes or get bogged down in the details of system operation.

And the ICE-86 emulator's powerful logic analysis capability helps find the cause and correct the problem when bugs do appear.

PL/M-86 for the Architecture of the Future.

The most powerful microcomputer ever deserves the most powerful microcomputer programming language. That's PL/M-86, an extension of the world's most widely used development language.

PL/M-86 is an ideal example of the block-structured languages the 8086's futuristic architecture can support. It gives you 32-bit floating point arithmetic and 16-bit signed integer arithmetic. And it takes full advantage of the program-compacting features of the 8086, such as hardware multiply and divide and byte-string operations.

PL/M-86 is best for fast composition of large and complex programs. For those who prefer the efficiency of assembly language, there's ASM-86. And CONV-86 converts 8080/8085 code to the 8086.

The future is even brighter. Planned expansion of the Intellec system promises programming in Pascal and FORTRAN and the added flexibility of a macro assembler. It's true today and will be true long into the future—the 8086 is the best supported 16-bit microcomputer you can buy.

Modular programming is here.

The Intellec system gives you the flexibility of modular programming. You can develop routines in small, manageable modules, choosing the best language for each. Then using the Intellec system's powerful relocation and linkage capabilities, you can merge modules using symbolic references.

We optimized Intellec hardware for 8086 development, providing a dual diskette, expandable to four drives and 2.5 megabytes of memory. And we'll be expanding the Intellec system with a 7-megabyte hard disk, enough memory to extend the 8086's capabilities into the realm of large mainframe computers.

A manual for your success.

We've compiled an in-depth Success Manual for 8086 Users, detailing the Intellec Microcomputer Development System, ICE-86 and the full software package for 8086 program development. For your copy, contact your local Intel sales office. Or write: Intel Corporation, Literature Dept., 3065 Bowers Avenue, Santa Clara, CA 95051.




intel® delivers.

Circle no 4 for information

See us at Computer Caravan, Houston, May 8-10

Mostek distributors.

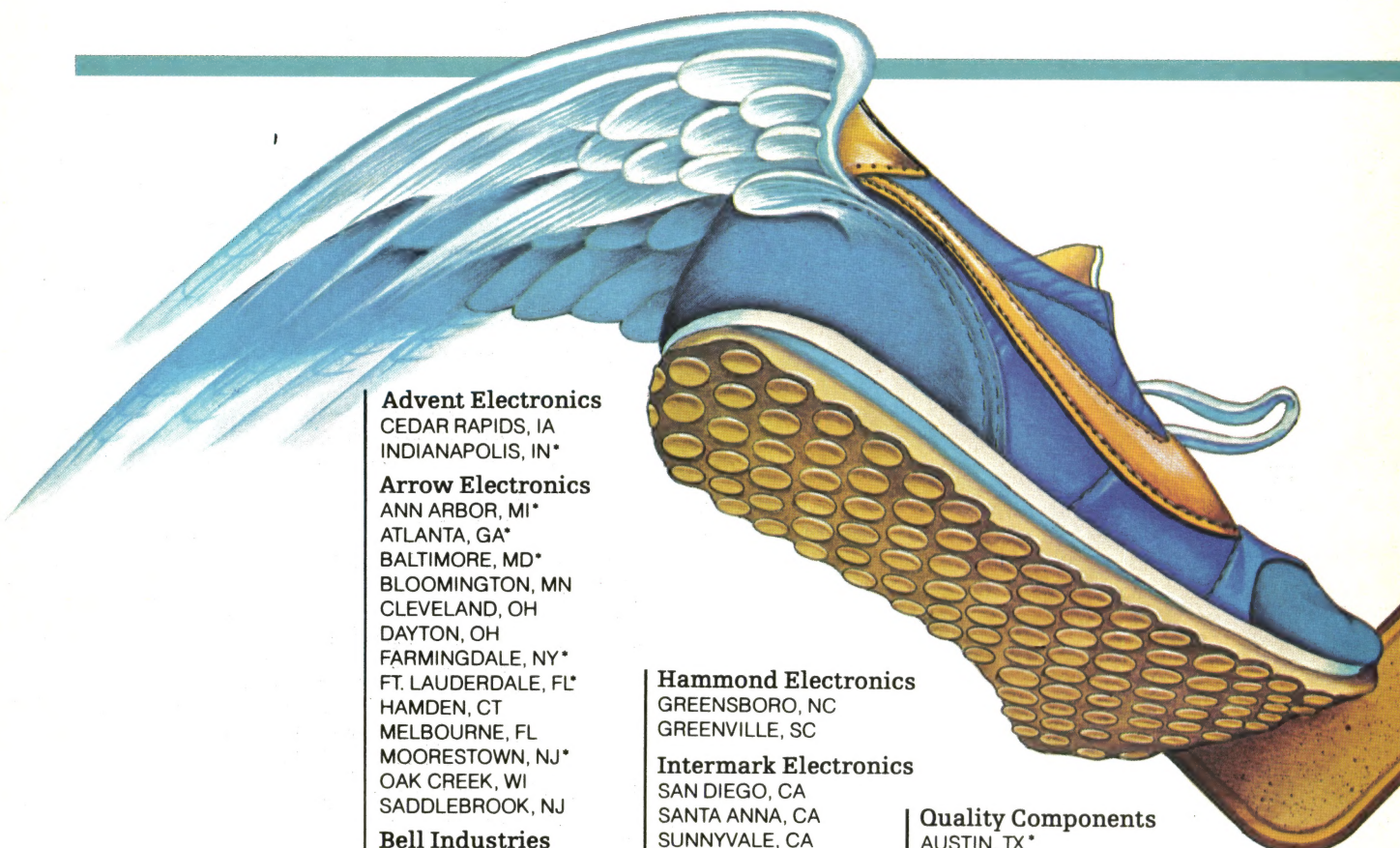

Advent Electronics
CEDAR RAPIDS, IA
INDIANAPOLIS, IN*

Arrow Electronics
ANN ARBOR, MI*
ATLANTA, GA*
BALTIMORE, MD*
BLOOMINGTON, MN
CLEVELAND, OH
DAYTON, OH
FARMINGDALE, NY*
FT. LAUDERDALE, FL*
HAMDEN, CT
MELBOURNE, FL
MOORESTOWN, NJ*
OAK CREEK, WI
SADDLEBROOK, NJ

Bell Industries
ALBUQUERQUE, NM
CHICAGO, IL*
DENVER, CO*
SALT LAKE CITY, UT
SUNNYVALE, CA*

Cramer Electronics
DALLAS, TX*
EDINA, MN*
GAITHERSBURG, MD*
NEWTON, MA*
ROCHESTER, NY*
SOLON, OH*
SUNNYVALE, CA*
SYRACUSE, NY*

Diplomat Southland
TAMPA, FL

Ft. Wayne Electronics
FT. WAYNE, IN *

Graham Electronics
INDIANAPOLIS, IN

Hammond Electronics
GREENSBORO, NC
GREENVILLE, SC

Intermark Electronics
SAN DIEGO, CA
SANTA ANNA, CA
SUNNYVALE, CA

Kierulff Electronics
BILLERICA, MA*
CHICAGO, IL*
DENVER, CO*
LOS ANGELES, CA
PALO ALTO, CA*
PHOENIX, AZ*
RUTHERFORD, NJ*
ST. PETERSBURG, FL
SAN DIEGO, CA
SEATTLE, WA*

Lionex Corp.
BOSTON, MA
WOODBURY, NY

Olive Electronics
ST. LOUIS, MO

Prelco Electronics
MONTREAL, CANADA*
OTTOWA, CANADA*
TORONTO, CANADA*

Quality Components
AUSTIN, TX*
DALLAS, TX*
HOUSTON, TX*

R.A.E. Industrial
VANCOUVER, CANADA

Schweber Electronics
ATLANTA, GA
BEACHWOOD, OH
BEDFORD, MA*
DANBURY, CT*
HORSHAM, PA*
HOUSTON, TX*

IRVINE, CA*
LIVONIA, MI*
ROCHESTER, NY*
SOMMERSET, NJ
WESTBURY, NY*




Semiconductor Specialists
KANSAS CITY, MO


W.E.S. Ltd.
WINNIPEG, CANADA

*Demonstration Center

© 1979 Mostek Corp.

The quick step to Z80 power.

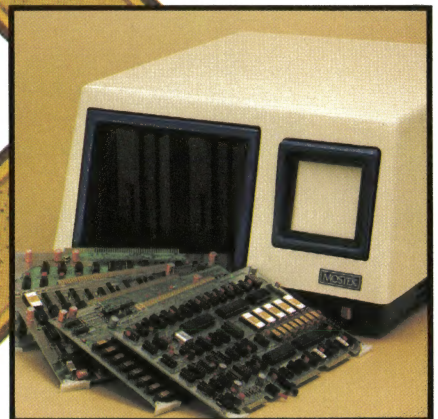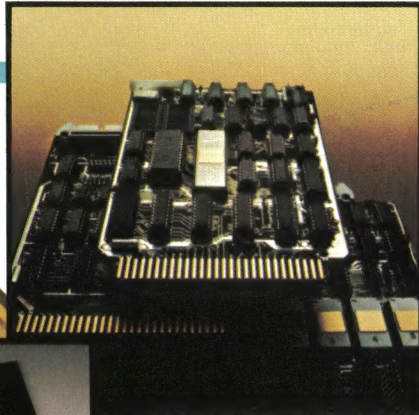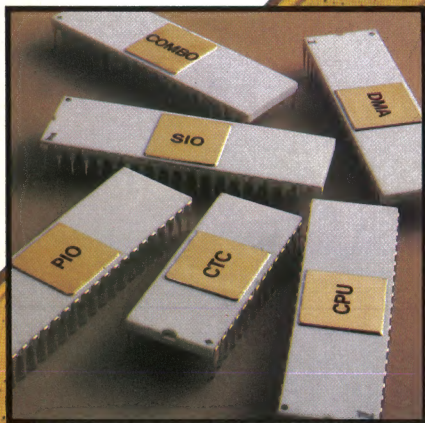

 Get on the fast track to Z80 power with your local Mostek distributors. They have everything you need, including factory trained engineers and demonstration centers at many locations.

Start with our MK 3880 line of Z80 components, industry's most powerful 8-bit microcomputer family.


Or begin with our MD Series™ of OEM microcomputer boards. It features our MDX-line of STD-Z80 BUS compatible modules for building your system one function at a time. You buy only what you need, and reduce hardware design time.

Plus you only need one development system, Mostek's AID-80F™, to develop and debug software for all our microcomputer products. BASIC and FORTRAN are also available for use on the AID-80F.

For components, boards, or systems, take the quick step to your nearest Mostek distri-

butor. Or contact us directly for more information at 1215 West Crosby Road, Carrollton, Texas 75006; phone 214/242-0444. In Europe, contact Mostek Brussels; phone (32) 02/660.25.68.

MOSTEK®

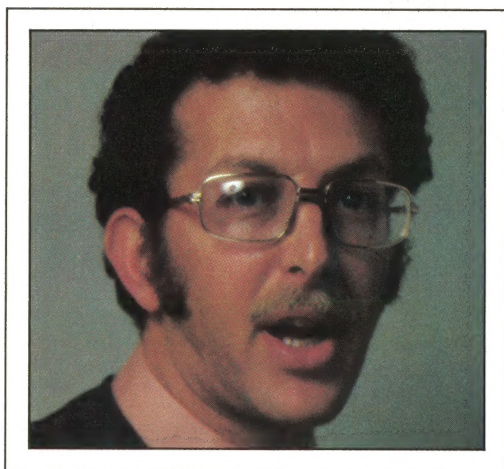

"It's As Different
From Other Systems
As The Steam Shovel
Is From The Shovel."

Mark Levi
General Manager, Microcomputer Systems

StarplexTM Development System



"Right now, what's holding back new developments in microprocessing are the existing development systems.

The Starplex System is going to change all that.

And as of this moment, if you're in the business of designing or programming 8080/8085 based products, this is the tool that can make your life infinitely less tedious.

So sophisticated is the Starplex System, it can virtually take you by the hand and walk you through its own operation.

Where other systems require scores of individually typed instructions, the Starplex System can do the same job at one stroke of a key.

Where other systems offer you blood, sweat, and repetition, the Starplex System offers HELP, PAUSE, EDIT, DEBUG, CONTINUE. To name a few of the unique functions on our keypad.

Where other systems leave you fumbling

	STARPLEX	INTEL	TEKTRONIX
SIMPLE KEYSTROKE CONTROLS	EDITOR SYSTEM UTILITIES	NONE	NONE
SYSTEM OPERATING MODES	FORMS OR COMMAND DRIVEN	COMMAND DRIVEN ONLY	COMMAND DRIVEN ONLY
CRT-ORIENTED EDITOR	YES	NO	NO
HIGH LEVEL LANGUAGES	2	2	NONE
ISE CAPABILITY	MULTI- PROCESSOR	SINGLE PROCESSOR	SINGLE PROCESSOR
PROM PROGRAMMER	INTE- GRATED OPTION	SEPARATE	SEPARATE
PRINTER	STANDARD	OPTIONAL	OPTIONAL
TOTAL PRICE <small>(Exclusive of PROM Programmer and ISE)</small>	\$13,800	\$21,870	\$21,230

through thick manuals looking for escape clauses, the Starplex System guides you through your work path with a series of menus, prompts, lights, and audible signals.

And while some systems can communicate only in assembly, ours is fluent in BASIC and FORTRAN. Languages which can be loaded — as usual — with one keystroke.

Now others may have claimed their systems were "easy" before. But we've got the software to prove it. Which is why we

standard ASCII keyboard in addition to the special function keypads.

All the software you'll need is included in the package. A powerful operating system, macro assemblers, editor, debugger, and other key software modules.

We also offer the In-System Emulator (ISE), an extremely valuable option for hardware development. It works through an easily understood command interface. ISE uses its own memory for memory mapping — a time-saving feature which also allows true real-

time debugging.

Because Starplex ISE incorporates symbolic debugging, you can debug code in the same assembly mnemonics in which it was written. And it's the only system emulator capable of debugging two microprocessors simultaneously in a multi-processor system.

By any standard of comparison, the Starplex Development System represents a colossal leap-frog over the field in every category, save one: Price. And so, while others ask in excess of \$20,000 for the



do not hesitate to publish here a comparison chart which will show at a glance where things really stand.

The Starplex System is designed to be used with current and future National microprocessors, as well as BLC/SBC Series/80 microcomputers.

It's fully expandable, with four chassis slots allowing the addition of standard Series/80 boards. Plus a programming station which accepts optional personality boards for 2708 and 2716 PROMs.

Integrated into the Starplex package are five microprocessors, 64K bytes of memory, dual 256K byte floppy discs, a 1920 character CRT, a 50 CPS printer, and stan-

dard ASCII keyboard in addition to the special function keypads.

We would jump at the chance to tell you the whole story in detail. Write or call me for a complete brochure on the Starplex Development System. Address your request to Mark Levi, General Manager, Microcomputer Systems, National Semiconductor Corporation, Drawer 31, 2900 Semiconductor Drive, Santa Clara, California 95051. Or dial these toll-free numbers: 800-538-1866; 800-672-1811 in California.

In Europe, write National Semiconductor GmbH, Industriestrasse 10, 8080 Fuerstenfeldbruck, West Germany."

Computer Products Group
≈ **National Semiconductor Corporation**

EDN 4/5 9-5

No one portable everyone's needs. So we built 21.

Everyone's needs are different. Some want the same versatility in the field they get from a bench model in the lab. Others are more concerned about weight. Some require basic performance models at an economical price. Tektronix offers a selection of 21 portable scopes — 15 real-time and 6 storage models — to satisfy just about everyone.

Take your pick. You can't beat our 400 Series when it comes to high performance. Choose from 9 models ranging in bandwidth from 50 MHz to 350 MHz. All under 26 pounds (11.8 kg). Five with an optional DMM and delta time read out.

If you're looking for a battery-powered model that fits into a briefcase or toolbox, there's our 200 Series. Bandwidths to 5 MHz. Weights less than 3.7 pounds (1.7 kg).

In between, there's the compact 300 Series, with bandwidths to 35 MHz. Each scope weighs less than 11 pounds (5.0 kg). And finally, we offer the low cost T900 Series, priced from just \$795.00*.

Our worldwide service team goes where you go. We're with you all the way, with more than 500 service personnel at 46 Tektronix centers in the U.S.A. and hundreds of Tektronix-supported service engineers in over 50 other countries to calibrate and maintain your Tektronix scope.

So let us show you the model that's right for you. Simply contact your Tektronix Sales Engineer. He'll arrange for a demonstration of our portable or laboratory oscilloscopes. And for our latest portable oscilloscopes brochure, write: Tektronix, Inc., P.O. Box 500, Beaverton, OR 97077. In Europe: Tektronix Limited, P.O. Box 36, St. Peter Port, Guernsey, Channel Islands.

For technical data Circle no 23

For demonstration Circle no 24

*For immediate action dial our toll free automatic
answering service 1-800-547-1512*

**We're
going
places**




scope meets

	Product	Bw	Dual Trace	Delayed Sweep	Fastest Sweep Rate	Other Special Features	Price*
Storage Models	466	100 MHz @ 5 mV/div	yes	yes	5 ns/div	3000 div/ μ s stored writing speed	\$5355
	464	100 MHz @ 5 mV/div	yes	yes	5 ns/div	110 div/ μ s stored writing speed	4375
	434	25 MHz @ 10 mV/div	yes		20 ns/div	Split-screen storage	3480
	314	10 MHz @ 1 mV/div	yes		100 ns/div	Only 10.5 lbs (4.8 kg)	2645
	214	500 kHz @ 10 mV/div	yes		1 μ s/div	Only 3.5 lbs (1.6 kg)	1595
	T912	10 MHz @ 2 mV/div	yes		50 ns/div	Low-cost bistable storage	1545
Nonstorage Models	485	350 MHz @ 5 mV/div	yes	yes	1 ns/div	Widest bw in a portable	5725
	475A	250 MHz @ 5 mV/div	yes	yes	1 ns/div	High-performance 250-MHz portable	3800
	475	200 MHz @ 2 mV/div	yes	yes	1 ns/div	Highest gain-bw in a portable	3435
	465	100 MHz @ 5 mV/div	yes	yes	5 ns/div	Cost effective for 100-MHz bw	2495
	465M	100 MHz @ 5 mV/div	yes	yes	5 ns/div	Triservice standard 100-MHz scope	2620
	455	50 MHz @ 5 mV/div	yes	yes	5 ns/div	Cost effective for 50-MHz bw	2055
	335	35 MHz @ 10 mV/div	yes	yes	20 ns/div	Only 10.5 lbs (4.8 kg)	2175
	305	5 MHz @ 5 mV/div	yes		0.1 μ s/div	Autorangeing DMM	1725
	221	5 MHz @ 5 mV/div			100 ns/div	Only 3.5 lbs (1.6 kg)	1190
	213	1 MHz @ 20 mV/div			400 ns/div	DMM/Oscilloscope @ 3.7 lbs (1.7 kg)	1595
	212	500 kHz @ 10 mV/div	yes		1 μ s/div	Low cost for dual trace & battery	1190
	T935A	35 MHz @ 2 mV/div	yes	yes	10 ns/div	Delayed sweep and differential	1535
	T932A	35 MHz @ 2 mV/div	yes		10 ns/div	Variable trigger-holdoff and differential	1245
	T922	15 MHz @ 2mV/div	yes		20 ns/div	Low-cost dual-trace scope	975
	T922R	15 MHz @ 2mV/div	yes		20 ns/div	Rackmount version of T922	1345
	T921	15 MHz @ 2mV/div			20 ns/div	Lowest-cost TEKTRONIX Portable	795
Time Interval Readout	DM44	Optional, factory-installed, direct numerical readout of time intervals and DMM functions for the 464, 465, 466, 475 and 475A					445

*U.S. sales prices are F.O.B. Beaverton, OR. For price and availability outside the United States, please contact the nearest Tektronix Field Office, Distributor or Representative. Prices are subject to change without notice.



Tektronix
COMMITTED TO EXCELLENCE

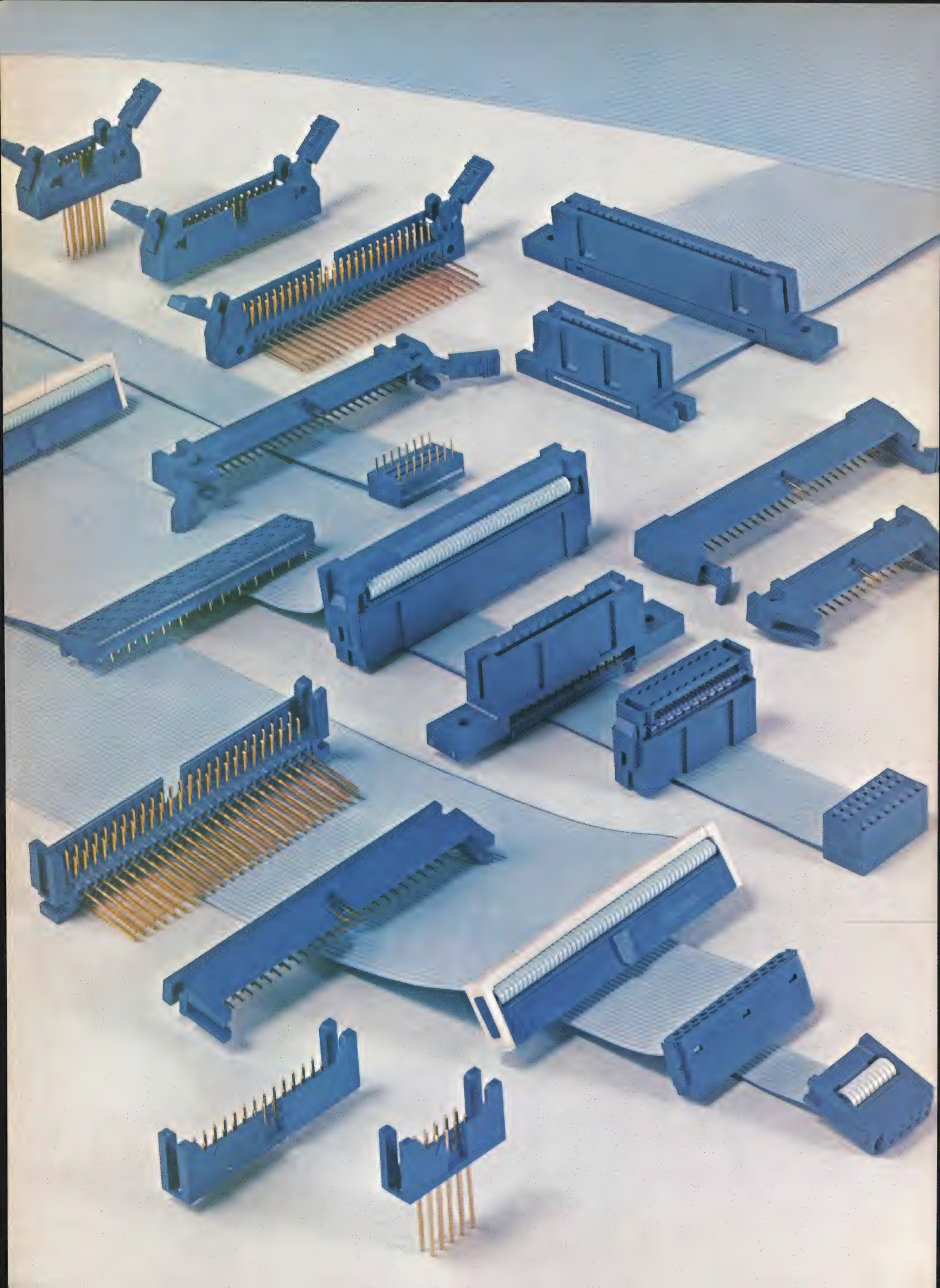


Quickie™: the total IDC System for design flexibility, fast assembly, reliable connections.

Meets a variety of interconnect needs.

- A wide choice of connectors: "Quickie" and "Quickie" low-profile females, female IC, edge card, male DIP, PCB, and quick-eject vertical and right-angle headers ... all in a broad range of sizes.
- Round conductor, flat cable on 0.050" centers.
- A selection of hand and air operated presses, cable shears, accessories and strain reliefs.


Efficient assembly saves time, material and money.

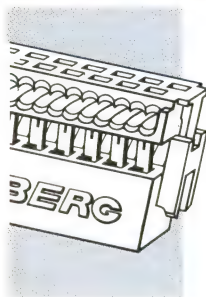All connectors in the Quickie* system deliver reliable terminations in just a few seconds because:



- Cable slot designed to precisely position conductor for reliable termination, higher yields.
- Sight holes in cover permit visual inspection before and after assembly assuring proper cable alignment.

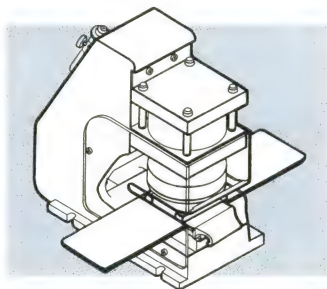• The semi-automatic applicator completes terminations with a slide motion reducing assembly time. Or choose the manual applicator designed to minimize operator fatigue.




Over seven years proven performance. You can rely on "Quickie".

"Quickie" connectors are now specified by many of America's most quality conscious

companies. Three high performance features demonstrate why:

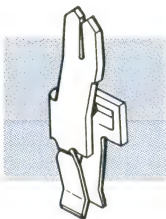1. Askewed tines firmly hold the wire for reliable termination.



2. Dual-beam contact assures redundant positive pin connection, even when subjected to vibration.

3. High-strength plastics withstand severe environments.

**For a brochure giving details
and complete specifications,
write or call:**

The Du Pont Company, Berg Electronics Division
New Cumberland, Pennsylvania 17070.
Telephone: (717) 938-6711.



BERG ELECTRONICS

For more information, Circle No 7

*Du Pont's trademark for its mass termination connectors, cable, presses and accessories.

"Use my program to enhance your design of networks and filters"

Vic Bennett

"I just couldn't stand the tedious parameter conversion and data re-entry needed to do good network design, but I don't like to use cut & try methods either. So... I tried to find a CAD program to do the job for me.

I wasn't able to find one sophisticated enough to do the job I wanted for less than \$10,000... so I decided to write my own instead.

I'm glad I did because it's quick and easy to use and gives me the exact information I want in the form I want to see it. In fact, it not only solves the problems of RF network design, but can also be used to enhance the design of low frequency networks. By using the program, I have found that I can greatly increase the bandwidth of a low frequency network without having to use costly components.

It occurred to me that lots of engineers may be in the same boat I was -- facing a very sophisticated design task with a very unsophisticated budget. To help you out (and to pay for all the time I spent writing the program), I am offering the use of the program to everyone... at a price anyone can afford.

To give you an idea of how you use the program, there are three modes of operation:

INTERACTIVE MODE

1. ENTER network configuration in plain English (6 network registers of up to 20 components each plus 4 registers of up to 10 sets each of S-parameter measurements).
2. INTERROGATE system to obtain -- for any frequency -- the following:
 - 2-port parameter matrix representation of the network in any parameter set (H,Y,Z,G,S,T)
 - Unilateral figure-of-merit
 - All power gains
 - Optimal source/load match
 - Rollett's stability factor

PLOT MODE

1. Select any or all items to be plotted; enter frequency range of plot.
2. Plot selected items against frequency, with frequency on the x-axis.

AUTOMATIC SEARCH MODE

1. Without re-entering network data, enter permitted component variations and target performance curve.
2. Program determines optimum component values via gradient method of steepest decent.

SEND TODAY FOR YOUR MANUAL
WITH PROGRAM LISTINGS IN
FORTRAN IV AND BASIC

\$34.88
EACH



Security Research Laboratories, Inc.

P.O. Box 49, Dept. EDN2, Medfield, MA 02052

Name _____

Company _____

Street _____

City _____

State _____ Zip _____

No. of Manuals ordered _____ @ \$34.88 each

Enclosed is check/money order for \$ _____

(Mass. residents add 5% sales tax)

or charge to:

Master Charge Acct. No. _____

Visa Acct. No. _____

For more information, Circle No 77

Signals & Noise

Add this to your list

Dear Editor:

Your article on chips and filters for Touch Tone receivers (EDN, January 5, pgs 115-120) was very timely and well prepared. Unfortunately, the article omitted a major manufacturer.

Teltone Corp has manufactured Touch Tone devices since 1968 and has led in the development of these devices for interfacing with tone-related equipment. Our high-performance tone receivers of central-office quality are used by all major telephone companies throughout North America, in various applications internationally and by many equipment manufacturers.

Sincerely,

Earl L Mason

Vice President, Marketing
Teltone Corp
Kirkland, WA

Fine-tuning a keyboard

Dear Editor:

The EDN January 20 Special Report on keyboards (pgs 64-72) seems to ignore a difference in format which has been a problem for us.

The box on pg 65 presenting keyboard specifications for your hypothetical word-processing terminal mentions that the "operator is experienced with high-speed typing on an IBM Selectric." But every keyboard pictured in the article has a Teletype Model 33 format, which differs from the Selectric format in its placement of punctuation and other symbols such as *, +, ", etc. (It's interesting, though, that Teletype Corp's Model 45

uses the Selectric format, as do Digital Equipment's Decwriter and video terminals.)

If an operator had to switch often between an IBM Selectric and any of the keyboards shown in the article, I would expect an error rate substantially higher than if the operator only had to use either one of the two formats. Our experience has shown this to be the case, and we are now standardizing on the Selectric format, mostly because we use those typewriters and a DEC computer.

Very truly yours,

Howard Hamer

Chief Engineer

Dranetz Engineering Labs
South Plainfield, NJ

Misplaced decimal

Mr Sidney Chertok, Director of Information Services at Sprague Electric, has informed us of an error appearing in Table 1 (pg 124) of the January 5 EDN article, "Optimize ripple/EMI performance in switching-regulator designs." The Sprague and Mallory stacked-foil capacitors described there show a typical ESL (nH) of 15—the figures should read 1.5 nH.

JOB SHOPPING?

Check EDN's Career Opportunities

EDN: Everything Designers Need



Has your power supply vendor left you high & dry?

If you're involved in a program to replace a power supply that is no longer available or your previous supplier is no longer around or can't deliver, Powercube standard modular power circuits may be the answer.

Used for over a decade by contractors for major military and space programs, these proven 1" x 1" x 2" Circuitblock® modules meet the toughest specs for size, weight, performance and environment.

We can optimize your design and save you money without getting bogged down in component selection, vendor delays or interface problems. Most Circuitblock preregulators, power generators and output modules are available off the shelf.

Call the quick action company 617-667-9500 or circle the reader response number.

For more information, Circle No 10


 **POWERCUBE**
A SUBSIDIARY OF UNITRODE CORPORATION

POWERCUBE CORPORATION
EIGHT SUBURBAN PARK DRIVE
BILLERICA, MASSACHUSETTS 01821
(617) 667-9500

OE CRYSTAL OSCILLATOR ELEMENTS

International's OE Series of Crystal Oscillator Elements provide a complete crystal controlled signal source. The OE units cover the range 2000 KHz to 160 MHz. The standard OE unit is designed to mount direct on a printed circuit board. Also available is printed circuit board plug-in type.

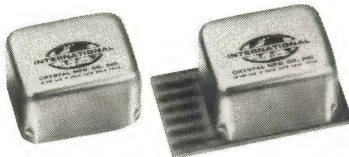The various OE units are divided into groups by frequency and by temperature stability. Models OE-20 and OE-30 are temperature compensated units. The listed "Overall Accuracy" includes room temperature or 25°C tolerance and may be considered a maximum value rather than nominal.



input supply less than 12 vdc.

Prices listed include oscillator and crystal. For the plug-in type add the suffix "P" after the OE number; eg OE-1P.

OE-1, 5 and 10 can be supplied to operate at 5 vdc with reduced rf output. Specify 5 vdc. when ordering.

Output — 10 dbm min. All oscillators over 66 MHz do not have frequency adjust trimmers.

All OE units are designed for 9.5 to 15 volts dc operation. The OE-20 and OE-30 require a regulated source to maintain the listed tolerance with

Catalog	Oscillator Element Type	2000 KHz to 66 MHz	67 MHz to 139 MHz	140 MHz to 160 MHz	Overall Accuracy	25°C Tolerance
035213 035214 035215	OE-1 OE-1 OE-1	\$14.24	\$16.35	\$20.57	±.01% -30° to +60°C	±.005%
035216 035217 035218	OE-5 OE-5 OE-5	\$17.67	\$20.83	\$27.43	±.002% -10° to +60°C	±.0005% 2 - 66MHz ±.001% 67 to 139 MHz ±.0025% 140 to 160 MHz
Catalog Number	Oscillator Element Type	4000 KHz to 20000 KHz			Overall Accuracy	25°C Tolerance
035219	OE-10	\$20.83			±.0005% -10° to +60°C	Zero trimmer
035220	OE-20	\$30.59			±.0005% -30° to +60°C	Zero trimmer
035221	OE-30	\$63.30			±.0002% -30° to +60°C	Zero trimmer




**INTERNATIONAL
CRYSTAL
MFG. CO., INC.**

10 North Lee
Oklahoma City, OK 73102
405/236-3741

For more information, Circle No 11

AUTHORIZED ASSEMBLER & DISTRIBUTOR

FOR
3M
COMPANY
Scotchflex
BRAND

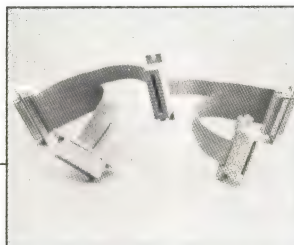

FLAT CABLE & CONNECTOR SYSTEMS



ASSEMBLY SYSTEMS DIV.

DISTRIBUTOR DIV.

FOR TECHNICAL INFORMATION, QUOTES, DELIVERY
CALL OUTSTATE — 800 • 325 • 3348 • LOCAL 314 • 946 • 6424

ASK FOR OUR PRODUCT LINE CARD

- 3M SCOTCHFLEX • BURNDY • ELCO • MOLEX
- WINCHESTER ELECTRONICS • KINGS • VERNITRON
- PANDUIT • CHERRY • GUARDIAN • HI-G • DALE
- AUGAT • USECO • CHICAGO MINIATURE • DRAKE
- VECTOR • SOLDER REMOVAL • WIRE AND CABLE
- PYLE NATIONAL • REMTEK • WOVEN CABLE

Write To: Dept. 3M

P.O. BOX 188 • 306 McDONOUGH ST. • ST. CHARLES, MO. 63301

For more information, Circle No 12

Books

Cut confusion with pocket-sized reference

Microprocessor Lexicon. 110 pgs; \$2.95; Sybex Inc, Berkeley, CA, 1978.

One definition of a lexicon is "the vocabulary of a language." Appropriately, this little book doesn't confine itself to the jargon of microprocessorists, but extends into the glut of acronyms that characterizes communications as well.

The bulk of this pocket-sized work attacks the vagaries of terminology. Although far from exhaustive, the definitions are accurate and sufficient for quick lookup.

Numbers play an important part in the dialogues of the digital world. Thus, one section is devoted to "The Numbers Game," wherein the book translates common numeric designations.

The lexicon also mysteriously includes two manufacturers lists: one for μ Ps, another for μ Cs. Perhaps such lists serve a purpose, yet the industry's quicksilver nature renders the completeness and accuracy of any list in book format doubtful.



Realistically, if you're in the business, you probably don't need this book. Giving it to an engineering manager (or a nontechnical friend, for that matter), though, could save time and effort for both of you.—**Ed Teja**

JOB SHOPPING?

Check EDN's Career Opportunities

EDN: Everything Designers Need

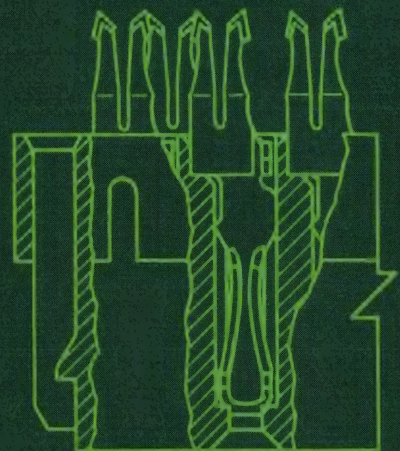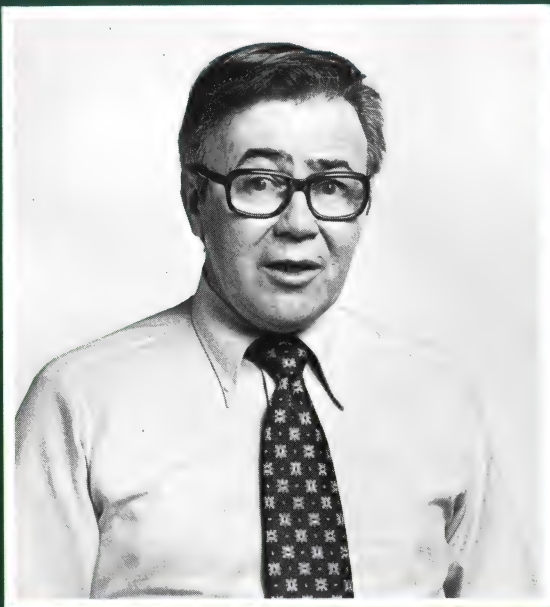“Look, I’ve got two challenges for my ribbon cable interconnects — to reduce manufacturing rejection rates and prevent contact damage during testing. Got any solutions?”



AMP Latch.



Some facts worth knowing about AMP Latch Connectors


Function: Simultaneous mass termination of all conductors without cable stripping.

Wire types: Small gauge solid or stranded discrete wires as well as flat ribbon, woven ribbon and other types flat cable with round conductors on .050" centers.

No. of positions: 10 to 60.

Connector types: Wide variety of cable-to-cable, card edge, DIP and receptacle connectors available.

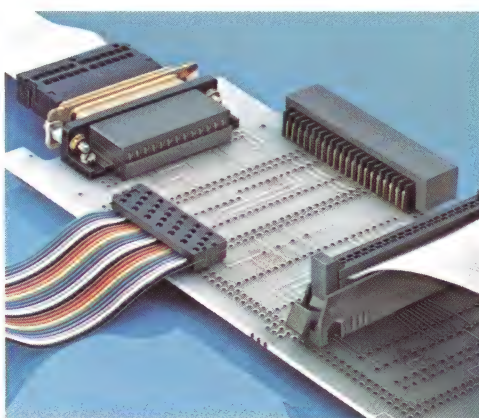Mates with: Full range of AMPMODU headers and pcb posts.



Electrical Current Rating:

1 Ampere (Continuous).

Operating Temperature Range:

-55°C to +105°C.


Dielectric Withstanding Voltage:

500 Volts, RMS.


Tooling available: Pneumatic and Manual Bench Mounted Models and a Hand Tool, each with interchangeable die sets.

Who to contact: Call AMP Latch Information Desk at (717) 564-0100. Ext. 8400. Or write AMP Incorporated, Harrisburg, PA 17105.

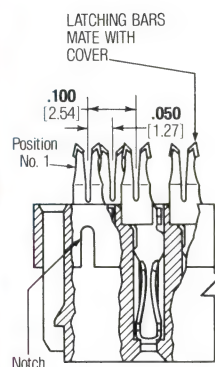Product Information: Check Reader Service Number 99.



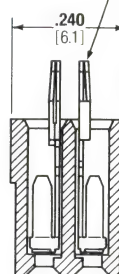FOLDED DESIGN FOR FOUR POINTS OF TERMINATION



As fast as you can say "downtime" your production, test or repair people can activate an AMP Latch Easy Release Header with one hand. Just squeeze and the cable half is disengaged. No wrenching on the cable. No wiggling. And no damaged contacts. An important matter when

We sure do.

neither your production costs nor your on-board costs can take a back seat to one another. And one of many reasons why AMP Latch has drawn the attention of designers in the data processing, instrument and communications industries.

Yet AMP Latch offers a unique feature that extends far beyond what other ribbon cable connectors can offer. It offers precision registration built into the tooling which minimizes rejection rates.


Unquestioned reliability. That's what AMP Latch is about, too. You get a four-point electrical contact and mechanical grip for each conductor.

Built-in inspection ports make test simpler than ever.




The fact is, nobody today has a wider range of easy-to-apply no-strip, no-solder, round conductor flat cable connectors than AMP.

For more details, see the opposite page and the page overleaf.

AMP has a better way.

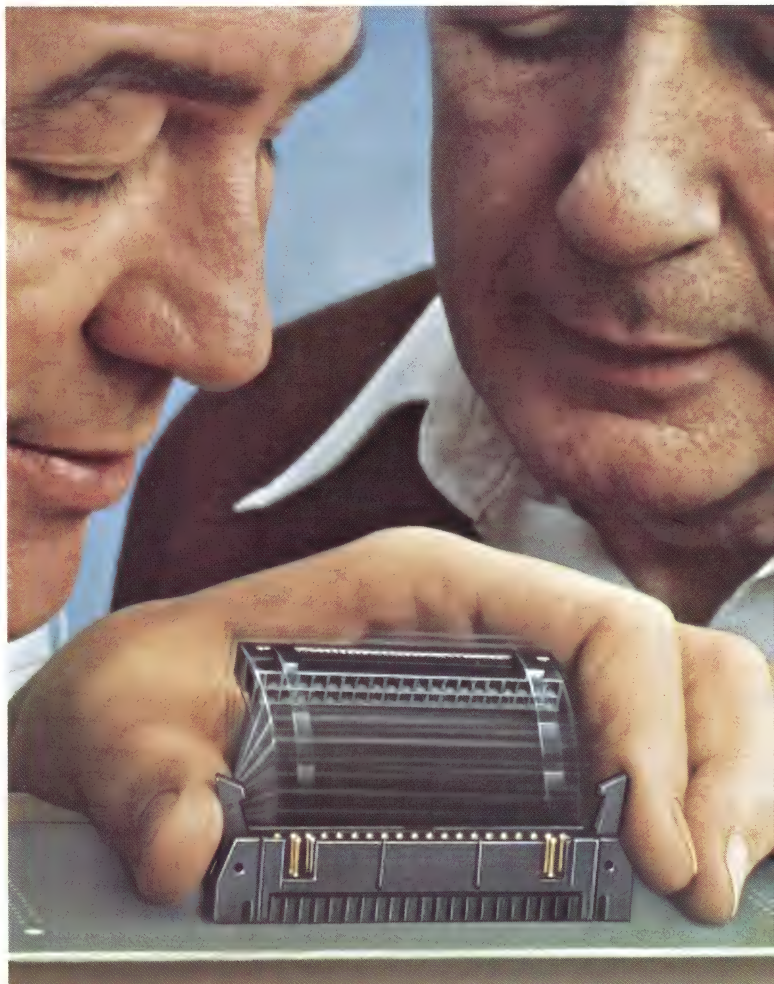

And cost effective tooling.

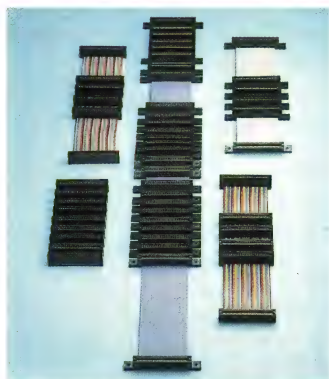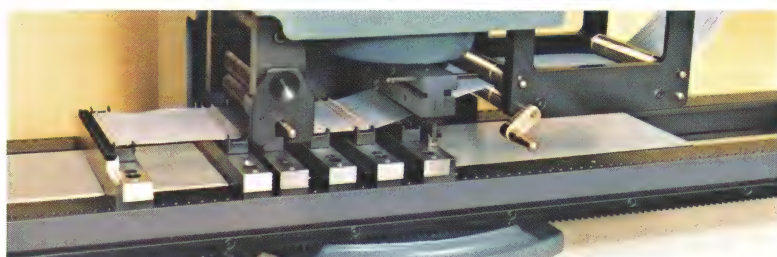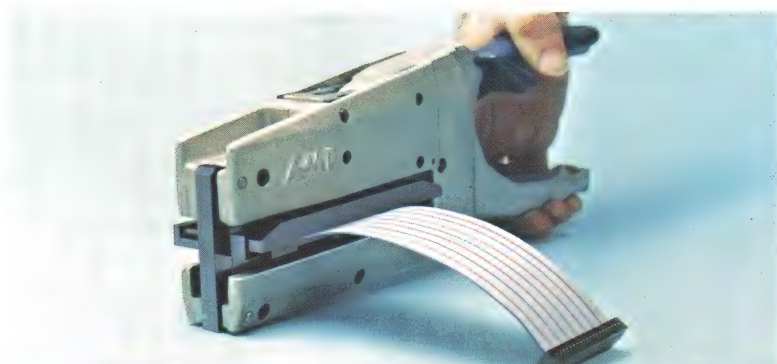

With AMP Latch Tooling the terminations are made quickly, easily and simultaneously. No need for pre-stripping the insulation. One tool will terminate virtually all popular round conductor flexible cable, including those with flat side down or ribbed side down.

Two basic bench-mounted AMP Latch tools include: a heavy-duty pneumatically powered unit and a manually operated unit. Both are reliable. Both are easy to load. And precision cable registration is built in. Alignment is automatic and positive. Six different precision die sets are available for terminating receptacle, plug, card edge, paddle board and pin connectors as well as discrete wire.

Also available is equipment for daisy chain terminations, and a hand tool with interchangeable dies.

For the complete story on AMP Latch Connectors, AMP Latch Tooling, and the AMP Technical Support that goes with them, call AMP Latch Information Desk at (717) 564-0100. Ext. 8400. Or write AMP Incorporated, Harrisburg, PA 17105.

AMP and AMPMODU are trademarks of AMP Incorporated.

AMP

The last time you saw a really new bench/portable DMM was 1972.

That's the year our 8000A was introduced. Its custom LSI and solid owner benefits quickly established it as the world's leading DMM.

Now, look at the new 8010A and 8012A: single-chip CMOS designs for problem-solving in the eighties!

RAZOR-SHARPLCD for large, no-strain answers at first glance—in any light.

TOUCH AND HOLD probe option, so you can thread your way through a component jungle and capture the reading you need.

FUNCTIONPOWER: 22 ranges of AC and DC volts and current, six ranges of resistance, and three ranges of conductance — the missing function on other bench multimeters.

CONDUCTANCE RANGES for noise-free leakage measurements to 10,000 M Ω . A valuable function for bench-testing boards and components, conductance also measures transistor beta (using a bias resistor) and light intensity (by using a photocell).

OVERLOAD-PROTECTED — like no other DMM, including rejection of 6000V transients and up to 600V applied to the current terminals.

HONEST AC ANSWERS derived from a Fluke hybrid true rms converter. You'll even see the difference on your AC line between the correct value and what your average-responding meter reads. And 50 kHz bandwidth won't let any significant distortion products go unmeasured. Plus, 10 times the basic response you may be limited to now!

SPECS YOU EXPECT from Fluke — like $\pm 0.1\%$ on DC for one year. Both models available with rechargeable batteries, and backed by the same solid warranty and worldwide service that helped make the 8000A the industry standard.


LEADERSHIP HAS TO BE EARNED. And we're committed to keeping the price of your confidence as realistic as possible. Like \$239 for the 8010A with a 10A current range, and \$299 for the 8012A with two extra-low ohms ranges that allow measurements from 0.001 Ω to 10,000 M Ω — making it the widest range ohmmeter available!

Contact one of the more than 100 Fluke offices and representatives, worldwide, or CALL (800) 426-0361* TOLL FREE. In the U.S., and all countries outside Europe, write: John Fluke Mfg. Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043, U.S.A.

In Europe, contact Fluke (Nederland) B.V., P.O. Box 5053, Tilburg, The Netherlands. Telephone: (013) 673973. Telex: 52237.

Prices U.S. only.

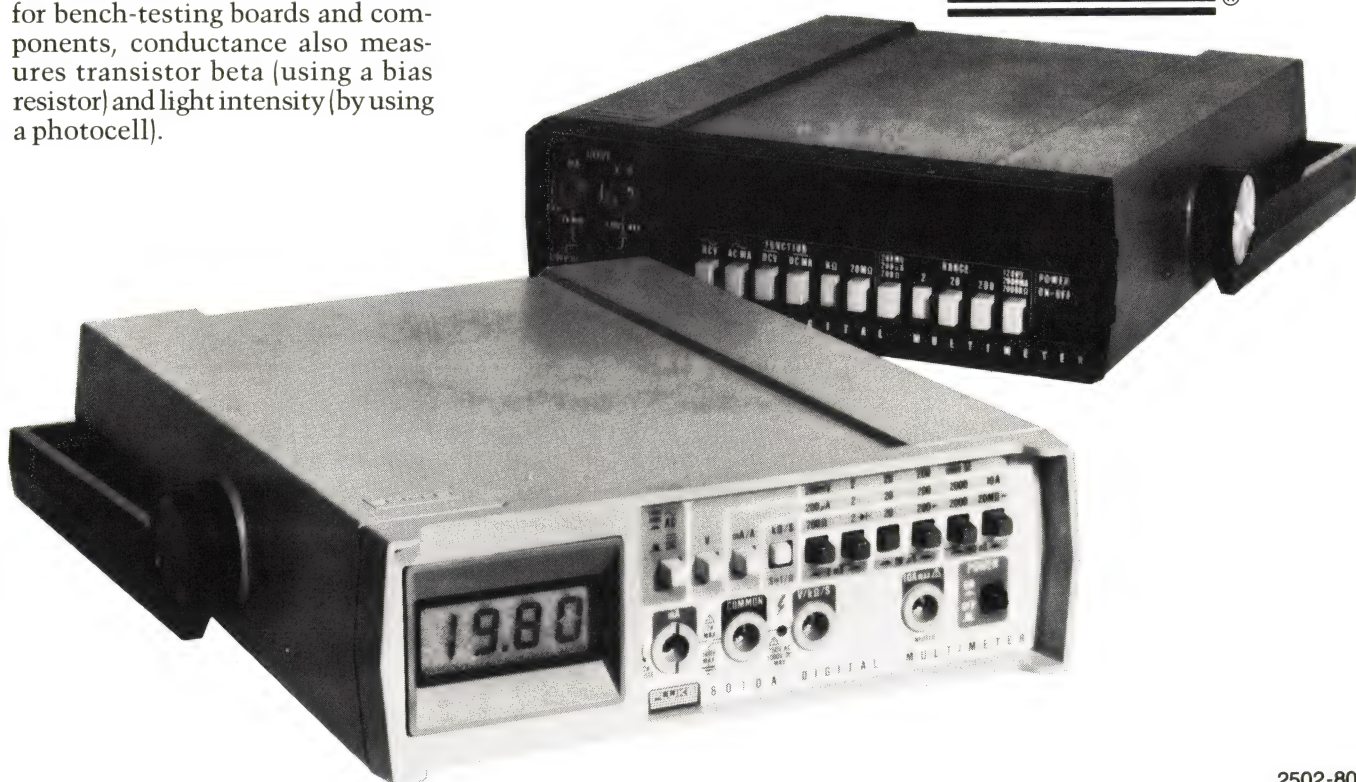*Alaska, Hawaii, Washington residents — please call (206) 774-2481.



2502-8010



**Big linear IC test systems have
finally come down to this.**

The new GenRad 1731. All the big system capability you need at one-fourth the price.

The GenRad 1731 is the first microprocessor-controlled linear IC test system.

It's no bigger than a benchtop tester, but offers the kind of capabilities that have only been available with a roomful of hardware. You not only get the flexibility of software-controlled measurements, but also qualitative readouts on each IC, summary sheets, binning, and data logging.

The GenRad 1731 system comes already programmed for most currently used ICs. And our high-level software lets workers with minimal experience develop new programs in minutes.

We also offer unique socket adaptor kits, which let you assemble new adaptors as you need them—for about one-tenth of what it would cost to buy them complete. And in a lot less time.

GenRad's 1731. Thorough diagnostics. Easy on-site programming. Fast turnaround.

It's the kind of test system you've dreamed about. At a price you never imagined.

For details, call toll-free 800-225-7335 (in Massachusetts, 617-779-2825) or write GenRad, Concord, MA 01742.

TEST CONDITIONS		DUAL OP-AMP	
LM158 FAMILY			
	+Vcc (V)	-Vcc (V)	
C1	15.0	15.0	
C2	5.00	5.00	
C3	5.00	5.00	2.00k
C4	15.0	15.0	2.00k
C5			
C6			
C7			
C8			

Condition numbers are shown on the right edge of the TEST-LIMITS screen.

Programming the GenRad 1731 system for new ICs is as simple as filling in the blanks. Our software prompts you every step of the way.




GenRad

Put our leadership to the test.

For more information, Circle No 16

How Litronix' opens a new world

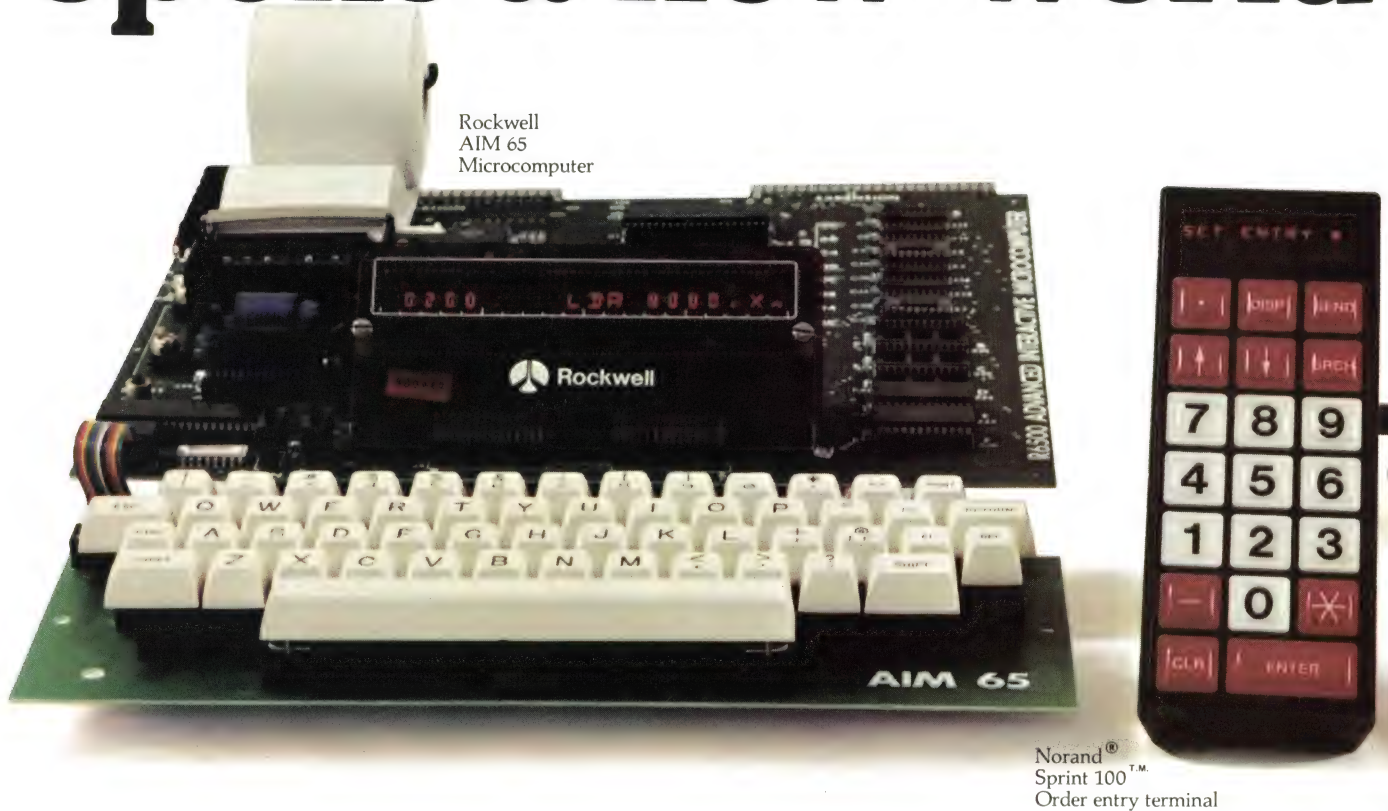

Now designers have a communications peripheral perfectly matched in size and cost to the world of microcomputers.

Litronix invented the Intelligent Display* to give microcomputers a new way of "talking" to users in words, numbers or even sentences. And not surprisingly, these displays are already

Part Number	Features	Character Height	Horizontal Row Spacing	Vertical Row Spacing	Viewing Angle	Character Positions	Character Segments
DL-1416	Standard General Purpose Display	.160"	.250"	1.200"	±25°	4	16
DL-1414	Compact Display For Hand Held Equipment	.112"	.175"	.800"	±50°	4	16
DL-2416	Premium Display New Rugged Package	.160"	.250"	.800"	±50°	4	17

*Intelligent Display is a trademark of Litronix, Inc.

beginning to create a new class of microcomputer-based products.

The Intelligent Display is an alphanumeric LED readout that incorporates ASCII decoder, multiplexer, memory and LED driver in a built-in CMOS IC. It interfaces simply and directly to any microprocessor bus, much like a RAM. Power is from a single +5V supply, and operating current is low enough for any battery powered device.

Litronix puts intelligent communications in the palm of your hand or anywhere panel space is limited. Three versions of the Intelligent Display are already available to fit a wide variety of applications. The smallest lets you fit 20 characters side by side in a space of only 3.5 inches.

Litronix' Intelligent Displays are already being used in the portable terminal, the low cost microcomputer and electronic translator above. They're also ideally suited for applications like control panel readouts. Handheld computer

DESIGN BECKMAN TRIMMERS IN. DESIGN PROBLEMS OUT.



Presenting the 93P. Our new half-inch trimmer with its built-in dial is a turn for the better.

For the first time, you can have a cermet half-inch single-turn, with dial setting capabilities. A variable resistor that's somewhere between trimmer and precision pot, designed to save labor costs with screwdriver position adjustability, and high-resistance capabilities.

Now you can write your manuals, and specify fast setting instructions. Using the 93P means reduced labor. It'll take less time to make that initial setting, less time to check the board. Calibration time is minimized. And the

93P has custom dial setting capabilities, too. Cermet technology has many advantages over wire wound. With 10% tolerance, and 100 ohms to 2 meg

ohms resistance range, it wins hands-down at high resistances. Inductive problems are eliminated. And the 93P is sealed for environmental stability.


Why a larger cermet part? The longer the element, the more the power dissipation. And it stands to reason, you can get more marking and more adjustability.

Design in a trimmer that's not a trimmer as you've known it until now. The 93P.

Call your local Beckman Helipot distributor for free evaluation samples. To get his number, or immediate technical literature, call (714) 871-4848, ext. 1776. Start designing problems out today.

BECKMAN®

For more information, Circle No 20

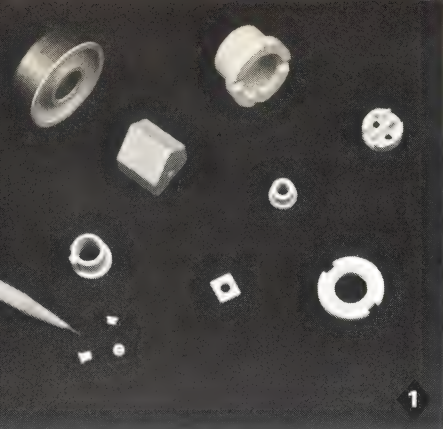


1




2




3

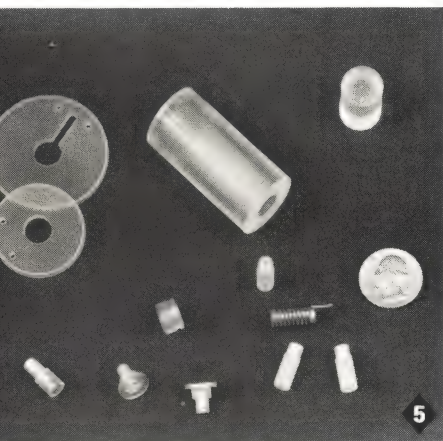


5

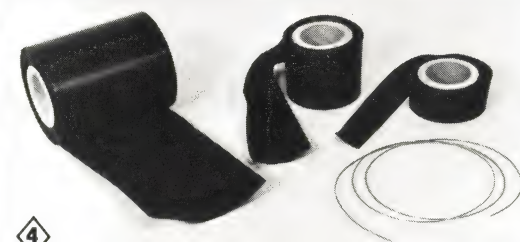

4

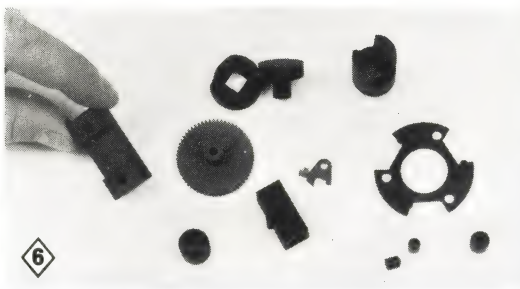

6

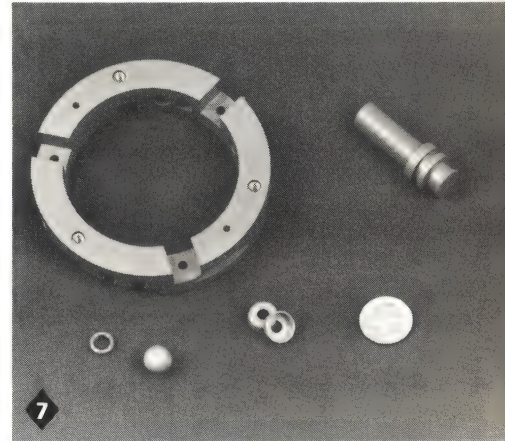

7

❖ **Fluorosint® 500** — A proprietary synthetic mica-filled TFE with a low coefficient of thermal expansion, Fluorosint 500 offers a wide continuous service temperature range. Form stability remains constant to 650°F and the dielectric constant is only slightly affected by frequency changes. Ideal for coil forms, standoff insulators and electrically insulating wear parts. **Circle no 53**

❖ **Conductive Fluorosint® 220 and 221** — TFE type materials are well known for their wear characteristics. Now Polymer has gone them all one better, because Fluorosint 220 and 221 provide excellent conductive properties as well. Natural choices for contact, non-static or conductive bearings and potentiometer applications. **Circle no 54**

❖ **Polymet® AG and CZ** — A proprietary metal-polymeric alloy designed to operate at temperatures to 500°F with greater strength and stability than conventional metal-filled plastics. Good wear resistance, high thermal and electrical conductivity and dimensional stability are its trademarks. Should be evaluated for sliding and rolling contacts, instrument bearings, and self-lubricating high thermal transfer bearings. **Circle no 55**

❖ **Conductive TFE** — Processed into tape, this TFE, with a volume resistivity in the range of 2 - 3.5 ohm/cm, makes meeting design requirements of static bleed-offs and conductive chute linings an easy assignment. Wound as a .030" diameter monofilament sheathed in .005" nylon for strength, it provides 20-30,000 ohms/ft. resistance. Also transparent to microwave radiation. **Circle no 56**

❖ **Polypenco® Q200.5** — A cross-linked polystyrene whose dielectric constant stays virtually unchanged from 10^1 to 10^{10} Hertz. Rigid enough to produce only 1.15% deformation under load, Q200.5 is superior to TFE in radiation resistance. **Circle no 57**

❖ **Nylasint® M4** — A proprietary combination of specially processed nylon for toughness and wear plus MoS₂ solid lubricant. Used for high wear bearings or bushings in electrical or electronic components. **Circle no 58**

❖ **Torlon® 4203** — Exhibits very good electrical properties at temperatures to 500°F. and displays excellent resistance to radiation with only minimal changes after exposure to 10^9 rads of gamma radiation for seven months in a nuclear reactor. A natural for many electrical components such as insulators. **Circle no 59**

WHICH ONE'S FOR YOU? Whenever your designing in plastics for electronic or electrical applications Polymer can help. Have a question or need some help? Call Bob Alberts, Marketing Manager for electronic applications at (215) 929-5858 or write to him at The Polymer Corporation, Reading, PA 19603. In Canada, we're Polypenco Canada Limited.

*TM of Amoco Chemicals Corp.



THE Polymer CORPORATION

For More Information Circle No 60

IMAGINATION IS ALL THAT LIMITS OUR PLASTICS FOR ELECTRONIC/ELECTRICAL APPLICATIONS

Polymer manufactures a wide range of plastics that have been proven successful for use in electronic and electrical components. Applications as diverse as trolley car collector shoes and thermistor leads. Each material has its own unique set of electrical and mechanical properties, and one of them may just be the answer to your next tough design problem.

Plus...a new Professional Advancement Seminar Program.

Designed to provide in-depth coverage of those topics most essential to the power conversion specialist, POWERCON 6 Professional Advancement Seminars offer designers, managers and users a comprehensive selection of invaluable learning opportunities under the direction of some of the world's leading authorities.

- Power converter circuit modeling, analysis, and measurement.
- Shaping and controlling feedback loop response.
- Assessing and controlling power converter EMI.
- High frequency magnetics... materials and design.
- Ultra-high-frequency power converter design.
- An introduction to switched-mode design.
- Automated testing and functional specification of power supplies.
- ...and for those in the "business end" of the field, a special market awareness seminar.

In the interest of providing a quality learning experience, seminar registrations will be limited, and may not be available to last-minute registrants.

POWERCON is a registered service mark of POWER CONCEPTS, INC. (Ronald I. Birdsall, President), an independent consulting and educational firm dedicated to the advancement and dissemination of power conversion technology.

Hotel Headquarters for POWERCON 6...

The Fontainebleau-Hilton.

Located only 20 minutes from Miami International Airport, on Miami Beach, this world-famous resort hotel has been only recently

refurbished by Hilton from the ground up. Combining the ultimate in pleasant surroundings with tennis, bowling, jacuzzis, an olympic-size swimming pool, incredible room rates, and an incomparable location on the Atlantic Ocean, Hilton has welcomed POWERCON 6 with open arms.

Special half-price room rates for POWERCON 6 attendees extend from 3 days prior to the conference until 3 days after:
Singles: \$30-\$35
Doubles: \$35-\$41

For further information concerning POWERCON 6, please call: (805) 985-6978 or (805) 486-5463.

POWERCON 6, PO Box 5226, Ventura, CA 93003

Please register me for:

- ☐ Conference and Exhibit, May 2 thru 4 (all 3 days), \$195.00*
- ☐ Conference and Exhibit, May____ (1 day only), \$120.00*
- ☐ Seminars: _____

(Please call for schedule and fees.)

Name _____ Title _____

Company _____

Address _____


City, State, Zip _____

☐ Check or P.O. enclosed.

☐ Please bill my company. Address invoice attention of: _____

I understand that this reservation cannot be confirmed until my company's check is received in full payment.

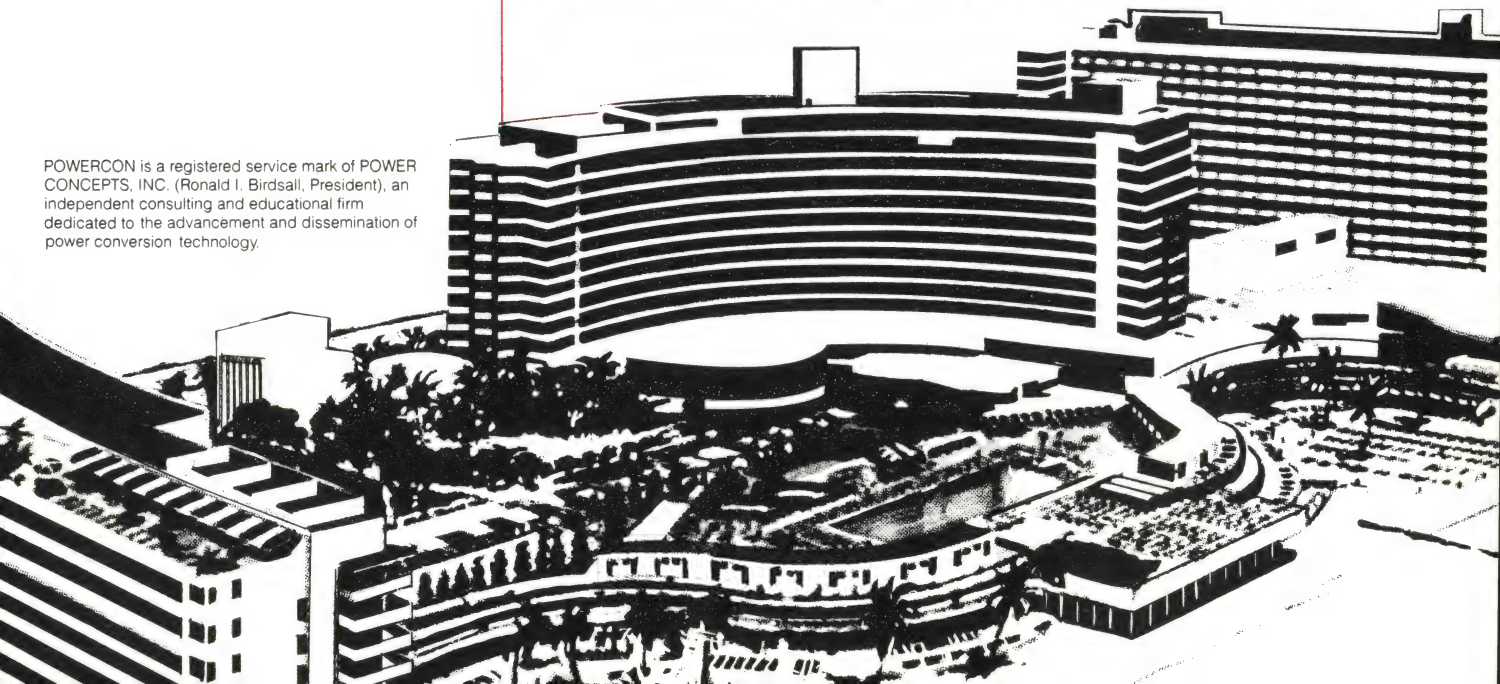*Includes proceedings and POWERCON 6 luncheon on Thursday. Press by invitation only.



POWERCON

Sixth National Solid-State Power Conversion Conference and Exhibit

**May 1-4, 1979
Fontainebleau-Hilton
Hotel
Miami Beach, Florida**


Some facts about POWERCON...

Over 85% of the attendees at a POWERCON conference are practicing engineers and engineering managers.

POWERCON conferences, seminars and tutorial exhibits are designed by practicing power conversion technologists, like you. That means we know what you need most.

A POWERCON must be *experienced*, for the value of even the most exemplary technical presentation cannot begin to compare to the catalytic effect of being among, and comparing notes and experiences with, the hundreds of your contemporaries who attend.

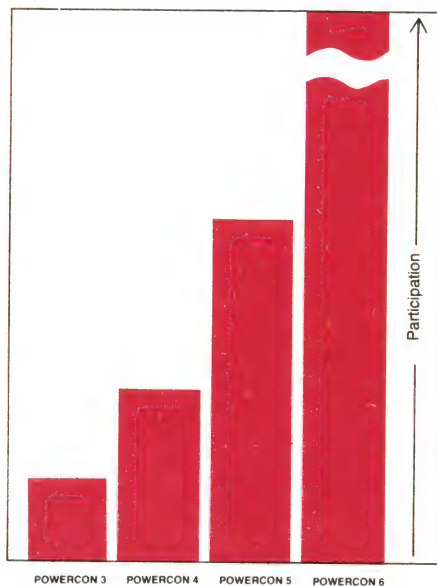The participation in POWERCON's has more than doubled each year since 1976. And POWERCON 5 sold out.



POWERCON. Once a technical luxury. Now a professional and practical necessity.

The Conference.

Sixth in a series of annual national technical conferences devoted exclusively to the practical design and application of solid-state power conversion equipment and components. Emphasizing the modern trend to switched-mode and other "non-dissipative" technologies, the POWERCON 6 conference offers a comprehensive and intensive three-day examination of the latest and most important developments in the power conversion field.

- Three full days of technical presentations.
- Over 30 papers, presented by outstanding authorities.
- Nine sessions, chaired by distinguished experts.
- VMOS... Proportional drive... Sinewave synthesis... Micro-processors as feedback elements... Controlled resonant conversion... Reliability... Computer-aided design... High voltage... EMI... Non-dissipative load-line shaping... Motor control... plus much, much more.

The Tutorial Exhibit

Informal tutorial and "hands-on" (fully instrumented and working) demonstration exhibits presented by technologists from over 50 major suppliers in and to the power conversion field. Each exhibit is specifically configured to enhance your technical expertise through improvement of your detailed knowledge of the supplier's technology and processes.

- Investigate working circuits and waveforms.
- See new devices in action.
- See working demonstrations of new power conversion topologies.
- See new instrumentation and test equipment for power conversion.
- Magnetics. Capacitors. EMI/RFI. Heat transfer. IC's and hybrids. Complete power supplies and inverters. Motor controls.
- and much, much more.



Leadtime Index

PASSIVE COMPONENTS

PRODUCT	LEADTIME IN WEEKS			PRODUCT	LEADTIME IN WEEKS		
	Min	Max	Trend		Min	Max	Trend
CAPACITORS				Single-sided	7	10	=
Ceramic, disc	6	12	=	RELAYS AND TIMERS			
Ceramic, monolithic	8	14	=	Crystal can	11	15	up
Electrolytic, aluminum	9	15	=	General purpose	6	9	=
Electrolytic, tantalum	8	11	=	Reed, dry	7	11	=
Film	7	12	=	Reed, mercury-wetted	7	10	=
Mica	11	18	up	Solid state	5	7	=
Paper	9	14	up	Telephone	7	13	=
Trimming	7	10	=	Time delay and timer	8	11	=
CRYSTALS, FILTERS AND NETWORKS				RESISTORS, FIXED			
Filter, active	7	10	=	Carbon film	4	6	=
Filter, EMI	14	16	=	Composition	4	8	=
Filter, lumped-constant	10	13	=	Metal film	11	16	up
Filter, quartz (monolithic)	12	16	up	Network	14	22	↔
Frequency determining crystal	10	12	up	Nonlinear	10	14	=
ENCLOSURES				Wirewound	10	14	=
Custom	9	12	=	RESISTORS, VARIABLE			
Modified standard	8	12	up	Pot, nonprecision WW	10	12	=
Standard	6	8	up	Pot, precision WW	14	16	=
FANS AND BLOWERS	20	24	↔	Pot, nonprecision comp	6	8	=
FRACTIONAL HP MOTORS	14	18	=	Pot, precision comp	10	14	=
INTERCONNECTION COMPONENTS				Trimmer, WW	9	12	=
Back panel	4	12	up	Trimmer, comp	7	11	=
Flat cable	4	12	up	SWITCHES AND KEYBOARDS			
Multipin circular high-density	14	19	up	Circuit breaker	9	14	=
Multipin circular standard	12	18	up	Dual in-line	6	8	=
Packaging panel	4	12	up	Keyboard and keyswitch	7	10	=
PC, one-piece	4	12	up	Lighted pushbutton	9	12	=
PC, two-piece	4	12	up	Pushbutton	8	12	=
Rack and panel	4	12	up	Rotary	6	9	=
RF coaxial	11	16	up	Snap action	3	5	=
Socket	4	12	up	Thumbwheel	8	10	=
MAGNETIC COMPONENTS				Toggle	6	9	up
Coil	8	12	up	TRANSDUCERS			
Solenoid	7	12	up	Pressure	6	8	=
Transformer, power	8	12	up	Temperature	5	8	=
Transformer, other	7	12	=	WIRE AND CABLE			
PRINTED CIRCUITS				Coaxial	3	8	=
Double-sided	9	11	up	Flat and ribbon	4	6	up
Flexible	8	10	up	Single conductor hookup	4	8	=
Multilayer	12	14	=	Multiconductor	3	8	=

Leadtimes are based on recent figures supplied to *Electronic Business* magazine by a composite group of major manufacturers and OEMs. They represent the typical times necessary to allocate manufacturing capacity to build and ship a medium-sized order for a moderately popular item. Trends represent changes expected for next month.

"Choosing Intel gave us a twelve month jump on the competition."



Dr. Wang: "We were first with a unique, new approach to word processing—using microcomputers to implement distributed intelligence in multiple station systems. That approach has enabled us to increase our market share 50% a year in a market that's growing 40% a year. This year our word processing sales will pass \$100 million. In 1974 they were just \$9 million.

"We decided on Intel's 8080 microprocessor for our distributed logic system. Only Intel offered PL/M, the microcomputer programming language we needed to get our software written quickly. So quickly that we introduced our system a year ahead of any competition. And Intel's tools for programming have continued to help us offer our customers the high quality software they expect from Wang."

Intel's extensive microcomputer design tools have helped hundreds of companies just like Wang Labs capture the marketing advantage with Intel microcomputers and semiconductor memory.

Our Intellec® Microcomputer Development System makes it possible and profitable for companies like yours to take full advantage of the promise and potential of the microcomputer. For example, the world's most advanced microcomputer, our new 16-bit 8086, is the first and only 16-bit microcomputer supported by a high-level programming language—PL/M, part of the total 8086 software development package available for the Intellec system.

To begin writing your own success story, contact Intel Corporation, 3065 Bowers Avenue, Santa Clara, CA 95051 408/987-8080.



Intel's Intellec® Development System

intel® delivers.

Intelligent Display™ of microcomputer applications.



Lexicon™
LK-3000
Electronic translator


terminals. "Smart" games and appliances. Educational products, and more.

Use
Intelligent
Displays
in any

product that calls for alphanumeric. They'll reduce component count and cut costs dramatically. Since everything is encapsulated in a single package, design and production costs are

minimal. And because no display interface PC board is needed, component costs are typically reduced by 25%. Typical OEM volume pricing per digit will range from

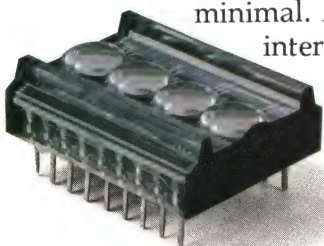\$2 to \$5 per digit, depending on display type. For easy bread-boarding with Intelligent Displays, ask about



our inexpensive, prewired Evaluation Kit. To get data sheets and a copy of our applications note



on Intelligent Displays, or for a demonstration, phone or write Litronix, Inc., 19000 Homestead Road, Cupertino, CA 95014. Telephone (408) 257-7910.

litronix

AN AFFILIATE OF SIEMENS

For more information, Circle No 17



The VTR's day in court

An important trial is currently underway in the Federal District Court in Los Angeles: the copyright-infringement suit brought by Universal Studios and Walt Disney Productions against Sony Corp. At issue is the use of the Betamax videotape recorder (VTR) to record and replay copyrighted material—in this case, movies produced by the two studios and broadcast on TV. Meanwhile, VTR buyers remain totally

unaware that the outcome of this suit might determine the manner in which they can legally operate their versatile home-entertainment equipment.

Lawyers for the plaintiffs claim that studios, advertisers and creative employees will suffer economic hardships because VTR recordings will significantly reduce the audiences for live TV programming. Replying to this argument, Sony's lawyers challenge the validity of all copyrights related to TV-broadcast material, then cite surveys indicating that most VTR users record programs intact (with commercials) for viewing at a more convenient time, not to build permanent libraries of material.

Against the background of this court trial, MCA (Universal's parent company) and Magnavox have launched a program to market the video-disc player, the VTR's prime competition. A read-only device, the video-disc machine uses special "records"—rugged media containing appropriately copyrighted material. Initial sales of the player are encouraging, thanks to three factors: the availability of considerable "software" (discs containing a wide spectrum of entertainment); the unit's novel operating features, including stop frame; and the rugged nature of the medium. The last factor, incidentally, could encourage the development of a significant swap/sell used-disc market and thus greatly reduce owner costs.

Final disposition of the court case, however, remains some time in the future, because after the judge hands down his ruling (promised within 90 days of final arguments) an appeal to the US Supreme Court is possible. And beyond that, Congress might have to address this public-policy issue.

Yet all this legal maneuvering could be academic. If the VTR/video-disc consumer market develops to a significant size, as it quickly might, and if buyers overwhelmingly choose one video-recording concept over the other, lawyers and lawmakers will be forced to reconfigure the law to accommodate the established reality.

An Award*-Winning Magazine
1978 Staff-Written Series —
System Design Project
1978 Contributed Series —
Designer's Guide to Fiber Optics
1977 Contributed Series —
Software Design Course
1976 Special Issue —
Microprocessor Reference Issue
1975 Staff-Written Series —
Microprocessor Design Series

*Jesse H Neal Editorial Achievement
Awards are the business-press Pulitzer
Prize equivalent.

Walt Patstone
Editor

monolithics lexicon



Selectivity: The ability to accept signals within a specified frequency band while rejecting all others. Formerly a problem. See monolithic crystal filter.

Monolithic crystal filter: The solution to most selectivity problems in radio communication. See PTI. Their filters define the best and most economical in the field. Dozens of standard models, or custom production models from 5 to 180 MHz. Write for their catalog.

The standard in monolithic crystal filters.


WE WROTE THE BOOK.

Pti

Piezo Technology Inc.

2525 Shader Rd., Orlando, FL 32804
(305) 298-2000

For more information, Circle No 21

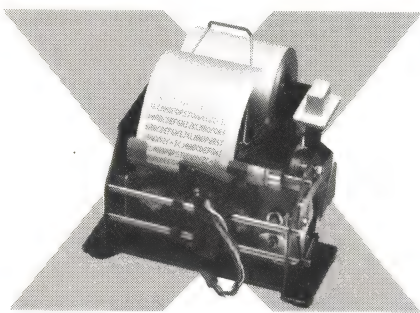

Fast reliable printer.

The DC-1606B/DC2106D discharge printer prints 16 or 21 column alpha numerics in a 5 x 7 dot matrix format. Its MTBF is 3.0 million lines on 2.25" paper costing about 1/2¢ per foot. Just 3.8" H x 5.4" W x 5.5" D, it is as low as \$120 in 100 quantity. Interface electronics, other printers available.

Call or write HYCOM, 16841 Armstrong Ave., Irvine, CA 92714 — (714) 557-5252

HYCOM


For more information, Circle No 22

Closer LCD Contacts

with STAX Elastomeric Connectors
—up to 50 display contacts per inch!

Many millions now in use in watches, calculators, digital voltmeters, clocks, etc. STAX provide multiple, redundant paths for each connection, permitting wider tolerance for pad alignment.

Here's how it works:

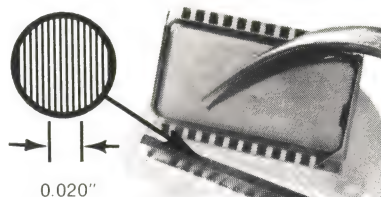

Black layers are conductive silicone rubber; white layers are non-conductive. Each layer is approximately 0.002" thick. Current travels from circuit contact pad below to display contact pad above through one or more conductive layers.

Call or write for literature, samples or quote.

Hulltronics, Inc.

Davisville Road, Hatboro, PA 19040
215-672-0787

For more information, Circle No 25

Staff

Executive VP/Publisher
H Victor Drumm

Editorial Director
Roy Forsberg

Editor
Walt Patstone

Managing Editor
Jordan Backler

Special Features Editors
Bob Cushman
Jim McDermott

Editorial Staff
Earle Dilatush, *Senior Editor*
Tom Ormond, *Senior Editor*
Jack Hemenway, *Associate Editor*
Bob Peterson, *Associate Editor*
David Ranada, *Associate Editor*
Edward Teja, *Associate Editor*
Dale Zeskind, *Contributing Editor*
Jesse Victor, *Senior Copy Editor*
Randall Howe, *Copy Editor*
Joan Morrow, *Editorial Assistant*

Western Editorial Offices
Sam Davis, *Manager South*
Andy Santoni, *West Coast Editor*

Consulting Editor
Carol A Ogdin

Art Staff
Daniel S Kicilinski, *Director*
Denise Duben, *Assistant*
Wasy Bidalack, *Illustrator*
Bill Lindsay, *Illustrator*
Vicki Blake, *Illustrator*

Production Staff
Wayne Hulitzky, *Director*
Bill Tomaselli, *Supervisor*
Pamela Gordon, *Assistant*

Circulation
Earl Mosley, *Manager*


Research
Ira Siegel, *Vice President*

Editorial Consultant
John Peter

Editorial Office Addresses
Boston (617) 536-7780, 221 Columbus Ave, Boston, MA 02116. **New York** (212) 949-4416, 205 E 42nd St, New York, NY 10017. **San Francisco** (408) 377-6777, Pruneyard Towers, 1901 S Bascom St, Suite 1100, Campbell, CA 95008. **Los Angeles** (213) 347-2123, 22543 Ventura Blvd, Suite 222A, Woodland Hills, CA 91354.

Reprints of EDN articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Art Lehmann, Cahners Reprint Service, 5 S Wabash, Chicago, IL 60603. Phone (312) 372-6880.

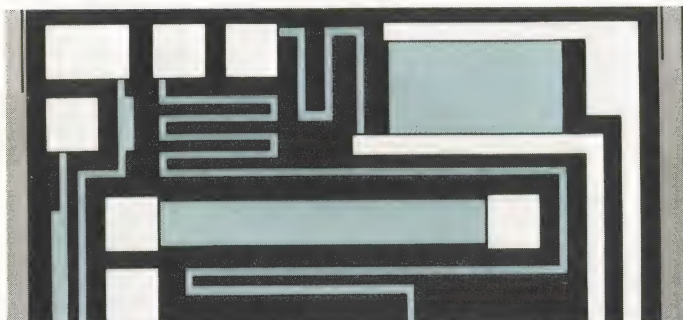
Hybrid Systems Precision Resistors: Less Cost, Less Space, Less Hassle



Chips . . . a million in stock right now.

Single value center tapped. Standard absolute tolerances to 1% (custom to 0.1%). Typical $\pm 2\text{ppm}/^\circ\text{C}$ tracking. Standard RETMA values from 10Ω to $301\text{K}\Omega$. Also standard and custom networks . . . 10, 20, 30 or more resistors per chip . . . combined resistance 2, 3, 4 $\text{M}\Omega$ or more. Processed to MIL-STD-883 or commercial.

For more information Circle No 33

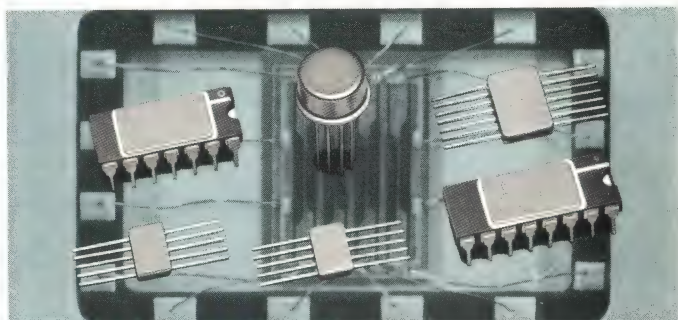

Packaged Networks . . . to your specs . . . or from our library of over 500 mask sets.

Standard R/2R networks or custom arrays. Computer laser trimming, absolute values to 0.1%, ratios to 0.01%, $\pm 2\text{ppm}/^\circ\text{C}$ tracking. Hermetic TOs, DIPs, and flat packs. MIL-STD-883 or commercial processing.

For more information Circle no 34

The largest producer of thin-film resistors in the world, Hybrid Systems can deliver 100,000 center tapped chips or 25,000 network chips per customer per week. More than a decade of experience and state-of-the-art thin-film processing technology keep us on top.

Whatever the challenge, on land, sea, or in the air — in commercial/industrial and military applications — Hybrid Systems meets the highest standards for reliability and performance. The quality control begins on the drafting board, continues through every step of the manufacturing process — and never quits.

For fast results, call or write. Or circle the number(s) on the reader service card.

When the chips are down . . .


Hybrid Systems

CORPORATION

Crosby Drive,
Bedford, MA 01730
Phone (617) 275-1570
(TWX 710-326-7584
HYBRIDSYS BFRD)

In Europe: Hybrid Systems GmbH.
61 Darmstadt, Luisenplatz 4, Germany
Tel. 6151-291595
(TELEX 419390 HYSY D)

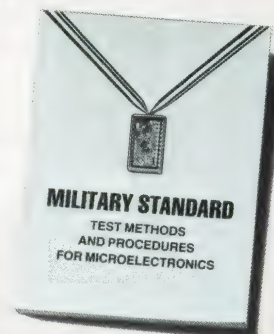In the United Kingdom:
Hybrid (Component) Systems U.K. Ltd.
12A Park Street, Camberley, Surrey
Tel. (0276) 28128
(TELEX 858720 HYBRID G)



Microcomputer Design Courses

Hardware, software, systems design. You can now learn about all aspects of microcomputers through EDN's exclusive design courses.

NEW 1978 Microcomputer Systems Reference Issue (420 pages) **\$5.00**

Features: EDN's 7-chapter "Software Systems Design Course" (a step-by-step tutorial for a μ C disc operating system), μ P Directory, μ C Support Chip Directory, μ C Board Directory.

1977 Microcomputer Systems Reference Issue (314 pages) **\$4.00**

Microcomputer Design Course (11 chapters, 83 pages) **\$4.00**

(Add \$1.00 to each of the above for non-USA)

Buy in combination and save even more

Any two items — Deduct \$1.00

Any three items — Deduct \$2.00

Payment must be included with your order. Make checks payable to: EDN Reprints

Send to: **μ C Reprints / EDN Magazine** / 221 Columbus Ave. / Boston, MA 02116

Please send:

_____ copies 1978 μ C Systems Reference Issue — \$5.00

_____ copies 1977 μ C Systems Reference Issue — \$4.00

_____ copies μ C Design Course — \$4.00

Total \$ _____ (Non-USA, add \$1.00 to each item)

Check or money order must accompany each order. No COD. MA residents add 5% Sales Tax.

Send to:


Name _____ Title _____

Company _____

Address _____

City _____ State _____ Zip Code _____

Quality, at any price.

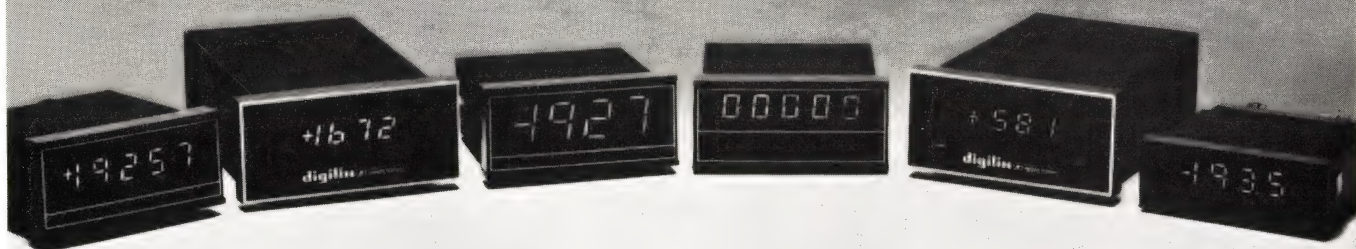

From low cost DPM's to sophisticated digital panel instruments.

Dynamic Sciences manufactures panel meters—a complete line of panel meters. From our brand new \$29.95 model 72 (in OEM quantities) which outperforms any meter in its class, to our microprogrammable non-linear indicators at the top of the line.

In between, we have a full range of counters, meters and instruments to handle all your needs. And each instrument we sell reflects a

total commitment to produce a superior quality product, at a price that can't be matched.

Call today for an evaluation unit or to discuss your particular applications. Or send for our new short form catalog.

Dynamic Sciences
16150 Stagg Street, Van Nuys, CA 91406
(213) 893-6341 TWX 910-495-1780




Dynamic Sciences

We also manufacture former Fairchild Models 53, 70, 75, 78, 40, 54, & 55.

For more information, Circle No 26

The big switch

**...is to
full cycle holdup.**

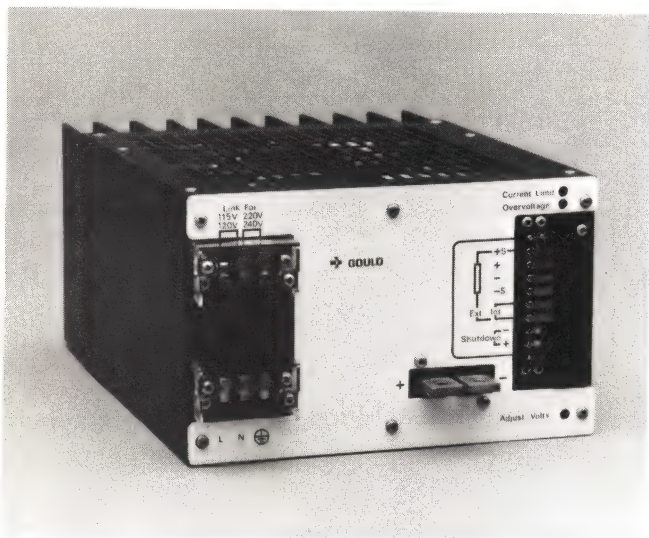

The 500 watt MG5-100: 28 millisecond holdup.

Switching power supplies offer substantial holdup. Linears don't.

A Gould switcher will give you full regulated output at -20% line. Or during complete loss of power you'll get full output power for more than a missing line cycle.

Switchers offer other benefits too. They're 1/3 the size and 1/4 the weight of linears.

And they save energy with efficiencies of up to 85%.

Gould offers single and multiple output switchers with power levels from 8 to 2,250 watts. Custom designs can be provided to meet your exact specifications. You'll be backed by a high volume production capability and worldwide service network that only a \$1.6 billion company like Gould could offer.

For more information or to arrange for an evaluation unit, contact Gould Inc., Electronic Power Supply Division, P.O. Box 6050, El Monte, CA 91731. Phone (213) 575-4777.

For more information, Circle No 27

Gould.
The power in switching power supplies.

 **GOULD**

Technology News

Alternative production technologies promise increased solar-cell use

Dale Zeskind,
Contributing Editor

Solar-cell researchers are investigating a variety of alternative cell technologies, which could lend themselves to less expensive production requirements than current designs. If these researchers succeed in their efforts, photovoltaic energy conversion — once limited primarily to outer-space applications—will quickly be brought to earth in a variety of terrestrial uses.

The US Department of Energy (DOE) is aiding these research efforts. Through its National Photovoltaic Program, the DOE aims to ensure that photovoltaic conversion systems

significantly contribute to the nation's energy supply by the year 2000.

Today, ten US manufacturers produce single-crystal silicon cells and cell

arrays (modules). Unfortunately, these cells require energy- and time-consuming, labor-intensive manufacturing techniques, so their costs are high—on

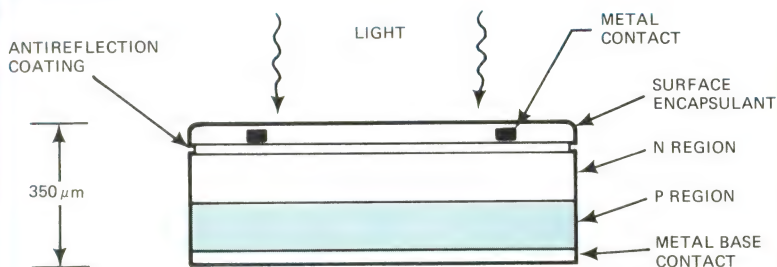


Fig 1—Conventional pn-junction silicon solar cells, made from a wafer of high-quality single-crystal silicon, are commercially available, though expensive. Efficiencies for these cells range between 10 and 15%; the US Dept of Energy hopes that improvements in manufacturing processes and/or the use of alternative cell technologies will eventually make photovoltaic energy conversion cost-competitive with other forms of electric-power generation.


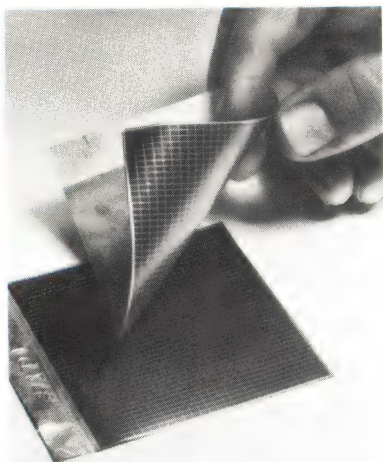


Fig 2—Thin-film solar cells could sell for \$0.25/W (1975 dollars) by 1982. Produced by vapor deposition of CdS onto plastic- or metal-film substrates, these cells readily adapt to continuous-processing techniques. (Courtesy Institute of Energy Conversion)

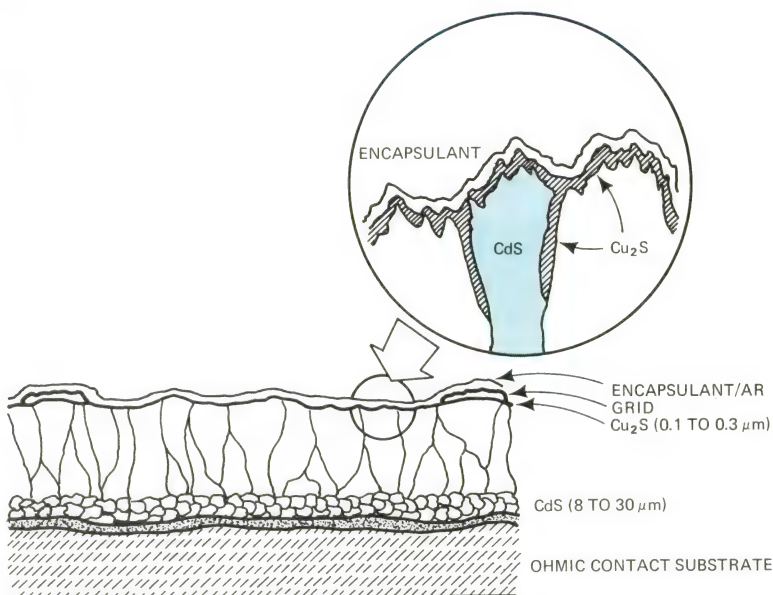

the order of \$12/W. This high cost limits the terrestrial use of conventional cells to geographically remote applications, such as radio repeaters and navigational aids.

As part of its program, however, the DOE has set a cost goal of \$2/W by 1982 and \$0.50/W by 1986 (in 1975 dollars). At the latter price level, photovoltaic systems should compete for some distributed and larger-load-center utility applications. The resulting increased demand would encourage large-scale cell production and spur a further improvement in availability and cost.

Thin films offer promise

A conventional pn-junction silicon cell (Fig 1) is made from a thick wafer of high-quality single-crystal silicon cut from a slowly grown ingot. (The cutting process turns much of the material to dust—an additional drawback to conventional cell technology.)

After this cutting step, the wafers must be polished, their pn junctions grown by means of high-temperature diffusion, and the necessary contacts plated. These conventional cells have typical solar-to-electric-power conversion efficiencies of 10 to 15%.

To reduce manufacturing costs, one experimental cell-fabrication technique uses single-crystal silicon grown from continuous sheets rather than ingots. Such sheets require less polishing than the conventional ingots, and less material is wasted during cutting.

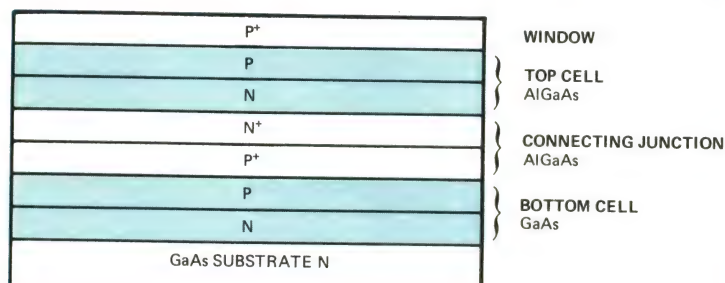


Fig 3—Stacking cells monolithically improves solar-to-electric-power conversion efficiency. But the approach requires optimizing the cells to respond to different portions of the solar spectrum. Each layer is approximately 1 to 2 μ m thick. (Courtesy Research Triangle Institute)

The CdS/Cu₂S thin-film cell pictured in Fig 2, for example, is constructed by vapor-depositing a thin-film CdS layer onto a thin metal substrate or metallized plastic film. Reaction in a solution of CuCl forms the Cu₂S layer.

These cells consume miniscule amounts of materials in their fabrication, and their construction lends itself to continuous (as opposed to batch-type) processing. J D Meakin, director of solar-cell research at the University of Delaware's Institute of Energy Conversion in Wilmington, reports that the CdS/Cu₂S cells are theoretically capable of achieving 16% conversion efficiencies; the practical goal is an 11% figure.

Meakin has to date observed efficiencies as high as 9.15% and hopes to exceed 10% some time this year. His group is currently designing a pilot production plant that he expects will demonstrate the feasibility of producing these or similar cells at a selling price of \$0.25/W by 1982.

Composite methods

Most solar cells respond efficiently only to a limited portion of the solar spectrum, so much of the light that strikes them converts to heat rather than electricity. To solve this problem, researchers have built cells that respond to different portions of the spectrum. Then, by spectrally splitting the incident light and directing the appropriate portions of it to the proper cells, they have improved overall system conversion efficiency.

A group at the Research Triangle Institute, Research Triangle Park, NC, recently achieved a significant advance with this approach. The group fabricated two spectrally tailored cells monolithically; the cells are deposited one on top of the other and internally connected so they operate in series, both optically and electrically (Fig 3).

This structure's layers are grown by liquid-phase epitaxy (LPE). The heavily doped connecting region acts as a tunnel diode, providing a low-impedance electrical

path between the two cells.

Researcher S M Bedair reports observing 15% conversion efficiencies in these experimental stacked cells, and he expects to achieve efficiencies of up to 30% within the next 2 yrs—a figure that makes this approach attractive despite its complexity.

As an added benefit, the stacked cells have an open-circuit voltage of 2V, compared with 0.7V for conventional silicon cells. As a result, they can deliver more power than the conventional units at a given current level.

Increasing concentration

Rather than reducing cell-manufacturing costs, several laboratories hope to meet the DOE's goals by taking a system-optimization approach. They aim at demonstrating cost effectiveness by utilizing extensive optical systems to

concentrate sunlight onto cells.

In such systems, because the cost of the cell is a relatively small part of total system cost, system designers can freely use highly efficient (though costly) cells; the stacked-cell concept could prove particularly well suited to these concentrator applications.

Researchers are also developing unusual new materials for solar-cell applications. For example, Energy Conversion Devices recently unveiled an amorphous (noncrystalline) material which it claims could serve as the basis for a low-cost class of cells. However, other solar-cell researchers find it difficult to evaluate the Troy, MI company's claims because it has failed to release sufficient data.

In another development, investigator M J Cohen of Rockwell International, Thousand Oaks, CA, has

reported on the development of the first polymer/GaAs Schottky-barrier cell—one with output voltages about 40% higher than those of metal/GaAs cells. The latter devices have also been investigated as low-cost replacements for silicon cells.

Is silicon doomed?

In light of all of these recent solar-cell developments, do single-crystal silicon cells have any future? Most researchers agree that these conventional cells will play a major interim role in energy conversion for at least the next 10 yrs; silicon technology has been refined considerably over the past 20 yrs, and a sizable industry already exists.

Which of these new technologies will dominate? Most observers agree that no one technology will "win"; instead, most expect several complementary approaches to develop. **EDN**

Switching-power-supply improvements will dominate Powercon 6

Sam Davis, Manager,
Western Editorial Office (S)

Power-conversion design techniques—many of them relating to switching supplies—will provide the main attraction at Powercon 6. Highlighting the more than 30 papers, 60 exhibits and several short courses will be "how-to" presentations on

- A 1-kW on-line switcher

- A simple method to correct switcher power factors from 0.6 to almost unity
- An 8048- μ P-controlled switcher
- Computer modeling of semiconductor power-supply components.

Innovative switcher design

The most important Powercon presentations could well be those describ-

ing a 1-kW (60V at 15A) on-line switching power supply that inherently eliminates pulsating currents in both its input and output. The unit thus requires no input filtering and no output-filter capacitor. This switcher is the first application of a concept—termed optimum topology—described in 1978 at Powercon 5 by Assistant Professor Slobodan Čuk of the Califor-

nia Institute of Technology, Pasadena.

Prof Ćuk, assisted by graduate students Loman Rensink, Art Brown and Shi-Ping Hsu, will report on such design considerations as component sizing, methods of driving the power switch and the choice of the switcher's transformer turns ratio. This last factor is the result of a tradeoff between the switcher's ON current and OFF voltage.

In a tutorial seminar scheduled for the day before the conference, Prof Ćuk

and Prof R D Middlebrook, also of Cal Tech, will explain how to model a switching converter and measure the magnitude and phase of the device's small-signal response in the presence of high switching noise. And because many engineers have trouble measuring these response parameters, according to Middlebrook, he and Ćuk will demonstrate on an actual power supply.

Middlebrook will also explain how to analyze the response-measurement results, and he will present a

small-signal model of the converter and regulator. Generally, he intends to show how designers can apply simple, physically interpretable analytic techniques to real circuits to obtain correspondingly simple, useful and practical design criteria.

Reduce line current

Another switching-supply-related paper will detail a dynamic power-factor (PF) correction technique that reduces line current below values possi-

Powercon 6: Who, what, when, where

Powercon 6 will be held May 1-4 at the Fountainebleau-Hilton Hotel in Miami Beach, FL. The conference is sponsored by Power Concepts Inc, a consulting and educational firm specializing in applied power-conversion technology, and will be chaired by the firm's president, Ronald I Birdsall.

You can obtain additional Powercon information by contacting Powercon 6, Box 5226, Ventura, CA 93003. Phone (805) 985-6978.

Tutorial short courses

In addition to its exhibits and papers, Powercon 6 will also offer a number of short courses oriented toward power-supply designers, including:

- A high-frequency-magnetics design course presented by members of the Magnetic Material Producers Association; it will focus on available magnetic materials and their limitations
- A course on high-frequency (over 400 kHz) converters that reduce the size and weight of subsystems usually required in a switcher (EDN, January 20, pg 44), delivered by Rudy Severns, VMOS applications manager at Intersil, Cupertino, CA

- A presentation on the causes of—and methods for controlling—EMI/RFI, by Edith Kamm, an EE at the Naval Ocean Systems Center, San Diego, CA
- A practical circuit-design technique for controlling a power supply's frequency response—including a simple method for transient-response design—shown by Bill Wise, president of WIC Inc and a member of the EE staff at Lawrence Livermore Labs, Livermore, CA
- A short course on power-supply testing presented by Robert Cox, VP of Autotest, San Antonio, TX, and Jim Burens, president of California DC, Westlake Village, CA.

The more than 60 exhibits at Powercon 6 will include such offerings as a demonstration of supply transient response using an electronic load by ACDC Electronics; automated power-supply testing by Autotest; new VMOS power FETs by International Rectifier, El Segundo, CA; isolated-case power transistors by General Semiconductor Industries, Tempe, AZ; μ P power supplies by Texas Instruments, Dallas; Silicon General's power hybrids; a safe-operating-area transistor tester from Hewlett-Packard; and Cal Tech's 1-kW switcher.

Surprise!



2 KHz-1500 MHz Power Splitter/Combiners

OFF-THE-SHELF FOR IMMEDIATE DELIVERY...

FROM **\$31.⁹⁵** (4-24)

Satisfy just about any two-way power-splitter/combiner need with Mini-Circuits ZFSC-2 series. . . covering 2 kHz—1500 MHz, with a choice of BNC, TNC, SMA or Type N connectors. Also, three convenient mounting options are available; threaded inserts, through holes, and flange mounting. Units are available from stock for immediate delivery and prices start at only \$31.95. Mini-Circuits extensive experience in high volume manufacturing, coupled with exacting quality control and thorough testing makes this price/performance breakthrough possible.

Examine your power splitter/combiner specifications and select a highly reliable, low-cost ZFSC-2 model to meet your systems requirements.

Model	Freq. Range (MHz)	Minimum Isolation (Mid-band)	Maximum Insertion Loss (Mid-band)	Price (Quantity)
ZFSC-2-1	5-500	20 dB	0.6 dB	\$31.95 (4-24)
ZFSC-2-1W	1-750	20 dB	0.8 dB	\$35.95 (4-24)
ZFSC-2-2	10-1000	20 dB	1.0 dB	\$39.95 (4-24)
ZFSC-2-4	0.2-1000	20 dB	1.0 dB	\$44.95 (4-24)
ZFSC-2-5	10-1500	20 dB	1.0 dB	\$49.95 (4-24)
ZFSC-2-6	.002-60	20 dB	0.6 dB	\$36.95 (4-24)

BNC connectors standard. TNC, SMA & Type N also available. SMA and Type N \$5.00 additional.

World's largest manufacturer of Double-Balanced Mixers

Mini-Circuits
MINI-CIRCUITS LABORATORY
A Division of Scientific Components Corp.

2625 East 14th Street Brooklyn, New York 11235 (212) 769-0200
Domestic and International Telex 125460 International Telex 620156

International Representatives: ☐ **AFRICA:** Alitra (PTY) Ltd. P.O. Box 9813, Johannesburg 2000, S. Africa. ☐ **AUSTRALIA:** General Electronic Services, 99 Alexander Street, New South Wales, Australia 2065. ☐ **ENGLAND:** Dale Electronics, Dale House, Wharf Road, Frimley Green, Camberley Surrey. ☐ **EASTERN CANADA:** B.D. Hummel, 2224 Maynard Avenue, Utica, NY 13502 (315) 736-7821. ☐ **FRANCE:** S.C.I.E. - D.I.M.E.S. 31 Rue George - Sand 91120 Palaiseau, France. ☐ **GERMANY, AUSTRIA, SWITZERLAND, DENMARK:** Industrial Electronics GMBH 6000 Frankfurt/Main Klüberstrasse 14 West Germany. ☐ **INDIA:** Gaekwar Enterprise, Kama Mahal, M.L. Dananukar Marg, Bombay 400 026, India. ☐ **ISRAEL:** Vectronics, Ltd., 69 Gordon Street, Tel-Aviv, Israel. ☐ **NETHERLANDS, BELGIUM, LUXEMBOURG:** Coimex Veldweg 11, Hattern, Holland.

☐ **NORWAY:** Datamatik AS, Ostensjoveien 62, Oslo 6, Norway. ☐ **SINGAPORE & MALAYSIA:** Electronics Trading Co. (PTE) Ltd., 87 Bukit Timah Road, Singapore 9, Malay Peninsula. ☐ **SWEDEN:** Intergrad Elektronik AB, Box 43, S-18251, Djursholm, Sweden.

U.S. Distributors: ☐ **NORTHERN CALIFORNIA:** PENN-STOCK Co., Foothill Office Center, 105 Fremont Avenue, Los Altos, CA 94022 (415) 948-6533. ☐ **SOUTHERN CALIFORNIA, ARIZONA:** Crown Electronics, 11440 Collins Street, No. Hollywood, CA 91601 (213) 877-3550. **NEW YORK:** NEW YORK MICROWAVE DISTRIBUTORS COMPANY, 61 Mail Drive, Commack, N.Y. 11725 516 543-4771

31/RevB

For more information, Circle No 28

Technology News

ble with conventional off-line switchers. As described by Derek Chambers, engineering manager of Sorensen Co, Manchester, NH, the technique can raise a typical supply's power factor from 0.6 to 0.95. As a result of this

PF correction, a supply originally drawing 18A would draw only 14A—an additional benefit for electronic equipment obtaining its power from lines equipped with standard 15A circuit breakers.

Chambers explains that off-line single-phase switchers typically impose a nonlinear power-line load produced by their rectifier/filter-capacitor inputs. To correct for this nonlinearity, his firm utiliz-

POWERCON® 6 CONFERENCE PROGRAM

WED MAY 2		THURS MAY 3	FRI MAY 4
8:30	SESSION A: THE POWER SUPPLY AS A SYSTEM ELEMENT Optimizing minicomputer power-subsystem design Design techniques for controlling the point-of-load high-frequency performance of power supplies Design techniques to limit EMI in switching-mode converters	SESSION D: HIGH-VOLTAGE AND HIGH-POWER TECHNIQUES Optimizing boost-chopper charger design Design techniques for miniaturized spacecraft HV supplies Eliminating power-supply interaction with high-power pulsed loads	SESSION G: SWITCHED-MODE CONVERSION: REDUCING ANALYTICAL METHODS TO PRACTICE Optimizing passive-input filter design Computer-predicted steady-state stability of pulse-width-controlled dc/dc converters Modeling and design of the Cuk converter
10:30	BREAK	BREAK	BREAK
11:00	SESSION B: CIRCUIT DESIGN TECHNIQUES Designing nondissipative current snubbers for switched-mode converters A new, improved and simplified proportional base-drive circuit Dynamic power-factor correction in capacitor-input off-line converters	SESSION E: CIRCUIT AND FUNCTIONAL INTEGRATION Toward a high-frequency, universal power switch Simplifying switching-regulator applications with a new class of self-contained hybrid regulators Functional power-conditioning modules: new building blocks for converter design	SESSION H: NEW DESIGN METHODS AND CONVERTER CONFIGURATIONS A μ P-controlled VMOS power supply Designing the off-line, high-efficiency venable converter Design of a kilowatt off-line switcher using a Cuk converter
1:00	LUNCH BREAK	POWERCON 6 LUNCHEON	LUNCH BREAK
3:00 TO 5:00	SESSION C: SEMICONDUCTORS FOR POWER CONVERSION Simplifying predictable converter design with CAD power-semiconductor models Using high-voltage power MOSFETs in off-line converter applications Applying ultrafast power thyristors in high-frequency-converter design	SESSION F: NEW DESIGN METHODS AND CONVERTER CONFIGURATIONS Reducing magnetic component size with reverse-biased ferrite cores A new PWM control technique that eliminates transformer-unbalance problems in power converters Designing improved high-frequency dc/dc converters with a new resonant thyristor technique A new technique for simplifying sine-wave-synthesis inverter design	SESSION I: SPECIAL POWER-CONVERSION TOPICS: ENERGY SYSTEMS AND RELIABILITY Optimizing solar photovoltaic power-system design Design techniques for achieving high reliability in switched-mode converters The effects of operating parameters on aluminum electrolytic capacitor reliability in switched-mode converters Factors affecting the application reliability of Schottky rectifiers
6:00 TO 7:30	INDUSTRY-SPONSORED COCKTAIL PARTY		

PROFESSIONAL ADVANCEMENT SEMINAR PROGRAM

TUES MAY 1	WED MAY 2	THURS MAY 3	FRI MAY 4
9:00 AM TO 5:00 PM Modeling and measurement of dc/dc switching converters and regulators <i>Dr R D Middlebrook and Dr Slobodan Cuk, California Institute of Technology</i>	2:00 PM TO 5:30 PM A simplified technique for achieving predictable closed-loop performance <i>W L Wise, Lawrence Livermore Laboratory, and president, WIC Inc</i>	8:30 AM TO 12:00N Designing very high-frequency VMOS FET converters <i>Rudolf Severns, VMOS applications manager, Intersil</i>	2:00 PM TO 5:30 PM Predicting and controlling EMI in state-of-the-art power converters <i>Edith Kamn, electronic engineer, Naval Ocean Systems Center</i>
9:00 AM TO 1:00 PM The "business end" of the business: market awareness <i>Chairman: Robert Boschert, President, Boschert Inc</i>			2:00 PM TO 5:30 PM Production verification of power-converter performance <i>Robert Cox, Autotest; James Burens, California DC; and Scott Noltenmeier, Intel</i>

There's much to be said about the Harris HM-6100 12-bit CMOS microprocessor system. Micro-12 says it all.


Sooner or later, you're going to evaluate the HM-6100 CPU family. You can do it now, simply and at low cost, with the new Harris Micro-12 printed circuit board. Fully assembled and tested, the compact Micro-12 is a complete CMOS system including the HM-6100 CPU, ROM and RAM memory, UART and Parallel I/O Port.

IC's produced with the Harris silicon-gate CMOS technology permit high speed, low power operation using inexpensive batteries.

Also, the HM-6100 emulates the software operation of the proven and widely used PDP-8/E* minicomputer. Other benefits include the use of new, low cost PDP-8 development systems, like the DECstation 78* and easy-to-program single-word instructions that significantly reduce development time.

Understanding of the Harris HM-6100 instruction set will come easily with the Micro-12. Uniquely, it interfaces with a teletype, CRT terminal or tape cassette. And its 8-digit display and 16-key keyboard are interactive, allowing direct program insertion, execution and examination.

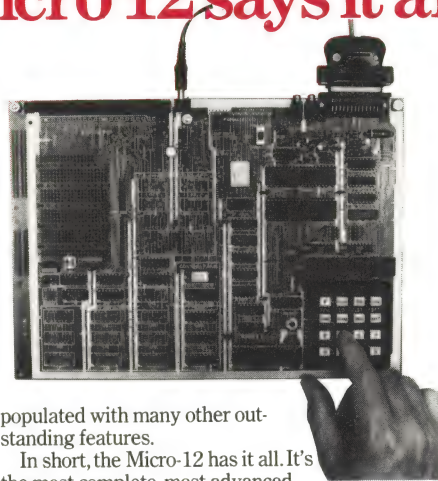For program debug, the Micro-12 has a system monitor with four independent breakpoints. Program memory includes a 256 x 12 RAM with space provided for expansion to 1K x 12, and the board—about the size of a magazine page—is



populated with many other outstanding features.

In short, the Micro-12 has it all. It's the most complete, most advanced CMOS microprocessor support system available in the industry. And it's easy to use.

To make it easier yet, you'll get a complete documentation package containing software/hardware examples and detailed information on use, theory and circuits when you buy your Micro-12 for just \$550.

Meantime, you can learn more about the Micro-12 and the HM-6100 family by calling


the Harris Hot Line. Or by writing Harris Semiconductor Products Division, P.O. Box 883, Melbourne, Florida 32901.

*Trademark of Digital Equipment Corporation

HARRIS HOT LINE!
1-800-528-6050, Ext. 455



Call toll-free (except Hawaii & Alaska) for phone number of your nearby Harris sales office or expedited literature service.

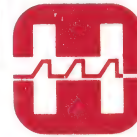*Harris Technology
... Your Competitive Edge*



HARRIS
SEMICONDUCTOR
PRODUCTS DIVISION
A DIVISION OF HARRIS CORPORATION

FUNCTIONAL BLOCK DIAGRAM.

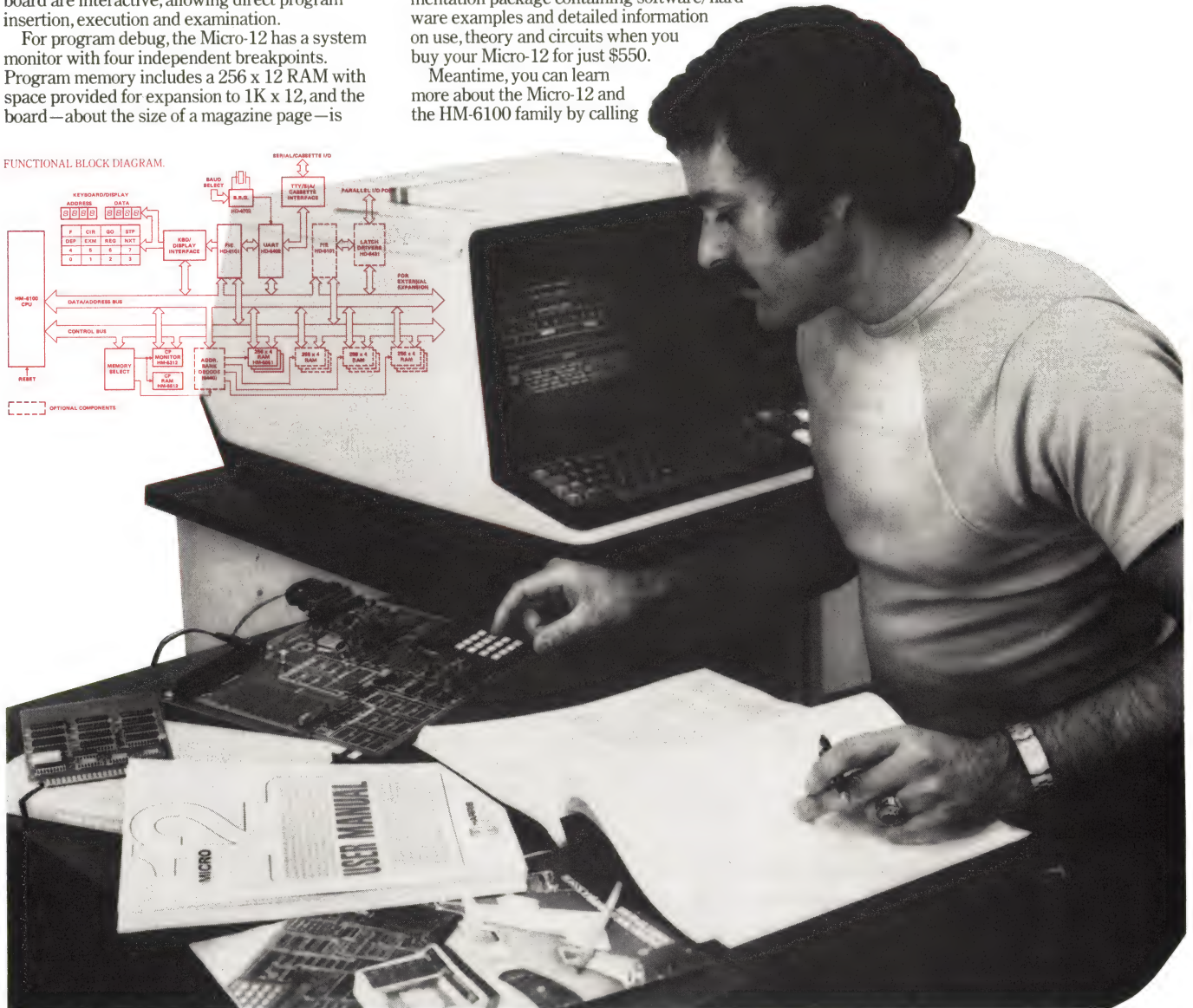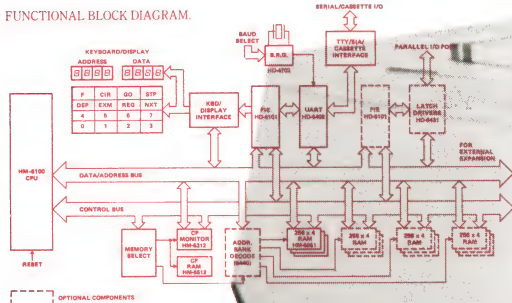

For more information, Circle No 29

es switching transistors and magnetic components that supply power from the line to the filter capacitor when the line voltage reaches about 30% of its peak value.


As a result, the capacitor current stays nearly in phase with the applied voltage for most of the power cycle; hence the supply's power factor improves almost to unity.

Sophisticated control

Another method of improving switching-supply performance utilizes an 8048 μ P, a PROM and a DAC to control a supply's regulation loop. Applications engineer Dave Hoffman, of Siliconix, Santa Clara, CA, will explain this control method, which also includes a firmware filtering algorithm to reduce line ripple.

The Siliconix unit's μ P generates a reference voltage (via the DAC) that's compared with the supply's output voltage. The comparator output then feeds back to the μ P, which responds with pulse-width-modulated control for the supply's VMOS power-FET switches. Thus, the system even allows keyboard control of the supply's output-voltage and waveform characteristics.

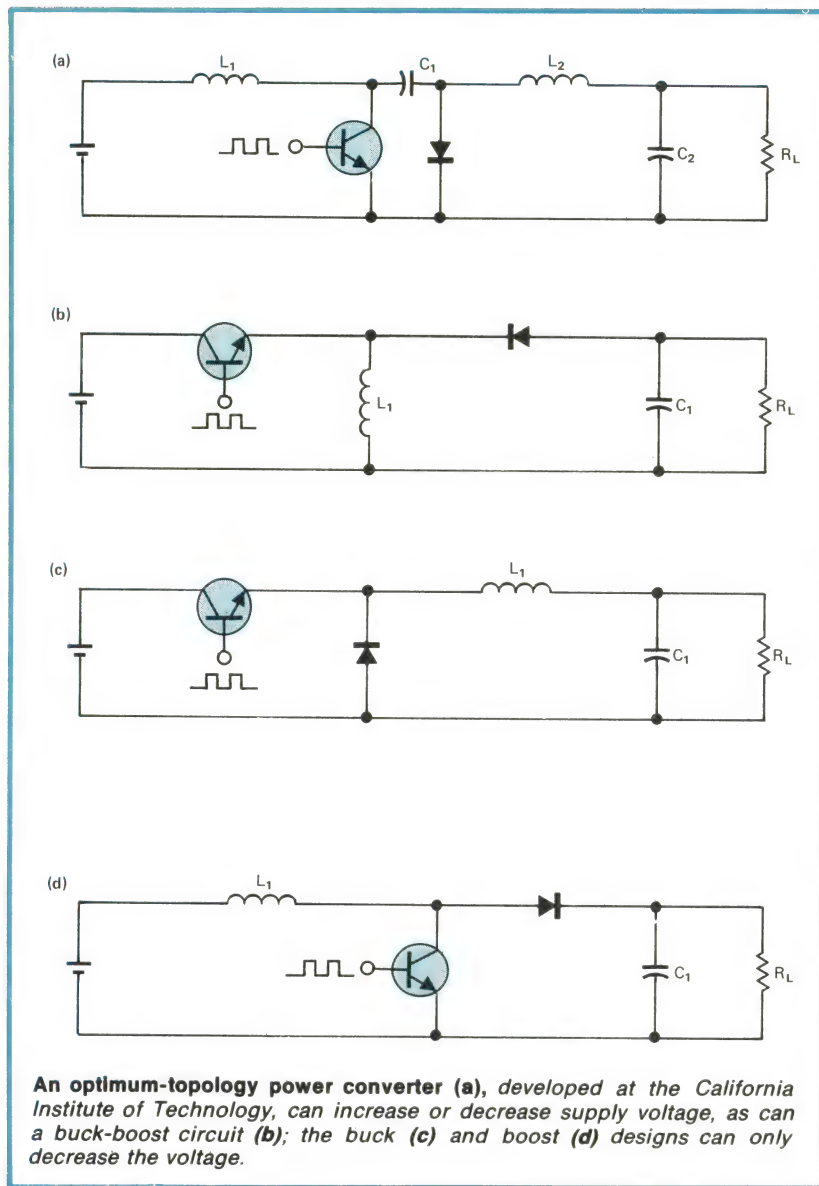Pulse-width modulation also eliminates transformer-imbalance problems in a switching supply scheduled for presentation by Walt Hirschberg, VP for product development at ACDC Electronics, Ocean-side, CA. He notes that these transformer imbalances can result from load-current modulation near the switching frequency and can cause



An optimum-topology power converter (a), developed at the California Institute of Technology, can increase or decrease supply voltage, as can a buck-boost circuit (b); the buck (c) and boost (d) designs can only decrease the voltage.

internal-component failure.

Building blocks


Circuit designers who would rather avoid some of the tedious component-level considerations associated with assembling a switcher might find an alternative in a family of switching-supply building blocks to be introduced at the show by Silicon General, Garden Grove, CA. Housed in 10-pin, $2.5 \times 1.5 \times 0.3$ -in. modules, these units can save assem-

bly time and money, as well as making RFI control easier because of their small size, according to applications manager Pete Wood. The hybrid modules dissipate up to about 3W—a figure made possible by a proprietary substrate with low thermal impedance.

One of the four modules contains a controlled phase-angle rectifier that charges an external input-filter capacitor to prevent large inrush currents. Another


Finally. Compatibility.

With Mostek's new 8K static RAM.

 Compatible with ROMs and EPROMs. Compatible with microprocessors. Mostek's new 8K static RAM offers total flexibility for your system. Organized as 1Kx8, the 4118 is a next generation Micro Memory,[™] available today.

It's a Micro Memory!

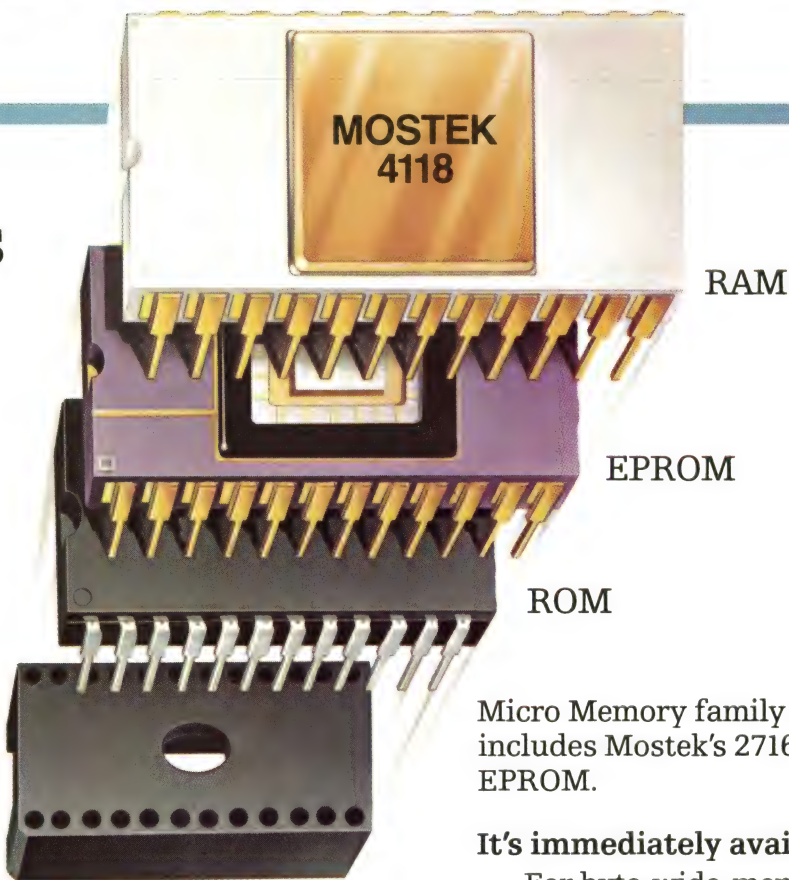Designed for 8-bit and 16-bit systems, the 4118 interfaces directly with all present and future generation microprocessors. A Chip Select control is provided for easy memory expansion and decoding, and internal latches are available to latch the Address and Chip Select inputs. If the Latch function is not needed, it can be easily bypassed. An Output Enable control provides easy user control of the



bus in all bus configurations. System design is simplified with the MK4118.

It's more than common!

With a pinout common to standard 24-pin ROMs, PROMs, and EPROMs, the 4118 still has more. Access time is a fast 120ns (max.) and power dissipation a low 200 mW (typ.). The 4118 is the newest addition to our compatible

Micro Memory family which includes Mostek's 2716 EPROM.

It's immediately available!

For byte-wide, memory applications requiring density, flexibility, and immediate availability, Mostek's 4118 is the one to choose. For the location of your nearest distributor, call 214/245-0266, Mostek Corporation, 1215 West Crosby Road, Carrollton, Texas 75006. In Europe contact Mostek Brussels; phone (32) 02/660.25.68.

MOSTEK[®]

module—a power-stage unit—accepts unregulated dc inputs from 100 to 400V at 10A; it operates between 50 and 100 kHz. The switching system's transformer and the output rectifier and filter are all external.

A bias-converter module supplies low-voltage power for the switching system's regulator circuit (which consists primarily of an SG1525 regulator IC). This low-power module operates from unregulated dc and produces a regulated output between 15 and 20V. The fourth module, a drive circuit still in development, amplifies the regulator IC's output to drive the power module.

Computer models help

A design-oriented Powercon paper that isn't restrict-

ed to switching power supplies will focus on the computer modeling of semiconductor power-supply components. Dr James Bowers, a professor at the University of South Florida in Tampa, will present a brief description of available computer-analysis programs, then describe his technique for measuring a power semiconductor's parameters, establishing its equivalent circuit and developing a corresponding computer model.

Dr Bowers and his colleagues have developed models for hundreds of diodes, SCRs, bipolar and MOSFET transistors, and integrated power op amps.

Engineers can use these models to save time and money when designing

power supplies, says Bowers. He notes that although a special device can often take 6 to 8 wks to obtain, an engineer using its computer model can accurately design a power-supply circuit on paper before receiving the part itself.

The models can also help determine a supply's worst-case design. "The computer model allows a variation of parameters—such as beta or collector current—and helps determine their impact on the circuit," Bowers notes. "There is no practical way to duplicate all the possible variations using the actual components." And, he adds, "We have never found a mistake in our computer-analysis technique." **EDN**

64-pin-chip packaging developers offer an alternative to JEDEC standard

Bob Peterson,
Associate Editor

Two manufacturers have joined forces to introduce a 64-pin quad-in-line packaging (QUIP) system that—compared with an equivalent DIP—saves pc-board space while still allowing easy access to the IC's pins for testing purposes. And although this packaging arrangement does not conform to the standardization guidelines proposed by JEDEC for space-saving IC packages (EDN, Sept 20,

1978, pg 119), it does offer certain advantages.

Developed jointly by Intel Corp, Aloha, OR, and 3M Co, St Paul, MN, the QUIP system consists of three parts: a zero-insertion-force socket with four rows of standard pins on 100-mil centers, a leadless ceramic chip carrier with two rows of leads on 50-mil centers and a metal clip that holds the chip carrier's contacts against the socket's contacts. The clip also helps dissipate heat generated by the chip.



While the 64-pin QUIP

requires less pc-board area than a DIP (2.1 vs 3.5 in.², respectively), the closest equivalent package suggested by JEDEC requires even less board area (1.4 in.² for a 68-pin device). On double-sided pc boards, however, the QUIP can save space by allowing designers to run traces between its leads. And because it also permits use of standard wave-soldering techniques in board fabrication, the QUIP can serve, in many cases, as an economical packaging scheme. **EDN**

Interested in network variety? Select from a spectrum of 542 standards.

Allen-Bradley has the popular configurations you need. Pull-ups, Pull-downs. Line Terminators. Networks to complement Core Memory Sense Amplifiers. TTL to ECL Translators. O-Pad Attenuators. R/2R Ladders. Interconnect Networks. All styles available from your Allen-Bradley *Electronic Distributor*. Call for specs or check your EEM Catalog.

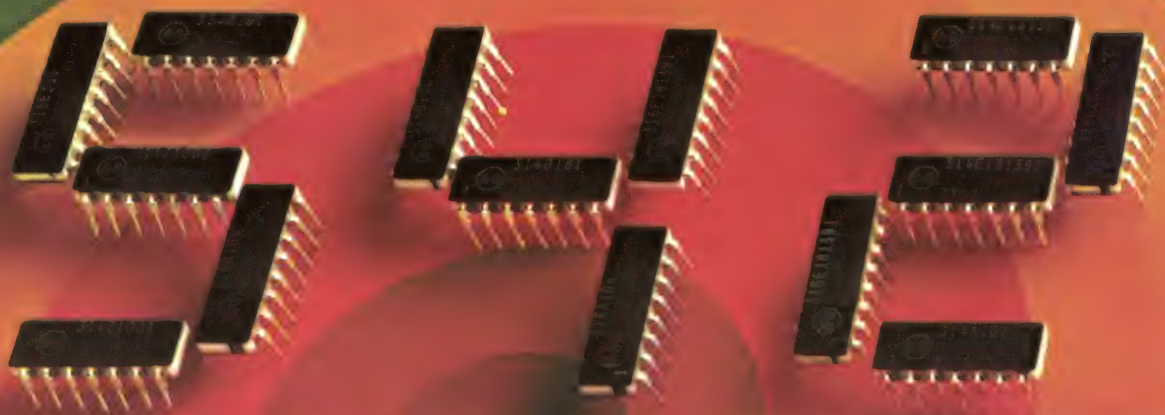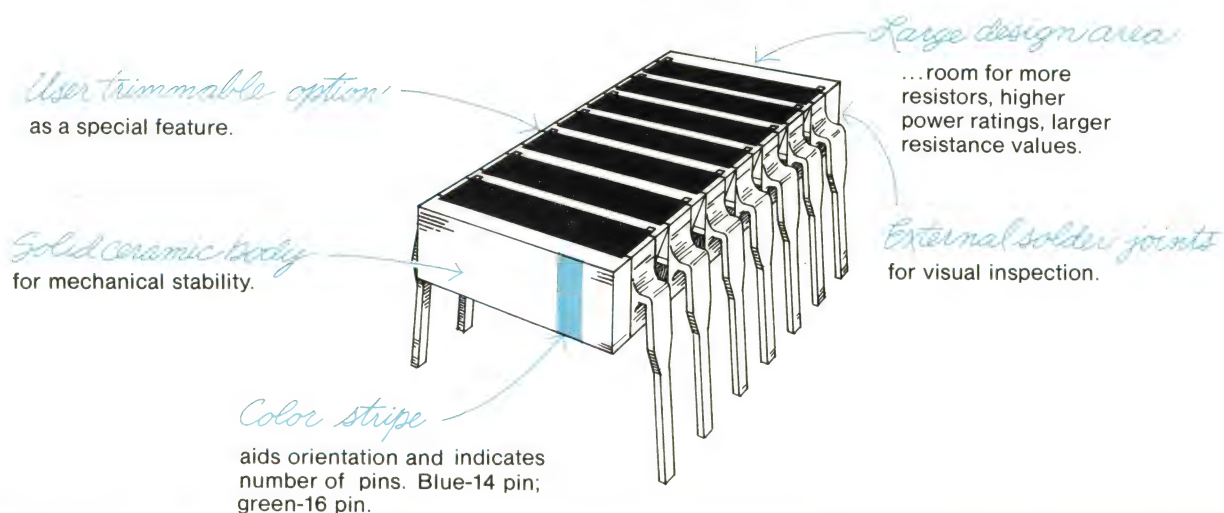If you need specials, contact your local Allen-Bradley district office for fast turnaround. Ask for Publication 5840. A-B is an experienced twin-film manufacturer, i.e. precision thin film and thick film.



Quality in the best tradition.



ALLEN-BRADLEY
Milwaukee, Wisconsin 53204

For more information, Circle No 31

EC149B

Versatile optoisolators, couplers move into new applications

Robert Grossman, Manager,
Western Editorial Office (N)


Optoelectronic isolators and couplers are replacing the slow and bulky electromechanical devices that previously isolated delicate circuitry—especially in telecommunications, which constitutes the devices' biggest market, according to an assessment by the top three suppliers. And as optoisolators mature in complexity and capability, they could become commonplace in all kinds of digital equipment.

With the increase in distributed processing, for example, optoisolators have taken on a new importance



Designed for high-performance applications, H-P's HCPL2601 provides 3000V isolation, with a 70% typical current-transfer ratio (I_c/I_o).

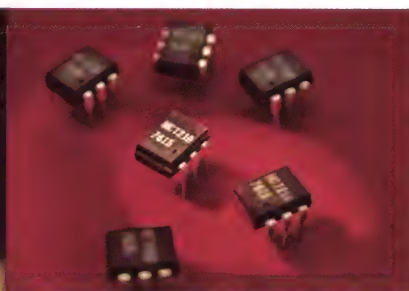to the computer industry. Optical devices can prevent unwanted interaction among any physically separable parts of a computer system—such as CRT terminals or printers—as well as isolating a system from the



Offering up to 2500V-dc surge isolation, Monsanto's MCT210 optoisolator drives up to 200 mW with an output-phototransistor collector-to-emitter voltage of 30V max.

outside world.

Industrial-noise solution

Industrial environments can present a very harsh "outside world" to a process-control computer; noise and damaging tran-

Illuminating the market

The steady growth of the optoisolator market indicates the importance and versatility of these products. Specifically, Monsanto's marketing manager for optoelectronic products, Bill Bottini, pegs the 1978 market for optoisolators at \$41 million—a figure supported by Hewlett-Packard's optocoupler product manager, Gary Labelle. Both men see a steady 20 to 25% annual market growth in the next few years.

Semiconductor houses such as Motorola, Fairchild and Texas Instruments are challenging the three optoisolator market leaders—General Electric, Hewlett-Packard and Monsanto—for a larger share of the market. The leaders are also feeling the increasing presence of smaller companies—Spectronics, Optron and Litronix, for example.

With regard to the leaders' overall marketing philosophy, GE, for one, does not intend to produce single-function parts for specialized industries. Joe McSweeney, the firm's

optoelectronic product planner, states that GE's product line will have a "broad-based market." With this strategy, the company hopes to continue its growth in industries where the trend is toward solid-state components and away from mechanical ones.

Monsanto sees optoisolators as common, reliable devices that designers can now utilize even when they are not absolutely required. This manufacturer feels that its growth in the optoelectronics field will be tied to the continuing computerization of American factories.

In contrast to the other market leaders, H-P has concentrated its efforts on the high end of the market. While all optocouplers employ some form of hybrid bipolar processing, H-P has designed its products to allow even more integration than usual on one chip. "Most devices have had to compromise performance between speed and efficient light capture," according to Labelle. "We combined the amplifier and optocoupler on the same chip for high-speed performance up to 10M bps."




Nothing but the best

Garry delivers the excellence you need for successful IC packages. Everything in boards from microprocessors to ECL logic, from dip sockets to wire wrap sockets. For over thirty years we've been making hundreds of millions of precision contacts a year for the connector industry. So we know all are top quality.

You don't pay top dollar, either. We're set up for in-house savings which we pass on. We have five Gardner-Denver vertical wire wrap machines and the most ultra-modern PC board facilities. Four plants — two U.S., two overseas — give us a turn-around edge. And support the largest inventory in the business.

We ship as fast as you can shop. Standard headers in as quick as 72 hours, up to 100,000 a week. Standard boards in as quick as two weeks. Any custom board from scratch in 6 to 10 weeks.

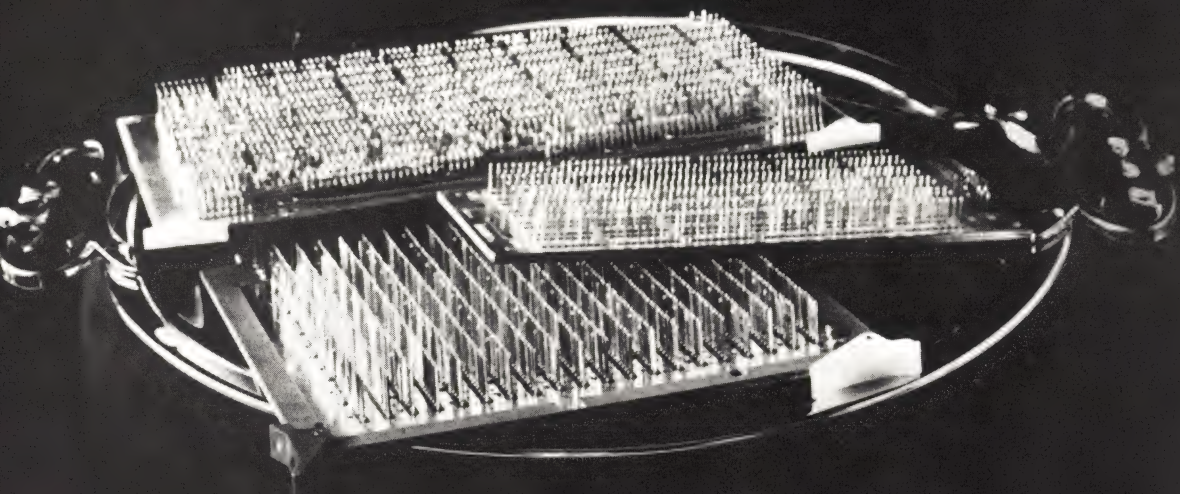At Garry you'll find superior quality and surprising speed. **Garry** Manufacturing Company, P.O. Box 94, New Brunswick, New Jersey 08902. (201) 545-2424.





Garry

Manufacturing Co.

For more information, Circle No. 32

matrox SBC-80 MULTIBUS displays

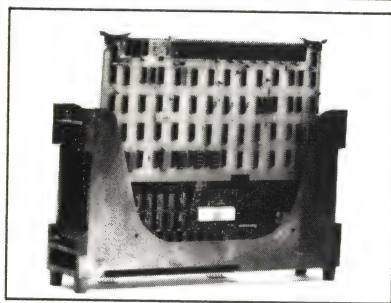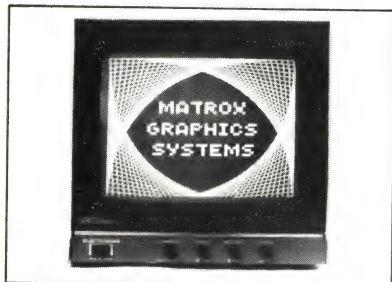

MATROX has the most complete line of CRT display boards for Intel's Multibus in the industry. We have alphanumeric; graphics; color; black and white; variable resolution; external/internal sync; 50/60 Hz; software and much, much more. Just plug the board in the Multibus, connect video to any standard TV monitor, and presto, you have added a complete display to your system at a surprisingly low cost.

MSBC-2480	24 lines x 80 character alphanumeric	\$ 350*
MSBC-256	256 x 256 dot graphics	\$ 650
MSBC-512x256	512 x 256 graphics	\$ 850
MSBC-512	512 x 512 graphics	\$1150
MSBC-1024	1024 x 256 graphics	\$1150
MSBC-24/320	24 x 80 alpha; 320 x 240 graphics combined	\$1150
RGB-256	256 x 256 x 4; 16 color or grey graphics	\$1250

And we have other uP displays and display controllers. These include state of the art OEM alphanumeric LED displays, alphanumeric video RAM's and CRT graphics controllers. They come as complete, ready to use sub-systems (single chips, modules, PCB's). Many of them are plug-in compatible with other buses (PDP-11, LSI-11, S-100, Prolog). If we don't have the display you require, we will design it for you.

IF YOU NEED A DISPLAY FOR YOUR uP, LET US KNOW.
WE ARE READY TO HELP YOU.

US. REPS WANTED *100 quant.

matrox electronic systems

2795 BATES RD., MONTREAL, QUE. H3S 1B5
TEL. (514) 481-6838 or (514) 735-1182; TLX. 05-825651
U.S. ONLY, TRIMEX BUILDING, MOORE'S, N.Y. 12958

Technology News

sients abound. Inserted between digital circuitry and this ac environment, optoisolators provide inexpensive circuit protection and permit control of high-current devices such as SCRs and triacs.

One potentially important industrial market that optoisolators have *not* yet entered is the automotive business. As electronic engine control becomes more prevalent (EDN, March 5, pg 37), Detroit might turn to inexpensive optical isolators as a solution to electrical-noise problems. For now, though, most optoisolators operate from 5V supplies rather than 12V, and Detroit's designers have other problems—such as emission control—on their minds, so penetration of the auto market remains but a possibility for optoelectronics.

Coupler or isolator?

Most of the current and prospective application areas utilize two separate capabilities of optoelectronic devices: coupling and isolating. Whereas *optocouplers* simply form an interface between two electrically independent circuits (configured from two incompatible logic families such as TTL and CMOS, for example), *optoisolators* must protect a circuit from potentially damaging voltage transients.

In reality, though, the only difference between opto-

isolators and optocouplers is one provided by marketing gamesmanship. Basically the same device, these optoelectronic components change names to suit the particular market segment in question.

Letting the light in

In its simplest form, an optoisolator/optocoupler contains two active devices on one die: an LED and a photodetector. The LED is fabricated in a standard manner. But it doesn't have an exposed emitting element; all of its light is directed onto the enlarged base region of the photodetector. Thus, when the isolator's input signal modulates the LED's light level, the photodetector senses the changes, and the input signal—now electrically isolated from the input—appears at the output.

Most of the actual differences between devices on the market stem from different output-stage designs. Most outputs utilize a 3-terminal semiconductor with one of its terminals (depending on semiconductor type) replaced by a photodetector: If a phototransistor is used, the photodetector replaces the transistor's base, while phototriacs and SCRs substitute the detector for their triggers. Some output stages also employ Darlington amplifiers to boost signal levels.


EDN

JOB SHOPPING?

Check EDN's Career Opportunities

EDN: Everything Designers Need

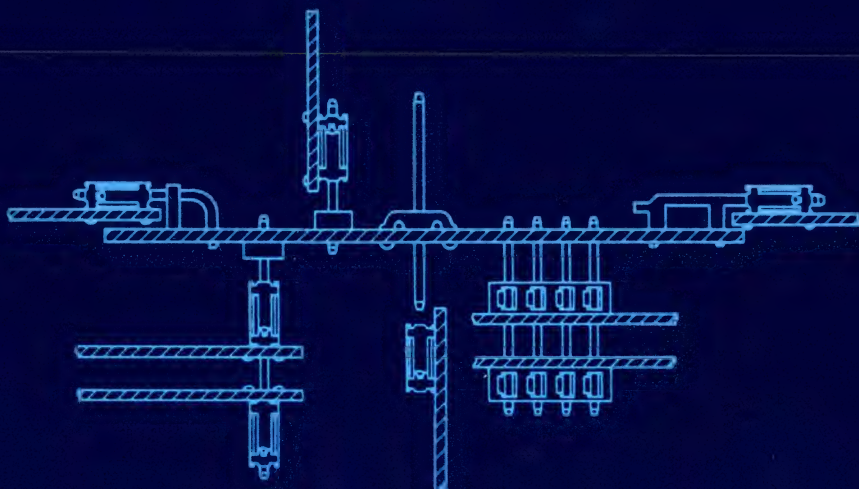Show me a truly
flexible packaging
system...something
we can grow on
right into the 80's."



The AMPMODU Interconnection System offers you both .100 centerline or larger packaging. It is a truly universal board-to-board and wire-to-board system that lets you expand your capabilities without obsolescence.

Take the receptacles. They offer a high degree of flexibility with electronic packaging schemes of all kinds. Board mount receptacles are available for both vertical use as well as for horizontal board stacking applications. Two classes of posts, five types of receptacles and 10 polarized header styles, in fact, make several thousand connection variations possible—now and in the future.

It's yours now. The


Headers mate with coaxial ribbon cable connectors, flat cable connectors, round conductor ribbon cable connectors, and AMPMODU Connectors for discrete wire and webbed cables.

With this kind of potential it is easy to switch, say, from "round" wires to flat wires by using the appropriate AMP Connector. Yet all this versatility is possible with a three-dimensional design that saves board real estate like never before.

At the front of the unique header receptacle is a dual cantilever spring beam design with a very forgiving nature and positive anti-overstress for unequalled contact protection. It assures a uniform, positive electrical contact with mating posts every time.


If you need a packaging system that can grow with your equipment design evolution, you need AMPMODU connectors...the interconnection system that lets you go board-to-board, wire-to-board and wire-to-wire—any time. Want more information?

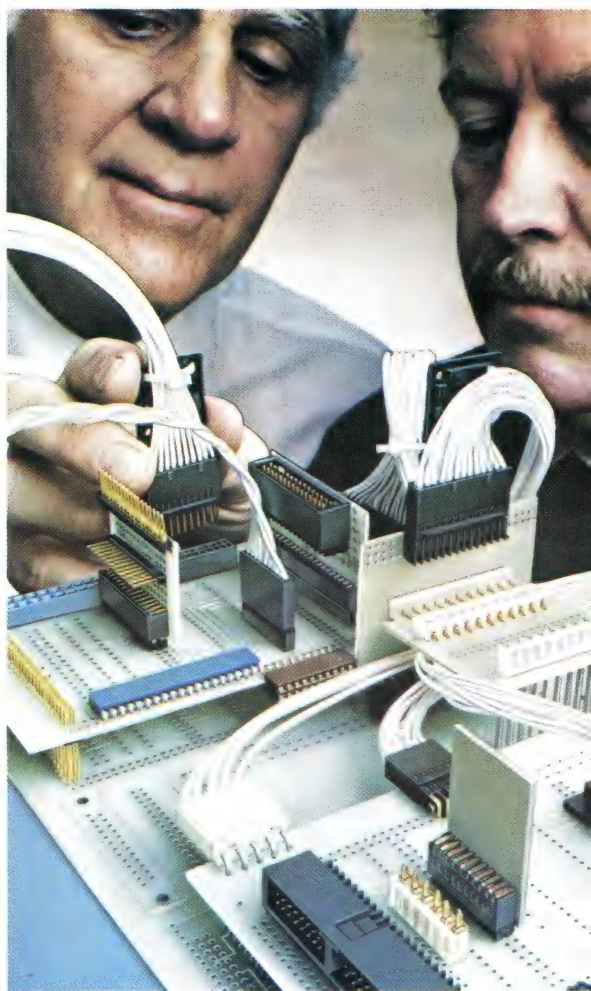See the opposite page and the page overleaf for complete tooling details.



AMP has a better way.


AMPMODU System.

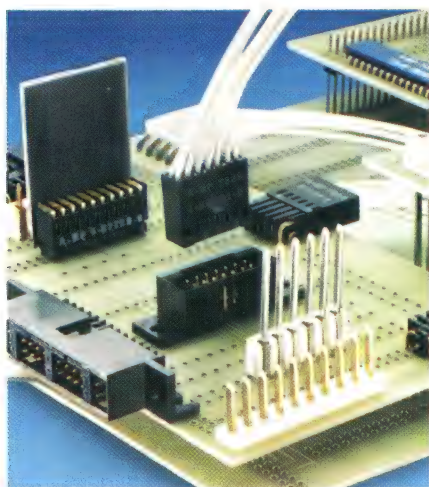

Some facts worth knowing about AMPMODU connectors

Function: The AMPMODU Interconnection System is a reliable, inexpensive way to provide three dimensional interconnections through a unique modular technique employing two mating members (posts) and female members (receptacles). The posts and receptacles fall into two general classifications:

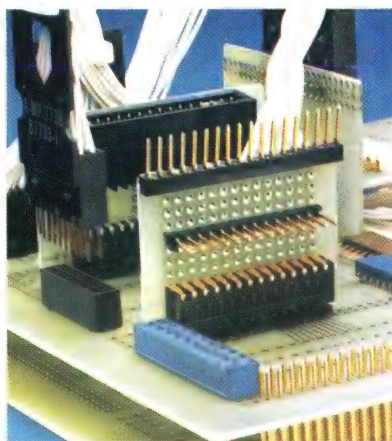.031" x .062" posts and mating receptacles and multicircuit housings. These are generally used in memory boards, power supplies and rugged interconnection systems.




.025" x .025" posts and mating receptacles incorporating standard, intermediate and high pressure receptacles for individual and multicircuit interconnections in a wide variety of sizes, styles and geometries to accommodate the higher density of sophisticated interconnection systems.



Where to telephone: Call AMPMODU Information Desk (717) 564-0100, Ext. 8400

Where to write: AMP Incorporated, Harrisburg, PA 17105

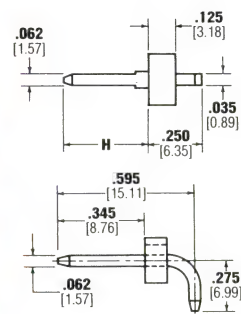
Product Information: Check Reader Service Card No. 100.



1. Headers for .031" x .062" technology

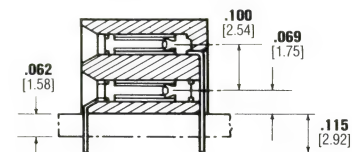
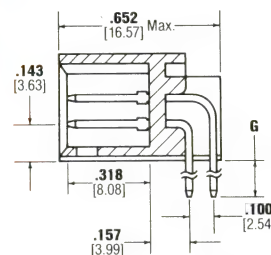


2. Headers for .025" x .025" technology

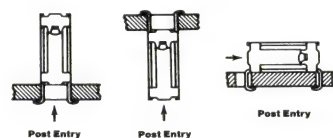

3. Board mount receptacle configurations

...and with cost effective tooling.

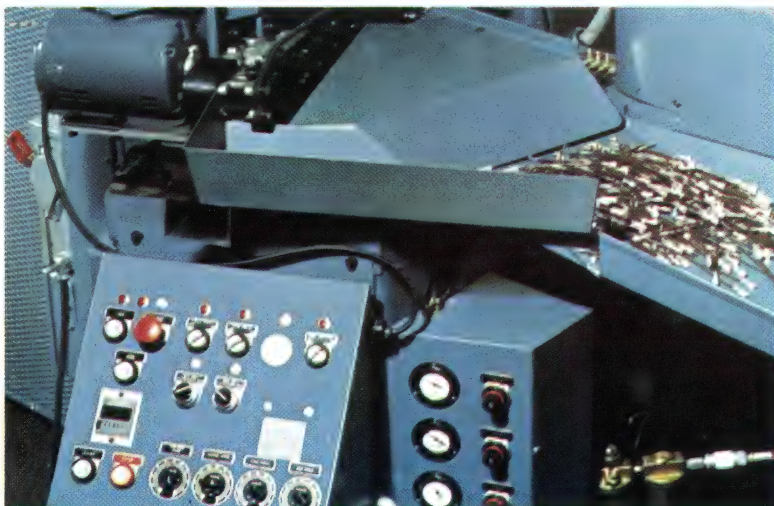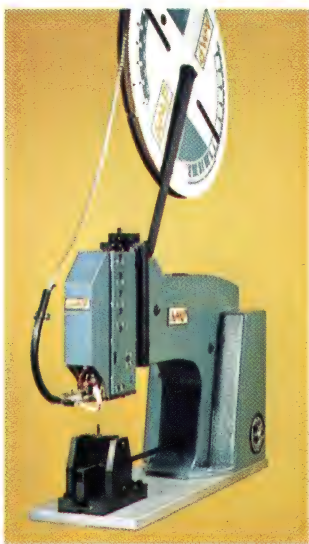

Quick staking, rapid terminations and low on-board costs are the hallmarks of AMPMODU Application Tooling.

The AMP Pantograph Machine, for instance, is a strip feed machine which stakes up to 12,000 posts and/or receptacles an hour. And it can do it with remarkable accuracy.

The production rate on the AMP Printed Circuit Board Insertion Machine can be as high as 2000 insertions per hour, depending on the operator. Styles are available for both the .031" x .062" and .025" x .025" components.

AMP also offers a complete range of wire terminating equipment, including bench machines, and high volume automatic lead making machines capable of terminating several thousand leads per hour.

Need more information about AMPMODU Tooling? Call the AMPMODU Information Desk at (717) 564-0100, Ext. 8400.

Or write AMP Incorporated, Harrisburg, PA 17105.

AMP, AMPMODU are trademarks of AMP Incorporated.

AMP

μ Computerist Corner

Simple circuit multiplies in 800 nsec

Prakash Dandekar

Andhra Valley Power Supply, Bombay, India

Currently available NMOS μ Ps require relatively long times (200 μ sec and more) to perform a multiplication; for high-speed control and signal-processing applications, designers usually opt for an expensive multiplier chip or a bipolar μ P to achieve times faster than this. You can reduce the multiplication bottleneck, however, by using a separate hardware subsystem interfaced to the μ P. The design presented here requires about 20 MSI/SSI ICs and costs less than \$30. With ordinary 7400 Series TTL, its highest usable clock frequency of 10 MHz permits 800-nsec 8-bit multiplication.

The subsystem (Fig 1) uses the simple shift-and-add algorithm flowcharted in Fig 2. The

hardware consists of two 8-bit operand registers accessible to the μ P (X and Y), a 16-bit result register (Z) and a counter that controls the multiplication sequence. Interfacing to a μ P system is simple: DEVSEL X and DEVSEL Y are two strobes generated by decoding the system address lines. These two signals load the X and Y registers; DEVSEL Y also clears the subsystem and starts the multiplication. Upon completion of the operation, the DONE flag goes HIGH; this flag is used by an interrupt-driven system.

The system clock period should be sufficiently long to provide a delay between the shifting-X and strobing-Z operations. The period must include the maximum clock-to-output delay of the 7495, the ripple-carry delay of the 7483 and the setup time and propagation delay of the 74175. Use of standard TTL permits a clock period of 100 nsec and thus a multiplica-

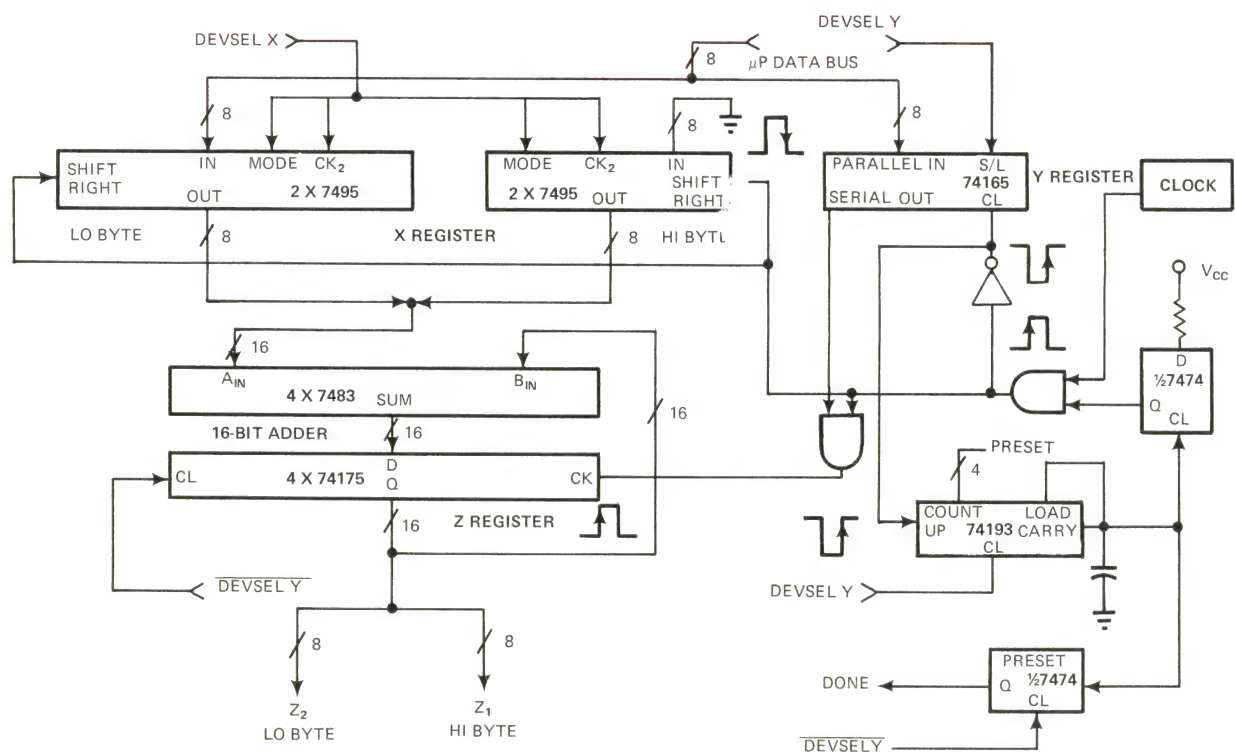


Fig 1—With careful selection of edge-triggered devices, this circuit performs an 8×8-bit multiplication in 800 nsec.

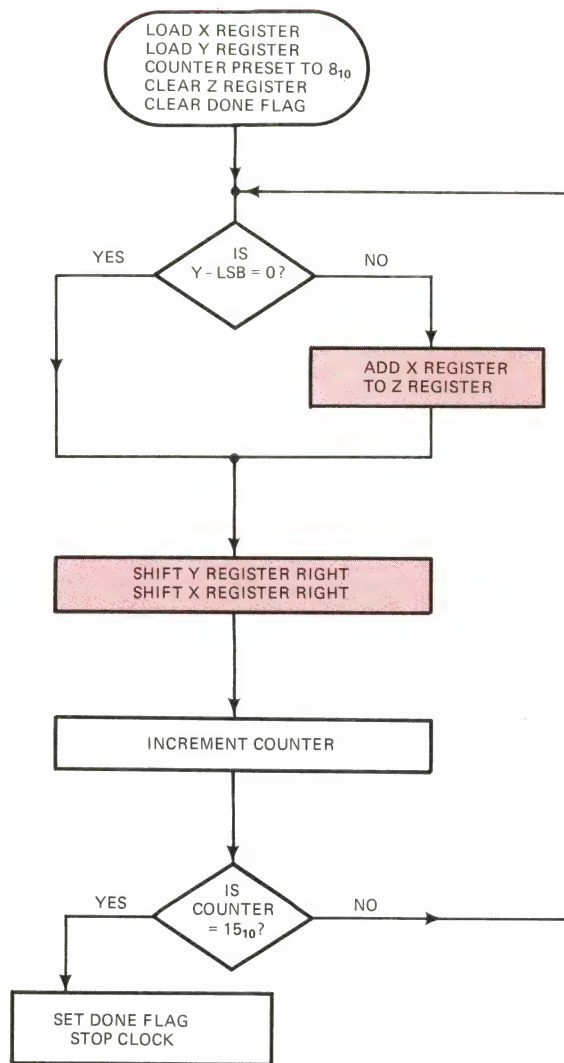


Fig 2—A shift-and-add algorithm makes the subsystem go.

tion time of 800 nsec.

Because most instructions of an NMOS μ P require 2 to 10 μ sec, an 800-nsec multiplication time represents engineering overkill. In such cases, you can use a lower clock frequency—using the CPU clock for this purpose saves circuitry.

In a typical 8080A-interfaced application, the X, Y, Z₁ and Z₂ registers are assigned consecutive memory locations; the X and Y operands are in the B and C registers, respectively. Use the code in Fig 3 to perform the multiplication; the 2-byte result is stored in DE.

The multiplication routine requires about 22 μ sec, compared with an all-software multipli-

```

MULT: LXI  H, X      ; X-register address loaded
                        ; in (H, L) pair
      MOV  M, B      ; X loaded
      INX  H          ; (H, L) incremented
      MOV  M, C      ; Y loaded, multiplication
      INX  H          ; proceeds
      MOV  D, M      ; Z1 (high-byte of result)
                        ; is brought into D register
      INX  H          ; address of Z2 register
      MOV  E, M      ; low-byte of result in E
      RET              ; register
  
```

Fig 3—Use this code when interfacing the multiplier with an 8080A system.

cation time of about 230 μ sec. Close examination of the routine reveals that the time between the loading of the Y register and the retrieval of the high byte from Z₁ is about 4 μ sec (eight microcycles at a 2-MHz clock frequency). Thus, using the 8080A's ϕ_2 clock, the subsystem clock frequency can be lowered so that the operation takes at most 4 μ sec.

This basic multiplier can be expanded to handle two 16-bit words. But in a hardwired system, the X, Y and Z registers double in width and thereby increase component count. If board space or parts cost is important, use the 8-bit subsystem as a byte multiplier together with an expanded software routine. **EDN**

Software notice

Access to more than 85 types of business, medical, accounting, research and hobby programs is free to members of the 8080 Etc users' group. Programs include routines in word processing, general accounting, billing, materials management, text editing, financial analysis, physics, and electrical, civil and chemical engineering. If you are interested in 8080 Etc membership, set your terminal for 300-baud transmission, dial (209) 638-6392 and type the passwords: Hello-w101, 8080-Etc. For a free list of program titles, send a self-addressed stamped envelope, together with a description of your system and any questions, to: Membership, The 8080 Etc, Box 894, Fresno, CA 93714.

EDN

Our new 64K ROM packs an on-time guarantee:

We'll deliver 64K, 32K or 16K ROMs in 8 weeks — or you'll get 100 parts free.

Everybody promises on-time delivery. Only Signetics *guarantees* it. In writing.

That means you'll get the first 100 pieces of our new 64K high-density MOS ROMs within eight weeks. After your written code verification, of course. If we slip delivery, you'll get 100 additional devices free. No questions asked.

Same offer goes for our industry standard 16K and 32K static ROMs.

We'll deliver those as promised. Or we'll add 100 free to your order for 1000 parts or more.

Signetics has a strong commitment to high-density ROMs. And we've packed that into our new 64K part. Higher circuit density

means fewer parts to meet storage requirements. That translates to cost savings in assembly time and board space.

Our 64K ROM is also a snap to interface. And it's available in 16K X 4 as well as 8K X 8. Since it's static, no clocking is needed. Couple that with ROM codes that work the first time out, and you'll cut the time lag from design to working hardware.

Compare the features of our 64K with other ROMs on the market. You'll see why it should be your first choice for design-ins.

And then try to find another supplier who'll guarantee delivery. You won't.

While we're meeting your ROM delivery schedule, Signetics will even *program your mask codes free*. That goes for every 16K, 32K, and 64K ROM on orders of 1000 up.

Whatever your design objectives are, Signetics will help you meet them. On time.

To get your on-time ROM guarantee certificate and technical literature, call us today on Signetics special *ROMLINE*: (408) 746-1756.

Or if another supplier has tied up your phone making delivery promises he won't keep, send us the coupon below.

signetics

a subsidiary of U.S. Philips Corporation

Signetics Corporation
P.O. Box 9052
811 East Arques Avenue
Sunnyvale, California 94086
Telephone 408/739-7700

Memories On Schedule

To: Signetics Information Services, 811 East Arques Ave
P.O. Box 9052, Sunnyvale, CA 94086

- ☐ Please send me complete details on miniMOS-4™ static ROMs and guarantee certificate.

Name _____ Title _____


Company _____ Division _____

Address _____ MS _____


City _____ State _____ Zip _____

- ☐ I'm tired of promises other suppliers won't back up. Please have an MOS Memory specialist phone me today at:

() _____ EDN 479 AC

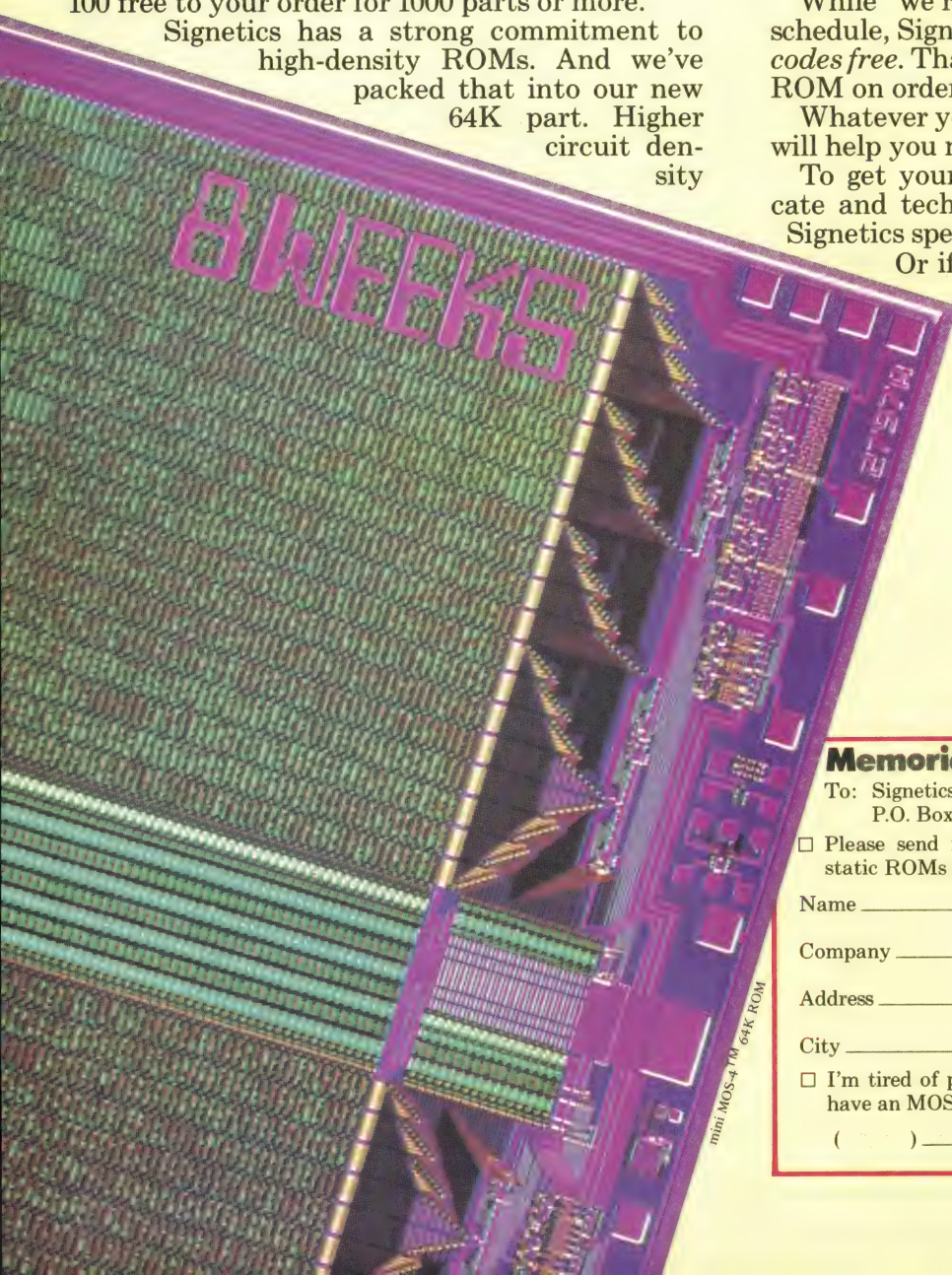

What's TRW up to now?

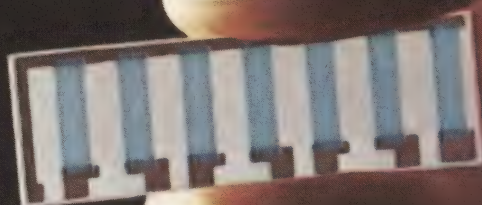

**BREAKING THE
PRECIOUS METAL BARRIER
IN THICK FILM NETWORKS.**

Photo: an 8 pin, 7 resistor SIP network substrate employing TanTin (cobalt blue) and copper terminations.

We've developed a series of non-noble cermet materials for our thick film networks . . . an industry first.

Gone are the increasing cost factors associated with precious metals like ruthenium, palladium, silver and gold.

Our TanTin™ system, for example, uses only non-precious metals and metal oxides suspended in a glass matrix. Fired to substrates at over 900° C, TanTin is both rugged and stable. Even in resistance ranges as high as 10 meg Ω /square.

Equally non-precious thick film copper conductor patterns are free from noble metal migration: conductivity is very high — up to 20 times better than palladium or platinum based materials.

The significance of our work in non-noble materials was underscored when TanTin received an IR100 award for 1978, Industrial Research/Development Magazine's award for the best industrial product developments of the year.

So, whether you now use resistor networks, or are in the design stage, think of TRW. The leader in discrete thick film technology is now making equally impressive networks.

For more information, contact TRW/IRC Resistors, an Electronic Components Division of TRW, Inc., Greenway Road, Boone, N.C. 28607. Dept. N. (704) 264-8861.

TRW IRC RESISTORS

ANOTHER PRODUCT OF A COMPANY CALLED TRW

For more information, Circle No 36

™TanTin is TRW's trademark for one of its proprietary thick film systems.

Electronics is carrying
through to our
capacitors.

GPR 5000
General Purpose
2% Film
Resistor.

GPC 6000
Axial Leaded
Tubular "Super K"
Ceramic Capacitor.

Success breeds
success!



MEPCO/ELECTRA, INC.
A NORTH AMERICAN PHILIPS COMPANY

Resistor/capacitor company with the tech
Columbia Road, Morristown, New Jersey 07960 (201) 539-2000

For more information

EDN Software Note #27

Execute MK3870 magnitude comparisons

Don Ward

Mostek Corp, Carrollton, TX

By testing the appropriate status bit(s) of an MK3870, you can make magnitude comparisons without altering the contents of the device's accumulator or memory.

The μC's instruction set provides two comparison instructions which do not store a result: CI (compare immediate) and CM (compare memory). These instructions add the two's-complement value of the accumulator to the immediate byte (CI) or to the memory byte (CM) referenced by the data counter. Although a comparison's result is discarded, the operation alters the status register according to the rules of two's-complement addition.

For two numbers, A and B (signed or unsigned magnitudes), the **table** indicates the status conditions necessary for each comparison.

RELATION	UNSIGNED	SIGNED
	O Z C S	O Z C S
A = B	- 1 - -	- 1 - -
A <> B	- 0 - -	- 0 - -
A > B	- - 0 -	0 - - 0 or 1 - - 1
A <= B	- - 1 -	0 - - 1 or 1 - - 0
A < B	- 0 1 -	1 - - 0 or 0 0 - 1
A >= B	- - 0 - or - 1 - -	0 - - 0 or 1 - - 1 or - 1 - -

A magnitude comparison in an MK3870 sets testable status conditions. A "-" in this reference table indicates a "don't-care" bit.

son. The routines in the **figure** test for each condition and perform a branch if the relation is true. Although these routines use CI, CM can be substituted for memory comparison.

EDN

```

>0000      0007 B      EQU      H'00'      ASSIGN B TO SOME VALUE.
           0008 *
           0009 * (A)  A = B
           0010 *      Same as Example 1.0 (A).
           0011 *
           0012 *
           0013 *
           0014 * (B)  A <> B
           0015 *      Same as Example 1.0 (B).
           0016 *
           0017 *
           0018 *
           0019 * (C)  A > B
'0000 2500      0020      CI      B      COMPARE VALUES.
'0002 990E      0021      BF      9,AGTB  BRANCH IF OVFS=0.
'0004 9803      0022      BNO     ALEB    S=1 IF OVFS=0.
'0006 810A      0023      BP      AGTB    BRANCH IF OVFS=1.
'0008 2B        0024 ALEB      NOP      FLOW HERE IF OVFS=1, S=0.
           0025 *
           0026 *
           0027 *
           0028 * (D)  A <= B
'0009 2500      0029      CI      B
'000B 9905      0030      BF      9,AGTB  BRANCH IF OVFS=0.
'000D 98FA      0031      BNO     ALEB    S=1 IF OVFS=0.
'000F 91F8      0032      BM      ALEB    BRANCH IF S <> 0.
'0011 2B        0033 AGTB      NOP      CONTINUE HERE IF OVFS=S.
           0034 *
           0035 *
           0036 *
           0037 * (E)  A < B
'0012 2500      0038      CI      B

```

In this code for signed and unsigned magnitude comparisons, "A" represents the accumulator and "B" the comparison value. (Continued on next page)

μComputerist Corner

'0014	9905	0039	BF	9,AGEB	BRANCH IF OVF=S=0.
'0016	9C0C	0040	BF	12,ALTB	BRANCH IF OVF=Z=0.
'0018	910A	0041	BM	ALTB	BRANCH IF S=Z=0.
'001A	2B	0042	AGEB	NOP	CONTINUE HERE IF OVF=S
		0043	*		OR Z=1.
		0044	*		
		0045	*		
		0046	*		
		0047	*(F)	A >= B	
'001B	2500	0048	CI	B	
'001D	99FC	0049	BF	9,AGEB	BRANCH IF OVF=S=0.
'001F	9C03	0050	BF	12,ALTB	BRANCH IF OVF=Z=0.
'0021	81F8	0051	BF	AGEB	BRANCH IF S=1.
'0023	2B	0052	ALTB	NOP	CONTINUE HERE IF C <> S
		0053	*		AND Z=0.
		0054	*		
		0055	*		
		0056	*(F)	A >= B	
		0057	CI	B	
		0058	BF	9,AGEB	BRANCH IF OVF=S=0.
		0059	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0060	BF	AGEB	BRANCH IF S=1.
		0061	ALTB	NOP	CONTINUE HERE IF C <> S
		0062	*		AND Z=0.
		0063	*		
		0064	*(F)	A >= B	
		0065	CI	B	
		0066	BF	9,AGEB	BRANCH IF OVF=S=0.
		0067	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0068	BF	AGEB	BRANCH IF S=1.
		0069	ALTB	NOP	CONTINUE HERE IF C <> S
		0070	*		AND Z=0.
		0071	*		
		0072	*(F)	A >= B	
		0073	CI	B	
		0074	BF	9,AGEB	BRANCH IF OVF=S=0.
		0075	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0076	BF	AGEB	BRANCH IF S=1.
		0077	ALTB	NOP	CONTINUE HERE IF C <> S
		0078	*		AND Z=0.
		0079	*		
		0080	*(F)	A >= B	
		0081	CI	B	
		0082	BF	9,AGEB	BRANCH IF OVF=S=0.
		0083	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0084	BF	AGEB	BRANCH IF S=1.
		0085	ALTB	NOP	CONTINUE HERE IF C <> S
		0086	*		AND Z=0.
		0087	*		
		0088	*(F)	A >= B	
		0089	CI	B	
		0090	BF	9,AGEB	BRANCH IF OVF=S=0.
		0091	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0092	BF	AGEB	BRANCH IF S=1.
		0093	ALTB	NOP	CONTINUE HERE IF C <> S
		0094	*		AND Z=0.
		0095	*		
		0096	*(F)	A >= B	
		0097	CI	B	
		0098	BF	9,AGEB	BRANCH IF OVF=S=0.
		0099	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0100	BF	AGEB	BRANCH IF S=1.
		0101	ALTB	NOP	CONTINUE HERE IF C <> S
		0102	*		AND Z=0.
		0103	*		
		0104	*(F)	A >= B	
		0105	CI	B	
		0106	BF	9,AGEB	BRANCH IF OVF=S=0.
		0107	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0108	BF	AGEB	BRANCH IF S=1.
		0109	ALTB	NOP	CONTINUE HERE IF C <> S
		0110	*		AND Z=0.
		0111	*		
		0112	*(F)	A >= B	
		0113	CI	B	
		0114	BF	9,AGEB	BRANCH IF OVF=S=0.
		0115	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0116	BF	AGEB	BRANCH IF S=1.
		0117	ALTB	NOP	CONTINUE HERE IF C <> S
		0118	*		AND Z=0.
		0119	*		
		0120	*(F)	A >= B	
		0121	CI	B	
		0122	BF	9,AGEB	BRANCH IF OVF=S=0.
		0123	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0124	BF	AGEB	BRANCH IF S=1.
		0125	ALTB	NOP	CONTINUE HERE IF C <> S
		0126	*		AND Z=0.
		0127	*		
		0128	*(F)	A >= B	
		0129	CI	B	
		0130	BF	9,AGEB	BRANCH IF OVF=S=0.
		0131	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0132	BF	AGEB	BRANCH IF S=1.
		0133	ALTB	NOP	CONTINUE HERE IF C <> S
		0134	*		AND Z=0.
		0135	*		
		0136	*(F)	A >= B	
		0137	CI	B	
		0138	BF	9,AGEB	BRANCH IF OVF=S=0.
		0139	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0140	BF	AGEB	BRANCH IF S=1.
		0141	ALTB	NOP	CONTINUE HERE IF C <> S
		0142	*		AND Z=0.
		0143	*		
		0144	*(F)	A >= B	
		0145	CI	B	
		0146	BF	9,AGEB	BRANCH IF OVF=S=0.
		0147	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0148	BF	AGEB	BRANCH IF S=1.
		0149	ALTB	NOP	CONTINUE HERE IF C <> S
		0150	*		AND Z=0.
		0151	*		
		0152	*(F)	A >= B	
		0153	CI	B	
		0154	BF	9,AGEB	BRANCH IF OVF=S=0.
		0155	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0156	BF	AGEB	BRANCH IF S=1.
		0157	ALTB	NOP	CONTINUE HERE IF C <> S
		0158	*		AND Z=0.
		0159	*		
		0160	*(F)	A >= B	
		0161	CI	B	
		0162	BF	9,AGEB	BRANCH IF OVF=S=0.
		0163	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0164	BF	AGEB	BRANCH IF S=1.
		0165	ALTB	NOP	CONTINUE HERE IF C <> S
		0166	*		AND Z=0.
		0167	*		
		0168	*(F)	A >= B	
		0169	CI	B	
		0170	BF	9,AGEB	BRANCH IF OVF=S=0.
		0171	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0172	BF	AGEB	BRANCH IF S=1.
		0173	ALTB	NOP	CONTINUE HERE IF C <> S
		0174	*		AND Z=0.
		0175	*		
		0176	*(F)	A >= B	
		0177	CI	B	
		0178	BF	9,AGEB	BRANCH IF OVF=S=0.
		0179	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0180	BF	AGEB	BRANCH IF S=1.
		0181	ALTB	NOP	CONTINUE HERE IF C <> S
		0182	*		AND Z=0.
		0183	*		
		0184	*(F)	A >= B	
		0185	CI	B	
		0186	BF	9,AGEB	BRANCH IF OVF=S=0.
		0187	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0188	BF	AGEB	BRANCH IF S=1.
		0189	ALTB	NOP	CONTINUE HERE IF C <> S
		0190	*		AND Z=0.
		0191	*		
		0192	*(F)	A >= B	
		0193	CI	B	
		0194	BF	9,AGEB	BRANCH IF OVF=S=0.
		0195	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0196	BF	AGEB	BRANCH IF S=1.
		0197	ALTB	NOP	CONTINUE HERE IF C <> S
		0198	*		AND Z=0.
		0199	*		
		0200	*(F)	A >= B	
		0201	CI	B	
		0202	BF	9,AGEB	BRANCH IF OVF=S=0.
		0203	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0204	BF	AGEB	BRANCH IF S=1.
		0205	ALTB	NOP	CONTINUE HERE IF C <> S
		0206	*		AND Z=0.
		0207	*		
		0208	*(F)	A >= B	
		0209	CI	B	
		0210	BF	9,AGEB	BRANCH IF OVF=S=0.
		0211	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0212	BF	AGEB	BRANCH IF S=1.
		0213	ALTB	NOP	CONTINUE HERE IF C <> S
		0214	*		AND Z=0.
		0215	*		
		0216	*(F)	A >= B	
		0217	CI	B	
		0218	BF	9,AGEB	BRANCH IF OVF=S=0.
		0219	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0220	BF	AGEB	BRANCH IF S=1.
		0221	ALTB	NOP	CONTINUE HERE IF C <> S
		0222	*		AND Z=0.
		0223	*		
		0224	*(F)	A >= B	
		0225	CI	B	
		0226	BF	9,AGEB	BRANCH IF OVF=S=0.
		0227	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0228	BF	AGEB	BRANCH IF S=1.
		0229	ALTB	NOP	CONTINUE HERE IF C <> S
		0230	*		AND Z=0.
		0231	*		
		0232	*(F)	A >= B	
		0233	CI	B	
		0234	BF	9,AGEB	BRANCH IF OVF=S=0.
		0235	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0236	BF	AGEB	BRANCH IF S=1.
		0237	ALTB	NOP	CONTINUE HERE IF C <> S
		0238	*		AND Z=0.
		0239	*		
		0240	*(F)	A >= B	
		0241	CI	B	
		0242	BF	9,AGEB	BRANCH IF OVF=S=0.
		0243	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0244	BF	AGEB	BRANCH IF S=1.
		0245	ALTB	NOP	CONTINUE HERE IF C <> S
		0246	*		AND Z=0.
		0247	*		
		0248	*(F)	A >= B	
		0249	CI	B	
		0250	BF	9,AGEB	BRANCH IF OVF=S=0.
		0251	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0252	BF	AGEB	BRANCH IF S=1.
		0253	ALTB	NOP	CONTINUE HERE IF C <> S
		0254	*		AND Z=0.
		0255	*		
		0256	*(F)	A >= B	
		0257	CI	B	
		0258	BF	9,AGEB	BRANCH IF OVF=S=0.
		0259	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0260	BF	AGEB	BRANCH IF S=1.
		0261	ALTB	NOP	CONTINUE HERE IF C <> S
		0262	*		AND Z=0.
		0263	*		
		0264	*(F)	A >= B	
		0265	CI	B	
		0266	BF	9,AGEB	BRANCH IF OVF=S=0.
		0267	BF	12,ALTB	BRANCH IF OVF=Z=0.
		0268	BF	AGEB	BRANCH IF S=1.
		0269	ALTB	NOP	CONTINUE HERE IF C <> S
		0270	*		AND Z=0.
		0271	*		
		0272	*(F)	A >= B	
		0273	CI	B	
		0274	BF	9	

Lowpass Active Filters

4-Pole Butterworth/Bessel/Tchebyscheff

Models: 7E7L4B-f_c Butterworth • 7E7L4L-f_c Bessel
7E7L4YA5W-f_c Tchebyscheff • 7E7L4A2W-f_c Tchebyscheff
7E7L4Y1W-f_c Tchebyscheff

f_c Range
f_c Tolerance
DC Offset
Linear Signal
Gain

10Hz - 20kHz
± 5%
± 20mV
± 10V
0 ± 0.02dB

These filters pass all signals from DC up to the corner frequency f_c.

*\$12.00 in 2,500 Quantity; \$8.00 in 10,000 Quantity.



**Frequency
Devices INC.**

25 Locust Street, Haverhill, MA 01830

FACTORY CONTACT: William C. Morse
Tel: (617) 374-0761, TWX: 710-347-0314

\$12.00 ea.*

FLUKE'S MICROPROCESSOR-BASED SCANNER IS COMPATIBLE WITH EITHER IEEE 488 OR RS232.

Or scans automatically without a controller!

That's right — the new Fluke 2204A scanner is so flexible you can use it for R&D applications like component research, life-cycle and environmental testing, quick-change production line test set-ups, and even precise process monitoring jobs that demand the highest possible reliability.

System building block

When you build your system around the 2204A, you have a mainframe capacity up to 100 channels, and scan speeds up to 125 channels/second. Whatever capacity you need up to 1000 total channels is easily provided by chassis extenders.

Choose from either general purpose (2-wire) or low thermal ($<1 \mu\text{V}$, 3-wire) relay scanner cards. Both switch up to 170 VDC and have excellent high frequency AC response. We provided for convenient four-terminal ohms measurements, and high-accuracy temperature measurements through an exclusive isothermal

input connector.

When it comes to checking out or trouble-shooting your system, you can do it conveniently and quickly in the manual mode right from the front panel of the 2204A. The whole system can be synchronized by using the scanner's output trigger pulse.

Now, about what voltmeter to use.

The 2204A and our 8502A $6\frac{1}{2}$ -digit voltmeter make an ideal pair that we call the 7600A system. The combination of these two precision instruments gives some unique system advantages that no other scanner/DVM combination can provide:

- Utilization of the maximum speed potential of the scanner on the bus, afforded by the 8502A's high speed.
- Excellent noise rejection due to the 8502A's unique digital filtering characteristics.
- Scanner data that can be massaged without a controller. The 8502A's strong math capabilities plus scal-

ing, offsetting, peak reading, and "hi-pass-lo" decisions give you immediately useful information, with no additional computation necessary.

• Time and money savings, because the 7600A system comes factory tested and shipped together, with all the cables and connectors you need. And at no increase in cost over individual instrument prices!

CALL (800) 426-0361, TOLL FREE* or contact any of the 100 Fluke offices and representatives, worldwide. In the U.S. and countries outside Europe write: John Fluke Mfg. Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043, U.S.A.

In Europe, contact: Fluke (Nederland) B.V., P.O. Box 5053, Tilburg, The Netherlands. Telephone: (013) 673973 Telex: 52237.

* Alaska, Hawaii, Washington residents — please call (206) 774-2481.

FLUKE®



The Fluke 2204A IEEE-compatible scanner (top) — a perfect match for the Fluke 8502A DVM.

For literature Circle no 39
For demonstration Circle no 118

μ P μ P and away

Going μ P? Our 8-lane universal expressway to μ P development is wide open.



**Get μ P to speed
with our multistation
development network.**

Eliminate the traffic jam in your microprocessor development lab. Get off that one-way road to μ P-based product design (with just one chipmaker's microprocessor support) and reduce your per-station cost at the same time. How? With our Universal Multistation Development Network — a distributed processing system that shares disk and printer with up to eight users simultaneously. Give each user his own AMDS station with integral CPU, CRT and keyboard; any one of six supported processors (8086, 8085,

8080, 6800, 6802, Z-80 and more soon); optional in-circuit emulator, logic analyzer and every software aid, including BASIC compilers, relocating macro-assemblers and disassembling symbolic debuggers. It's the first sensible alternative to the high cost of multi-user development support and confining single-chip systems. Futuredata, 11205 S. La Cienega Blvd., Los Angeles, CA 90045. (213) 641-7700 TWX: 910-328-7202.

futuredata

μ C development



Regardless of its physical condition, a prototype can often benefit from some form of development-system diagnostics. (Photo of System 65 Courtesy Rockwell International)

systems

No two development systems are alike, but no two development tasks are, either. The ideal system remains flexible, satisfying your specific needs.

Edward Teja, Associate Editor

Although nearly every μ C system currently on the market features some development tools, many of these systems are not designed for complex development work. And even if you consider only those systems touted specifically for development tasks, their sheer variety will confuse any attempt at specific point-by-point comparisons.

Clearly, though, a \$500 system does not offer the same capabilities as a \$20,000 one; they don't compete directly. The question, then, is not which development system is the best, but which development tools best suit your task. After ascertaining that requirement, you can then determine which system provides these tools in the most cost-effective package.

Start by defining the development task; realistically assess the minimum and maximum requirements your system must meet. The questions in the nearby **box** can serve as a guide to a first-level evaluation. For example, if your end product's available memory is limited, writing programs in PASCAL would be unrealistic—even though many development systems either now

offer it or will add it during the next year. The requisite interpreter alone resides in approximately 10k of ROM in most PASCAL versions—and that does not include the program size. FORTRAN, to name a second example, compiles nicely, yet its run-time package, whose size varies from compiler to compiler, requires additional memory. In fact, for products with less than 8k of memory, programming in anything higher than assembly language can prove to be a blue-sky proposition.

Evaluating the suppliers

In the beginning, development systems were created for one purpose: to sell silicon. Semiconductor manufacturers realized that the ease of producing software for a processor correlated with the volume of that device's sales. Although these manufacturers still produce development systems to sell their chips, the entry of independent equipment manufacturers into the market has led some semiconductor makers to market their systems as independent-profit-center products. The successful entry of independent firms has made it clear that selling development systems and development tools is profitable in



All the tools for software and hardware development and debug for Z80 and 3870 μ Ps come in Mostek's AID-80F. The enclosure, a CPU with 32k of RAM, two single-sided drives, a card case and cabling cost \$5995 total.



Costing \$14,500, Intel's Intellec Series II Model 230 comprises 64k of RAM; two dual-density floppy-disc drives; a 2000-character CRT and the ISIS-II operating system. (The ICE module for 8086 emulation and the SDK-86 board shown in the photo are not included in this price.)

Independent vendors add features to dedicated systems

and of itself.

The independent equipment manufacturers (companies not engaged in making μ Ps) typically offer universal systems. ("Universal," in this context, means only that a system, rather than being committed to a particular processor, functions as a development station for several processors.) Tektronix, one of the best-known independents, views the market as one for test equipment. Thus, its Model 8002's emulator circuitry and debug capability were developed by logic-analyzer designers.

The 8002's Real-Time Prototype Analyzer option, for example, provides a trace of up to eight locations on a prototype circuit. This sophistication is costly, though: An 8002 with F8, 3870 and 3872 support packages costs \$13,700. The system also supports 6800, 8080A, 8085, Z80 and TMS 9900 μ Ps.

The time lag between the appearance of a new μ P and the availability of development systems that serve it is significant to OEMs. Naturally, the chip's manufacturer will offer first delivery on development support; the availability of support for the chip on universal systems, though, typically awaits mass-market acceptance of the device. Thus, if you can't wait for an indefinite period of time for a software or hardware module that supports the new device on your universal system, you'll either have to write your own cross assembler or buy the appropriate dedicated system from the chip manufacturer.

Independents perform another service beyond broadening the variety of available alternatives—they provide products that make dedicated systems slightly more universal. Proc-



Development tools don't always come in system packages. Applied Microsystems' EZ-80 permits full emulation of Z80 μ Ps while providing built-in diagnostics.



Several users can share a single CPU and mass-storage devices when working on Futuredata's Microsystems. These systems range from \$11,500 to \$69,450, depending on configuration.



An all-in-one configuration, Zilog's ZDS-1 provides emulator, logic analyzer and ROM/RAM-simulator functions.



A general-purpose system designed more for business than development work, Pertec's 8085-based PCC 2000 can nonetheless serve for some development tasks.

essor Innovations, for example, can (for \$1500) utilize the magic of cross assembly to provide Intel development-system users with TMS 9900, SBP 9900 and S9900 development capabilities.

As another alternative, Solid State Scientific Inc proffers a \$500 macro assembler that permits use of Intel's Inteltec system as an SCP1802 development system. In the same manner, cross assemblers can convert any μ C into a development system—EDN did it for the 8086 (EDN, February 5, 1979, pg 115). Incidentally, Intel used cross assemblers and cross compilers (PL/M) to make the 8080-based Inteltec system do development work for the 8086.

Just as adding software increases the versatility of an existing system, a similar approach can compensate for a shortage of specialized development hardware. Intersil, for example, provides its Model 6920 EPROM programmer for use with any system having either an RS-232 or current-loop interface. Thus, for approximately \$1000, virtually any system can program PROMs.

In short, just because a development system is purchased as a dedicated configuration doesn't mean it must stay that way.

Making more than a development system

There's another alternative, though. Many higher priced systems, such as National Semiconductor's Starplex, offer blandishments (such as FORTRAN) unrelated to their systems' use in

the development task. National assumes that many OEMs can't afford to pay \$10,000 or more for "only" a development system and that a system offering full-service computational power covers a broader range of applications. The extra capability isn't free, of course, but bundled into the price of a development system, it becomes less noticeable.

Assume, for example, that your company can afford (or will authorize) only part of the necessary cash for a development system; assume also that some EEs in the firm are using time sharing to solve problems in FORTRAN. If you are willing to share access to the system, all of you can combine budgets to buy one system that does both jobs.

Contrast this approach with the method used by companies such as Futuredata: It believes multiuser development systems are an effective means of reducing development costs. Its Six Station Network, for example, provides facilities for six users simultaneously, including four software-development stations; two hardware-development stations; four double-sided, double-density floppy discs; and a 300-lpm printer. The system accommodates five different user-specified 8-bit processors. Cost per programmer is about \$11,575—not cheap by any standard—but Futuredata feels that each programmer must have a separate console in a realistic development effort. Tools such as symbolic debug

Defining the development task

In order to select a system that will maximize your development effort, you must first define your job in terms of the available development tools. The necessary questions divide into hardware and software categories.

Hardware

1. How many different types of μ Ps must the system be able to accommodate?
2. Will the code to be developed reside in PROM?
3. Is the application hardware sufficiently complex that it would benefit from in-circuit emulation?
4. Will the system be available for uses other than development?
5. How many programmers must have access to the system at any one time?

Software

1. Is the code to be developed sufficiently long (and complex) to require modularized writing? If so, make sure that the assemblers and compilers provided with the development system produce relocatable, linkable code. The former permits modification of its addresses at load time; the latter uses pseudo-ops to maintain communication between separately compiled modules and the main program. For detailed discussions of these features, see "The software wall and what you need to scale it" (EDN, March 5, 1978, pg 75).
2. Can your code be written in a high-level language? A secondary question here should be: What languages do members of your development

team already know? You shouldn't have to spend time learning new languages unnecessarily.

3. Will programmers be using the system to write code for processors other than the resident CPU? If so, can cross assemblers be produced in-house? Are cross assemblers that produce code for the target processor available on the development system?

4. Will some routines be used repeatedly? What hardware/software does the system offer to facilitate building libraries of subroutines?

5. Will the system be shared for other engineering tasks? If yes, you will want FORTRAN or some high-level language for the individuals involved in those tasks. Don't expect BASIC to be adequate.

Extra capability makes dedicated systems generally useful

and interactive editing, hallmarks of this kind of system, make system development this network's primary purpose.

Setting system guidelines

Are there such things, then, as standard system tools? No; they depend on the application. You wouldn't consider hardware emulation necessary if the target product were relatively trivial, yet for complex products, Intel's ICE, National's In-System Emulation or one of the numerous other emulator products can save time and effort—permitting a real-time analysis of code as it executes on your hardware.


And if the software in your job is trivial, the best solution might not be a development system at all. A stand-alone emulator, such as the EM-6800 or EZ-80 from Applied Microsystems,

provides an alternative for testing hardware prototypes. To emulate a chip, the EM-68 plugs into a 6800 CPU socket. You can take one home for \$1860.

Millennium Systems also uses plug-in modules in its Microsystem Analyzer, supporting 6800, 8080, 8085A-2 and Z80 μ Ps. You can equip this stand-alone emulator, which costs \$2750, with a \$1000 signature-analysis option for time-domain capability.

Although the necessary set of tools is entirely task dependent, though, it *is* possible to outline requirements that apply to any μ C system used in a commercial environment. These general system requirements don't relate specifically to the required set of development tools, but rather to the concept of realistic system hardware and software. Your system's capabilities will be more flexible if the system is chosen according to these guidelines:

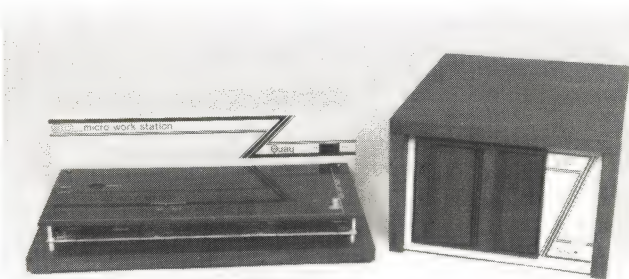- Include at least two floppy-disc drives.



Flexible enough to expand into any application, Quay Corp's Model 90MWS, equipped with 4k of RAM but without floppy discs, starts at \$1050.




Putting everything in an integrated package, Tano's Outpost features a macro assembler and STRUBAL+ compiler.

From tutor to tool

Rockwell's Aim 65 began as a teaching tool but is currently finding use as a development system. As such, it's one example of the diverse nature of "development systems."

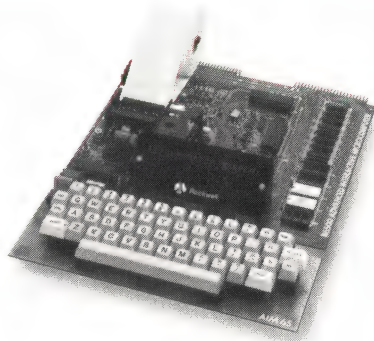The company wanted to design a portable system that furnished enough tools to illustrate the power of its 6502 processor and peripheral chips. To that end, the Aim 65 board houses a thermal printer, keyboard and alphanumeric display; two 4k ROMs store an advanced monitor. An interface permits adding a cassette, thereby extending the unit's system-software base. The fully equipped board



Not initially intended for use as a development system, Rockwell's Aim 65 has become a fierce competitor in that field.

retails for about \$500—a reasonable price for a teaching machine.


The marketplace had different applications in mind for the unit, though; engineers

began buying it as a development system. Rockwell's management suspects that one reason for this unexpected trend is that the system's price tag suits an engineering department's petty-cash budget, thus keeping accounting and purchasing departments out of the buy decision. After a project can be justified to upper management—with the Aim 65 running the software—the department gets budget approval for a development system.


An unrealistic scenario? Perhaps, but the systems are selling to people and companies who already know how a 6502 works.

Regardless of the storage capacity of these drives, it makes sense to use one write-protected disc for a system disc and one for development. Also, disc copying for backup purposes is much easier when you can perform a straight disc-to-disc copy. Why opt for discs at all? Using paper tape can add hours to each stage of the development process; a single edit-and-assemble session can take hours. Furthermore, magnetic tape is limited in speed and capacity, and more importantly, its files are strictly sequential, whereas discs support directories of named files—another factor that reduces development time. In addition, most high-level-language implementations are disc based—for large development tasks, you will want this design and development aid.

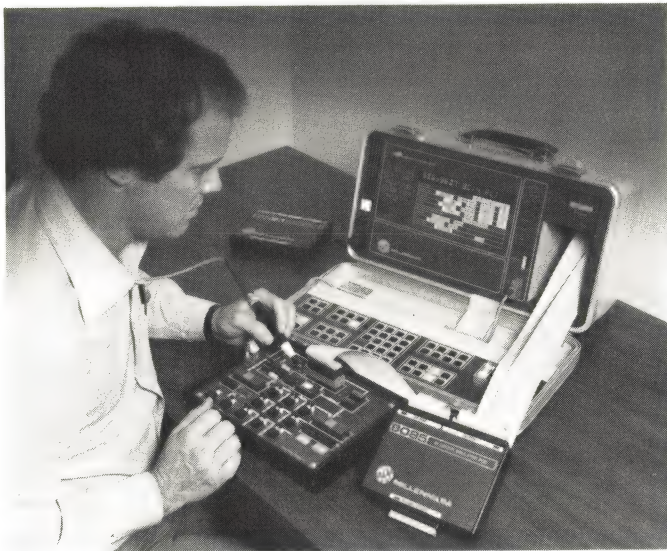- Look for a good text editor. Regardless of



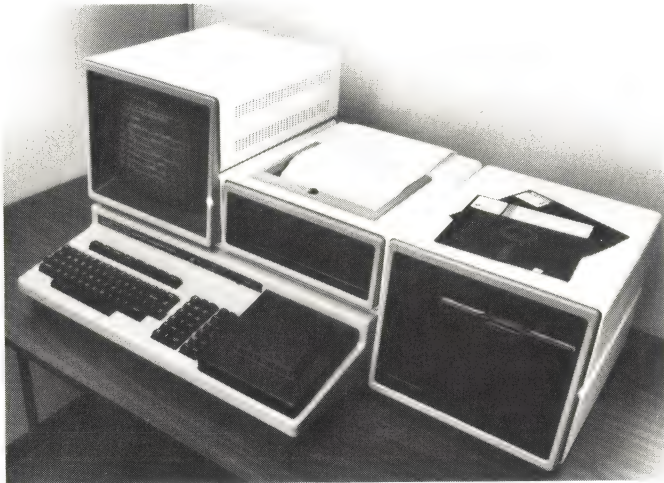Plug-in modules emulate the 6800, 8080, 8085A-2 and Z80 μ Ps, making Millennium's Microsystem Analyzer a reasonable alternative to a full development system.




Hoping to capitalize on the Starplex's nondevelopment-system capabilities, National Semiconductor expects the system to find a home with customers who can't afford to buy just a development system.

the type of development your task entails, a large percentage of your time will be spent interfacing with the editor, so ensure that it is powerful and easy to use. Compare many of these editors before committing to one.

- Large jobs require a high-speed printer. Making a top-notch programmer wait for a teletypewriter printout is akin to hiring top-notch hardware designers and making them do their own drafting.
- Make sure that the operating system provides flexible utilities. An impressive array of hardware can be misleading; you must ensure that the operating system will actually transfer data and information to desired locations and devices from designated locations and devices assigned by dynamically alterable utilities. See EDN's Software Design Course (November 20, 1978) for a description of the work you can reasonably expect an operating system to do. Some powerful operating systems are available; the bogus ones will be obvious after you spend a little time comparing systems.



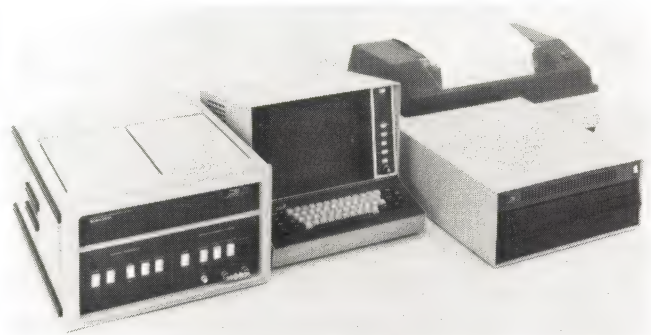Incorporating complete hardware and software for any 6800-based development task, Motorola's Exorterm 220 costs either \$8600 or \$9200, depending on whether you choose dynamic or static memory.



Designs using bit-slice μ Ps can take advantage of Advanced Micro Computers' System 29, aimed at microprogramming applications (\$18,850).

Consider the human factor

As a final consideration before deciding on a system, spend some time with a demonstrator. Type in some code; do an assembly; print out some listings. Once you purchase the system, it and its quirks become part of your work environment. *Before* you buy is the time to discover that you can't stand the clunk the discs make when the heads load, or that the printer slides across the table as it prints.

Sound a bit like kicking the tires on a used car? Perhaps it is. Perhaps it is also time to recognize that you are more efficient (substitute "cost effective" in reports to management) in a comfortable environment. And efficient production of error-free code, after all, is the sole object of buying a development system.

EDN

Article Interest Quotient (Circle One)
High 470 Medium 471 Low 472

Manufacturers of development systems and related equipment

For more information on development systems, development-system software, stand-alone emulators or general-purpose μ C systems used in development-system applications, contact these manufacturers directly or circle the appropriate numbers on the Information Retrieval Service card.

Advanced Micro Computers

901 Thompson Pl
Sunnyvale, CA 94086
(408) 732-2400
Circle No 405

American Microsystems Inc

3800 Homestead Rd
Santa Clara, CA 95051
(408) 246-0330
Circle No 406

Applied Microsystems

Box 245
Bothell, WA 98011
(206) 827-9111
Circle No 407

Compucorp

1901 S Bundy Dr
Los Angeles, CA 90025
(213) 820-5611
Circle No 408

Computer Interface Technology

2080 S Grand
Santa Ana, CA 92785
(714) 979-9920
Circle No 409

Control Logic Corp

9 Tech Circle
Natick, MA 01760
(617) 655-1170
Circle No 410

Computer Products

1400 NW 70th St
Fort Lauderdale, FL 33307
(305) 974-5500
Circle No 411

Data General Corp

Rte 9
Westboro, MA 01581
(617) 366-8911
Circle No 412

Digital Microsystems

4448 Piedmont Ave
Oakland, CA 94611
(415) 568-8650
Circle No 413

Diversified Technology

Box 465
Ridgeland, MS 39157
(601) 856-4121
Circle No 414

Fairchild Camera & Instrument Corp

MOS Div
464 Ellis St
Mt View, CA 94042
(415) 962-3371
Circle No 415

Futuredata Corp

11205 S La Cienega Blvd
Los Angeles, CA 90045
(213) 641-7700
Circle No 416

General Robotics

57 N Main St
Hartford, WI 53027
(414) 673-6800
Circle No 417

Harris Corp

Semiconductor Products Div
Box 883
Melbourne, FL 32901
(305) 724-7000
Circle No 444

Imsai Manufacturing Corp

14860 Wicks Blvd
San Leandro, CA 94544
(415) 483-2093
Circle No 418

Intel Corp

3065 Bowers Ave
Santa Clara, CA 95051
(408) 249-8027
Circle No 419

Intersil Inc

711 Stierlin Rd
Mt View, CA 94043
(408) 996-5164
Circle No 420

Microtec

Box 60337
Sunnyvale, CA 94088
(408) 733-2919
Circle No 421

Millennium Systems

19020 Pruneridge Ave
Cupertino, CA 95014
(408) 996-9109
Circle No 422

Mostek Corp

1215 W Crosby Rd
Carrollton, TX 75006
(214) 242-0444
Circle No 423

Motorola Microsystems

Box 20906
Phoenix, AZ 85036
(602) 962-3561
Circle No 424

Mupro Inc

424 Oakmead Pkwy
Sunnyvale, CA 94086
(408) 737-0500
Circle No 425

National Semiconductor

Computer Products Div
2900 Semiconductor Dr
Santa Clara, CA 95051
(408) 737-5261
Circle No 426

Northwest Microcomputer Systems

121 E Eleventh Ave
Eugene, OR 97401
(503) 485-0626
Circle No 427

Omnibyte Corp

2711-B Curtiss St
Downers Grove, IL 60515
(312) 852-8320
Circle No 428

Pertec Computer Corp

20630 Nordhoff St
Chatsworth, CA 91311
(213) 998-1800
Circle No 429

Plessey Peripheral Systems

17466 Daimler
Irvine, CA 92714
(714) 540-9945
Circle No 430

Processor Innovations

118 Oakland St
Red Bank, NJ 07701
(201) 842-8110
Circle No 431

Processor Technology Corp

7100 Johnson Industrial Dr
Pleasanton, CA 94566
(415) 829-2600
Circle No 432

Pro-Log Corp

2411A Garden Rd
Monterey, CA 93940
(408) 372-4593
Circle No 433

Quay Corp

Box 386
Freehold, NJ 07728
(201) 681-8700
Circle No 434

RCA Solid State Div

Box 3200
Somerville, NJ 08876
(201) 685-6380
Circle No 435

Rockwell International Corp

Microelectronic Devices
3310 Miraloma Ave
Anaheim, CA 92803
(714) 632-1650
Circle No 436

Signetics

811 E Arques Ave
Sunnyvale, CA 94086
(408) 739-7700
Circle No 437

Solid State Scientific Inc

1674 Commerce Dr
Montgomeryville, PA 18936
(215) 855-8400
Circle No 438

Tano Corp

4301 Poche Ct West
New Orleans, LA 70129
(504) 254-3500
Circle No 439

Tektronix Corp

Box 500
Beaverton, OR 97077
(503) 644-0161
Circle No 440

Texas Instruments Inc

Digital Systems Div
Box 1443, MS 6404
Houston, TX 77001
(713) 491-5115
Circle No 441

Western Digital Corp

3128 Red Hill Ave
Newport Beach, CA 92663
(714) 557-3550
Circle No 442

Zilog

10340 Bubb Rd
Cupertino, CA 95014
(408) 446-4666
Circle No 443

TEKTRONIX thinks your logic analyzer should be as versatile as you are

So ours let you sample *synchronously* and *asynchronously*.



Use the 7D01F
for hardware
and software
applications.

As a digital designer you must be versatile enough to do the *entire* design job. Logic and timing. Software and hardware analysis. Activity on and off the bus.

And so you need a logic analyzer that lets you synchronously verify logic and trace program flow on the bus; then asynchronously verify timing sequences and examine chip to chip transactions off the bus. A logic analyzer, in short, as versatile as you are.

Tektronix Logic Analyzers are versatile. In the synchronous mode, examine software flow using the clock of the system under test—up to 20 ns sampling rate. Switch to asynchronous and sample with the Logic Analyzer's own clock—up to 10 ns sampling rate. Pulse anomalies and timing problems are out in the open, where you can see them. With *one* logic analyzer.

Synchronous and asynchronous sampling: it helps

make our Logic Analyzers versatile. So you can do today's job and tomorrow's. So you can change applications without changing your logic analyzer.


Contact Tektronix Inc., P.O. Box 500, Beaverton, OR 97077. In Europe, Tektronix, Ltd. P.O. Box 36, St. Peter Port Guernsey, Channel Islands.

Tektronix
COMMITTED TO EXCELLENCE

For technical data Circle no 43
For demonstration Circle no 44
For immediate action dial our toll free
automatic answering service 1-800-547-1512

TEKTRONIX LOGIC ANALYZERS **THE VERSATILE ONES**


THE ONLY 32K BYTE COMPUTER FOR UNDER \$1000. (QTY=1)



**NAKED
MINI
4/10**
16 BIT CPU
W/32K BYTE RAM
\$995
LIST PRICE

Our NAKED MINI 4/10 is a genuine price/performance breakthrough. For OEM quantity discounts that'll improve your bottom line even more, call one of the following sales offices: Santa Ana, CA, (714) 546-9550; Santa Clara, CA, (408) 985-6800; Denver, CO, (303) 399-1383; Orlando, FL, (305) 896-1440; Atlanta, GA, (404) 455-1649; Elk Grove Village, IL, (312) 860-1810; Waltham, MA, (617) 890-7190;

Livonia, MI, (313) 261-5170; Bloomington, MN, (612) 854-2305; Bloomfield, NJ, (201) 338-8300; Greensboro, NC, (919) 294-5367; Cincinnati, OH, (513) 771-7530; N. Olmsted, OH, (216) 777-8700; King of Prussia, PA, (215) 265-5770; Nashville, TN, (615) 383-3315; Dallas, TX (214) 350-5681; Houston, TX, (713) 981-8859; Bethesda, MD, (301) 656-1217; Bellevue, WA, (206) 455-9650; or write us at 18651 Von Karman, Irvine, CA 92713.

 **Computer Automation**
Naked Mini Division
WHERE OEM'S COME FIRST.
For more information, Circle No 41

Top-octave generators make beautiful music

Add musical sounds to your products with top-octave generators— μ P-controllable chips providing in-tune, multiple-frequency outputs.

Bill Schweber, Instron Corp

If you're designing a product that requires audible signals to inform or attract its user, consider using a top-octave generator (TOG) IC as the tone source. Of course, as an alternative you could always use individually tuned oscillators (perhaps made from 555s), but the TOG offers the following advantages:

- A single IC provides up to 12 simultaneous pitches.
- The pitches are musically related and can be joined into pleasing combinations.
- A TOG contains no critical or drift-sensitive components; thus, its tones are always in tune with each other.
- TOG circuitry is easily expanded to produce almost any number of pitches.
- You can interface a TOG to analog and digital controlling circuitry, including μ Ps.

Top-octave generators divide and conquer

Although a basic understanding of musical pitch helps in applying a TOG (see box) the chip itself is simple and easy to use. A TOG divides a master frequency, usually one well above the audible range, by twelve different integers to produce a complete chromatic octave within the audible range. Because these output frequencies

must be related by an irrational number ($2^{1/12}$) to match the Western equal-tempered scale, no integer divisors can result in perfect pitch accuracy. In fact, the set of twelve divisors itself is not unique, because different master frequencies can be used. TOGs use the divider set tabulated in Fig 1. That set yields an octave with normally inaudible tuning errors and employs the shortest on-chip dividers.

From a practical standpoint, then, only the relative relationships of the pitches, not their absolute accuracy, are critical in determining the "correctness" of the scale as perceived by the ear. In this respect, the TOG excels. Deriving all its pitches from a master oscillator, it produces notes whose relative accuracies depend only on the digital divisors used. The master oscillator need not be especially accurate or stable, unless, for example, you are designing a tuning aid for musical instruments.

Dividers add flexibility to a TOG

A basic TOG circuit (Fig 2) consists of a master oscillator and a TOG chip like the Mostek

NOTE	EQUAL-TEMPERED FREQ AT A4 = 440 Hz	TOG DIVISOR	TOG OUTPUT FREQUENCY	PERCENT ERROR	CENTS ERROR
C	261.63 Hz	478	261.54 Hz	-0.034	-0.58
C \sharp OR D \flat	277.18 Hz	451	277.20 Hz	+0.005	+0.08
D	293.66 Hz	426	293.46 Hz	-0.069	-1.19
D \sharp OR E \flat	311.13 Hz	402	310.98 Hz	-0.046	-0.80
E	329.63 Hz	379	329.85 Hz	+0.069	+1.19
F	349.23 Hz	358	349.20 Hz	-0.007	-0.12
F \sharp OR G \flat	369.99 Hz	338	369.87 Hz	-0.034	-0.59
G	391.99 Hz	319	391.89 Hz	-0.025	-0.44
G \sharp OR A \flat	415.30 Hz	301	415.33 Hz	+0.006	+0.11
A	440.00 Hz	284	440.19 Hz	+0.044	+0.76
A \sharp OR B \flat	466.16 Hz	268	466.47 Hz	+0.066	+1.15
B	493.88 Hz	253	494.13 Hz	+0.050	+0.87

Fig 1—This TOG-output-frequency error table assumes a master-oscillator frequency of 125.015 kHz. The cents-error column has been recalculated and might differ from manufacturers' specifications.

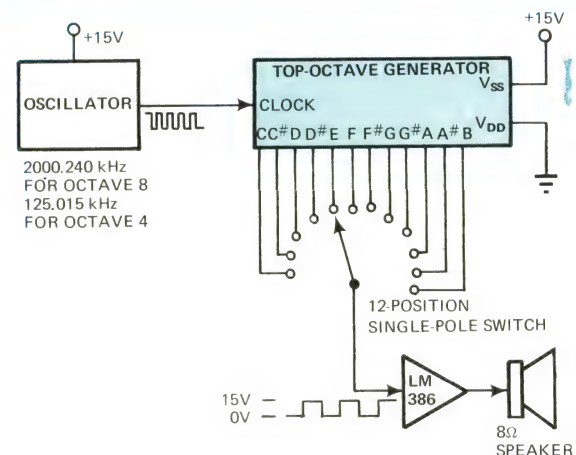


Fig 2—When constructing this basic TOG circuit, choose the master-oscillator frequency according to the desired output-frequency range.

A top-octave generator is never out of tune

MK50240. (As the nearby table shows, AMI, GI, SGS-ATES and National Semiconductor also make TOGs.) The circuit uses a single +15V supply and generates 0 to +15V square waves. All twelve pitches are available simultaneously, making system expansion easy. With the addition of a selector switch, amplifier and speaker, the circuit becomes an electronic tuning fork: To use it, match the pitch of the instrument to be tuned to the TOG note.

You can gain additional flexibility by adding a binary divider between the master oscillator and the TOG; selecting different taps of the divider chain in turn selects different octaves (Fig 3a). However, this circuit only provides one octave span at a time. You can overcome this limitation by connecting dividers to the TOG outputs instead of to the master oscillator (Fig 3b). Each stage of division produces the same note in

descending octaves, thus making the highest octave and all those below it simultaneously available.

Because TOG pitches are square waves, they can be controlled using ordinary CMOS digital gates—there is no need for more expensive analog switches. As shown in Fig 4, a level-shifting transistor implements TTL-level con-

Continued on pg 74

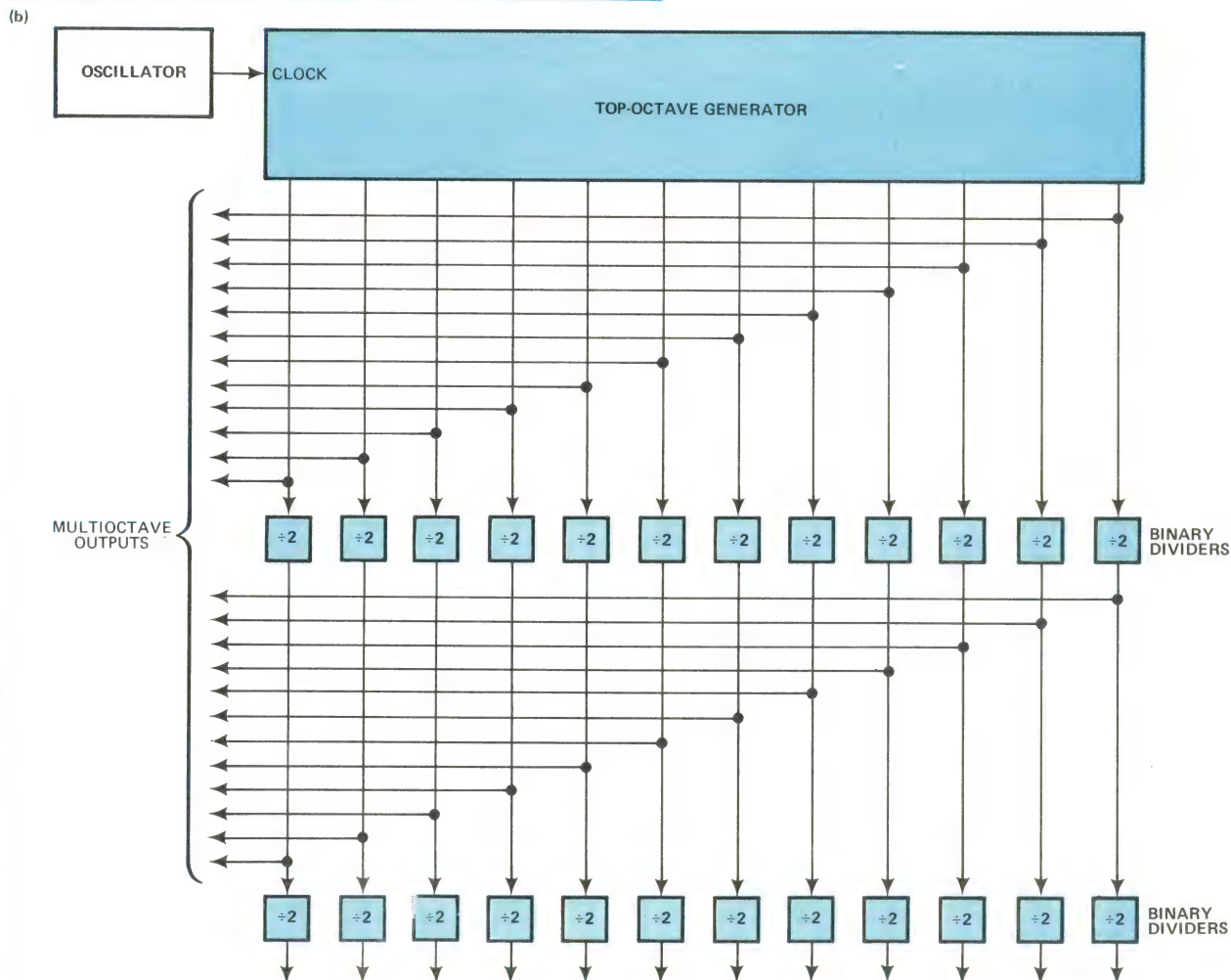
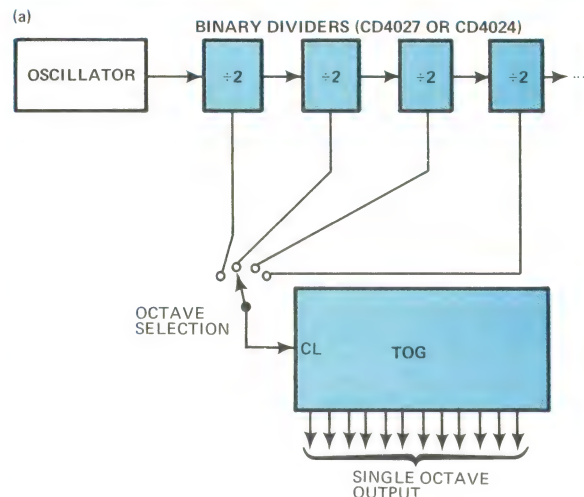


Fig 3—Adding binary dividers between the oscillator and TOG produces octave-switchable outputs (a). Placing the dividers on the TOG outputs makes all notes in all desired octaves available simultaneously (b).

Scales, spectra and common cents


David Ranada, Associate Editor

In Western music, the scale is based on the division of the octave (a 2:1 frequency ratio) into twelve relatively equally spaced pitches (logarithmically speaking). The equal-tempered system of tuning, predominant since the 18th century, has all pitches separated by the same ratio: $2^{1/12}$. With equal temperament, sharpening a note (raising it a half step or semitone; ie, multiplying its frequency by $2^{1/12}$) is musically equivalent to flattening the note above it (dividing that note's frequency by $2^{1/12}$). (Not all systems of tuning, though, retain an audible equivalence between sharpened and flattened notes.) Note that there are "natural" half steps between E and F and between B and C (see figure).

The frequency standard for musical pitches, promulgated only since the period between the two world wars, makes the A above middle C exactly equal 440 Hz; all other pitches can be derived from this standard. A top-octave generator, however, has no inherent pitch; it simply covers one octave. The octave you choose may start and end on any note at any frequency, depending on the master-oscillator frequency. By convention, however, musical octaves begin and end on Cs.

Almost all music concentrates its fundamental frequencies in the two octaves above and below middle C (261.62 Hz); remember this fact if you don't want your design to sound unnatural.

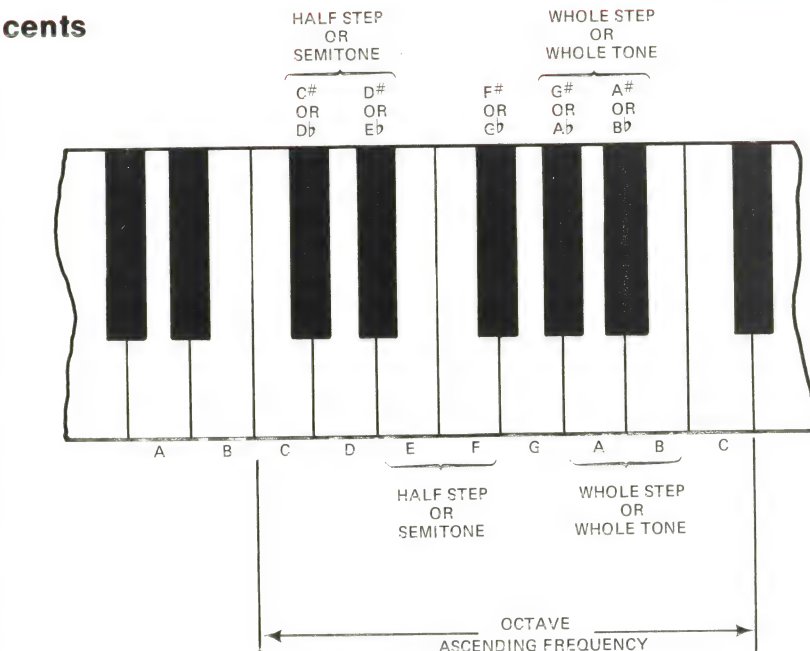The musical spectrum of a complex tone is called its timbre. Each note produced by a nonelectronic instrument exhibits a characteristic



A section of a piano keyboard illustrates the basic pitch relationship. Pitches separated by a frequency ratio of $2^{1/12}$ constitute a semitone or half step. Two adjacent semitones make up a whole step (with a frequency ratio of $2^{2/12}$). If the leftmost C were the one nearest the center of the keyboard (middle C), the A above it would have a frequency of 440 Hz.

growth and decay of the amplitudes of its harmonics in relation to each other during the note's first few milliseconds. Differences among these initial spectral fluctuations, more than the following steady-state portion of the note, enable listeners to tell musical instruments apart.

Electronic musical instruments generally have very simple initial spectrum fluctuations, if any. TOGs, being digital devices, usually output only square waves, which contain only odd harmonics (TOGs with non-50% duty cycles do contain some even harmonics, however). In contrast, all nonelectronic instruments generate some even harmonics. Thus, the lack of initial spectral fluctuations and of even harmonics makes imitating an instrument by processing TOG square waves extremely difficult.

To the piano tuner—and the tuner-machine maker—accuracy in tuning is measured in "cents." In this case,

a cent divides a semitone into 100 logarithmically spaced increments. A deviation of ± 3 cents from the correct pitch is considered barely tolerable; the best tuning machines should have errors below ± 1 cent. You can determine how far off a frequency is in cents by using the equation

$$\text{Deviation (in cents)} = (1200 / \log_2(\log(\text{frequency ratio}))).$$

A check of many of the TOGs' data sheets reveals that the published error specs are too low; keep this fact in mind. Also, when designing a piano-tuning instrument, include a provision for varying the master-oscillator frequency. All piano strings generate harmonics shifted in varying degrees from their "true" frequencies by the nonideal nature of the strings. Piano technicians compensate for this shift by tuning the harmonics and not the fundamentals. A piano that sounds "in tune" thus has deliberately mistuned fundamental frequencies.

Gain flexibility by adding binary dividers to a TOG

trol. Command signals can come from a μ P port or other digital device. With μ P control, the software merely *controls* the tone by enabling and disabling it. This method of μ P control contrasts with conventional μ P tone production, where the μ P actually *generates* the tones by toggling an output bit at the note frequency, using software timing loops or software/hardware timers and interrupts. Processor control of a TOG considerably reduces software overhead, especially if you desire simultaneous notes.

For chimes and annunciators, hardware sequencers can activate the tones in the required sequences and durations. One sequencing method uses a counter and PROM (Fig 5). Here, the counter steps slowly through the addresses of the PROM, whose output data bits then control the tones; different TOG tones are enabled each time the data lines change.

Obviously, PROM width (in bits) determines the number of tones that can be controlled simultaneously, while PROM length (in number of addresses) affects the complete sequence duration. Even a small PROM, though, can generate reasonably long tone sequences, because you can trade off sequence length against tone duration. A 2-Hz clock driving a 32-word PROM, for example, produces a 16-sec sequence with notes 0.5 sec in duration. And a 512-word PROM driven by a 10-Hz clock generates a sequence 8 min and 32 sec long, yet notes remain

controlled to 0.1 sec.

Because TOG square waves contain many odd harmonics, they might sound too "buzzy" for some applications. Filtering the outputs, however, makes a tone's timbre more natural sounding. If you are using only one octave, filtering is straightforward: A simple RC low-pass filter with a -3-dB point about an octave above the highest pitch suffices. Too much filtering, on the other hand, turns the square waves into sine waves, which sound very dull and lack crispness to the ear.

If your application requires more than two or three octaves, it's best to have a filter for each one. A single filter either cuts off too many of the higher frequencies' harmonics or allows too many of the lower frequencies harmonics to pass. Keep in mind that a piano's fundamental frequencies span a 27.5- to 4186-Hz range—7-1/2 octaves. Don't worry about phase shift in the filters; the human ear and brain are relatively insensitive (under many circumstances) to such shifts.

Simulating the sound spectrum (timbre) of a particular instrument presents a much more

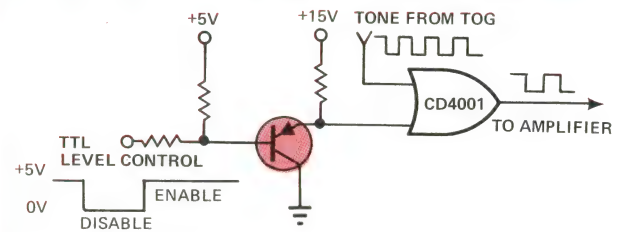


Fig 4—A level-shifting transistor implements TTL-level control over the CMOS gate that enables and disables the TOG tone.

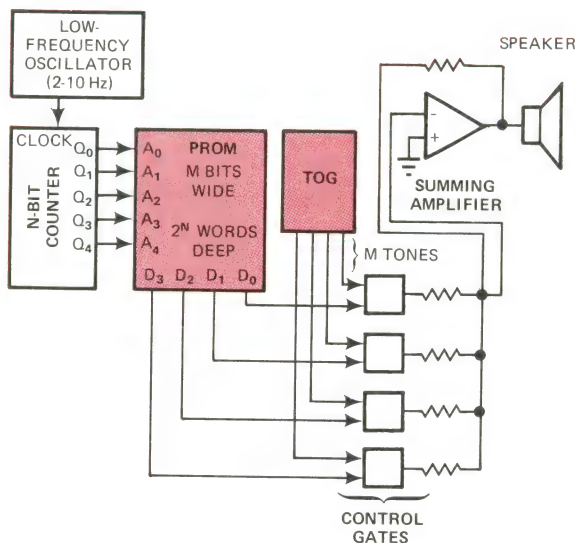


Fig 5—In a tone sequencer, the PROM is cycled through its addresses, and its output bits control the TOG outputs. The PROM can generate any sequence and combination of tones.

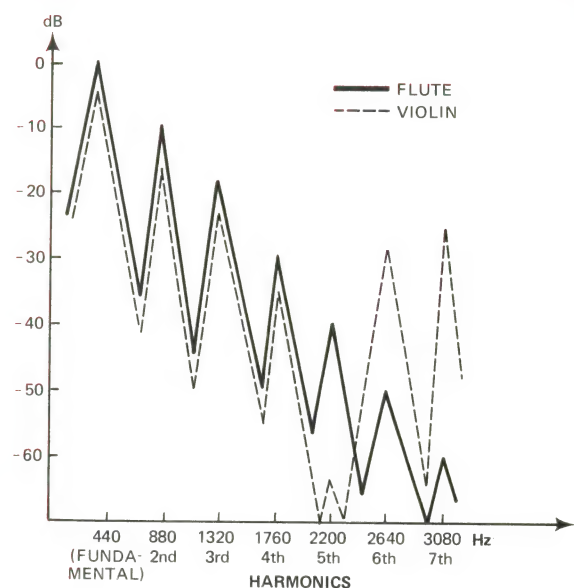


Fig 6—The differing harmonics of the same fundamental tone (440 Hz) for a flute and a violin illustrate the difficulty involved in filtering TOG output to simulate a specific instrument.

[Faint, illegible handwritten notes]

voltage change and load regulation rated at $\pm 0.1\%$ Optional on all models except EMA-A, ETA-B.

	EMA A	EMA B	EMA C	EMA D	EMA E	EMA F	EMA G	EMA H	EMA I	EMA J	EMA K	EMA L	EMA M	EMA N	EMA O	EMA P	EMA Q	EMA R	EMA S	EMA T	EMA U	EMA V	EMA W	EMA X	EMA Y	EMA Z	EMA AA	EMA AB	EMA AC	EMA AD	EMA AE	EMA AF	EMA AG	EMA AH	EMA AI	EMA AJ	EMA AK	EMA AL	EMA AM	EMA AN	EMA AO	EMA AP	EMA AQ	EMA AR	EMA AS	EMA AT	EMA AU	EMA AV	EMA AW	EMA AX	EMA AY	EMA AZ	EMA BA	EMA BB	EMA BC	EMA BD	EMA BE	EMA BF	EMA BG	EMA BH	EMA BI	EMA BJ	EMA BK	EMA BL	EMA BM	EMA BN	EMA BO	EMA BP	EMA BQ	EMA BR	EMA BS	EMA BT	EMA BU	EMA BV	EMA BW	EMA BX	EMA BY	EMA BZ	EMA CA	EMA CB	EMA CC	EMA CD	EMA CE	EMA CF	EMA CG	EMA CH	EMA CI	EMA CJ	EMA CK	EMA CL	EMA CM	EMA CN	EMA CO	EMA CP	EMA CQ	EMA CR	EMA CS	EMA CT	EMA CU	EMA CV	EMA CW	EMA CX	EMA CY	EMA CZ	EMA DA	EMA DB	EMA DC	EMA DD	EMA DE	EMA DF	EMA DG	EMA DH	EMA DI	EMA DJ	EMA DK	EMA DL	EMA DM	EMA DN	EMA DO	EMA DP	EMA DQ	EMA DR	EMA DS	EMA DT	EMA DU	EMA DV	EMA DW	EMA DX	EMA DY	EMA DZ	EMA EA	EMA EB	EMA EC	EMA ED	EMA EE	EMA EF	EMA EG	EMA EH	EMA EI	EMA EJ	EMA EK	EMA EL	EMA EM	EMA EN	EMA EO	EMA EP	EMA EQ	EMA ER	EMA ES	EMA ET	EMA EU	EMA EV	EMA EW	EMA EX	EMA EY	EMA EZ	EMA FA	EMA FB	EMA FC	EMA FD	EMA FE	EMA FF	EMA FG	EMA FH	EMA FI	EMA FJ	EMA FK	EMA FL	EMA FM	EMA FN	EMA FO	EMA FP	EMA FQ	EMA FR	EMA FS	EMA FT	EMA FU	EMA FV	EMA FW	EMA FX	EMA FY	EMA FZ	EMA GA	EMA GB	EMA GC	EMA GD	EMA GE	EMA GF	EMA GG	EMA GH	EMA GI	EMA GJ	EMA GK	EMA GL	EMA GM	EMA GN	EMA GO	EMA GP	EMA GQ	EMA GR	EMA GS	EMA GT	EMA GU	EMA GV	EMA GW	EMA GX	EMA GY	EMA GZ	EMA HA	EMA HB	EMA HC	EMA HD	EMA HE	EMA HF	EMA HG	EMA HH	EMA HI	EMA HJ	EMA HK	EMA HL	EMA HM	EMA HN	EMA HO	EMA HP	EMA HQ	EMA HR	EMA HS	EMA HT	EMA HU	EMA HV	EMA HW	EMA HX	EMA HY	EMA HZ	EMA IA	EMA IB	EMA IC	EMA ID	EMA IE	EMA IF	EMA IG	EMA IH	EMA II	EMA IJ	EMA IK	EMA IL	EMA IM	EMA IN	EMA IO	EMA IP	EMA IQ	EMA IR	EMA IS	EMA IT	EMA IU	EMA IV	EMA IW	EMA IX	EMA IY	EMA IZ	EMA JA	EMA JB	EMA JC	EMA JD	EMA JE	EMA JF	EMA JG	EMA JH	EMA JI	EMA JJ	EMA JK	EMA JL	EMA JM	EMA JN	EMA JO	EMA JP	EMA JQ	EMA JR	EMA JS	EMA JT	EMA JU	EMA JV	EMA JW	EMA JX	EMA JY	EMA JZ	EMA KA	EMA KB	EMA KC	EMA KD	EMA KE	EMA KF	EMA KG	EMA KH	EMA KI	EMA KJ	EMA KK	EMA KL	EMA KM	EMA KN	EMA KO	EMA KP	EMA KQ	EMA KR	EMA KS	EMA KT	EMA KU	EMA KV	EMA KW	EMA KX	EMA KY	EMA KZ	EMA LA	EMA LB	EMA LC	EMA LD	EMA LE	EMA LF	EMA LG	EMA LH	EMA LI	EMA LJ	EMA LK	EMA LL	EMA LM	EMA LN	EMA LO	EMA LP	EMA LQ	EMA LR	EMA LS	EMA LT	EMA LU	EMA LV	EMA LW	EMA LX	EMA LY	EMA LZ	EMA MA	EMA MB	EMA MC	EMA MD	EMA ME	EMA MF	EMA MG	EMA MH	EMA MI	EMA MJ	EMA MK	EMA ML	EMA MM	EMA MN	EMA MO	EMA MP	EMA MQ	EMA MR	EMA MS	EMA MT	EMA MU	EMA MV	EMA MW	EMA MX	EMA MY	EMA MZ	EMA NA	EMA NB	EMA NC	EMA ND	EMA NE	EMA NF	EMA NG	EMA NH	EMA NI	EMA NJ	EMA NK	EMA NL	EMA NM	EMA NN	EMA NO	EMA NP	EMA NQ	EMA NR	EMA NS	EMA NT	EMA NU	EMA NV	EMA NW	EMA NX	EMA NY	EMA NZ	EMA OA	EMA OB	EMA OC	EMA OD	EMA OE	EMA OF	EMA OG	EMA OH	EMA OI	EMA OJ	EMA OK	EMA OL	EMA OM	EMA ON	EMA OO	EMA OP	EMA OQ	EMA OR	EMA OS	EMA OT	EMA OU	EMA OV	EMA OW	EMA OX	EMA OY	EMA OZ	EMA PA	EMA PB	EMA PC	EMA PD	EMA PE	EMA PF	EMA PG	EMA PH	EMA PI	EMA PJ	EMA PK	EMA PL	EMA PM	EMA PN	EMA PO	EMA PP	EMA PQ	EMA PR	EMA PS	EMA PT	EMA PU	EMA PV	EMA PW	EMA PX	EMA PY	EMA PZ	EMA QA	EMA QB	EMA QC	EMA QD	EMA QE	EMA QF	EMA QG	EMA QH	EMA QI	EMA QJ	EMA QK	EMA QL	EMA QM	EMA QN	EMA QO	EMA QP	EMA QQ	EMA QR	EMA QS	EMA QT	EMA QU	EMA QV	EMA QW	EMA QX	EMA QY	EMA QZ	EMA RA	EMA RB	EMA RC	EMA RD	EMA RE	EMA RF	EMA RG	EMA RH	EMA RI	EMA RJ	EMA RK	EMA RL	EMA RM	EMA RN	EMA RO	EMA RP	EMA RQ	EMA RR	EMA RS	EMA RT	EMA RU	EMA RV	EMA RW	EMA RX	EMA RY	EMA RZ	EMA SA	EMA SB	EMA SC	EMA SD	EMA SE	EMA SF	EMA SG	EMA SH
--	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	-------	--------	--------	--------	--------	--------

Self-restoring current limiting (foldback type).

depth and ready to be shipped the same day your order

Cooling

EMA-A, ETA-B

EMA-D, ETA-C, D, ETR-E 4 Surfaces

at 47-63 Hz. Derate output current 10% for 50Hz

order. Every model shown on this page is stocked in

Regulation

So, if you're looking for an economically priced

500,000 in the field and still going strong) just give Better than 1mV RMS; 3mV peak to peak

us a call.		EMA-A, ETA-B	2 Surfaces
Your supplies are waiting . . . so <u>you</u> won't have to.	Remote Sense	EMA-A, ETA-B	3 Surfaces
	All except EMA-A, ETA-B.	EMA-B, C, CC	4 Surfaces
		EMA-D, ETA-C, D, ETR-E	

EMA "A" CASE \$27.00 1.7" X 3.03" X 3.78"			EMA "B" CASE \$35.00 2.07" X 4.00" X 4.87"			EMA "C" CASE \$59.00 2.95" X 4.87" X 5.62"			EMA "CC" CASE \$74.00 3.23" X 4.90" X 7.03"			EMA "D" CASE \$94.00 3.23" X 4.87" X 9.00"		
Model	Voltage/Current Rating Chart		Model	Voltage/Current Rating Chart		Model	Voltage/Current Rating Chart		Model	Voltage/Current Rating Chart		Model	Voltage/Current Rating Chart	
EMA-5/6A	5V @ 1.2A 6V @ 1.0A		EMA-5/6B	5V @ 3.0A 6V @ 2.5A		EMA-5/6C	5V @ 6.0A 6V @ 5.0A		EMA-5/6CC	5V @ 11.0A 6V @ 10.0A		EMA-5/6D	5V @ 15.0A 6V @ 12.5A	
EMA-9/10A	9V @ .75A 10V @ .75A		EMA-9/10B	9V @ 1.8A 10V @ 1.8A		EMA-9/10C	9V @ 3.8A 10V @ 3.6A		EMA-9/10CC	9V @ 8.0A 10V @ 7.5A		EMA-9/10D	9V @ 10.5A 10V @ 10.0A	
EMA-12/15A	12V @ 0.5A 15V @ 0.5A		EMA-12/15B	12V @ 1.5A 15V @ 1.3A		EMA-12/15C	12V @ 3.0A 15V @ 2.8A		EMA-12/15CC	12V @ 6.0A 15V @ 5.0A		EMA-12/15D	12V @ 8.8A 15V @ 8.0A	
EMA-18/20A	18V @ 0.4A 20V @ 0.4A		EMA-18/24B	18V @ 1.2A 20V @ 1.0A		EMA-18/20C	18V @ 2.5A 20V @ 2.3A		EMA-18/24CC	18V @ 4.5A 20V @ 4.0A		EMA-18/24D	18V @ 7.1A 20V @ 7.0A	
EMA-24A	24V @ 0.4A			24V @ 1.0A		EMA-24C	24V @ 2.3A			24V @ 3.8A			24V @ 6.5A	

ETA "C" CASE \$68.00 2.98" X 4.03" X 7.90"		ETA "B" CASE \$48.00 2.25" X 4.03" X 4.90"		ETA "D" CASE \$96.00 3.23" X 4.90" X 9.40"		ETR "E" CASE \$115.00 2.20" X 4.88" X 11.00"	
Model	Voltage/Current Rating Chart	Model	Voltage/Current Rating Chart	Model	Voltage/Current Rating Chart	Model	Voltage/Current Rating Chart
ETA-12/15C	12V-1.5A 12V-1.5A or 15V-1.3A or 15V-1.3A	ETA-12/15B	12V-0.5A 12V-0.5A or 15V-0.5A or 15V-0.5A	ETA-12/15D	12V-3.0A 12V-3.0A or 15V-2.8A or 15V-2.8A	ETR-122E	5V,6A + 12V,1.5A — 12V,1.5A or 6V,5.5A or + 15V,1.3A or — 15V,1.3A
ETA-5C	5V-3.0A 5V-3.0A or 6V-2.5A or 6V-2.5A	ETA-5B	5V-1.2A 5V-1.2A or 6V-1.0A or 6V-1.0A	ETA-5D	5V-6.0A 5V-6.0A or 6V-5.0A or 6V-5.0A	ETR-142E	5V,6A 12V,1.5A or 6V,5A or 9V,1.2A or 15V,1.3A or 5V,0.8A
ETA-515C	5V-3.0A 15V-1.3A or 6V-2.5A or 12V-1.5A	ETA-515B	5V-1.2A 15V-0.5A or 6V-1.0A or 12V-0.5A	ETA-515D	5V-6.0A 15V-2.8A or 6V-5.0A or 12V-3.0A	ETR-113E	5V,6A 5V,3A 18V,1.0A or 6V,5A or 6V,2.5A or 20V,1.0A or 24V,1.0A
ETA-524C	5V-3.0A 24V-1.0A or 6V-2.5A	ETA-524B	5V-1.2A 24V-0.4A or 6V-1.0A	ETA-524D	5V-6.0A 24V-2.3A or 6V-5.0A	ETR-132E	5V,6A 18V,1.0A or 6V,5A or 20V,1.0A or 15V,1.3A or 24V,1A

Circle No. 42

Preferred for their quality, precision and small size.

(Their low, low price is a pleasant surprise.)

Digital Multimeter	DM 450	DM 350	DM 235	PDM 35
Digits	4½	3½	3½	3½
Functions*	6	6	6	5
Ranges	34	34	21	21
Basic Accuracy	0.05%	0.1%	0.5 to 1.5%	1 to 1.5%
Price, Qty. One	\$199.00	\$139.00	\$89.00	\$59.95

*Resistance; DC Voltage; DC Current; AC Voltage; AC Current; and Diode Test on all except PDM 35 which does not have AC Current.



Sinclair

SINCLAIR RADIONICS, INC.

Plaza 66, 66 Mount Prospect Ave., Clifton, New Jersey 07013
(201) 472-7600 Toll Free (800) 526-7845 (except New Jersey)

SALES REPRESENTATIVES

Alabama Rakes Engineering & Marketing Corp. (REMC0) Tel: 205-883-9260 Arizona Par Associates Tel: 505-881-5000 Northern California International Standard Components Tel: 415-964-4171 Southern California Interstate Marketing Assoc. Tel: 213-883-7606	Colorado Par Associates Tel: 303-355-2363 Connecticut Datcom Tel: 203-288-7005 203-248-0100 Delaware Omega Electronic Sales Tel: 215-947-4135 Florida QXI Inc. Tel: 305-331-0341 (North) 305-485-6030 (South) 813-821-2281	Georgia Rakes Eng. & Mktg. Corp. TEL: 404-476-1730 Illinois (Northern) Microsales Tel: 312-956-1000 Indiana Jack Harvey & Assoc. Tel: 317-297-1441 Maryland Tri Mark Tel: 301-768-2800	Massachusetts Datcom Tel: 617-891-4600 Michigan Electronic Salesmasters Tel: 800-321-1848 Minnesota Quantum Sales, Inc. Tel: 612-831-8583 New Jersey (Northern) Crane & Egert Tel: 516-488-2100	New Jersey (Southern) Omega Electronic Sales Tel: 215-947-4135 New Mexico Par Assoc. Tel: 505-881-5000 New York (Downstate) Crane & Egert Tel: 516-488-2100 New York (Upstate) Nyccom Tel: 315-437-8343	North Carolina Rakes Eng. & Mktg. Corp. Tel: 919-787-1461 North Dakota Quantum Sales, Inc. Tel: 612-831-8583 Ohio Electronic Salesmasters Tel: 216-831-9555 800-362-2616 Pennsylvania (Eastern) Omega Electronic Sales Tel: 215-947-4135	Pennsylvania (Western) Electronic Salesmasters Tel: 800-321-1848 South Dakota Quantum Sales, Inc. Tel: 612-831-8583 Texas Par Associates Tel: 505-881-5000 Virginia Tri Mark Tel: 301-768-2800	Washington, D.C. Tri Mark Tel: 301-768-2800 West Virginia Electronic Salesmasters Tel: 800-321-1848 Wisconsin (Eastern) Microsales Tel: 312-956-1000 Wisconsin (Western) Quantum Sales, Inc. Tel: 612-831-8583
---	--	---	--	--	--	---	---

INDUSTRIAL DISTRIBUTORS

Alabama Pioneer Standard Tel: 205-837-9300 Arizona Metermaster Tel: 602-243-4111	California Metermaster Tel: 213-685-4340 Florida Metermaster Tel: 415-968-0313 Illinois Metermaster Tel: 714-560-4841	Canada Gladstone Electronics Tel: 416-787-1448 Florida Pioneer Standard Tel: 305-859-3600	Georgia Southern Peripherals Tel: 404-455-3518 Illinois Metermaster Tel: 312-593-8650 Indiana Pioneer Standard Tel: 312-437-9680	Massachusetts Impact Electronics Tel: 617-964-7740 Michigan Startronic Tel: 313-477-7700	New York Ossman Instruments Tel: 315-437-6666 North Carolina Pioneer Standard Tel: 919-273-4441	Ohio Pioneer Standard Tel: 216-587-3600 Pennsylvania Pioneer Standard Tel: 215-674-4000 South Carolina Southern Peripherals Tel: 803-233-1469 Texas Metermaster Tel: 214-271-5671 Virginia Scientific Enterprises Tel: 703-573-8787
---	--	--	---	---	--	--

For more information, Circle No 45

VENDOR	IC NO	INPUT FREQ RANGE (kHz)	NUMBER OF OUTPUTS	OUTPUT DUTY CYCLE	MAXIMUM SPECIFIED ERROR (CENTS)	POWER SUPPLIES (V)	POWER (mW)	NOTES
NATIONAL SEMICONDUCTOR	MM5555	7-2200	7	30%	0.51	-27, -14, -10	650	G TO C
	MM5556	7-2200	6	30%	0.51	-27, -14, -10	650	C# TO F#
	MM5832	7-2100	7	30%	1.16	-27, -14, -10	585	G TO C
	MM5833	7-2100	6	30%	1.16	-27, -14, -10	585	C# TO F#
	MM5891AA	100-2500	13	50%	1.16	-11 TO -16	560	5891AB WITH 30% DUTY CYCLE
GENERAL INSTRUMENT	AY-1-0212	250-1500	12	50%	1.16	-12 TO -16, -23 TO -28	750	HIGH ACCURACY
	AY-1-0212A	250-2500	12	50%	1.16	-12 TO -16, -23 TO -28	750	
	AY-3-0214	100-4500	12	50%	0.5	+10 TO +16	1.9W	
	AY-3-0215	100-4500	13	50%	1.16	+10 TO +16	1.9W	
	AY-3-0216	100-4500	13	30%	1.16	+10 TO +16	1.9W	
MOSTEK	MK50240	100-2500	13	50%	1.16	-11 TO -16	600	
	MK50241	100-2500	13	30%	1.16	-11 TO -16	600	
	MK50242	100-2500	12	50%	1.16	-11 TO -16	600	
AMI	550240	100-2500	13	50%	1.16	-11 TO -16	600	
	550241	100-2500	13	30%	1.16	-11 TO -16	600	
	550242	100-2500	12	50%	1.16	-11 TO -16	600	
	550243	100-800	13	50%	1.16	-11 TO -16	600	
	550244	100-800	13	30%	1.16	-11 TO -16	600	
	550245	100-800	12	50%	1.16	-11 TO -16	600	
SGS-ATES	M 087	15-2500	12	NA	1.16	-5, +5, -12	400	

The specifications on these TOGs come from their manufacturers' data sheets.


difficult challenge. Because of the different amplitudes of its harmonics, a flute note sounds very different from the same pitch on a violin (Fig 6). Note that for the flute, each harmonic's amplitude decreases about 10 dB from the

preceding one. For the violin, the fifth harmonic is negligible, but the sixth and seventh harmonics are louder than the fourth. Piano spectra, incidentally, are extremely complex and difficult to recreate electronically.

EDN

Author's biography

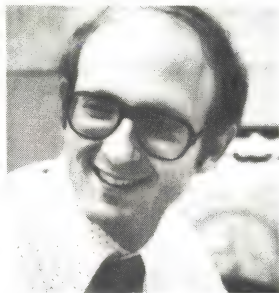Bill Schweber, an engineer with Instron Corp, Canton, MA, designs μ P-based controls for materials-testing equipment. He received a BS degree from Columbia University and an MS from the University of Massachusetts. Bill's hobbies include bicycling, photography and model railroading.



Article Interest Quotient (Circle One)

High 473 Medium 474 Low 475

Manufacturers of top-octave-generator ICs

For more information on top-octave generators and other music-related circuits, contact these manufacturers directly or circle the appropriate number on the Information Retrieval Service card.


American Microsystems Inc
3800 Homestead Rd
Santa Clara, CA 95051
(408) 246-0330
Circle No 446

General Instrument Corp
Microelectronics Div
600 W John St
Hicksville, NY 11802
(516) 733-3107
Circle No 447

Mostek Corp
1215 W Crosby Rd
Carrollton, TX 75006
(214) 242-0444
Circle No 448

National Semiconductor Corp
2900 Semiconductor Dr
Santa Clara, CA 95051
(408) 737-5000
Circle No 449

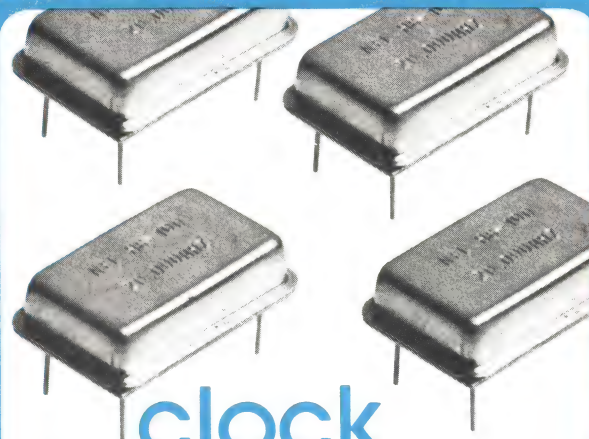SGS-ATES
79 Massasoit St
Waltham, MA 02154
(617) 891-3710
Circle No 445




clock oscillators

Let NEL's years of frequency control experience work for you. Our clock oscillators are available over the frequency range 600~ to 60 MHz. We supply either TTL or CMOS compatible units in our all-metal, resistance weld sealed Dip package. Write or call for Data Sheets 7810A (TTL), 7810B (CMOS), or 7902A (Overtone).



*Northern Engineering
Laboratories, Inc.*

357 BELOIT ST., BURLINGTON, WI 53105 (414) 763-3591

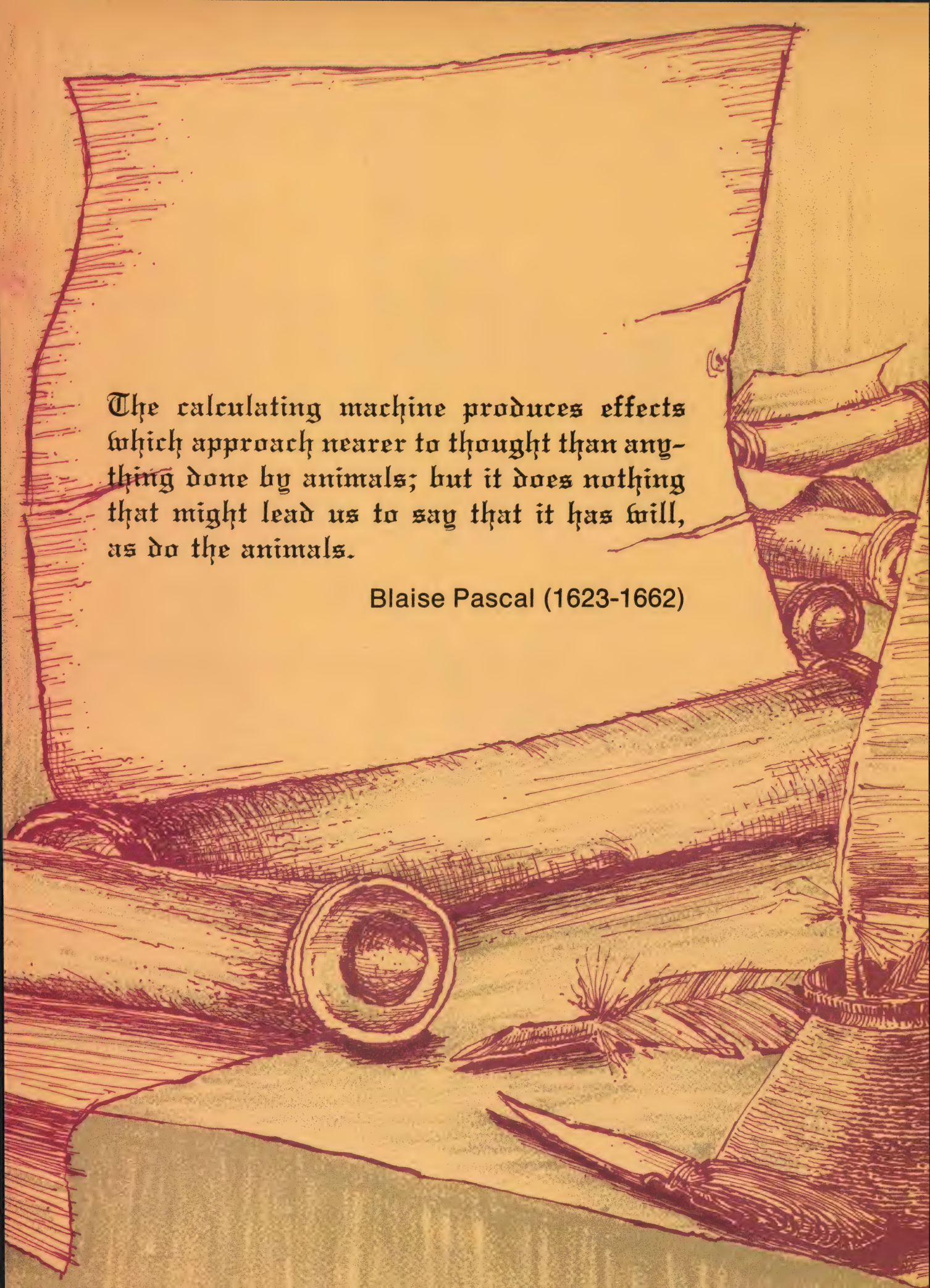A detailed illustration in a reddish-brown ink style. It features a large, unrolled scroll that dominates the lower half of the image. The scroll has a textured, fibrous appearance. To the right of the scroll, a quill pen lies horizontally. The quill has a long, straight shaft and a small, dark, feathery tip. The background is a light, textured surface, possibly a piece of parchment or paper. The overall style is reminiscent of a woodcut or a detailed pen-and-ink drawing.

The calculating machine produces effects
which approach nearer to thought than any-
thing done by animals; but it does nothing
that might lead us to say that it has will,
as do the animals.

Blaise Pascal (1623-1662)

PASCAL

With origins in the academic world, PASCAL has now become the darling of commercial computer makers and users. Why this enthusiasm? And what can the language do for you?

Jack Hemenway and Edward Teja,
Associate Editors

In the rush to be the first into print with statements and comments about a new language, the obvious facts—what the language offers and what its disadvantages are—often get lost in the shuffle. Here we tune into a description of what PASCAL is, how it is implemented (including the differences of opinion among implementers) and what it offers to programmers.

Pascal wasn't a programmer

Niklaus Wirth drafted the first version of PASCAL in 1968; he designed it as a teaching tool and incorporated into it the valuable features of older languages. PASCAL grew out of the ALGOL family of languages and thus has proved easy to learn, highly readable and easy to compile. Today nearly every manufacturer of computers is either currently selling or promising future availability of a version of the language on its machines.

It's important to stress the words "a version," because there is no one "Version," or even a PASCAL standard. Despite the numerous descriptions extant, PASCAL is not yet officially defined.

In order of popularity, there are three possible standards. Industrial μ C users and makers tend to favor the version being sold by the University of California at San Diego (UCSD)—largely because of its \$200 price. Both the IEEE PASCAL Standards Committee and the ANSI X3J9 technical committee are considering a document presented to them by the International Standards Organization (ISO)—a document originated by a working group within the British Standards Institution (BSI) and spearheaded by A M Addyman of the University of Manchester. The third standard is simply a referral back to the Wirth book—all proposed versions seem to claim this historical link to some extent.

Nor is this the end of the confusion. UCSD endorses the BSI document as a definition of the basic language, yet not as a complete standard. The PASCAL User's Group (headquartered at the University of Minnesota) is pushing hard to have the BSI document adopted as it stands. And certain corporate representatives present at the recent ANSI meeting expressed serious reservations about letting "academics" such as Wirth and UCSD's Kenneth Bowles play any significant role in the serious matter of defining a commercial-language standard.

Making the world structured

The catch phrase for PASCAL is structured programming—in the sense of block structure in the style of ALGOL. The concept refers to the process of declaring identifiers inside a procedure or function that have no meaning outside that subprogram. Alternatively, identifiers declared outside a subprogram can generally be used inside it. The specific set of rules governing this process constitutes PASCAL's scope rules.

The PASCAL format thus supports

The PASCAL mania

Everywhere you look today, it seems as though there is another article on PASCAL; the interest in the language appears intense enough to classify it as a fad. Posters of Blaise Pascal decorate booths at computer shows; books by Niklaus Wirth and Kathleen Jensen, and more recently by Dr Kenneth Bowles of the University of California at San Diego, turn out to be their publishers' best-selling textbooks; Dr Bowles finds himself facing 350 students in this semester's PASCAL course.

In short, a language written to teach programmers how to program has become the rage outside academia. This Special Report helps resolve the resulting trauma and confusion.

Interpretive versions of PASCAL don't usually support interrupts

a responsive chord in the marketplace.)

Manufacturers find the PASCAL Microengine technique practical in one important respect—the PASCAL it implements is UCSD's; if the industry standardizes on another version, all Western Digital must do is alter the microcode to accommodate that version. An additional benefit arises directly from UCSD's incarnation of the language—the software package that provides the interpreter also furnishes a complete operating system, an editor and BASIC capability.



PASCAL versus disc systems

Lack of I/O capability represents PASCAL's major drawback. Because business-oriented I/O is given short shrift in computer-science classrooms, it accordingly receives similar treatment

in the Jensen/Wirth draft. The emphasis in an "ideal" classroom language centers on teaching algorithms, rather than relating a program to its environment (peripherals). Thus, the language places little emphasis on random and indexed-sequential (ISAM) files—these are of serious concern to the commercial programmer and anyone with hopes of competing in a commercial setting.

On the other hand, available PASCAL compilers have given rise to controversy merely because they *attempt* to provide customers with a state-of-the-art I/O package; some PASCAL boosters shriek at any deviance from Jensen and Wirth.

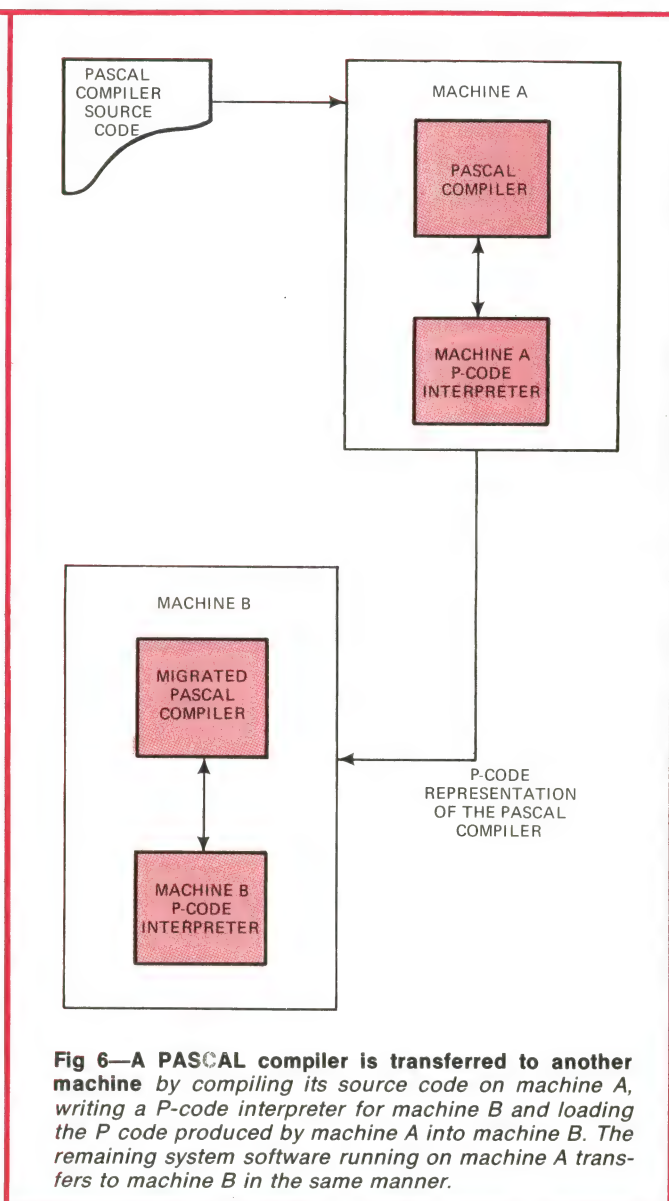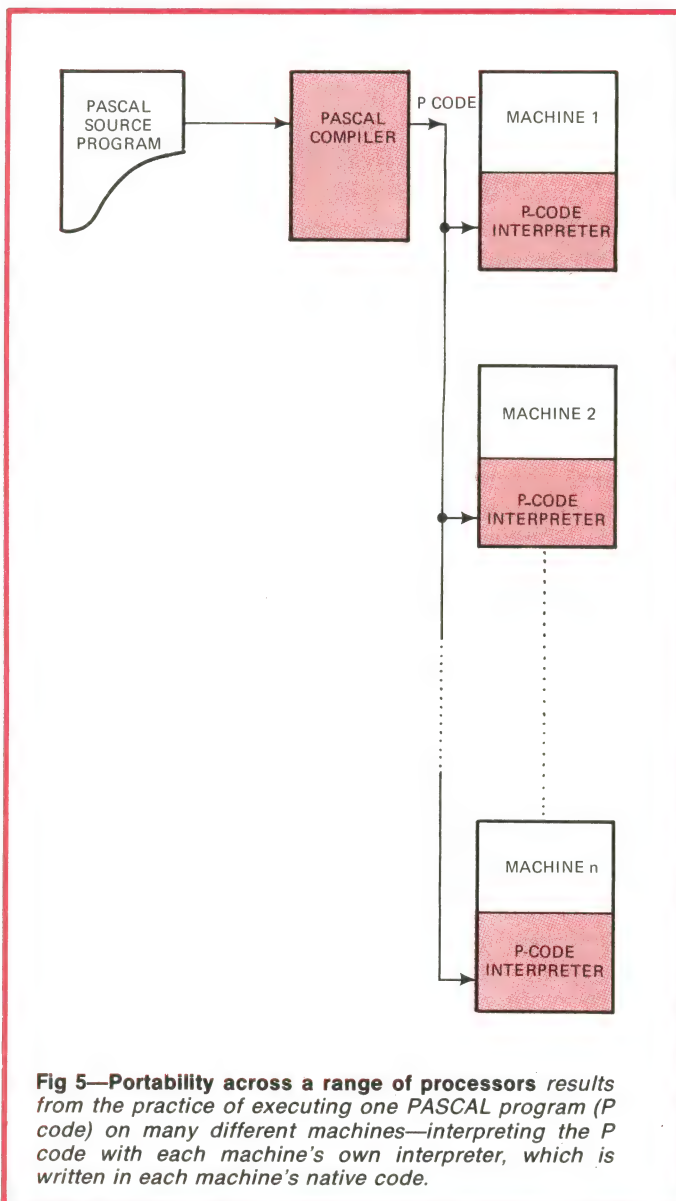However, the fact remains that Jensen and Wirth did not define adequate I/O capabilities for business applications, and adherents who wish to create a PASCAL standard must thus deal with a complete overhaul of the language's I/O package—which could mean creating extensions. UCSD's version, for example, furnishes both the



Jensen/Wirth tape-I/O capability and extensions to provide disc I/O; the operating system assumes that I/O is disc-based unless the operator specifies otherwise. According to UCSD's Dr Bowles, this procedure, although it accommodates the commercial user's day-to-day applications, is frowned upon by language purists.

In any event, the question of I/O must be resolved before use of the language makes any sense in a real-world computer system. When you're evaluating various PASCAL compilers, this capability (or the lack of it) can be a good starting point.

PASCAL escalation escalates

And so PASCAL expands its influence. This year alone, Apple Computer, Cromemco and Heath, to name a few firms, will add UCSD PASCAL to their offerings. Responding to market pressure, Intel intends to produce a PASCAL compiler for the 8086, although the firm is also maintaining a definite commitment to PL/M. Furthermore, rumor has it that a UCSD-based compiler will appear on Intel's Intellec system, running under ISIS. Finally, National Semiconductor talks of making PASCAL an in-house standard. In many companies, it already is—standard version or no.


EDN

References

1. Findlay, W; Walt, D A, *PASCAL: An Introduction to Methodical Programming*, Computer Science Press Inc, 1978.
2. Grogono, Peter, *Programming in PASCAL*, Addison-Wesley Publishing Co Inc, 1978.
3. Wirth, Niklaus, *Algorithms+Data Structures=Programs*, Prentice-Hall Inc, 1976.
4. Bowles, K L, "UCSD PASCAL: A (Nearly) Machine Independent Software System (for Microcomputers and Minicomputers)", *Byte*, May 1978.
5. PASCAL News, No 14, January 1979.
6. Addyman, A M, "A Draft Description of PASCAL."
7. Model 990 Computer TI PASCAL User's Manual, Texas Instruments Inc, Digital Systems Div, 1978.
8. Bowles, K L, "UCSD (Mini-Micro Computer) PASCAL, Release Version 1.4," 1978.
9. ESI PASCAL Reference Manual, Electro Scientific Industries, 1978.
10. Jensen, K; Wirth, N, *PASCAL User Manual and Report*, Springer-Verlag Publishers, 1978.

Article Interest Quotient (Circle One)
High 476 Medium 477 Low 478


Dialight illuminated switches

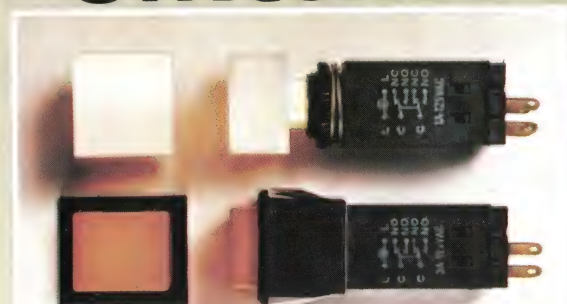

554 SERIES Snap-action illuminated switches with gold or silver contacts . . . Wiping-action switches with gold contacts. Rated life: up to 750,000 operations. Bezel or panel mounting available. Choice of over 300 cap shapes, sizes and colors . . . choice of legends. Listed by Underwriters Laboratories and CSA approved.



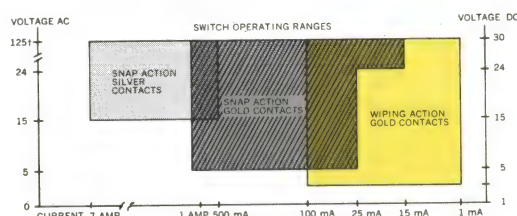554 SERIES A variety of over 240 illuminated switches to choose from with momentary or alternate actions. Low cost . . . computer grade, easy mounting. Over 100,000 switch combinations.



This chart is intended to be used as a general guide only.
†125 VAC applies to snap action switches only.


554 SERIES You'll find a Dialight illuminated switch within your desired operating range. The above chart will make your selection easier.

Dialight meets your needs. So talk to the specialists at Dialight, first. Send for your free copy of Dialight's current catalog today.

DIALIGHT

Dialight, A North American Philips Company
203 Harrison Place, Brooklyn, N. Y. 11237
(212) 497-7600


For more information, Circle No 47

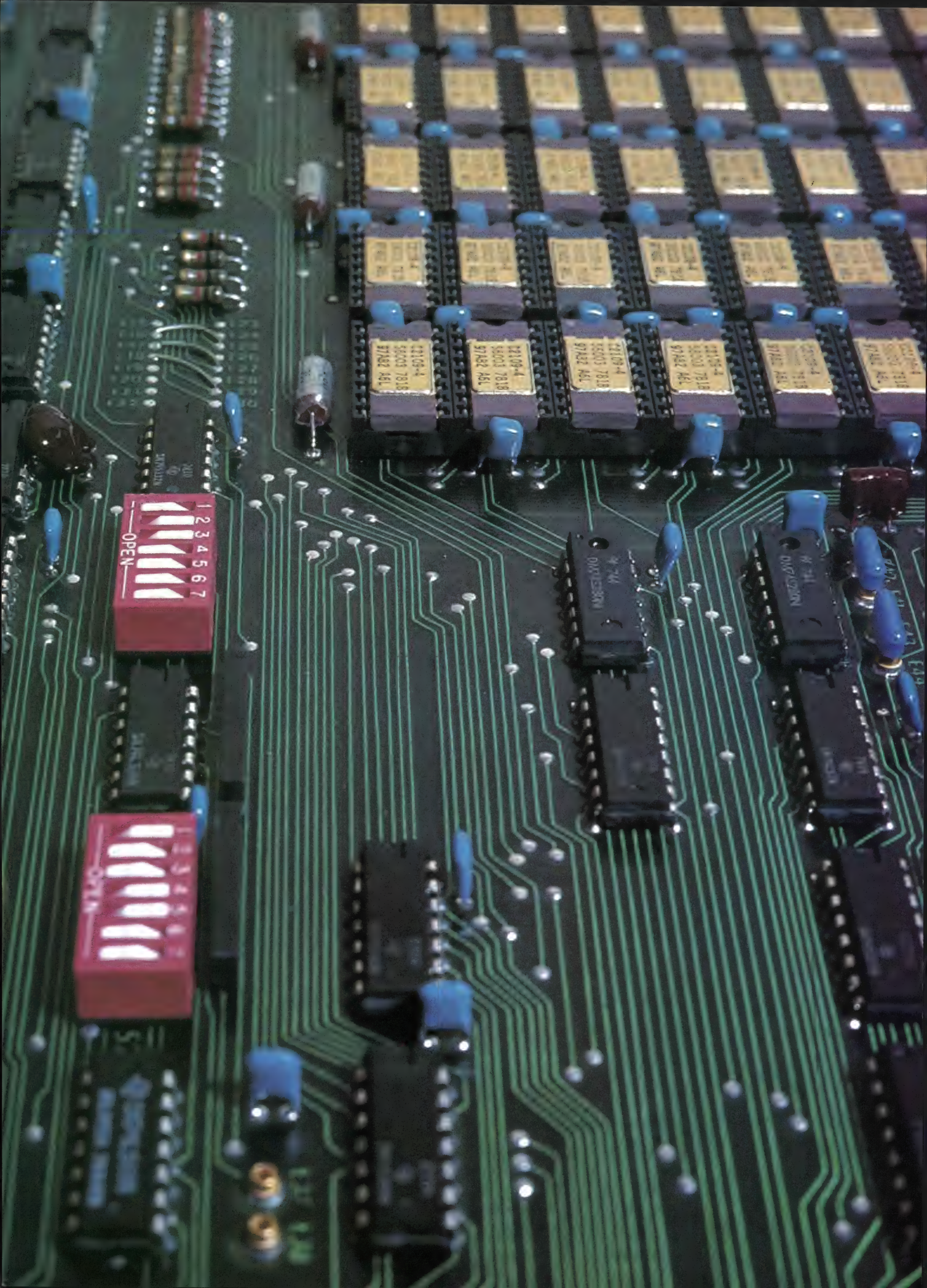

When you're decoupling dynamic RAM's... Get AVX on board.


Dynamic RAM's have large and fast transient currents which generate harmonic noise components in the 10MHz and above frequency region.

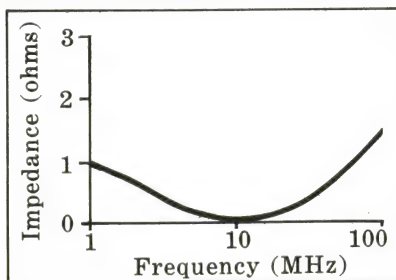AVX SkyCaps® are ideal for decoupling these high frequency noises. Effective decoupling requires capacitors which maintain low impedance at these frequencies. Most manufacturers of memory circuits recommend ceramic multilayer capacitors for use in these decoupling applications because of their lower series inductance when



compared to bulk-type electrolytic capacitors.

AVX SkyCaps are small in size which

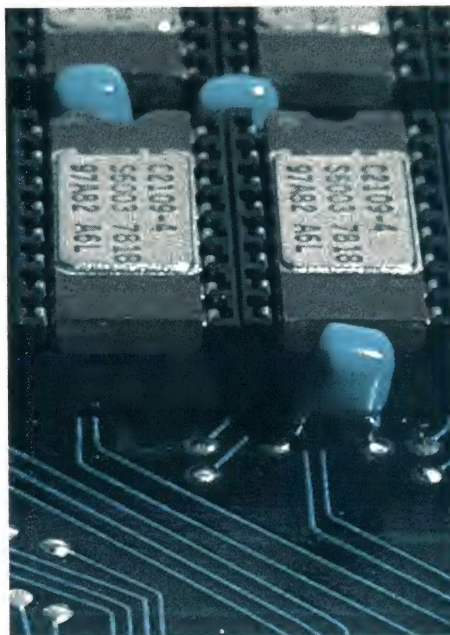

means less inherent self-inductance, and their construction allows minimum lead lengths for lower impedances at high frequencies.

And AVX SkyCaps are economical. Their small size means greater circuit density. They have the lowest cost construction for the typical decoupling capacitance ranges — from 0.1 mfd to 1.0 mfd.

Better performance and greater economy. Just two good reasons for SkyCaps' tremendous popularity in memory circuit decoupling applications. And reason enough to get AVX SkyCaps on board for your decoupling requirements.

To get more information on AVX multilayer ceramic capacitors and their use in decoupling memory circuits, fill in the coupon below and mail it today, to: AVX Ceramics, Technical Application Information, P.O. Box 867, Myrtle Beach, SC 29577.

YES, I want more information on using AVX SkyCaps for decoupling...

Name: _____

Title: _____

Company: _____

Address: _____

Zip: _____

AVX Ceramics
P.O. Box 867
Myrtle Beach, SC 29577

AVX CERAMICS

The Leader

AVX Ceramics, P.O. Box 867, Myrtle Beach, SC 29577 (803) 448-9411
TWX: 810-661-2252/2253; Olean, NY 14760 (716) 372-6611 TWX: 510-245-2815
AVX Limited, Aldershot, Hampshire, GU12 4RG England, Tel: Aldershot (0252) 312131 Telex: 858473

For more information, Circle No 61

Zilog's 4 MHz emulator is for designers who think fast.

Zilog's emulator in the ZDS 1/40 development system operates at a fast, 4MHz. Now you can test your Z-80™ designs in real-time at their true operating speeds.

But real-time emulation isn't the whole story. Zilog also gives you: memory mapping, write protection,

internal/external clocking, clock integrity verification, a disk-based debug package, programmable hardware breakpoint and a 256-event real-time trace module.

And, vexing propagation delays and cable noise are totally eliminated by Zilog's unique, hybrid emulator.

Use your choice of programming languages: assembly language, FORTRAN, BASIC, or Zilog's systems oriented, multi-level, PLZ language family.

All from Zilog, of course, the company that's pledged to stay a generation ahead in microcomputers.

10460 Bubb Road, Cupertino, California 95014
(408) 446-4666 TWX 910-338-7621
EASTERN REGION: (617) 667-2179
MIDWESTERN REGION: (312) 885-8080
SO. WESTERN REGION: (714) 549-2891
NO. WESTERN REGION: (408) 446-4666
EUROPE (ENGLAND): (0628) 36131/2/3
WEST GERMANY, GMBH: (8106) 4035
JAPAN: 03-476-3010

An affiliate of
EXON ENTERPRISES INC.



We want you to know more
about microcomputer
design tools.



For more information, Circle No 49

TM: Z80 is a trademark of Zilog, Inc.

Measure switcher efficiency without a wattmeter

Although switching power supplies draw pulsed ac currents, you don't need a wattmeter to measure their efficiency. But use of that instrument does yield the most accurate results.

Jeff Wolking, Hewlett-Packard Co

With a dual-trace oscilloscope and a programmable calculator, you can measure the efficiency of a switching power supply to within 8% of the more accurate value obtainable with a wattmeter. And if you're willing to sacrifice even more accuracy for greater convenience, use of a dual-trace scope alone yields results between +5% and -20% of the wattmeter's reading.

The ability to measure power-supply efficiency—and thus optimize it—grows more important as electric utility rates increase. But the measurement task isn't necessarily easy, particularly for switchers. A look at the basics of switching-supply operation reveals why.

Understanding power and efficiency

Power-supply efficiency equals dc output power divided by ac average input power. The latter quantity, in turn, is the time average of the product of instantaneous voltage and current:

$$P_{AVG} = \frac{1}{T} \int_0^T v(t)i(t)dt. \quad (1)$$

Here T is the voltage (or current) waveform period, and $v(t)$ and $i(t)$ are the instantaneous voltage and current magnitudes, respectively. You'll sometimes see average power termed "active" or "real" power.

Another way to calculate average power is to use

$$P_{AVG} = V_{rms} \times I_{rms} \times F_p \quad (2)$$

where V_{rms} and I_{rms} are the root-mean-square values of voltage and current, and F_p is the power factor. For sinusoidal voltage and current,

F_p is the cosine of the phase angle between the voltage and current waveforms. The quantity $V_{rms} \times I_{rms}$ is sometimes termed "apparent" power. Unfortunately, though, because switching supplies draw nonsinusoidal input currents, the concept of a simple phase angle is inappropriate.

For the conventional switching regulator diagrammed in Fig 1, the ideal input current (Fig 1b) instantaneously rises to its maximum value, then decreases cosinusoidally. RFI filters (not shown) and power-line impedance modify this idealization; the actual waveforms appear as in Fig 1c.

In a switcher incorporating preregulation (Fig 2), the preregulator triac maintains relatively constant voltage across the energy-storage capacitor. This technique simplifies the design of the main regulating control loop but can increase overall power-supply cost. The input current for such a preregulated supply is a combination of sinusoidal and ramp functions.

Measuring efficiency two ways

Fig 3 illustrates the easiest and most accurate way to determine a power supply's efficiency: Measure dc output current and voltage with a DVM, then measure ac input power directly with a wattmeter and calculate the necessary ratio. Conventional electrodynamic wattmeters work well in this application, although the need for increased accuracy could require instruments more responsive to the low power factors and sharp, nonsinusoidal current pulses associated with switchers. Comparison measurements for this article were made with a Bell HPM-501, which capitalizes on the Hall effect to provide voltage-current multiplication and makes power measurements sufficient to determine efficiency to within $\pm 4\%$.

It's hard to calculate apparent power for a switcher

A second approach permits estimation of ac input power with a dual-trace oscilloscope and a programmable calculator. Arrange the equipment as shown in Fig 4, and simultaneously display current and voltage on the oscilloscope as shown in Fig 5. Then, from the scope traces, you can directly read values for instantaneous volt-

age and current. An HP-67/97 calculator program (Fig 6) then multiplies and time-averages these values (by using Eq 1), producing an estimate of average power. The following list summarizes the approach:

- Enter the program into the calculator.
- Connect the power-supply output to a load of sufficient capacity to operate the supply at the desired output. Realize that efficiency varies with load and line conditions.
- Display both the voltage and current waveforms on the scope. (Use a current shunt,

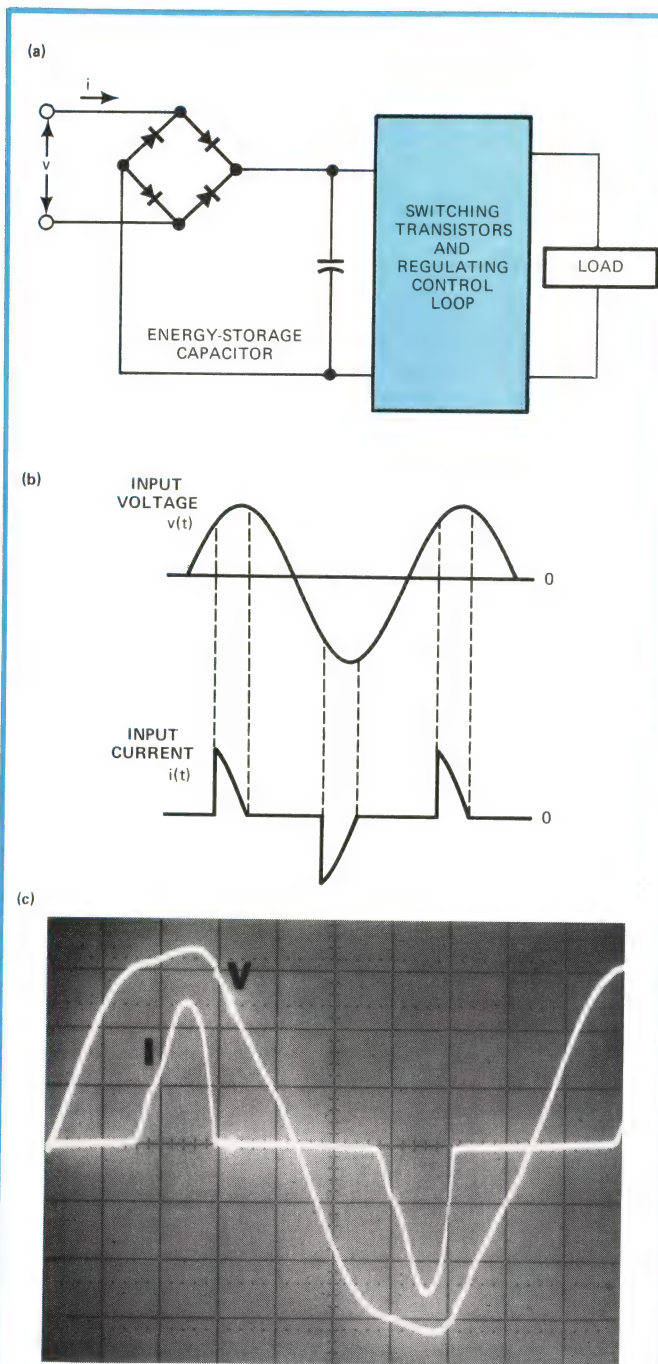


Fig 1—A conventional switching supply (a) draws pulsed ac input currents. The actual current (c) differs from the ideal or expected current (b) because of power-line and RFI-filter impedances not shown in the diagram.

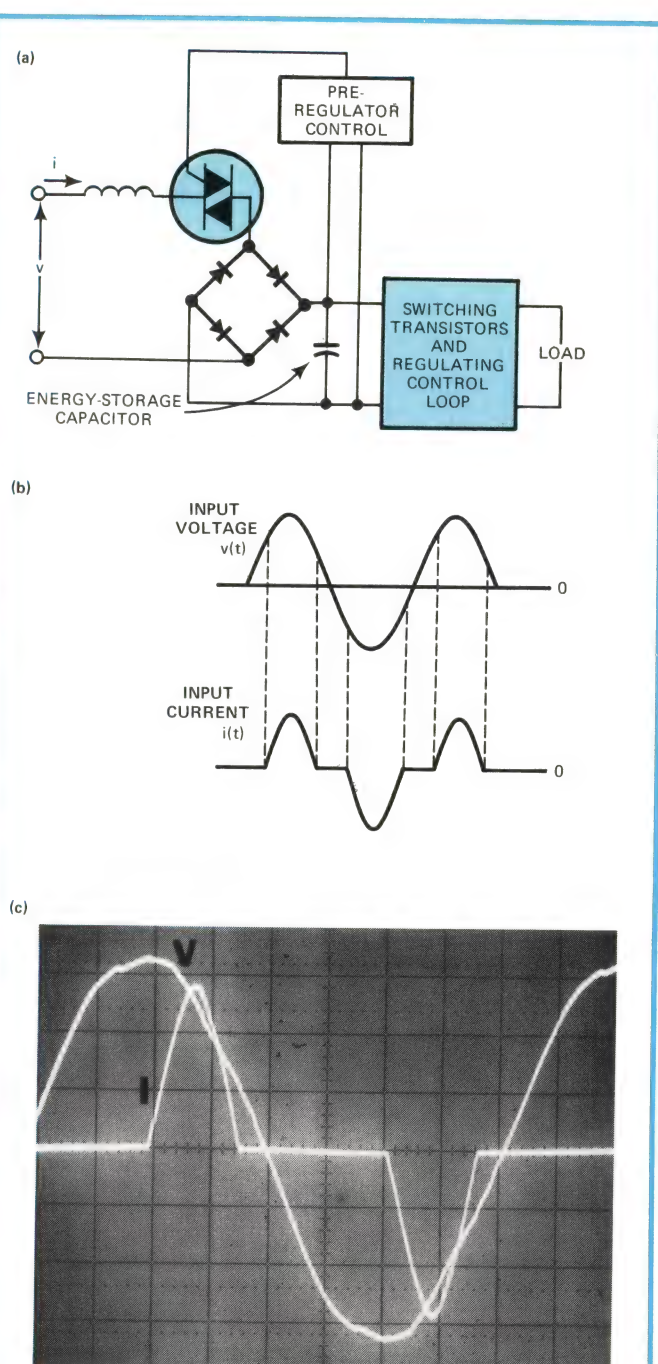


Fig 2—The preregulator triac in a preregulated switcher (a) maintains relatively constant voltage across the energy-storage capacitor. Expected (b) and actual (c) input waveforms differ.

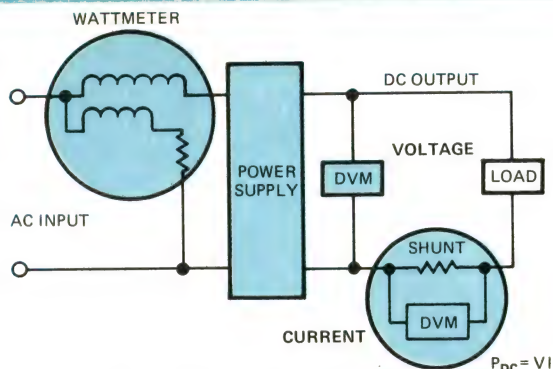


Fig 3—Calculate power-supply efficiency by dividing dc output power by ac input power. You can measure the former quantity with a DVM and the latter with a wattmeter.

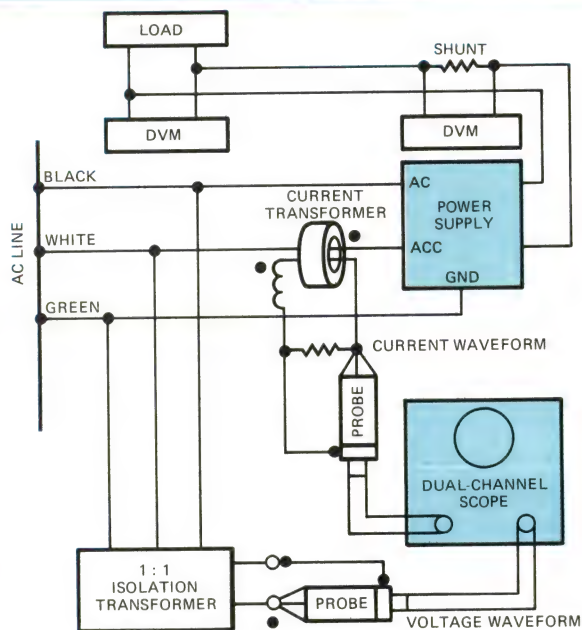


Fig 4—A dual-channel scope forms the basis of a measurement technique that doesn't require a wattmeter.


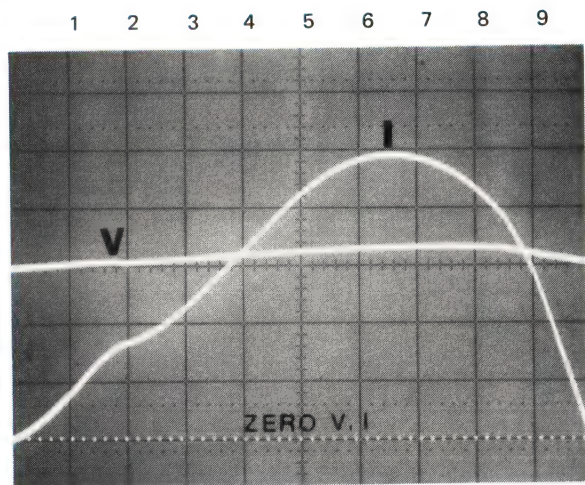


Fig 5—For the oscilloscope + calculator measurement approach, determine corresponding voltages and currents at nine points along their waveforms.

(a)

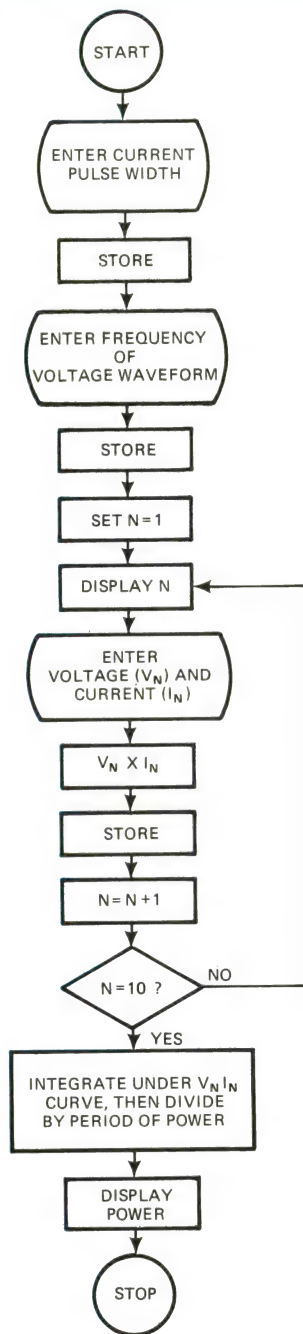

(b)

001	#LBLA	21 11	026	x	-35
002	CLR6	16 53	027	3	03
003	CF2	16 22 02	028	0	00
004	STOI	35 01	029	+	-24
005	9	05	030	SPC	16-11
006	CHS	-22	031	PRTX	-14
007	X2I	16-41	032	RTN	24
008	RTN	24	033	#LBL6	21 16 12
009	#LBLC	21 13	034	RCL1	36 46
010	x	-35	035	1	01
011	F20	16 23 02	036	0	00
012	GT06	22 16 11	037	+	-55
013	SF2	16 21 02	038	SPC	16-11
014	2	02	039	PRTX	-14
015	x	-35	040	RTN	24
016	#LBL6	21 16 11	041	#LBLB	21 12
017	2	02	042	2	02
018	x	-35	043	x	-35
019	ST+3	35-55 03	044	STO2	35 02
020	ISZ1	16 26 46	045	1	01
021	GT06	22 16 12	046	SPC	16-11
022	RCL3	36 03	047	PRTX	-14
023	RCL1	36 01	048	RTN	24
024	x	-35	049	R/S	51
025	RCL2	36 02			

Fig 6—Enter the voltage and current values obtained via Fig 5's scheme into this HP-67/HP-97 program to obtain average power. For the HP-67, delete steps 30, 31, 38, 39, 46 and 47.

Display voltage and current, then use measured values to get P_{AVG}

- probe, etc, for the current waveform.
- Measure the current pulse's width. Enter this value (in seconds) into the calculator, then press key A.
- Measure the frequency of the voltage waveform. Enter this value (in Hertz) into the calculator, then press key B.
- Expand the waveforms across the scope screen so that the current pulse is exactly 10 div wide (Fig 5). Adjust the waveform amplitudes so you can easily measure them simultaneously.
- Record nine corresponding voltage and current measurements at equal time intervals. Note that each pair of readings corresponds to the intersection of the I and V traces with a major vertical division on the scope screen. (These divisions are labeled 1 to 9 in Fig 5.)
- Enter the voltage and current readings into the calculator as follows (voltage in volts, current in amps):

Item / Press /	Item / Press /	Calculator Displays
Volts ₁ ENTER	amps ₁ C	2
Volts ₂ ENTER	amps ₂ C	3
...continue...		4-9
Volts ₉ ENTER	amps ₉ C	Power (watts).

After you enter the ninth voltage and current pair, the calculator displays the average input power.

To calculate efficiency, measure the dc output power with a DVM, then compute:

$$\text{EFFICIENCY} = \frac{\text{OUTPUT POWER}}{\text{INPUT POWER}} \times 100\%. \quad (3)$$

A third—less accurate—approach

Another technique for estimating ac average input power requires only a dual-trace oscilloscope. A re-examination of Figs 1 and 2 reveals that both the voltage and current waveforms appear approximately sinusoidal when the current is nonzero. You can estimate power, then, by using sine waves to represent both current and voltage (Fig 7). You then calculate average power by averaging the current-voltage product over the voltage's period. This double sine-wave procedure is equivalent to integrating the current-voltage product over only a half cycle of the sine approximation of the current (the current is zero elsewhere), then dividing the result by half the voltage-waveform period.

Let

$$i = I_m \sin\left(\frac{2\pi}{T_p}t\right), \quad 0 < t < T_p \quad (4)$$

and

$$v = V_m \sin\left(\frac{2\pi}{T_v}t + \frac{2\pi\alpha}{T_v}\right) \quad (5)$$

where I_m and V_m are the current and voltage maxima. The quantity $2\pi\alpha/T_v$ is the phase difference between the voltage and current half sine waves (see Fig 7); T_p defines the current pulse width and T_v the voltage-waveform period, both in seconds. Recall that the average-power calculation comes from Eq 1; substituting Eqs 4 and 5 into Eq 1 produces

$$P_{AVG} = \frac{V_m I_m}{T_v/2} \int_0^{T_p} \sin\left(\frac{\pi}{T_p}t\right) \sin\left(\frac{2\pi}{T_v}t + \frac{2\pi\alpha}{T_v}\right) dt. \quad (6)$$

Remember, despite the fact that you average over a time interval of length $T_v/2$, you need only integrate from $t=0$ to $t=T_p$, because i is zero elsewhere.

The integral in Eq 6 is of the form

$$\int \sin(ax) \sin(cx + d) dx = \frac{\sin[(a-c)x - d]}{2(a-c)} - \frac{\sin[(a+c)x + d]}{2(a+c)}, \quad (7)$$

where $a^2 \neq c^2$. Thus,

$$P_{AVG} = V_m I_m \left[\frac{\sin\left[\left(\frac{\pi}{T_p} - \frac{2\pi}{T_v}\right)t - \frac{2\pi\alpha}{T_v}\right]}{\left(\frac{\pi}{T_p} - \frac{2\pi}{T_v}\right)T_v} - \frac{\sin\left[\left(\frac{\pi}{T_p} + \frac{2\pi}{T_v}\right)t + \frac{2\pi\alpha}{T_v}\right]}{\left(\frac{\pi}{T_p} + \frac{2\pi}{T_v}\right)T_v} \right] \Bigg|_{t=0}^{t=T_p} \quad (8)$$

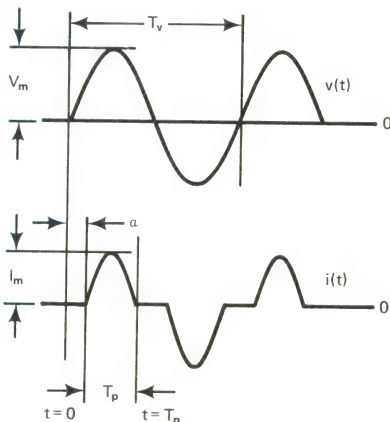


Fig 7—You won't even need a calculator if you approximate the input waveforms as sine waves. Use of Figs 8a and 8b then permits graphical estimation of average power.

A REAL TIME CLOCK FOR OUR 10th ANNIVERSARY



The 1845A Real Time Of Day Module features software selectable interrupts, sockets for up to 4K of optional EPROM memory (with the ability to jumper-select 4 EPROM types). Memory can be enabled or disabled, and the base starting address selected, by simply using the appropriate "on-board" switches. In addition to these features, counter output may be read in either hexadecimal or BCD code.

TIME CONTROL: The 1845A module gives you time control of software execution and processor operation. It provides timing for applications such as the real time monitor, executive software support, time-scheduled instrumentation programs, high resolution A/D support, process control monitoring and effective real time software development.

BATTERY BACK-UP: The battery back-up designed into our module can keep it running, even if power fails, for up to 30 days. The back-up power system features automatic recharging.

PCS/INDUSTRIAL MICROCOMPUTERS: The 10th anniversary of PCS celebrates 10 years of dynamic design and manufacturing experience that had led to one of the most complete lines of industrial microcomputers in the industry. So, whatever your industrial microcomputer requirements demand - complete systems, industrial microcomputer packages, or a broad line of modules, including super-intelligent microprocessor modules, memory modules and a wide assortment of interfaces, the PCS standard product line is the solution.

For complete information contact your local PCS representative or call the PCS HOTLINE (313) 429-4971.



Process Computer Systems Inc.
750 North Maple Road, Saline,
Michigan 48176
(313) 429-4971 TWX: 810-223-8153

For more information, Circle No 52

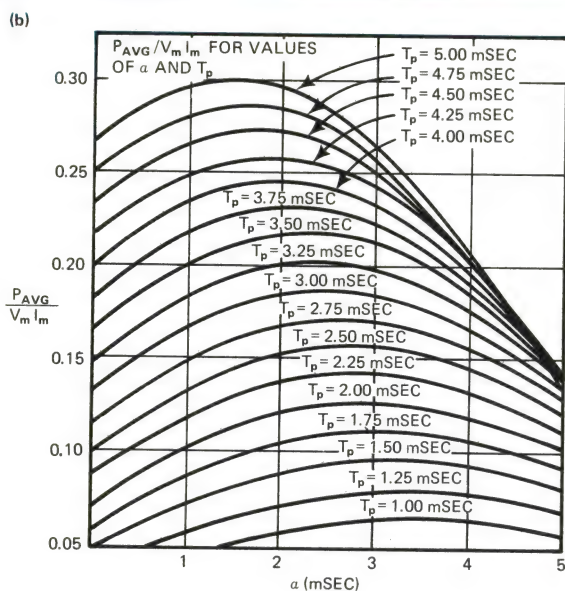
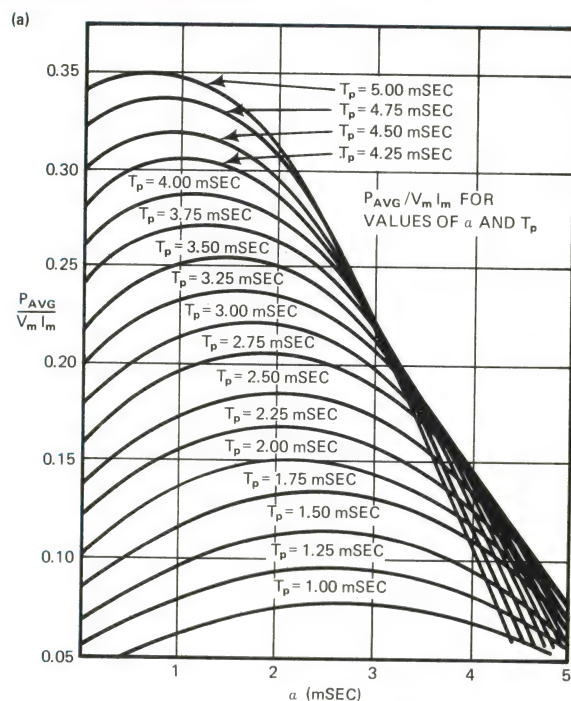


Fig 8—Determine the input waveform parameters V_m , I_m , T_p , α and T_v from Fig 7, then estimate average power directly from these graphs. Graph (a) applies to 60-Hz power-line frequencies; (b), to 50-Hz cases.


You can measure V_m , I_m , T_p , α and T_v using the equipment setup shown in Fig 4. Find average power directly from Eq 8, or alternatively, find the value $P_{AVG}/V_m I_m$ from either Fig 8a or Fig 8b

and multiply that value by V_m and I_m . (Note that the ratio $P_{AVG}/V_m I_m$ on the vertical axes of Figs 8a and 8b is not the power factor (Eq 2) because V_m and I_m are peak, not rms, values.) Figs 8a and 8b are derived, of course, from Eq 8. The first applies to 60-Hz power-line frequencies ($1/T_v = 60$ Hz); the second, to 50-Hz cases.

EDN

GREAT MOMENTS

... in electrical history

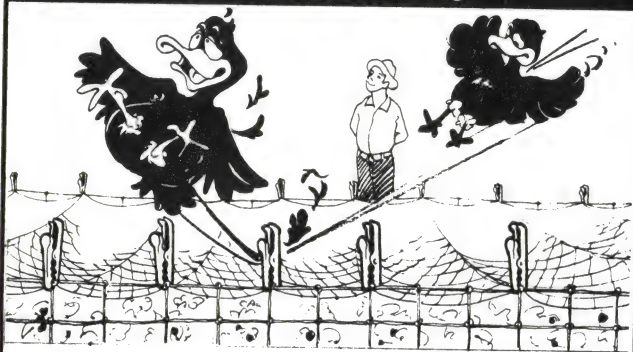

... the day Peter Sluka of Glen Ellyn, Ill. found a brand new use for Mueller Clips, right in his own strawberry patch, oft raided by a feathered air force. He clipped a canopy of bird netting atop his surrounding low wire fence, getting protection that worked to perfection and was quickly unclipped for picking or weeding. Mueller Clips: For quick, sure electrical connections ... and wild uses you never dreamed of. Dream of some!

At distributors everywhere—USA & worldwide

Write factory for **FREE** sample clips and catalog

Mueller Electric Co.

1583 East 31st Street, Dept. 14 • Cleveland, Ohio 44114

For more information, Circle No 51

Author's biography

Jeff Wolking—is currently pursuing his MBA degree at the Wharton School. He wrote this article while working as a summer employee in the marketing department of Hewlett-Packard's Rockaway, NJ facility. Jeff earned a BSEE at the Univ of Calif at Irvine and hopes to complete his MBA this May; he has also spent 2 yrs with Rockwell International, working on secure systems and VLF communications. Jeff enjoys tennis, swimming and oenology in his free time.



Article Interest Quotient (Circle One)

High 482 Medium 483 Low 484

JOB SHOPPING?

Check EDN's Career Opportunities
EDN: Everything Designers Need

Synchronous static CMOS RAMs increase system performance

It's a challenge to design a RAM array with synchronous memories, but an ever-increasing number of μ Cs can benefit from their use.

Charles Hochstedler, Harris Corp

Synchronous RAMs offer faster access times, lower power dissipation and easier common-bus interfacing than equivalent asynchronous designs. But effectively utilizing these devices in your memory system requires understanding how they operate.

A synchronous RAM derives its name from the fact that the chip-enable signal synchronizes the memory's internal operations with external-system timing demands (Fig 1). Because access is initiated by this signal's falling edge, a synchronous RAM's access time is usually 30 to 40% faster than that of an equivalent asynchronous device. Additionally, a synchronous RAM uses the chip-enable HIGH time before every access to prepare itself by presetting (or precharging) the condition of key internal nodes—an operation that allows you to optimize the condition of critical timing paths to ensure the fastest possible access.

By contrast, an asynchronous RAM has no signal available to indicate that an access operation is about to begin. And no precharging

operations are possible because the chip-select signal can remain LOW throughout many successive cycles.

Note that synchronous memory operation (often called clocked operation) is not identical to dynamic-memory refresh. Synchronous static memory utilizes the common 6-transistor, fully static, latch-type cell; chip enable is used to increase performance, not to refresh data.

Easier on the draw, too

Lower operating power than asynchronous devices is a second major benefit afforded by synchronous techniques—a comparison that's valid, of course, only between RAMs using identical technologies: (You can't compare the power dissipation of CMOS units with that of NMOS devices.)

Because in synchronous CMOS designs, power consumption becomes a function of the frequency of repetitive accessing plus a small leakage current, the memory consumes power only when it is in active use. It consequently conserves

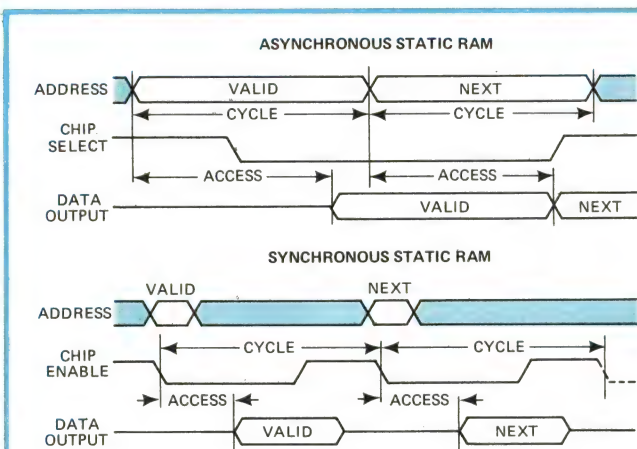


Fig 1—A marked difference in access time appears in these timing diagrams for typical RAM devices. In addition to exhibiting faster access, the synchronous RAM has less stringent requirements for maintaining valid address inputs.

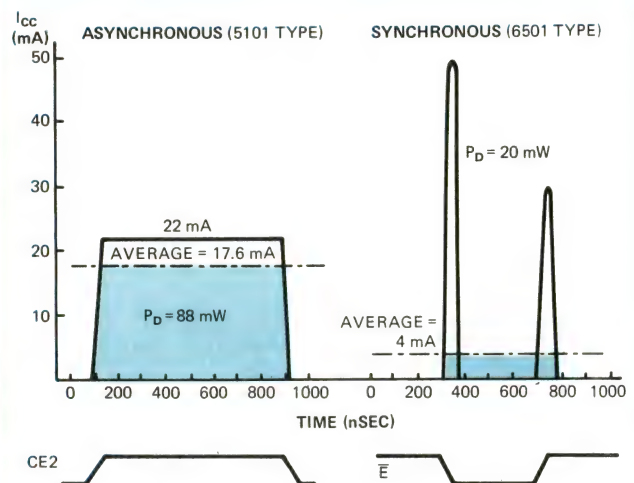


Fig 2—Average power dissipation is dramatically lower in synchronous RAMs than in equivalent asynchronous memories, despite the fact that peak current demands are much higher.

Power is lower, even though peak current is higher

power when not being accessed. In contrast, an asynchronous CMOS RAM requires dc current paths and consumes power whenever enabled.

Fig 2 charts the relationship between chip-enable waveforms and supply current for two pin-compatible devices—one synchronous, the other asynchronous. As shown, the synchronous 6501 draws a higher peak current. However, these peaks are so narrow that the asynchronous 5101 has more than four times the power dissipation. The table summarizes the speed and power specifications for both standard and prime grades of the 5101 and 6501.

Multiplexed bus structures made easy

The differences in RAM addressing between synchronous and asynchronous units highlight another point in favor of synchronous memories. Because these units require such a short valid-address time, it's easy to implement common address, data-in and data-out bus systems using them. And because in a synchronous-RAM array, valid data output need not be timed to coincide with valid address information, address informa-

SPEED AND POWER COMPARISONS FOR CMOS STATIC RAMs

	ASYNCHRONOUS 5101 ⁽¹⁾		SYNCHRONOUS 6501	
	STANDARD	PRIME	STANDARD	PRIME
MAXIMUM ACCESS (nSEC)	650	450	300	220
MINIMUM CYCLE (nSEC)	650	450	400	320
MAXIMUM STANDBY (μ A)	200	10	100	10
MAXIMUM OPERATING (mA) ⁽²⁾	22	22	4	4
TYPICAL ACCESS (nSEC) ⁽³⁾	—	—	160	120
TYPICAL CYCLE (nSEC) ⁽³⁾	—	—	210	170
TYPICAL STANDBY (μ A) ⁽³⁾	—	—	1	0.1
TYPICAL OPERATING (mA) ⁽³⁾	9	9	1.5	1.5

NOTES

⁽¹⁾ 5101 SPECIFICATIONS FROM 1978 INTEL DATA CATALOG

⁽²⁾ SYNCHRONOUS OPERATING CURRENT SPECIFIED AT REPETITIVE ACCESS RATE OF 1 MHz

⁽³⁾ TYPICAL PARAMETERS SPECIFIED AT 25°C, 5V

Defining some terms

When using a conventional asynchronous RAM, you must hold its address inputs valid throughout a read or write cycle; this address, together with the device selected, defines the cycle time. If necessary, you can reaccess the RAM while still in this initial select mode.


With a synchronous static RAM, on the other hand, you only need a valid address for a short time at the beginning of a cycle. However, cycle initiation requires an edge or transition of the chip-enable signal. Additionally, a finite period of time occurs after access, during which the device must be disabled before the next cycle can begin.

tion and data do not overlap, and it's easy to multiplex these signals on a single bus.

Although at first glance, this type of multiplexed bus structure appears a bit complex, many μ P manufacturers are using it to keep pin counts at a reasonable level. And as more μ Ps appear with common address and data-bus structures, the usefulness of synchronous RAMs with internal address latches will increase. **EDN**

Author's biography

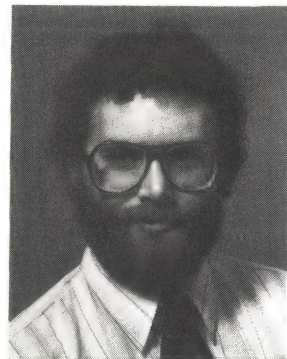Charles Hochstedler is a memory-applications engineer at Harris' Semiconductor Products Div, Melbourne, FL, where he provides customer applications support and generates information for data sheets and application notes. Charles earned his BS degree in electrical engineering technology at Purdue Univ. His spare-time interests include personal computing, sailing and chess.



Article Interest Quotient (Circle One)
High 479 Medium 480 Low 481

MUCON[®]

CERAMIC CAPACITORS

NPO

ULTRA-STABLE
MU-CAPS[®]
QPL to MIL-C-20F

CCRO5

.0033
±1%

CCRO6

.022
±1%

CCRO7

.22
±1%

CCR79

.22
±1%

TIGHT CAPACITANCE TOLERANCES as low as ±1/2%

CAPACITANCE
1/2 PF. to .22 MF.


Q GREATER
THAN 1000

ULTRA-STABLE
±.3% max. change

write for NEW CATALOG

REPUBLIC ELECTRONICS CORP.
176 E. 7th St., PATERSON, N.J. 07524
201-279-0300 TWX 710-988-5908

For more information, Circle No 62

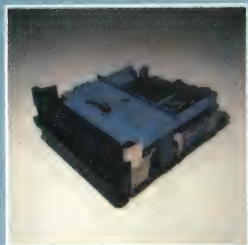

Reliability in precision technology.

Looking for precision DC motors that save time, trouble and money?

You'll save time with AIRPAX because you'll find a large variety of DC motors available with just one phone call to us. We have brushless kits, iron rotor and ironless rotor motors in many sizes and performance ratings. (In fact, many of our ironless rotor models can save you even more time because 100 piece quantities are available from stock.)

You'll save trouble because AIRPAX motors are precision components designed for long life. The brushless type can be electronically driven for accurate speed and they feature low RFI. The iron rotor type is a "workhorse" motor that offers good efficiency and rugged construction. The ironless rotor features low cogging, high efficiency, excellent acceleration and an optional tach that gives you precise speed control.

Finally, you'll save money. All are remarkably low priced in production quantities. For example, one of our reversible 12VDC ironless rotor models, with a 29 millimeter diameter is just \$16.00 in 500 piece lots!

For complete information on AIRPAX brushless, iron rotor or ironless rotor DC motors for computer peripherals and instrumentation, contact AIRPAX/North American Philips Controls Corp., Cheshire Industrial Park, Cheshire, CT 06410. Telephone: (203) 272-0301.




AIRPAX®


NORTH AMERICAN PHILIPS CONTROLS CORP.

Cheshire Division

For immediate need Circle no 63
For reference only Circle no 114

Design your 64K system now.

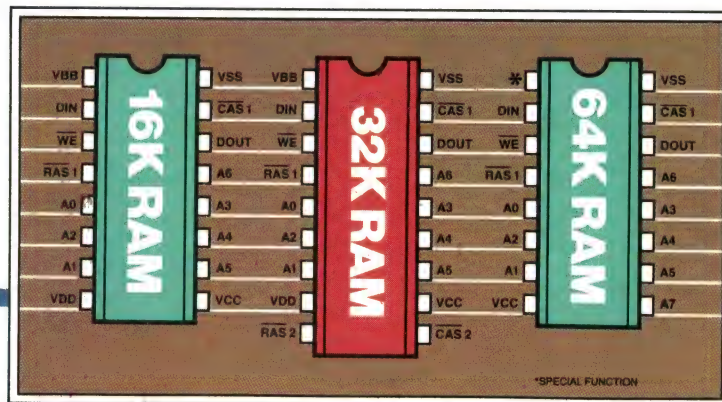

 Design now. Start production now. You don't have to wait for the 64K RAM.

Mostek's new 32K RAM is available and offers twice the density of 16K RAMs.

When 64K RAMs are available, your 32K system can be totally compatible.

Design in flexibility.

You can design memory systems that interchange 4K, 16K, 32K and 64K dynamic RAMs. The MK4332, organized as 32K x 1, mounts two 4116s in leadless chip carriers connected to a standard 18-pin dual-in-line package. The two chips share common Address, Data In, Data Out, Write Enable and power pins. Separate RAS and CAS clocks for each 4116 are provided for easy device selection and control. The arrangement of all other pins is identical to the indus-

try standard 16-pin configuration for 4K and 16K RAMs. The pin configuration is also compatible with Mostek's soon-to-be-announced 64K RAM, the MK4164.

Design in high performance.

Access time for the high density 4332 is a fast 200ns with a cycle time of just 375ns. Because both 16Ks feature an Edge-Activated™ selection mode, one chip remains in standby while the other is activated. This means the 4332 dissipates just 482mW while active and 40mW during standby. It allows a $\pm 10\%$ tolerance on all power supplies ($+12V$, $\pm 5V$).

Design with confidence.

With 16K RAMs in high volume production, you can be certain of 32K RAM availability. And alternate sourcing will soon be an-


nounced. You can count on Mostek's reliability. Mostek's 4116 quality standards set the pace for the industry. Every 16K RAM we ship is thoroughly tested to rigorous screens and stresses. With the same package dimensions as an 18-pin cerdip, the 4332 is compatible with your automatic handling and test equipment.

For more information on Mostek's 32K RAM, call your local Mostek representative or 214/245-0266 for location of the nearest sales office. Mostek Corporation, 1215 W. Crosby Road, Carrollton, Texas 75006. In Europe, contact Mostek Brussels; phone (32)02/660.25.68.

MOSTEK®

For more information, Circle No 64

With our 32K RAM.

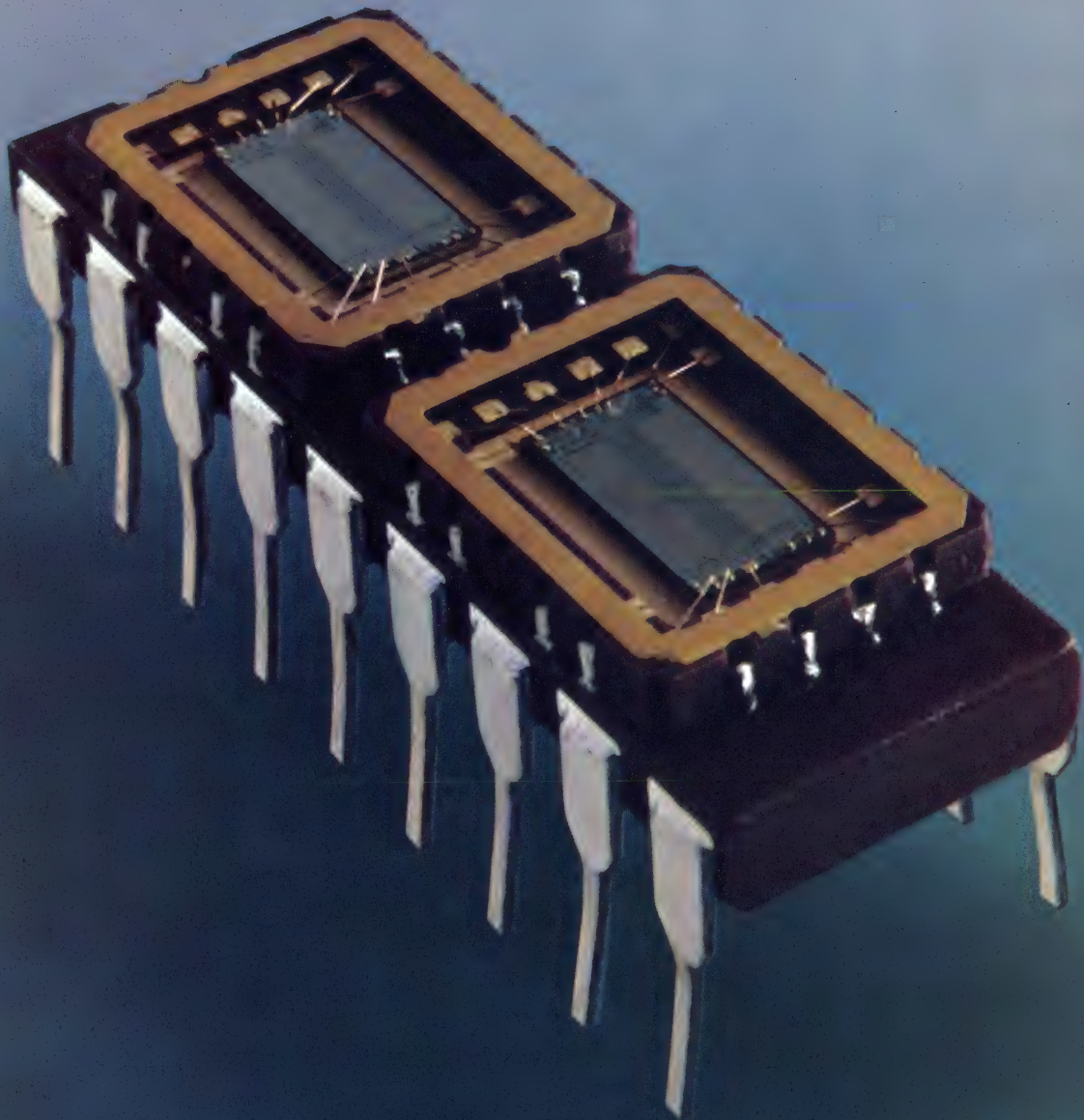

MOSTEK 3870

Three of them together make flying a breeze.



"Our OC-1401 navigation computer uses three Mostek 3870s to distribute the complex processing tasks. While one controls the keyboard and display, all three operate independently, calling on each other to perform the mathematical functions and sub-routines necessary for computing in-flight navigational data." *Bruce Trump, Project Engineer, and Rod Brahman, Software Engineer, Heath Company.*



Toledo Scale: "We use Mostek's 3870 three ways: (1) to perform all the logic functions associated with A/D conversion; (2) to provide selectable operating features using multiple program switches; (3) to generate bit serial output in ASCII format." *Roger Williams, Engineering Manager for Electronic Products.*

Tokheim: "Using the 3870's 2K ROM memory, we incorporated two separate software programs. Now we can use the 3870 in a control console or individual gasoline pumps, depending on mechanical connections." *Earl Langston, Project Manager.*

There are hundreds of applications using Mostek's 3870 single-chip micro-computer. Get information for your design by contacting Mostek, 1215 West Crosby Road, Carrollton, Texas 75006; phone (214) 242-0444. In Europe, contact Mostek Brussels; phone (32) 02/660.25.68.

MOSTEK®

For more information, Circle No 65



Learn the peculiarities of low-end- μ C architectures

The odd architectures and instruction sets of low-end, calculator-based 1-chip μ Cs are very cost effective—if you know how to take advantage of them.

Robert H Cushman, Special Features Editor

Because they have so many curious features, today's calculator-like 1-chip μ Cs demand more individual study than their minicomputer-like, midrange- μ P relatives—a realization that grew clearer when we began research for the article originally scheduled for this issue. The advantages of using these versatile low-end devices are lost without adequate groundwork; underestimating the amount of groundwork required can be fatal. And so we have postponed that article—describing an industrial-control application of the National Semiconductor COP402 emulator—until next time. Here we focus on delving more deeply into the architectures and instruction sets of today's low-end 1-chip μ Cs.

As in previous articles (Refs 1 and 2) we'll focus on the Texas Instruments TMS-1000, Rockwell PPS-4/1, National COP400 and AMI S2000. These families are described in capsule form in EDN's annual μ P Directory (Ref 3), which also lists two Japanese 1-chip- μ C families (NEC's μ COM-43 and Panasonic's MN1400) belonging to this calculator-derived category. To a lesser degree, some of the other low-end 1-chip μ Cs—the Intel 8048, General Instrument PIC1650 and Zilog Z8, for example—have similar features.

Split architectures are the rule

The most obvious architectural feature of the calculator-derived μ Cs is the way they are split into three distinct parts: program ROM, data RAM and I/O (Fig 1). From the perspective of computer history, these split-up organizations would appear to be throwbacks to the early "Harvard" architectures—the opposite of the

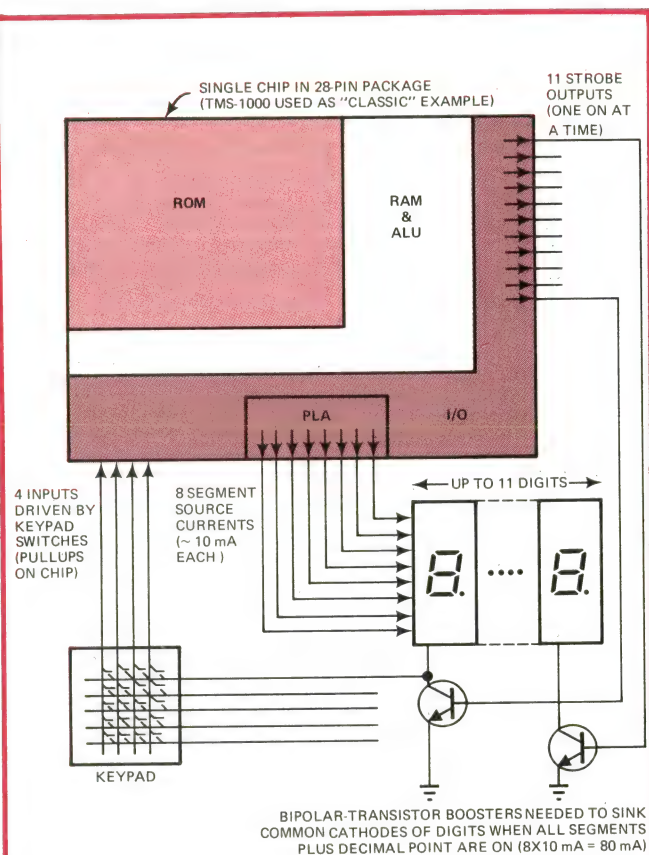


Fig 1—In a typical calculator system, there is ideally only one semiconductor device: the LSI " μ C" itself. Internally, this device divides into three subsystems—program ROM, data RAM and I/O. Externally, the I/O interfaces as directly as possible with a numeric keypad input and a multidigit 7-segment-plus-decimal-point display. Multiplexing via strobe outputs from the LSI device saves pins—an approach that's possible despite the slow clock speeds because the system is used by a human operator. Except when the tiniest LED displays are used, external transistors must sink the displays' common cathodes.

Low-end 1-chippers optimize RAM, ROM and I/O separately

now-prevailing "Princeton" configurations, in which program and data (and often also I/O) share a common memory space.

A compelling reason for adopting the single memory space of Princeton architectures is that with it, one instruction set can apply uniformly to program, data and I/O. The programmer can freely merge these subsystems in a sophisticated, fluid manner, and the single instruction set is supposedly easier to remember and troubleshoot. Indeed, the advance sales publicity for the forthcoming Z8000 and 68000 "super μ Ps" has been extolling the benefits of the uniform instruction sets resulting from "clean" Princeton architecture.

As Fig 2 shows, though, there isn't enough spare silicon in the tiny low-end 1-chip μ Cs to permit the luxury of treating their subsystems identically. Instead, each subsystem is optimized separately to perform its special tasks without forcing design compromises in the name of uniformity. In fact, the different addressing-register reaches, word widths and circuit performances of the three sections *preclude* uniformity.

The architectural differences in the ROM, RAM and I/O sections in turn are responsible for their instruction-set differences. And before you

compare these differences unfavorably with the uniformity prevailing at the higher end of the μ P spectrum, we suggest you first examine how much they can contribute to end-product cost effectiveness.

ROMs have regular 8-bit width

In general, the ROM of a low-end 1-chip μ C is the least "strange" of its subsystems; RAM is slightly "peculiar," and I/O is very specialized.

Most of the calculator-derived μ Cs use byte-sized (8-bit) program words—a width adequate for single-word instructions because the addressing spaces involved in these little machines are so restricted. The width also proves handy during prototyping emulation, because it permits use of standard PROMs and RAMs.

The overriding design criterion for the ROM section is maximum effective code capacity. The greater the amount of effective code you can pack into the ROM, the more competitive your end product. As far as users are concerned, this emphasis on ROM code capacity translates into an emphasis on short, 1-byte instructions. Because an 8-bit byte isn't wide enough to contain the address operand for full-length "long" jumps through the basic 1k ROMs used in the 1-chip μ Cs, various types of "short" jump instructions are provided, typically with 6-bit address operands (and thus 64-byte reaches). Thus, a low-end 1-chip μ C's basic 1k ROM is typically broken up into 16 64-byte pages. The instruction set of the COP400 family (Fig 3) provides an example.

The compartmentalization of the ROM-address space necessitated by the emphasis on single-byte instructions also leads to a number of "nuisance" rules and restrictions for jump and call instructions. Here's an overview of these restrictions for the TMS-1000, COP400 family, S2000 and PPS-4/1:

- The earliest of the designs, the TMS-1000 is also the most primitive; it has only six bits in its PC (program counter). Thus the PC can only fetch instructions within one of the 64-byte ROM pages; when it reaches the end of the page, it wraps around and fetches the next instruction from the page's beginning. Unaided, then, the TMS-1000's jump and call instructions only branch execution within a page. If you want the execution to jump to another page, you must insert an LDP (load page buffer immediate) instruction to select that page from among the other 15. In addition, because all branches are conditional and might not occur, you must remember to insert a second LDP before a branch whenever a subroutine-call instruction directs execution to another page. That way, the page buffer will be restored to the original page.

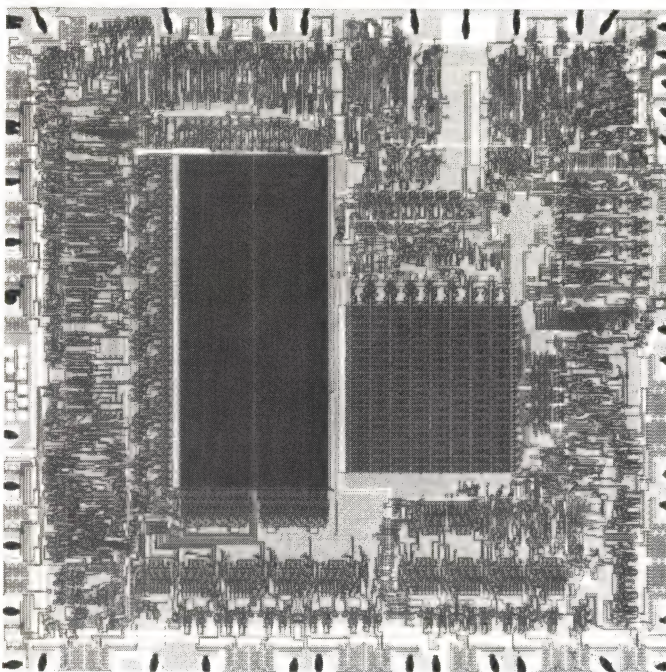


Fig 2—In the latest addition to AMI's S2000 family—the S2150—ROM and RAM are easily recognized, as are the large I/O devices around the edge. The original S2000 chip measures 162×172 mils, and the S2150 is not much larger (178×173) despite its 50%-larger ROM and 25%-larger RAM. The forthcoming S2200 and S2400, with their 2k and 4k ROMs, will measure 180×180 and 180×218 mils, respectively. Their on-chip, 8-channel, 8-bit A/D converters will occupy only 500 mil².

- The COP420 has a full 10-bit PC but nevertheless also uses 64-byte paging to provide short jumps and calls (Fig 4). A further complication: Pages 2 and 3 of the 16 ROM pages are treated as "subroutine pages"; the short-form JP (jump) instruction, which normally can only initiate a jump within a 64-byte page, can also cause a jump to one of these subroutine pages from the other. (Because the COP's PC preincrements before the instruction fetch, you must remember to treat the last address on a page as part of the next page.) The COP400 family's short-form subroutine call, JSRP, is a 1-byte instruction that permits jumping to subroutines in pages 2 or 3 from any other page. It's an efficient way of moving program execution to the subroutine pages; once execution is there, though, any further levels of subroutining must be called by the long-form, 2-byte JSR instruction. This requirement is unfortunate, because unlike the TMS-1000 (which is restricted to just one level of subroutine call), the COP400 family can nest up to three levels (if no interrupt is expected).
- The S2000 resembles the COP400 devices in that it has a full 10-bit PC and three levels of subroutine stack. But this μ C achieves short-form program jumps in a manner more akin to that used by the TMS-1000. Jumps must be preceded by a PP (prepare page) instruction. If, in addition to jumping within the internal 1k ROM, you wish to jump to one of up to seven externally addressed 1k banks, you must insert two PP instructions in tandem—the first to prepare the bank address and the second to select the page address. The S2000 architecture treats page 15 (in any of the 1k banks) as the subroutine page. The μ C's JMS (jump to subroutine) instruction automatically sets the page register to 15 unless it is overridden by a preceding PP instruction.
- The PPS-4/1's ROM architecture resembles those of the COP400 and S2000 families. However, it has a wider PC (11 bits) for directly addressing up to 2k of ROM, and some of its long jumps are a full three bytes long. It also has two levels of subroutine stack. Problems can arise with the multi-byte jump instructions, though, because the PPS-4/1 coding rules don't permit placing skip instructions ahead of these multibyte codes.

Do all these details of ROM addressing for the calculator-derived μ Cs sound confusing? They are at first, but after you've worked with these machines, you quickly catch on and learn to make their idiosyncrasies work for you. Originally, the

manufacturers of these chips were forced to do much of the programming for their customers, but now they say most of those customers are doing their own programming. Based on the number of development systems sold for the calculator-derived μ Cs, we estimate that there could be as many as 10,000 engineers familiar with the techniques of programming them.

RAMs are really CPU-register arrays

Only occasionally are low-end 1-chip μ Cs required to act on 4-bit words. More typically, they either process numbers in the form of strings of BCD digits or set and reset individual flag bits. This operation contrasts with that of larger machines, where the computer's word length is more likely to prove adequate for the data processed.

The tiny RAMs in the calculator-derived μ Cs are therefore organized less like regular memory RAMs than like CPU-register arrays and groups of flag bits. As shown in Fig 4, the two parts of their split address registers typically map these RAMs into four long 16-word strings. The strings' individual words or "digits" are addressed by a 4-bit lower ("d") register (to use COP-family terminology); the usual four strings of 16 digits are then selected by short 2-bit upper ("r") registers.

The 4-bit d register is usually intimately associated with the accumulator (and, as you'll see later, with one of the I/O ports). The two r bits are treated somewhat like the upper bits of the PC addressing the ROM; they should ideally be initialized only occasionally, although they might, in reality, get flipped-about frequently during program execution.

This split-up RAM-addressing scheme nicely suits the design goals for low-end 1-chip μ Cs: It produces maximum ROM-code density, because it permits packing RAM-addressing operands into 1-byte instructions. And because many of these RAM-referencing instructions are constantly used in typical application programs, it is essential that they be short. Further, because they are typically used in program loops, they can have a critical effect upon program execution speed—again, shortness pays off.

A look at the COP instruction set (Fig 3) shows why the μ C's architecture permits short, fast instructions. Consider the bit patterns for the XDS and XIS instructions, for example; these complementary commands are the key instructions found in so many numerical data-processing loops. They are single-byte entities, yet they contain the necessary RAM addressing as well as loop housekeeping. Two short software examples illustrate their power.

Suppose first that you want to bring the digits of a numerical string in RAM into the accumula-

Is a multiple- μ C 1-chip device next?

tor one by one, clear them, and return them to RAM. For this purpose, you can use the very short, tight, fast loop shown in Fig 5.

The string of interest in this case comprises the digits 0 to 12 of string 1. An LBI (load RAM-address register B immediate), which initializes both the r and d sections of the RAM-address register B, sets up the operation. The r=01 of this instruction's operand field points at RAM-register string 1, and the d=1011 points at the number 12 digit of that string. The loop itself consists of just three 1-byte instructions:

- The CLRA clears the accumulator.
- The XDS is a multifunction instruction that does practically all the loop's work. It exchanges contents with the pointed-to RAM location, loading in the ZEROS that clear that location. It exclusive-ORs the r address with the r field in the operand—an act that has no effect in this case because the r field is 00. Finally, it decrements the d address to shift the RAM address to the next digit and checks to see if the d part of the address has gone past 0000. If so, it causes the μ C to skip the next instruction.
- The final JP is a short 1-byte jump to the start of the loop. It is skipped when the last digit of the string has been processed because then the d address has gone past 0000. Note that the writer of this program has purposely mapped the string against the right-hand boundary of the RAM so that the XDS skip occurs after the last digit of the

RAM (& ALU) SECTION

Mnemonic	Operand	Hex Code	Machine Language Code (Binary)	Data Flow	Skip Conditions	Description
MEMORY REFERENCE INSTRUCTIONS						
CAMQ		33	[0 0 1 1 0 0 1 1]	A \rightarrow Q7:4 RAM(B) \rightarrow Q3:0	None	Copy A, RAM to Q
		3C	[0 0 1 1 1 1 0 0]			
COMA		33	[0 0 1 1 0 0 1 1]	Q7:4 \rightarrow RAM(B) Q3:0 \rightarrow A	None	Copy Q to RAM, A
		2C	[0 0 1 0 1 1 0 0]			
LD	r	-5	[0 0 r 0 1 0 1]	RAM(B) \rightarrow A Br \oplus r \rightarrow Br	None	Load RAM into A, Exclusive-OR Br with r
LDD	r, d	23	[0 0 1 0 0 0 1 1]	RAM(r, d) \rightarrow A	None	Load A with RAM pointed to directly by r, d
		--	[0 0 r d]			
LQID		BF	[1 0 1 1 1 1 1 1]	ROM(PCg, g, A, M) \rightarrow Q SB \rightarrow SC	None	Load Q Indirect
RMB	0	4C	[0 1 0 0 1 1 0 0]	0 \rightarrow RAM(B) ₀	None	Reset RAM Bit
	1	45	[0 1 0 0 0 1 0 1]	0 \rightarrow RAM(B) ₁		
	2	42	[0 1 0 0 0 0 1 0]	0 \rightarrow RAM(B) ₂		
	3	43	[0 1 0 0 0 0 1 1]	0 \rightarrow RAM(B) ₃		
SMB	0	4D	[0 1 0 0 1 1 0 1]	1 \rightarrow RAM(B) ₀	None	Set RAM Bit
	1	47	[0 1 0 0 0 1 1 1]	1 \rightarrow RAM(B) ₁		
	2	46	[0 1 0 0 0 1 1 0]	1 \rightarrow RAM(B) ₂		
	3	4B	[0 1 0 0 1 1 0 1]	1 \rightarrow RAM(B) ₃		
STII	y	7-	[0 1 1 1 y]	y \rightarrow RAM(B) Bd + 1 \rightarrow Bd	None	Store Memory Immediate and Increment Bd
X	r	-6	[0 0 r 0 1 1 0]	RAM(B) \leftrightarrow A Br \oplus r \rightarrow Br	None	Exchange RAM with A, Exclusive-OR Br with r
XAD	r, d	23	[0 0 1 0 0 0 1 1]	RAM(r, d) \leftrightarrow A	None	Exchange A with RAM pointed to directly by r, d
		--	[1 0 r d]			
XDS	r	-7	[0 0 r 0 1 1 1]	RAM(B) \leftrightarrow A Bd - 1 \rightarrow Bd Br \oplus r \rightarrow Br	Bd decrements past 0	Exchange RAM with A and Decrement Bd, Exclusive-OR Br with r
XIS	r	-4	[0 0 r 0 1 0 0]	RAM(B) \leftrightarrow A Bd + 1 \rightarrow Bd Br \oplus r \rightarrow Br	Bd increments past 15	Exchange RAM with A and Increment Bd, Exclusive-OR Br with r
REGISTER REFERENCE INSTRUCTIONS						
CAB		50	[0 1 0 1 0 0 0 0]	A \rightarrow Bd	None	Copy A to Bd
CBA		4E	[0 1 0 0 1 1 1 0]	Bd \rightarrow A	None	Copy Bd to A
LBI	r, d	--	[0 0 r (d - 1)] (d = 0, 9:15) or [0 0 1 1 0 0 1 1] [1 0 r d] (any d)	r, d \rightarrow B	Skip until not a LBI	Load B Immediate with r, d
LEI	y	33	[0 0 1 1 0 0 1 1]	y \rightarrow EN	None	Load EN Immediate
		6-	[0 1 1 0 y]			
XABR		12	[0 0 0 1 0 0 1 0]	A \leftrightarrow Br (0, 0 \rightarrow A3, A2)	None	Exchange A with Br
ARITHMETIC INSTRUCTIONS						
ASC		30	[0 0 1 1 0 0 0 0]	A + C + RAM(B) \rightarrow A Carry \rightarrow C	Carry	Add with Carry, Skip on Carry
ADD		31	[0 0 1 1 0 0 0 1]	A + RAM(B) \rightarrow A	None	Add A to RAM
ADT		4A	[0 1 0 0 1 0 1 0]	A + 10 ₁₀ \rightarrow A	None	Add Ten to A
AISC	y	5-	[0 1 0 1 y]	A + y \rightarrow A	Carry	Add Immediate, Skip on Carry (y \neq 0)
CASC		10	[0 0 0 1 0 0 0 0]	\bar{A} + RAM(B) + C \rightarrow A Carry \rightarrow C	Carry	Complement and Add with Carry, Skip on Carry
CLRA		00	[0 0 0 0 0 0 0 0]	0 \rightarrow A	None	Clear A
COMP		40	[0 1 0 0 0 0 0 0]	\bar{A} \rightarrow A	None	Ones complement of A to A
NOP		44	[0 1 0 0 0 1 0 0]	None	None	No Operation
RC		32	[0 0 1 1 0 0 1 0]	"0" \rightarrow C	None	Reset C
SC		22	[0 0 1 0 0 0 1 0]	"1" \rightarrow C	None	Set C
XOR		02	[0 0 0 0 0 0 1 0]	A \oplus RAM(B) \rightarrow A	None	Exclusive-OR A with RAM

Fig 3—The instruction set for the COP420 illustrates the separate instruction groups for each of the chip's three subsections. Although you won't be able to fully decipher these instructions because we haven't included important supplemental notes and provisos, you should be able to understand their general structure.

ROM SECTION

Mnemonic	Operand	Hex Code	Machine Language Code (Binary)	Data Flow	Skip Conditions	Description
TRANSFER OF CONTROL INSTRUCTIONS						
JID		FF	1 1 1 1 1 1 1 1	ROM (PC9:8, A, M) → PC7:0	None	Jump Indirect
JMP	a	6--	0 1 1 0 0 0 a9:8 a7:0	a → PC	None	Jump
JP	a	--	1 a6:0 (pages 2, 3 only) or 1 1 a5:0 (all other pages)	a → PC6:0 a → PC5:0	None	Jump within Page
JSRP	a	--	1 0 a5:0	PC + 1 → SA → SB → SC 0010 → PC9:6 a → PC5:0	None	Jump to Subroutine Page
JSR	a	6--	0 1 1 0 1 0 a9:8 a7:0	PC + 1 → SA → SB → SC a → PC	None	Jump to Subroutine
RET		48	0 1 0 0 1 0 0 0	SC → SB → SA → PC	None	Return from Subroutine
RETSK		49	0 1 0 0 1 0 0 1	SC → SB → SA → PC	Always Skip on Return	Return from Subroutine then Skip
TEST INSTRUCTIONS						
SKC		20	0 0 1 0 0 0 0 0		C = "1"	Skip if C is True
SKE		21	0 0 1 0 0 0 0 1		A = RAM(B)	Skip if A Equals RAM
SKGZ		33	0 0 1 1 0 0 1 1		G3:0 = 0	Skip if G is Zero (all 4 bits)
SKGBZ		33	0 0 1 1 0 0 1 1	1st byte		Skip if G Bit is Zero
	0	01	0 0 0 0 0 0 0 1		G0 = 0	
	1	11	0 0 0 1 0 0 0 1		G1 = 0	
	2	03	0 0 0 0 0 0 1 1		G2 = 0	
	3	13	0 0 0 1 0 0 1 1		G3 = 0	
SKMBZ		01	0 0 0 0 0 0 0 1		RAM(B)0 = 0	Skip if RAM Bit is Zero
	1	11	0 0 0 1 0 0 0 1		RAM(B)1 = 0	
	2	03	0 0 0 0 0 0 1 1		RAM(B)2 = 0	
	3	13	0 0 0 1 0 0 1 1		RAM(B)3 = 0	
SKT		41	0 1 0 0 0 0 0 1		A time-base counter carry has occurred since last test.	Skip on Timer

I/O SECTION

Mnemonic	Operand	Hex Code	Machine Language Code (Binary)	Data Flow	Skip Conditions	Description
INPUT/OUTPUT INSTRUCTIONS						
ING		33 2A	0 0 1 1 0 0 1 1 0 0 1 0 1 0 1 0	G → A	None	Input G ports to A
ININ		33 28	0 0 1 1 0 0 1 1 0 0 1 0 1 0 0 0	IN → A	None	Input IN Inputs to A
INIL		33 29	0 0 1 1 0 0 1 1 0 0 1 0 1 0 0 1	IL3, CKO, "0", IL0 → A	None	Input IL Latches to A
INL		33 2E	0 0 1 1 0 0 1 1 0 0 1 0 1 1 1 0	L7:4 → RAM(B) L3:0 → A	None	Input L Ports to RAM, A
OBD		33 3E	0 0 1 1 0 0 1 1 0 0 1 1 1 1 1 0	Bd → D	None	Output Bd to D Outputs
OGI	y	33 5--	0 0 1 1 0 0 1 1 0 1 0 1 y	y → G	None	Output to G Ports Immediate
OMG		33 3A	0 0 1 1 0 0 1 1 0 0 1 1 1 0 1 0	RAM(B) → G	None	Output RAM to G Ports
XAS		4F	0 1 0 0 1 1 1 1	A ↔ SIO, C → SK	None	Exchange A with SIO

INSTRUCTION SET SYMBOLS

Symbol	Definition
INTERNAL ARCHITECTURE SYMBOLS	
A	4-bit Accumulator
B	6-bit RAM Address Register
Br	Upper 2 bits of B (register address)
Bd	Lower 4 bits of B (digit address)
C	1-bit Carry Register
D	4-bit Data Output Port
EN	4-bit Enable Register
G	4-bit Register to latch data for G I/O Port
IL	Two 1-bit Latches associated with the INg or ING Inputs
IN	4-bit Input Port
L	8-bit TRI-STATE I/O Port
M	4-bit contents of RAM Memory Pointed to by B Register
PC	10-bit ROM Address Register (program counter)
Q	8-bit Register to latch data for L I/O Port
SA	10-bit Subroutine Save Register A
SB	10-bit Subroutine Save Register B
SC	10-bit Subroutine Save Register C
SIO	4-bit Shift Register and Counter
SK	Logic-Controlled Clock Output

INSTRUCTION OPERAND SYMBOLS

d	4-bit Operand Field, 0-15 binary (RAM Digit Select)
r	2-bit Operand Field, 0-3 binary (RAM Register Select)
a	10-bit Operand Field, 0-1023 binary (ROM Address)
y	4-bit Operand Field, 0-15 binary (Immediate Data)
RAM(s)	Content & RAM location addressed by s
ROM (t)	Content & ROM location addressed by t

OPERATIONAL SYMBOLS

+	Plus
-	Minus
→	Replaces
↔	Is exchanged with
=	Is equal to
\bar{A}	The ones complement of A
⊕	Exclusive-OR
:	Range of values

Split-up RAM-addressing schemes permit maximum ROM-code density

string has been cleared. Such clever RAM mapping is essential in 1-chip μ Cs (Refs 4 and 5). At this point we should mention a handy feature found in several of the calculator-derived μ Cs. You can create multiple-entry subroutines by starting off with a string of LBIs, with each one setting up a different starting point in RAM. When a subroutine is called, only the first LBI landed upon is executed—all following LBIs are

ignored. With this dodge, you could extend this clear routine to clear any number of different strings in RAM; the main program calls the desired clear by having the jump-to-subroutine command vector to the desired LBI.

Now suppose (as a second example) that you want to add two BCD strings. The code sequence shown in Fig 6 uses the XIS instruction because this example involves working up from the least significant digit. You map the two arguments to be added one above the other, with their most significant digits up against the high end of the RAM strings.

To make the XIS operate alternately on both

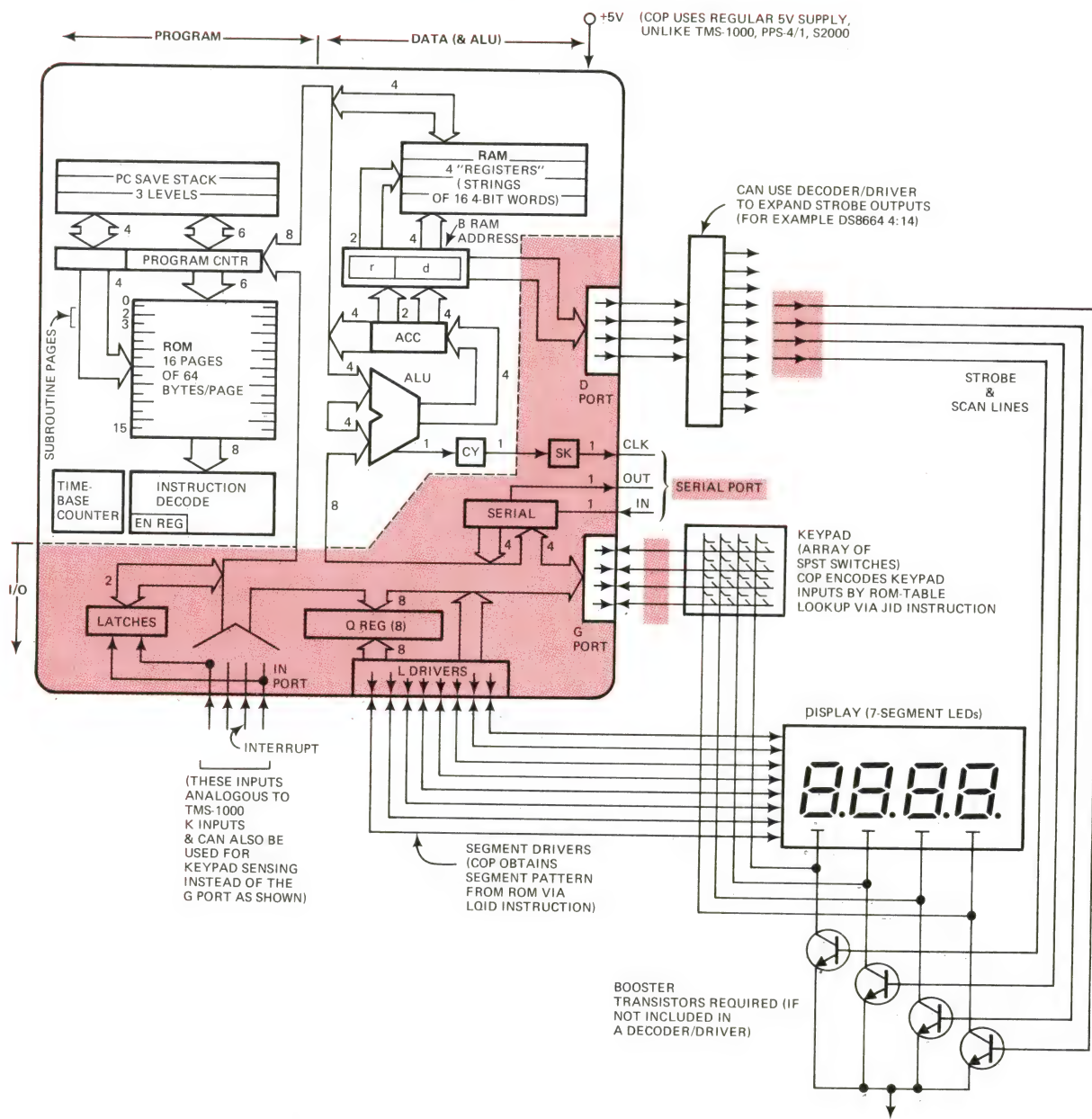


Fig 4—Architecture of the COP420 shows how the chip expands on the basic calculator configuration. Instead of using the same number of I/O pins for the strobes, as most calculators and the TMS-1000 do, National cut the number of strobe outputs to four. The seven freed pins

implement another 4-bit parallel port and a 3-line serial port. Note how many of the pins that were single-function unidirectional lines in the TMS-1000 are now multifunctional and bidirectional, and note the addition of true vectored interrupt on one of the IN pins.

arguments, you need only initialize the RAM-address register once (with the first LBI), and from then on you use the exclusive-ORing feature of XIS's r field to keep flipping back and forth between one string and the other. In the example, the r address for argument 1 is 00, while the r address for argument 2 is 01. Because there is a ONE in the operand field's least-significant-bit position, the exclusive-OR operation causes the least significant bit of the r address to flip back and forth, from ZERO to ONE and then ONE to ZERO. It's hard to imagine a more compact form of relative addressing.

Like the COP400 family, the PPS-4/1 and S2000 also have combined RAM-addressing and loop-control instructions. But the earlier TMS-1000 doesn't, and consequently it suffers in benchmark tests with respect to code compactness and execution speed. However, the TMS-1000 offers users the option of creating more powerful commands through mask-programmed microinstructions; knowledgeable users might thus be able to make it catch up in capability to the newer 1-chip devices.

When low-end 1-chip μ Cs aren't handling BCD strings, they are usually handling individual bits used as flags to remember states of an application's system. All the devices cited here, including the TMS-1000, have instructions that can set, reset and test individual bits in the 4-bit machine words (Fig 3).

However, the bit-manipulation instructions assume that the RAM-address register points at the word containing the desired bit. If that isn't the case (as, for example, with a less inspired arrangement of the RAM-location assignments and program flow), an instruction like the COP LBI must initialize the RAM pointer. (Note that there are two LBIs in the COP instruction set: a short 1-byte LBI and a long 2-byte LBI. Obviously you should try to place the flag bits in words that the short instruction can point to.)

I/O evolved from trials of calculators

To appreciate the peculiar architecture of the calculator-based μ Cs' I/O sections, you must recall what happened in the calculator marketplace during the brutal price wars of the early 1970s. The name of the game then for US manufacturers was combatting the advantage of cheap Asian assembly labor by reducing the number of parts the US products required; it was the only way a US manufacturer could stay in business as retail calculator prices tumbled from \$100 to \$10.

The goal was to have only three essential components:

- The calculator chip itself
- The output display
- The input keyboard.

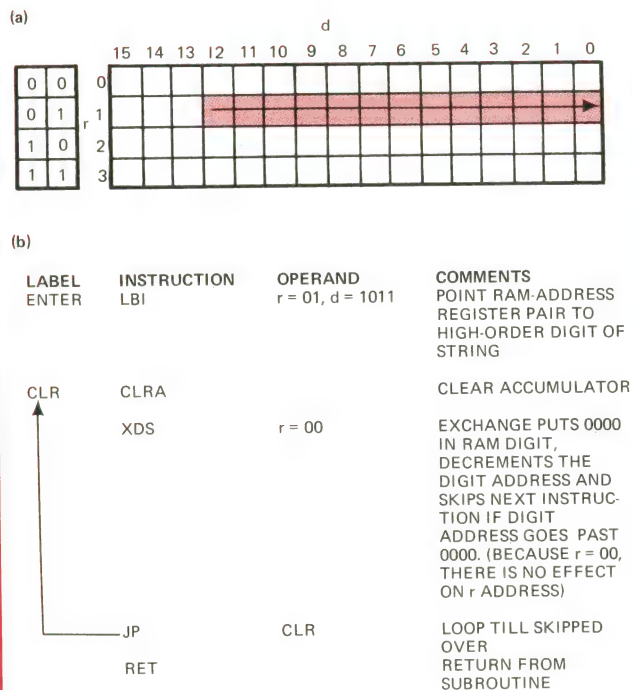


Fig 5—RAM mapping and software clear a COP420 digit string and illustrate how little ROM space is needed if you organize RAM mapping in "calculator" fashion (all instructions are single bytes).

All of these components would ideally mount on one pc board—and that's about all you see inside today's pocket calculators besides the batteries.

The TMS-1000 directly reflects this bare-bones calculator heritage, and part of its immense popularity arises from the way it has brought the economies of \$10 calculator chips within the reach of all product designers.

A diagram in one of our previous articles—Fig 1 of Ref 1—illustrated how closely the TMS-1000's I/O subsystem meets the calculator-market criterion of minimum off-chip parts; Fig 1 in this article shows an I/O configuration that's a capsule rendition of that earlier figure. You can see that the TMS-1000 fails to meet the goal only insofar as it needs external transistors to sink the collective common-cathode currents of the display digits. Each LED is sourced with 10 mA (directly from the TMS-1000), so if all seven segments plus the decimal point are ON, the digit strobe must sink 80 mA—too much to expect of a reasonably sized LSI-device I/O driver. (However, some calculator chips can directly handle the collective digit currents of small displays—for example, the General Instrument C-6XXD/C to C-16XXD Series).

The TMS-1000's 28-pin package has 11 strobe outputs, so the μ C can service 11 digits without external multiplexing. In calculators, these same strobes are used to scan the keyboard matrix, but in most units, except for the most complex

I/O subsystems permit use of a minimum number of parts

scientific calculators (and some of the newer alphanumeric language translators), some strobes are usually left over and are utilized by product designers to expand the TMS-1000's functions beyond mere calculation.

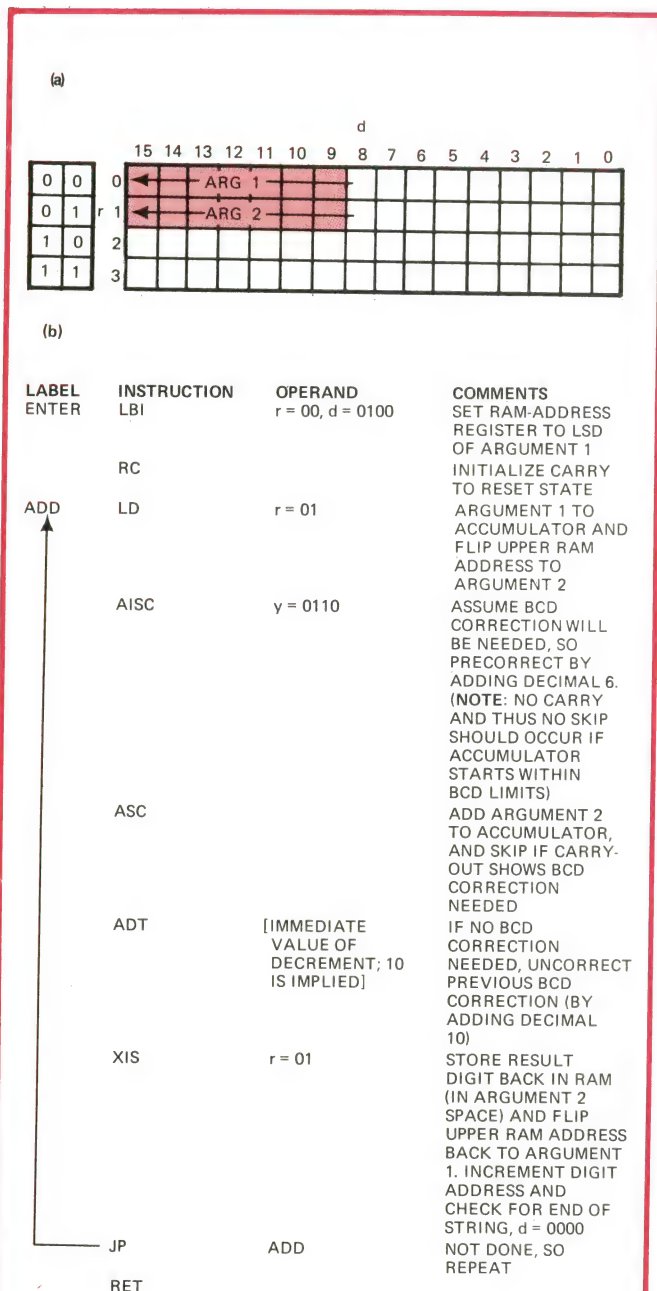


Fig 6—BCD addition of large numbers is something that any calculator should do well, and this COP420 program indicates how few precious ROM bytes the procedure can tie up if coded well. Note the decimal correction, implemented via a "precorrection-then-uncorrect-if-not-needed" process; several of the calculator-derived machines use this technique. An important advantage of the data-RAM section's 4-bit-wide words, compared with RAM in 8-bit machines, is that there is no wasted memory space used to accommodate numbers with an odd number of digits.

Internally, the I/O section's logic helps the TMS-1000 handle the calculator-type servicing of the display and keyboard in several ways. The strobe outputs are driven from the same addressing that accesses digits in the RAM strings. (In terms of the diagram of the COP-420 1-chip μ C architecture—Fig 4—this would be the d part of the B register.) As a result, the digit addressed in the RAM is the same one being refreshed in the display. A PLA associated with the segment outputs in the TMS-1000 aids the process by automatically translating each BCD digit into a 7-segment (or other) pattern.

The TMS-1000 has only four inputs. Many designers now consider that too few, but four are all that most calculator applications require, and the 4-bit-wide port matches up nicely with the 4-bit-wide data words on the RAM side of the machine. While the TMS-1000 can handle more inputs than shown in the illustration by means of further input multiplexing with the available leftover strobe outputs, these extra inputs—if they are other than the simple spst switches of keyboards—demand further external devices. Furthermore, the TMS-1000 has no interrupts, so it is usually restricted to handling external events within the rhythm of its basic repeating keyboard- and display-scanning loop.

The I/O sections of the newer μ Cs—the PPS-4/1, COP400 and S2000—are all variations and elaborations upon the TMS-1000 structure. These μ Cs' designers have tried to strengthen the strong points of the TMS-1000 architecture while adding flexibility and generality.

An I/O variation

Like the TMS-1000, the COP420 also comes in a small 28-pin package. National has attempted to redistribute the μ C's I/O resources to make it a more general-purpose controller; the firm has traded off some of the strobe outputs in favor of a 4-bit bidirectional port and a 3-line (one input, one output, one clock) serial I/O port. Thus, whereas the TMS-1000 has 11 strobe outputs, the COP420 has only four.

If a COP420 user wants to strobe more display digits than just four, he must add an external 4-to-16 decoder. This addition isn't necessarily a disadvantage, because available low-cost TTL decoders provide both the decoding and the high-current sinking for display digits.

The COP's serial I/O isn't too flexible—it only operates synchronously with the COP clock—but it provides (among other things) a handy means for communicating with low-cost shift-register devices and other COP units. For example, you could tie an inexpensive 8-pin miniDIP CMOS shift register to this port for additional nonvolatile RAM. If you don't need a serial port, you can software-program this same shift register to act

a multi-output* power supply

KEPCO

MPS 620M

a convenient bench-top power supply
offering voltage/current combinations
required for IC's and microprocessors

* 0 to 6 Volts, 5 Amps and 0 to ± 20 Volts, 1 Amp each



Call your local Kepco rep for a demonstration or write Dept. AZF-12.

KEPCO®

KEPCO, INC. • 131-38 SANFORD AVENUE • FLUSHING, N.Y. 11352 U.S.A. • (212) 461-7000 • TWX #710-582-2631 • Cable: KEPCOPOWER NEWYORK

For more information, Circle No 66

COP400 family is to retain the economies of a TMS-1000-class device but also broaden the device's general-purpose usefulness by offering a wide range of hardware and software options. The most extreme of these options, device-mask, permits direct connection to the midrange 8080's 8-bit bus—an action that uses up most of the I/O that would normally serve for calculating the classic calculator-type keyboard-display scan. But the COP device still has enough remaining ports to be used—with external logic or another COP device linked to it via the serial port—for a surprising variety of applications. Computer-system manufacturers are utilizing this part as an intelligent link to peripherals, according to National. The firm is also producing a preprogrammed version that services an alphanumeric keyboard and display.

In the S2000, AMI has taken a somewhat different tack in I/O-subsystem implementation than National has. Rather than trying to maintain the smallest possible chip sizes and thereby keep cost low, the firm has sought to produce a Cadillac version of the TMS-1000, even if that approach uses more chip area and puts the μ C at the high end of the 1-chip calculator-based- μ C marketplace. For example, AMI uses a special

though the AMI chip is NMOS. The firm also includes I/O to directly handle capacitive touch-keyboard inputs (the type popular in microwave ovens). Part of this I/O capability is an input that detects analog thresholds. And future S2000-family chips will incorporate 8-bit A/D converters and up to 4k of ROM.

Before we began to get hands-on experience with the low-end, calculator-derived 1-chip μ Cs, we had assumed they were just a passing fad—a case of calculator suppliers' trying to cash in on the μ P bonanza. Now we've reversed our opinion. Far from being makeshift, hand-me-down expedients, calculator-derived architectures appear to be nearly optimum for use in low-end markets.


Actually, the 1-chip μ C's multiplexed-I/O structure should also suit many electromechanical and simple electronic interfaces as well. A system's keyboard matrix's spst switches could be replaced by any similar device, from reed switches to snap-action limit units; any of the many variable-resistance, 2-terminal electronic devices, from photocells to thermistors, could also substitute for these keyboard switches. Similarly, the display's LEDs could be replaced by a whole host of output actuators.

The Microbus option and the serial I/O of National's COP family also portend how the \$1 to \$3 chips could be linked into the larger multiprocessing systems of the future, adding credibility to our thesis that 1-chip μ Cs will evolve into the equivalents of TTL building blocks. One National source has even predicted that you'll be seeing multiples of these computers on single chips. **EDN**

Extra

high quality switchers

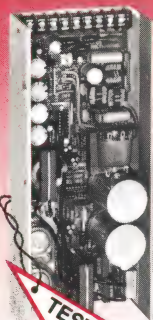Deltron offers switchers that are both high quality and versatile. These 100 to 300 watt singles, duals, triples and quads feature efficiencies to 82%, with brown out protection and 20 msec. loss of line hold-up. This is Deltron's unique answer to meet your design challenges of today at competitive prices.



- Built-in differential and common mode RFI suppression.
- Input surge and OV protection.
- UL 478 recognized.
- Split primary.
- Open and closed frame units.

Write for more information on Deltron's high performance switchers.

Deltron inc.

Wissahickon Avenue • North Wales, PA 19454
Tel: 215/699-9261 Tlx: 510/661-8061

AC31


For more information, Circle No 67

References

1. Cushman, Robert H, "Are single-chip microcomputers the universal logic of the 1980s?" *EDN*, January 5, 1979, pg 83.
2. Cushman, Robert H, "Use your midrange μ P equipment to explore today's 1-chip μ Cs," *EDN*, February 20, 1979, pg 84.
3. "Fifth Annual Microprocessor Directory," *EDN*, November 20, 1978, pg 86.
4. Kinney, Bruce W, "Simplify volume product design with single-chip microcomputers," *EDN*, April 5, 1978, pg 97.
5. Landau, Jack V, "Software removes limitations to single-chip μ P performance without boosting system cost," *Electronic Design*, February 1, 1979, pg 68.
6. "COP420/421 Single-Chip n-Channel Microcontrollers," (DA-B25K68, June 1978), National Semiconductor Corp, 2900 Semiconductor Dr, Santa Clara, CA 95051.

Article Interest Quotient (Circle One)
High 485 Medium 486 Low 487

For film capacitors in volume...

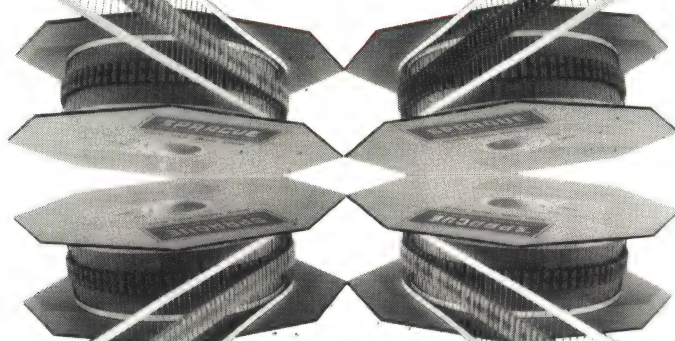

talk to the reel people.

SPRAGUE TYPE 192P

Plastic-sleeved
PACER® Capacitors

Polyester film. Unique construction... extended foil sections terminated in metal end caps to which leads are attached... outer protection is tough plastic sleeve. Capacitance values from .0001 to .39 μ F. Voltage ratings from 80 to 600 WVDC.

Write for Bulletin 2066C
or circle number 68

SPRAGUE TYPE 413P

Epoxy-coated
FILMITE® 'E' Capacitors

Polyester film. Conformal epoxy coating and excellent lead concentricity permit automatic insertion. Preferred where size and cost are important. Capacitance values from .001 to .1 μ F. Voltage ratings of both 100 and 200 WVDC.

Write for Bulletin 2061B
or circle number 69

SPRAGUE TYPE 416P

Film-wrapped
YELLOW JACKET® Capacitors

Polyester film. Extended foil sections protected against moisture by outer wrap of polyester or polyolefin film. Plastic resin end seals. This construction results in weight/space advantages. Capacitance values from .001 to 1 μ F. Voltage ratings, 50 to 600 WVDC.

Write for Bulletin 2063C
or circle number 70

SPRAGUE TYPE 433P

Epoxy-coated
METFILM® 'E' Capacitors

Closely-controlled metallized polyester film. Superior conformal epoxy coating. Low cost for use in entertainment electronics, yet dependable enough for industrial applications. Capacitance values from .027 to 1.0 μ F. Voltage ratings from 100 to 400 WVDC.

Write for Bulletin 2060A
or circle number 71

For complete technical data on the capacitor type(s) in which you are interested, write for appropriate engineering bulletin(s) as shown above, to: Technical Literature Service, Sprague Electric Co., 491 Marshall St., North Adams, Mass. 01247.

THE BROAD-LINE PRODUCER OF ELECTRONIC PARTS

SPRAGUE®


THE MARK OF RELIABILITY

Sprague® and ® are registered trademarks of the Sprague Electric Co.

Long-Life / Premium Grade Electrolytics

Chemicon® Switching Regulator Capacitors

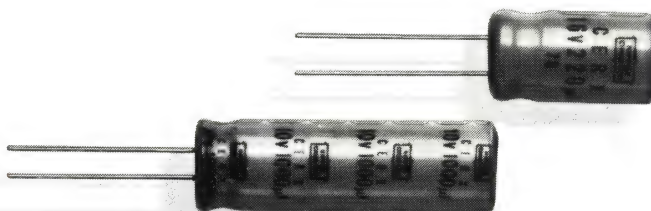- Low inductance • Low ESR
- High ripple current • Epoxy End Seal (optional)
- Temperature -55°C to +110°C
- Non-aqueous electrolyte
- 2,000 hrs. at 110°C
- Date coded
- Lot traceable



RX SERIES

Write for information
—attach business card to
your company letterhead.

Special Applications Invited

COMMERCIAL GRADES AVAILABLE



UNITED CHEMICON, INC.

9801 West Higgins Road, Rosemont, Illinois 60018 312/696-2000

Design Ideas

Conversion circuit handles binary or BCD

R Srinivasan, R Ramesh and D K Murthi
National Aeronautical Lab, Bangalore, India


Systems requiring arithmetic operations on data usually perform those operations in binary form. As a result, they must convert the data to BCD form for display purposes. Address-selection information from digit switches, on the other hand, must be converted to binary form for use in memory-addressing operations.

For applications not requiring fast conversion, a single circuit that can perform both

conversions proves adequate. One such circuit (see figure) utilizes up/down counters to obtain the desired results. To perform binary-to-BCD conversion, preset the binary value in the binary counter and clear the BCD counter. The binary counter counts down while the BCD counter counts up, and when the binary counter reaches zero, the BCD counter holds. For BCD-to-binary operation, the BCD counter counts down from the BCD value while the binary counter counts up.

EDN

To Vote For This Design, Circle No 450

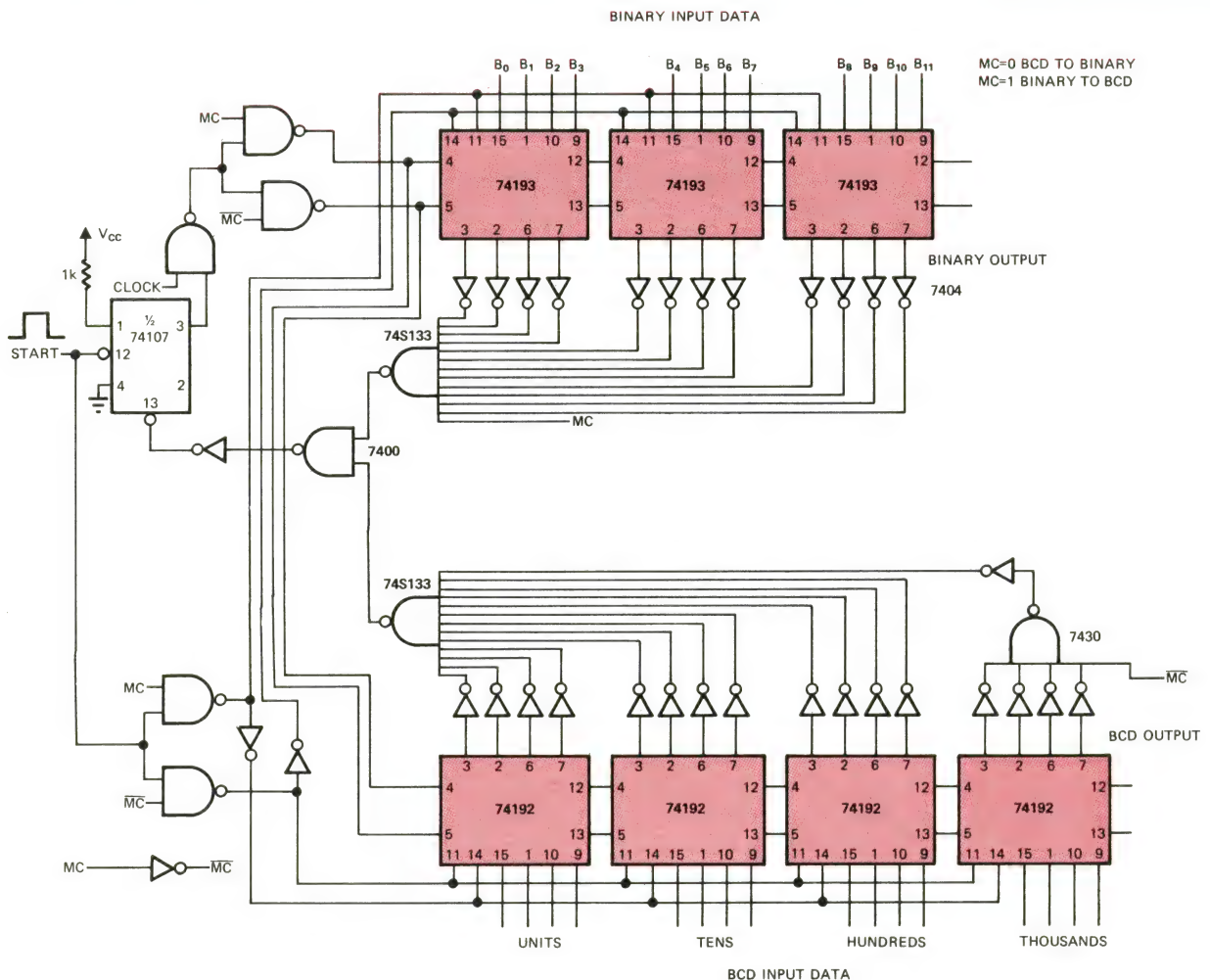

Separate binary and BCD up/down counters permit both binary-to-BCD and BCD-to-binary conversion in one circuit.

Comparator detects frequency

Robert Pease

National Semiconductor, Santa Clara, CA

A quad comparator forms the basis of a frequency detector (**figure**) that is faster and less expensive than more complex versions designed around F/V-converter chips.

Positive feedback through a 5-M Ω resistor allows the circuit to resolve changes as small as 2%; the output responds to those changes in about one cycle. When the input frequency is

high, V_2 is pulled LOW, it's never allowed to exceed $2/3V_S$. When the input frequency is lower than the limit, V_2 exceeds $2/3V_S$ once each cycle, but V_3 is held below that limit.


The trip frequency is defined by

$$F = 1/(1.1R_s C_s).$$

You can adjust R_2 to permit trimming of the trip point, but R_3 must remain larger than R_1 .

EDN

To Vote For This Design, Circle No 451

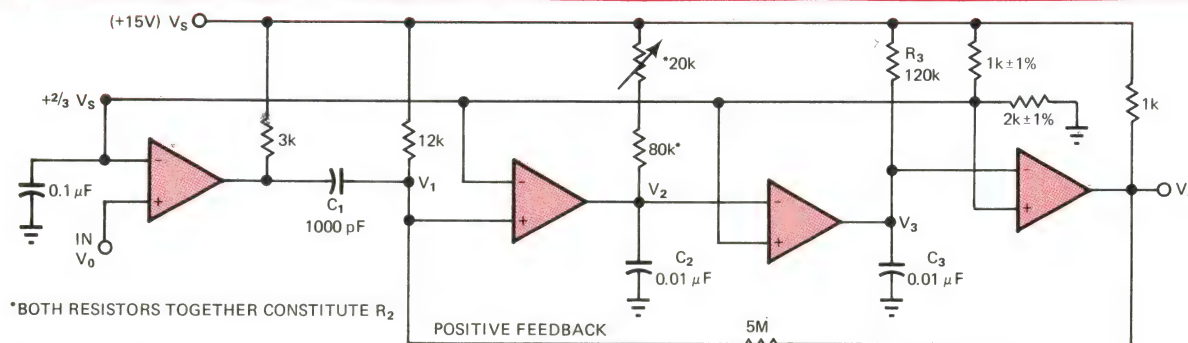

A single quad comparator finds use in a fast and simple frequency-detector circuit.

Op amp provides linear current source

Donald E Hall

Tektronix Inc, Beaverton, OR

A common 2-transistor differential amplifier provides a simple voltage-controlled method for driving circuits requiring such inputs. This approach, however, suffers from irregularities over much of the source's dynamic range, producing the familiar characteristic shown in **Fig 1**. Notice in this example that for operation with less than 1% nonlinearity, differential base voltage must remain within a $\pm 26\text{-mV}$ range—leaving a large portion of the dynamic range unused.

An improved circuit (**Fig 2**) uses a 741 op amp to overcome nonlinearity. With ideal op-amp response, the transfer function is described by

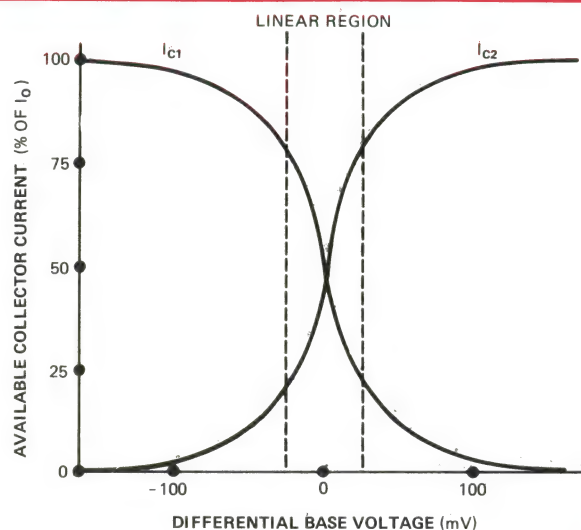


Fig 1—A typical 2-transistor differential amplifier proves linear only within a narrow range of base voltages.

"We needed a software tool that would give us direct control of a highly interactive system."

"We build Remote Switched Access Systems which provide circuit testing for Bell and Independent telephone companies nationwide. Our SAS is a microprocessor-based interactive test system with sophisticated diagnostic capabilities. The operator uses the terminal to call and test any circuit in the network. The software we developed to run our SAS was originally written in assembly language. It took a very talented programmer six months, 80 hours a week to write. Plus six months additional staff time. It hadn't been out in the field very long before our customers started requesting special routines and tests, all sorts of modifications. We tried every assembly language trick we could, but we couldn't modify the program economically."

—Gambera

"We had a crisis on our hands."—Morris

"We looked at Basic, Fortran, Pascal. They were all too complex. Then we looked at FORTH's micro package. At first we were skeptical. But we were faced with an urgent need. We figured 'What do we have to lose? If FORTH can do what they say, we can make it'."



Armand Gambera, Engineering Supervisor/Portable Products. Larry Morris, Engineering Supervisor/SAS Systems. Telecommunications Technology, Inc., Sunnyvale, CA.

"Within two days we were writing routines in FORTH that would have taken two to three weeks to write in assembler."—Morris

"That's when we decided to use FORTH. We were impressed by how quick and easy it is to use. A good programmer should be up on it in two days. We had all kinds of fun. Inside a month we were really confident with it."

"In three months, two of our people completely rewrote the program with significant enhancements."—Gambera

"We couldn't have delivered on our commitment without FORTH. Everyone in our organization is now using it for all but the most trivial routines."

"It's amazing the impact programming speed has had on our ability to work with customers."—Gambera

"FORTH programming is fast. We can be much more responsive now. FORTH's programming speed more than offset the cost of rewriting our first program. Target-compiling and de-bugging are quicker too. We target-

compiled FORTH in one day. It would have taken a week in assembler. And something that might take 30 hours to debug in another language takes two hours in FORTH. Editing is extremely simple."

"FORTH gives us the nuts-and-bolts control of Assembler without all the tedious coding."—Morris

"FORTH gives us better control over run time. It's very close to the micro-processor in terms of definitions so you can configure as you like, right at the hardware level. That's especially important to us since we have a lot of interfaces, a lot of driver routines."

"My advice to others is: 'Try It!'"—Gambera

"You won't believe it until you do. We all know how stubborn people can be when it comes to trying something new. Engineers can't afford to be. If a tool works, you use it. FORTH works for us. We wouldn't consider going back to assembler or switching to some other high-level language. We're sold on FORTH. We only wish we'd tried it sooner."

"Engineers can't afford to be stubborn about trying new tools. If it works, you use it!"

FORTH is a stand alone operating system and multi-level language for minis and micros. We also offer contract programming services. For full details or for information on a FORTH seminar in your area call (213) 372-8493 or send the coupon attached on your company's letterhead.

OK, I'm interested!

☐ Please rush full details on:
____microFORTH for μ P development
____miniFORTH for minicomputers
____fixed price applications

____programming services
☐ Contact us for immediate requirements

Phone: () _____

☐ Send dates and locations for your FORTH Seminars.

Name _____

Title _____

FORTH, Inc., 815 Manhattan Avenue,
Manhattan Beach, CA 90266.

FORTH, Inc.

For more information, Circle No 72

Design Ideas

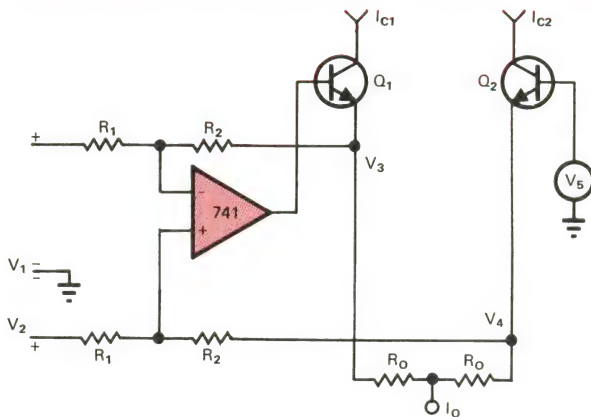


Fig 2—Adding an op amp linearizes the output of the current source.

$$(V_3 - V_4)/(V_2 - V_1) = R_2/R_1.$$

Because

$$I_{C1} - I_{C2} = (V_3 - V_4)/R_0,$$

then

$$(I_{C1} - I_{C2})/(V_2 - V_1) = R_2/R_0R_1.$$

This relationship indicates that even though transconductance of individual transistors can change, the op amp maintains a linear relationship in the current source. Linear opera-

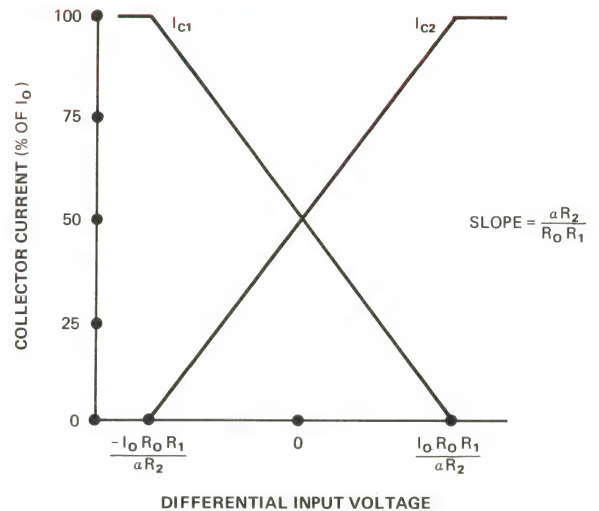


Fig 3—The improvement in linearity effects a significant increase in the circuit's dynamic range.

tion continues until I_{C1} or I_{C2} equals I_0 , as shown in Fig 3.

EDN

To Vote For This Design, Circle No 452


Single chip converts BCD to binary

Vaughn Martin

ITT Aerospace/Optical, Ft Wayne, IN

One 4-bit full adder with a carryout and a spdt switch can convert any BCD number up to 19 into its binary equivalent. The adder's A inputs accept the number's least significant digits from a 10-position BCD thumbswitch; the spdt switch provides the tens-place information. Held HIGH, the switch represents a 10; LOW, a zero. The figure illustrates conversion of the number 13.

The first binary addition of a logic ONE (A_0) and a logic ZERO (B_0) yields a logic ONE (Σ_0); the addition of two logic ONES (A_1 and B_1) yields a logic ZERO (Σ_1) and a carry. The third binary addition of two logic ZEROS (B_2 and A_2) and the carry yield a logic ONE (Σ_2). The last addition, a logic ONE (B_3) plus a logic ZERO (A_3), yields a logic ONE (Σ_3). For numbers greater than 15, the last addition causes a

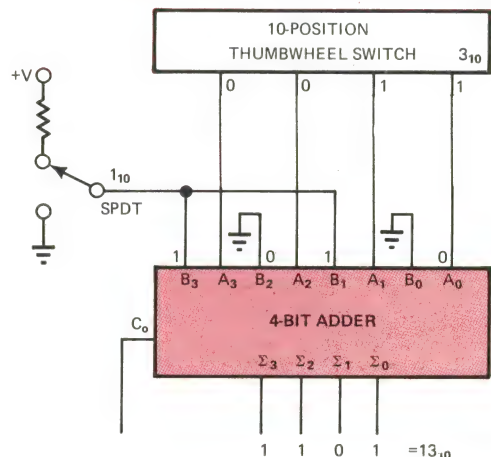


To convert BCD numbers less than 20 into binary form, this simple circuit uses only a 4-bit adder.

carry out (C_0).

EDN

To Vote For This Design, Circle No 453

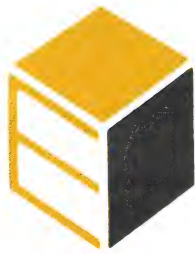

electrocube

PRODUCT SUMMARY

CAPACITORS/EMI FILTERS/RC NETWORKS/TRANSFORMERS/BALLASTS

Metallized Polycarbonate Wrap/Fill

50 VOLT

100 VOLT

200 VOLT

DIMENSIONS						CATALOG PART NUMBER	LEAD SIZE (AWG)	DIMENSIONS						CATALOG PART NUMBER	LEAD SIZE (AWG)	DIMENSIONS						CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ±.05"	W ±.05"	L ±.05"		MFD			T ±.05"	W ±.05"	L ±.05"		MFD	T ±.05"			W ±.05"	L ±.05"						
For .0010 thru .033 MFD - See Higher Voltages																							
.039	.09	.18	.40		650B1A393	26	.018	.09	.18	.40		650B1B183	26	.0039	.09	.18	.40		650B1C392	26			
.047	.09	.18	.40		650B1A473	26	.022	.09	.18	.40		650B1B223	26	Thru	.09	.18	.40		650B1C	26			
.056	.09	.18	.40		650B1A563	26	.033	.09	.18	.40		650B1B333	26	.015	.09	.18	.40		650B1C153	26			
.068	.09	.18	.40		650B1A683	26	.039	.09	.18	.40		650B1B393	26	.018	.10	.19	.40		650B1C183	26			
.082	.09	.18	.40		650B1A823	26	.047	.09	.18	.40		650B1B473	26	.022	.11	.20	.40		650B1C223	26			
.10	.09	.18	.40		650B1A104	26	.056	.10	.19	.40		650B1B563	26	.027	.09	.18	.53		650B1C273	26			
.12	.09	.18	.40		650B1A124	26	.068	.11	.21	.40		650B1B683	26	.033	.09	.18	.53		650B1C333	26			
.15	.10	.20	.40		650B1A154	26	.082	.09	.18	.53		650B1B823	26	.039	.10	.20	.53		650B1C393	26			
.18	.09	.18	.53		650B1A184	26	.10	.10	.19	.53		650B1B104	26	.047	.11	.21	.53		650B1C473	26			
.22	.09	.18	.53		650B1A224	26	.12	.11	.20	.53		650B1B124	26	.056	.13	.22	.53		650B1C563	24			
.27	.10	.19	.53		650B1A274	26	.15	.12	.22	.53		650B1B154	24	.068	.15	.24	.53		650B1C683	24			
.33	.11	.21	.53		650B1A334	26	.18	.14	.23	.53		650B1B184	24	.082	.16	.26	.53		650B1C823	24			
.39	.13	.22	.53		650B1A394	24	.22	.16	.25	.53		650B1B224	24	.10	.18	.28	.53		650B1C104	24			
.47	.14	.24	.53		650B1A474	24	.27	.18	.28	.53		650B1B274	24	.12	.21	.30	.53		650B1C124	24			
.56	.16	.25	.53		650B1A564	24	.33	.20	.30	.53		650B1B334	24	.15	.23	.33	.53		650B1C124	24			
.68	.18	.27	.53		650B1A684	24	.39	.23	.32	.53		650B1B394	24	.18	.21	.30	.68		650B1C184	24			
.82	.20	.29	.53		650B1A824	24	.47	.20	.30	.68		650B1B474	24	.22	.23	.33	.68		650B1C224	24			
1.0	.22	.32	.53		650B1A105	24	.56	.23	.32	.68		650B1B564	24	.27	.24	.33	.78		650B1C274	24			
1.2	.20	.29	.68		650B1A125	24	.68	.23	.32	.78		650B1B684	24	.33	.27	.36	.78		650B1C334	24			
1.5	.22	.32	.68		650B1A155	24	.82	.25	.35	.78		650B1B824	24	.39	.30	.40	.78		650B1C394	22			
1.8	.23	.32	.78		650B1A185	24	1.0	.28	.38	.78		650B1B105	24	.47	.33	.43	.78		650B1C474	22			
2.0	.24	.34	.78		650B1A205	24	1.2	.31	.41	.78		650B1B125	22	.56	.32	.41	.95		650B1C564	22			
2.5	.26	.37	.78		650B1A255	24	1.5	.37	.48	.95		650B1B155	22	.68	.25	.42	1.17		650B1C684	22			
3.0	.31	.41	.78		650B1A305	22	1.8	.34	.44	.95		650B1B185	22	.82	.28	.45	1.17		650B1C824	22			
3.5	.34	.43	.78		650B1A355	22	2.0	.44	.54	1.17		650B1B205	22	1.0	.32	.49	1.17		650B1C105	22			
4.0	.31	.40	.95		650B1A405	22	2.5	.51	.61	1.17		650B1B255	22	1.2	.36	.52	1.17		650B1C125	20			
4.5	.33	.42	.95		650B1A455	22	3.0	.55	.65	1.17		650B1B305	20	1.5	.41	.58	1.17		650B1C155	20			
5.0	.25	.42	1.17		650B1A505	22	4.0	.61	.71	1.17		650B1B355	20	1.8	.46	.62	1.17		650B1C185	20			
6.0	.28	.45	1.17		650B1A605	22	5.0	.67	.77	1.17		650B1B405	20	2.0	.49	.65	1.17		650B1C205	20			
8.0	.34	.50	1.17		650B1A805	22	6.0	.71	.81	1.17		650B1B455	20	2.5	.47	.64	1.45		650B1C255	20			
10.0	.39	.56	1.17		650B1A106	20	8.0	.77	.87	1.17		650B1B505	20	3.0	.47	.63	1.70		650B1C305	20			
12.0	.43	.60	1.17		650B1A126	20	10.0	.81	.91	1.17		650B1B555	20	3.5	.51	.67	1.70		650B1C355	20			
15.0	.49	.66	1.17		650B1A156	20	12.0	.84	.94	1.17		650B1B605	20	4.0	.50	.66	1.90		650B1C405	20			
18.0	.47	.64	1.45		650B1A186	20	15.0	.91	1.01	1.17		650B1B655	20	4.5	.53	.70	1.90		650B1C455	20			
20.0	.50	.67	1.45		650B1A206	20	18.0	.94	1.04	1.17		650B1B705	20	5.0	.57	.73	1.90		650B1C505	20			
30.0	.56	.73	1.70		650B1A306	20	20.0	.98	1.08	1.17		650B1B755	20	6.0	.63	.79	1.90		650B1C605	20			
40.0	.66	.83	1.70		650B1A406	20						650B1B805	20	8.0	.74	.90	1.90		650B1C805	20			
50.0	.75	.91	1.70		650B1A506	20						650B1B855	20	10.0	.84	1.00	1.90		650B1C106	20			

Epoxy Case

50 VOLT

100 VOLT

200 VOLT

DIMENSIONS													CATALOG PART NUMBER	LEAD SIZE (AWG)	DIMENSIONS													CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T			S	MFD	T			S	MFD	T				S														
	±.01"	(MAX.)	±.01"			±.01"	(MAX.)	±.01"			±.01"	(MAX.)				±.01"													
For .0010 thru .068 MFD													See Higher Voltages	For .0010 thru .022 MFD													See Higher Voltages		
.082	18	30	42	300	652A1A823	22	.027	18	30	42	300	652A1B273	22	.0056	18	30	42	300	652A1C562	22									
Thru	18	30	42	300	652A1A	22	.033	18	30	42	300	652A1B333	22	Thru	18	30	42	300	652A1C	22									
.15	18	30	42	300	652A1A154	22	.039	18	30	42	300	652A1B393	22	.015	18	30	42	300	652A1C153	22									
.18	18	30	55	400	652A1A184	22	.047	18	30	42	300	652A1B473	22	.018	18	30	42	300	652A1C183	22									
.22	18	30	55	400	652A1A224	22	.056	18	30	42	300	652A1B563	22	.022	18	30	42	300	652A1C223	22									
.27	18	30	55	400	652A1A274	22	.068	18	30	42	300	652A1B683	22	.027	18	30	55	400	652A1C273	22									
.33	18	30	55	400	652A1A334	22	.082	18	30	55	400	652A1B823	22	.033	18	30	55	400	652A1C333	22									
.39	18	30	55	400	652A1A394	22	.10	18	30	55	400	652A1B104	22	.039	18	30	55	400	652A1C393	22									
.47	24	37	55	400	652A1A474	22	.12	18	30	55	400	652A1B124	22	.047	18	30	55	400	652A1C473	22									
.56	24	37	55	400	652A1A564	22	.15	18	30	55	400	652A1B154	22	.056	24	37	55	400	652A1C563	22									
.68	24	37	55	400	652A1A684	22	.18	24	37	55	400	652A1B184	22	.068	24	37	55	400	652A1C683	22									
.82	30	43	55	400	652A1A824	22	.22	24	37	55	400	652A1B224	22	.082	24	37	55	400	652A1C823	22									
1.0	30	43	55	400	652A1A105	22	.27	24	37	55	400	652A1B274	22	.10	24	37	55	400	652A1C104	22									
1.2	30	43	67	500	652A1A125	22	.33	30	43	55	400	652A1B334	22	.12	30	43	55	400	652A1C124	22									
1.5	30	43	67	500	652A1A155	22	.39	30	43	55	400	652A1B394	22	.15	30	43	55	400	652A1C154	22									
1.8	30	43	82	600	652A1A185	22	.47	30	43	67	500	652A1B474	22	.18	30	43	67	500	652A1C184	22									
2.0	30	43	82	600	652A1A205	22	.56	30	43	67	500	652A1B564	22	.22	30	43	67	500	652A1C224	22									
2.5	40	55	82	600	652A1A255	22	.68	30	43	82	600	652A1B684	22	.27	30	43	82	600	652A1C274	22									
3.0	40	55	82	600	652A1A305	22	.82	40	55	82	600	652A1B824	22	.33	40	55	82	600	652A1C334	20									
3.5	40	55	82	600	652A1A355	20	1.0	40	55	82	600	652A1B105	20	.39	40	55	82	600	652A1C394	20									
4.0	40	55	1.04	800	652A1A405	20	1.2	40	55	1.04	800	652A1B125	20	.47	40	55	82	600	652A1C474	20									
4.5	40	55	1.04	800	652A1A455	20	1.5	40	55	1.04	800	652A1B155	20	.56	40	55	1.04	800	652A1C564	20									
5.0	40	55	1.24	1.100	652A1A505	20	1.8	40	55	1.04	800	652A1B185	20	.68	40	55	1.24	1.100	652A1C684	20									
6.0	40	55	1.24	1.100	652A1A605	20	2.0	40	55	1.24	1.100	652A1B205	20	.82	40	55	1.24	1.100	652A1C824	20									
8.0	40	55	1.24	1.100	652A1A805	20	2.5	40	55	1.24	1.100	652A1B255	20	1.0	40	55	1.24	1.100	652A1C105	20									
10.0	57	73	1.24	1.100	652A1A106	20	3.0	40	55	1.24	1.100	652A1B305	20	1.2	57	73	1.24	1.100	652A1C125	20									
12.0	57	73	1.24	1.100	652A1A126	20	3.5	57	73	1.24	1.100	652A1B355	20	1.5	57	73	1.24	1.100	652A1C155	20									
15.0	57	73	1.24	1.100	652A1A156	20	4.0	57	73	1.24	1.100	652A1B405	20	1.8	57	73	1.24	1.100	652A1C185	20									
18.0	57	73	1.75	1.600	652A1A186	20	4.5	57	73	1.24	1.100	652A1B455	20	2.0	57	73	1.24	1.100	652A1C205	20									
20.0	57	73	1.75	1.600	652A1A206	20	5.0	57	73	1.24	1.100	652A1B505	20	2.5	57	73	1.75	1.600	652A1C255	20									
							6.0	57	73	1.24	1.100	652A1B605	20	3.0	57	73	1.75	1.600	652A1C305	20									
							8.0	57	73	1.75	1.600	652A1B805	20	3.5	57	73	1.75	1.600	652A1C355	20									



Metallized Mylar* Wrap/Fill

100 VOLT

200 VOLT

MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)
	T ± .05"	W ± .05"	L ± .05"				T ± .05"	W ± .05"	L ± .05"		
For .0010 thru .015 MFD - See Higher Voltages											
.018	.09	.18	.40	23081B183-*	26	.0068	.09	.18	.40	23081C682-*	26
.022	.09	.18	.40	23081B223-	26	.010	.09	.18	.40	23081C103-	26
.033	.09	.18	.40	23081B333-	26	.012	.09	.18	.40	23081C123-	26
.039	.09	.18	.40	23081B393-	26	.015	.09	.18	.40	23081C153-	26
.047	.09	.18	.40	23081B473-	26	.018	.10	.20	.40	23081C183-	26
.056	.09	.18	.40	23081B563-	26	.022	.09	.18	.53	23081C223-	26
.068	.10	.19	.40	23081B683-	26	.027	.09	.18	.53	23081C273-	26
.082	.11	.20	.40	23081B823-	26	.033	.09	.18	.53	23081C333-	26
.10	.09	.18	.53	23081B104-	26	.039	.09	.18	.53	23081C393-	26
.12	.09	.18	.53	23081B124-	26	.047	.09	.18	.53	23081C473-	26
.15	.09	.18	.53	23081B154-	26	.056	.11	.20	.53	23081C563-	26
.18	.09	.18	.53	23081B184-	26	.068	.12	.22	.53	23081C683-	24
.22	.10	.20	.53	23081B224-	26	.082	.14	.23	.53	23081C823-	24
.27	.12	.22	.53	23081B274-	24	.10	.16	.25	.53	23081C104-	24
.33	.14	.23	.53	23081B334-	24	.12	.17	.27	.53	23081C124-	24
.39	.15	.25	.53	23081B394-	24	.15	.20	.29	.53	23081C154-	24
.47	.17	.27	.53	23081B474-	24	.18	.22	.32	.53	23081C184-	24
.56	.19	.28	.53	23081B564-	24	.22	.18	.28	.68	23081C224-	24
.68	.22	.31	.53	23081B684-	24	.27	.20	.29	.68	23081C274-	24
.82	.18	.27	.68	23081B824-	24	.33	.24	.33	.68	23081C334-	24
1.0	.20	.29	.68	23081B105-	24	.39	.21	.30	.78	23081C394-	24
1.2	.22	.32	.68	23081B125-	24	.47	.24	.33	.78	23081C474-	24
1.5	.21	.30	.78	23081B155-	24	.56	.26	.36	.78	23081C564-	24
1.8	.23	.33	.78	23081B185-	24	.68	.29	.39	.78	23081C684-	24
2.0	.25	.34	.78	23081B205-	24	.82	.33	.42	.78	23081C824-	22
3.0	.31	.41	.78	23081B305-	22	1.0	.32	.41	.95	23081C105-	22
4.0	.32	.41	.95	23081B405-	22	1.2	.25	.42	1.17	23081C125-	22
5.0	.26	.42	1.17	23081B505-	22	1.5	.29	.45	1.17	23081C155-	22
6.0	.29	.45	1.17	23081B605-	22	1.8	.32	.49	1.17	23081C185-	22
8.0	.35	.51	1.17	23081B805-	20	2.0	.35	.51	1.17	23081C205-	20
10.0	.46	.63	1.17	23081B106-	20	3.0	.44	.61	1.17	23081C305-	20
12.0	.51	.68	1.17	23081B126-	20	4.0	.44	.61	1.45	23081C405-	20
15.0	.50	.67	1.45	23081B156-	20	5.0	.45	.61	1.70	23081C505-	20
18.0	.56	.72	1.45	23081B186-	20	6.0	.49	.65	1.70	23081C605-	20
20.0	.52	.68	1.70	23081B206-	20	8.0	.53	.70	1.90	23081C805-	20
30.0	.59	.75	1.90	23081B306-	20	10.0	.70	.87	1.90	23081C106-	20
40.0	.72	.88	1.90	23081B406-	20	15.0	.87	1.04	1.90	23081C156-	20
50.0	.79	.95	1.90	23081B506-	20	20.0	1.01	1.18	1.90	23081C206-	20

100 VOLT

Epoxy Case


200 VOLT

MFD	DIMENSIONS			S ±.015"	CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			S ±.015"	CATALOG PART NUMBER	LEAD SIZE (AWG)
	T ±.01"	H (MAX.)	L ±.01"					T ±.01"	H (MAX.)	L ±.01"			
For .0010 thru .018 MFD - See Higher Voltages													
.022	.18	.30	.42	.300	232A1B223-	22	.0082	.18	.30	.42	.300	232A1C822-*	22
.027	.18	.30	.42	.300	232A1B273-	22	.010	.18	.30	.42	.300	232A1C103-	22
.033	.18	.30	.42	.300	232A1B333-	22	.012	.18	.30	.42	.300	232A1C123-	22
.039	.18	.30	.42	.300	232A1B393-	22	.015	.18	.30	.42	.300	232A1C153-	22
.047	.18	.30	.42	.300	232A1B473-	22	.018	.18	.30	.42	.300	232A1C183-	22
.056	.18	.30	.42	.300	232A1B563-	22	.022	.18	.30	.55	.400	232A1C223-	22
.068	.18	.30	.42	.300	232A1B683-	22	.027	.18	.30	.55	.400	232A1C273-	22
.082	.18	.30	.42	.300	232A1B823-	22	.033	.18	.30	.55	.400	232A1C333-	22
.10	.18	.30	.55	.400	232A1B104-	22	.039	.18	.30	.55	.400	232A1C393-	22
.12	.18	.30	.55	.400	232A1B124-	22	.047	.18	.30	.55	.400	232A1C473-	22
.15	.18	.30	.55	.400	232A1B154-	22	.056	.18	.30	.55	.400	232A1C563-	22
.18	.18	.30	.55	.400	232A1B184-	22	.068	.18	.30	.55	.400	232A1C683-	22
.22	.18	.30	.55	.400	232A1B224-	22	.082	.24	.37	.55	.400	232A1C823-	22
.27	.18	.30	.55	.400	232A1B274-	22	.10	.24	.37	.55	.400	232A1C104-	22
.33	.24	.37	.55	.400	232A1B334-	22	.12	.24	.37	.55	.400	232A1C124-	22
.39	.24	.37	.55	.400	232A1B394-	22	.15	.30	.43	.55	.400	232A1C154-	22
.47	.24	.37	.55	.400	232A1B474-	22	.18	.30	.43	.55	.400	232A1C184-	22
.56	.30	.43	.55	.400	232A1B564-	22	.22	.30	.43	.67	.500	232A1C224-	22
.68	.30	.43	.55	.400	232A1B684-	22	.27	.30	.43	.67	.500	232A1C274-	22
.82	.30	.43	.67	.500	232A1B824-	22	.33	.30	.43	.67	.500	232A1C334-	22
1.0	.30	.43	.67	.500	232A1B105-	22	.39	.30	.43	.82	.600	232A1C394-	22
1.2	.30	.43	.67	.500	232A1B125-	22	.47	.30	.43	.82	.600	232A1C474-	22
1.5	.30	.43	.82	.600	232A1B155-	22	.56	.40	.55	.82	.600	232A1C564-	20
1.8	.30	.43	.82	.600	232A1B185-	22	.68	.40	.55	.82	.600	232A1C684-	20
2.0	.40	.55	.82	.600	232A1B205-	20	.82	.40	.55	.82	.600	232A1C824-	20
3.0	.40	.55	.82	.600	232A1B305-	20	1.0	.40	.55	1.04	.800	232A1C105-	20
4.0	.40	.55	1.04	.800	232A1B405-	20	1.2	.40	.55	1.24	1.100	232A1C125-	20
5.0	.40	.55	1.24	1.100	232A1B505-	20	1.5	.40	.55	1.24	1.100	232A1C155-	20
6.0	.40	.55	1.24	1.100	232A1B605-	20	1.8	.40	.55	1.24	1.100	232A1C185-	20
8.0	.57	.73	1.24	1.100	232A1B805-	20	2.0	.57	.73	1.24	1.100	232A1C205-	20
10.0	.57	.73	1.24	1.100	232A1B106-	20	3.0	.57	.73	1.24	1.100	232A1C305-	20
15.0	.57	.73	1.75	1.600	232A1B156-	20	4.0	.57	.73	1.75	1.600	232A1C405-	20
							5.0	.57	.73	1.75	1.600	232A1C505-	20


*Add suffix letter to part number for capacitance tolerance desired: $\pm 20\%$ = None $\pm 10\%$ = K $\pm 5\%$ = J $\pm 2\%$ = G $\pm 1\%$ = F.

**Higher voltages and other case styles (round wrap and fill, rectangular epoxy, round and rectangular metal hermetically sealed) are available.

*Mylar is a registered TM of DuPont

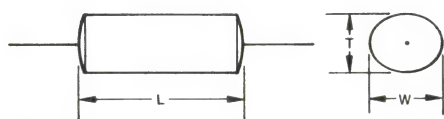

LEAD LENGTH: 2.0" + .50"

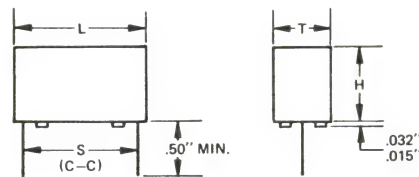

Miniature High Voltage

1000 VOLT

2000 VOLT

3000 VOLT

DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.12	.32	1.0	52081G102-	20	
.002	.16	.36	1.0	52081G202-	20	
.003	.19	.39	1.0	52081G302-	20	
.005	.21	.41	1.0	52081G502-	20	
.01	.33	.53	1.0	52081G103-	20	
.02	.33	.53	1.3	52081G203-	20	
.03	.41	.61	1.3	52081G303-	20	
.05	.43	.63	1.5	52081G503-	20	
.10	.64	.84	1.5	52081G104-	20	
.20	.79	.99	1.8	52081G204-	20	
.30	1.01	1.21	1.8	52081G304-	20	
.50	.75	1.05	3.3	52081G504-	20	
1.0	.93	1.23	4.3	52081G105-	20	

DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.12	.35	1.0	52081J102-	20	
.002	.19	.39	1.0	52081J202-	20	
.003	.25	.45	1.0	52081J302-	20	
.005	.23	.43	1.3	52081J502-	20	
.01	.34	.54	1.3	52081J103-	20	
.02	.40	.60	1.5	52081J203-	20	
.03	.52	.72	1.5	52081J303-	20	
.05	.45	.65	2.3	52081J503-	20	
.10	.55	.75	3.3	52081J104-	20	
.20	.60	.90	4.3	52081J204-	20	
.30	.76	1.06	4.3	52081J304-	20	
.50	1.02	1.32	4.3	52081J504-	18	
1.0	1.50	1.80	4.3	52081J105-	18	

DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.20	.40	1.0	52081L102-	20	
.002	.26	.46	1.0	52081L202-	20	
.003	.33	.53	1.0	52081L302-	20	
.005	.31	.51	1.3	52081L502-	20	
.01	.46	.66	1.3	52081L103-	20	
.02	.55	.75	1.5	52081L203-	20	
.03	.68	.88	1.5	52081L303-	20	
.05	.61	.81	2.3	52081L503-	20	
.10	.68	.88	3.3	52081L104-	20	
.20	.78	1.08	4.3	52081L204-	20	
.30	1.00	1.30	4.3	52081L304-	18	
.50	1.33	1.63	4.3	52081L504-	18	
1.0	1.95	2.25	4.3	52081L105-	18	

5000 VOLT

8000 VOLT

10,000 VOLT

DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.20	.40	1.3	52081N102-	20	
.002	.27	.50	1.3	52081N202-	20	
.003	.35	.55	1.3	52081N302-	20	
.005	.45	.65	1.3	52081N502-	20	
.01	.52	.72	1.5	52081N103-	20	
.02	.67	.87	1.8	52081N203-	20	
.03	.67	.87	2.3	52081N303-	20	
.05	.88	1.08	2.3	52081N503-	20	
.10	.96	1.18	3.3	52081N104-	18	
.20	1.13	1.43	4.3	52081N204-	18	
.30	1.42	1.72	4.3	52081N304-	18	
.50	1.87	2.17	4.3	52081N504-	18	

DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.35	.55	1.8	52081Y102-	20	
.002	.50	.70	1.8	52081Y202-	20	
.003	.60	.80	1.8	52081Y302-	20	
.005	.65	.85	2.0	52081Y502-	20	
.01	.78	.98	2.5	52081Y103-	20	
.02	.78	.98	3.5	52081Y203-	20	
.03	.99	1.19	3.5	52081Y303-	20	
.05	1.02	1.32	4.5	52081Y503-	18	
.10	1.50	1.80	4.5	52081Y104-	18	
.20						
.30						
.50						


DIMENSIONS					CATALOG PART NUMBER	LEAD SIZE (AWG)
MFD	T ± .05"	W ± .05"	L ± .05"			
.001	.40	.60	1.8	52081S102-	20	
.002	.60	.80	1.8	52081S202-	20	
.003	.60	.80	2.0	52081S302-	20	
.005	.66	.86	2.5	52081S502-	20	
.01	.98	1.18	2.5	52081S103-	20	
.02	.98	1.18	3.5	52081S203-	20	
.03	1.23	1.43	3.5	52081S303-	20	
.05	1.29	1.59	4.5	52081S503-	18	
.10	1.87	2.17	4.5	52081S104-	18	
.20						
.30						
.50						

*Add suffix letter to part number for capacitance tolerance desired: $\pm 20\%$ = None $\pm 10\%$ = K $\pm 5\%$ = J $\pm 2\%$ = G $\pm 1\%$ = F.
 **Higher voltages and other case styles (round wrap and fill, rectangular epoxy, round and rectangular metal hermetically sealed) are available.


Mylar*/Foil

250B OVAL												TYPE 250D ROUND																															
Cap. Mfd.		200 WVDC			400 WVDC			600 WVDC			Cap. Mfd.		200 WVDC			400 WVDC			600 WVDC																								
		Dash Number	T	W	L	Dash Number	T	W	L	Dash Number			T	W	L	Dash Number	D	L	Dash Number	D	L	Dash Number	D	L																			
.001	(See Higher Voltages)				(See Higher Voltage)																																						
.0015																																											
.0022																																											
.0033					1E332	.11	.20	.53	1F332	.11	.20	.68	.0033	1C332	.14	.53	1E332	.17	.53	1F332	.17	.68																					
.0047					1E472	.11	.20	.68	1F472	.14	.23	.68	.0047	1C472	.14	.53	1E472	.17	.68	1F472	.20	.68																					
.0068					1E682	.11	.20	.68	1F682	.14	.23	.81	.0068	1C682	.14	.53	1E682	.17	.68	1F682	.20	.81																					
.01		1C103	.11	.20	.53	1E103	.14	.23	.68	1F103	.19	.28	.81	.01	1C103	.17	.53	1E103	.20	.68	1F103	.24	.81																				
.015		1C153	.11	.20	.68	1E153	.14	.23	.81	1F153	.20	.29	.81	.015	1C153	.17	.68	1E153	.20	.81	1F153	.25	.81																				
.022		1C223	.14	.23	.68	1E223	.18	.28	.81	1F223	.25	.34	.90	.022	1C223	.20	.68	1E223	.24	.81	1F223	.31	.90																				
.033		1C333	.16	.26	.68	1E333	.20	.29	.81	1F333	.26	.35	.90	.033	1C333	.22	.68	1E333	.26	.81	1F333	.32	.90																				
.047		1C473	.17	.27	.81	1E473	.26	.35	.90	1F473	.33	.42	.90	.047	1C473	.23	.81	1E473	.32	.90	1F473	.39	.90																				
.068		1C683	.18	.28	.81	1E683	.31	.40	.90	1F683	.39	.48	1.17	.068	1C683	.24	.81	1E683	.37	.90	1F683	.45	1.17																				
.10		1C104	.21	.31	.81	1E104	.33	.42	.90	1F104	.41	.57	1.17	.10	1C104	.26	.81	1E104	.39	.90	1F104	.51	1.17																				
.15		1C154	.26	.35	.90	1E154	.39	.48	1.17	1F154	.45	.62	1.45	.15	1C154	.32	.90	1E154	.45	1.17	1F154	.55	1.45																				
.22		1C224	.26	.43	.90	1E224	.41	.57	1.17	1F224	.47	.63	1.45	.22	1C224	.35	.90	1E224	.51	1.17	1F224	.57	1.45																				
.33		1C334	.28	.45	1.17	1E334	.41	.57	1.45	1F334	.59	.75	1.68	.33	1C334	.38	1.17	1E334	.51	1.45	1F334	.69	1.68																				
.47		1C474	.35	.52	1.17	1E474	.47	.63	1.68	1F474	.66	.82	1.90	.47	1C474	.45	1.17	1E474	.57	1.68	1F474	.76	1.90																				
.68		1C684	.41	.57	1.17	1E684	.54	.70	1.90					.68	1C684	.51	1.17	1E684	.64	1.90																							
1.0		1C105	.41	.57	1.45	1E105	.66	.82	1.90					1.0	1C105	.51	1.45	1E105	.76	1.90																							
1.5		1C155	.54	.70	1.45									1.5	1C155	.64	1.45																										
2.0		1C205	.59	.75	1.68									2.0	1C205	.75	1.68																										
TOLERANCE $\pm .050$												LEAD LENGTH $2 \pm \frac{1}{8}$ INCHES																															

*Mylar is a registered TM of DuPont

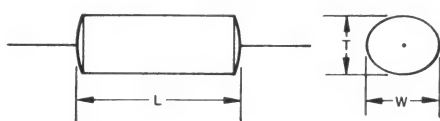

LEAD LENGTH: $2.0'' \pm .50''$

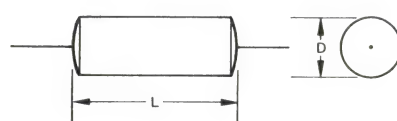

LEAD LENGTH: $2.0'' \pm .50''$

Metallized Polypropylene

135V (RMS)
270V (RMS)

MFD	DIMENSIONS			PNRP *** mA	POWER (MAX) mW	CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			PNRP *** mA	POWER (MAX) mW	CATALOG PART NUMBER	LEAD SIZE (AWG)
	T ± .05"	W ± .05"	L ± .05"						T ± .05"	W ± .05"	L ± .05"				
0010	.09	.18	.40	20	80	910B1C102-	26	0010	.12	.21	.68	20	147	910B1E102-	26
0015	.09	.18	.40	20	80	910B1C152-	26	0015	.12	.21	.68	20	147	910B1E152-	26
0022	.09	.18	.40	20	80	910B1C222-	26	0022	.12	.21	.68	20	147	910B1E222-	26
0033	.09	.18	.40	20	80	910B1C332-	26	0033	.12	.21	.68	20	147	910B1E332-	26
0047	.09	.18	.40	20	80	910B1C472-	26	0047	.12	.21	.68	57	147	910B1E472-	26
0068	.09	.18	.40	55	80	910B1C682-	26	0068	.12	.21	.68	83	147	910B1E682-	26
0082	.09	.18	.40	67	80	910B1C822-	26	0082	.12	.21	.68	100	147	910B1E822-	26
010	.09	.18	.40	81	80	910B1C103-	26	010	.12	.21	.68	122	147	910B1E103-	26
015	.09	.18	.53	52	98	910B1C153-	26	015	.16	.25	.68	183	193	910B1C153-	24
022	.09	.18	.53	77	98	910B1C223-	26	022	.20	.29	.68	270	245	910B1E223-	24
033	.12	.21	.53	115	126	910B1C333-	26	033	.17	.26	.95	204	255	910B1E333-	24
047	.15	.24	.53	164	157	910B1C473-	24	047	.21	.30	.95	288	316	910B1E473-	24
068	.18	.28	.53	237	190	910B1C683-	24	068	.26	.35	.95	417	400	910B1E683-	24
082	.20	.30	.53	286	214	910B1C823-	24	082	.28	.38	.95	501	436	910B1E823-	24
.10	.23	.32	.53	349	253	910B1C104-	24	.10	.32	.41	.95	602	511	910B1E104-	22
.15	.22	.32	.68	333	273	910B1C154-	24	.15	.28	.45	1.17	612	598	910B1E154-	22
.22	.23	.33	.78	358	310	910B1C224-	24	.22	.36	.52	1.17	897	756	910B1E224-	20
.33	.30	.39	.78	537	424	910B1C334-	24	.33	.46	.62	1.17	1344	1009	910B1E334-	20
.47	.32	.41	.95	650	511	910B1C474-	22	.47	.47	.64	1.45	1437	1191	910B1E474-	20
.68	.29	.45	1.17	616	598	910B1C684-	22	.68	.46	.63	1.90	1386	1363	910B1E684-	20
.82	.32	.49	1.17	742	686	910B1C824-	22	.82	.52	.69	1.90	1674	1566	910B1E824-	20
1.0	.36	.53	1.17	906	780	910B1C105-	20	1.0	.58	.75	1.90	2040	1781	910B1E105-	20
2.0	.47	.64	1.45	1395	1161	910B1C205-	20	2.0	.86	1.03	1.90	4080	2931	910B1E205-	20
5.0	.64	.81	1.90	2400	1968	910B1C505-	20								
10.0	.94	1.11	1.90	4800	3305	910B1C106-	20								

Polypropylene & Foil


135V (RMS)
270V (RMS)

MFD	DIMENSIONS			PNRP *** AMP	POWER (MAX) mW	CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			PNRP *** AMP	POWER (MAX) mW	CATALOG PART NUMBER	LEAD SIZE (AWG)
	T ± .05"	W ± .05"	L ± .05"						T ± .05"	W ± .05"	L ± .05"				
0010	.09	.18	.63	2	97	950B1C102-	26	0010	.12	.21	.68	4	147	950B1E102-	26
0015	.09	.18	.63	2	97	950B1C152-	26	0015	.12	.21	.68	4	147	950B1E152-	26
0022	.09	.18	.63	2	97	950B1C222-	26	0022	.12	.21	.68	4	147	950B1E222-	26
0033	.09	.18	.63	2	97	950B1C332-	26	0033	.12	.21	.68	11	147	950B1E332-	26
0047	.09	.18	.63	2	97	950B1C472-	26	0047	.12	.21	.68	16	147	950B1E472-	26
0068	.09	.19	.63	7	97	950B1C682-	26	0068	.13	.23	.68	23	158	950B1E682-	24
0082	.10	.20	.63	8	97	950B1C822-	26	0082	.15	.24	.68	28	181	950B1E822-	24
010	.11	.21	.63	10	97	950B1C103-	26	010	.17	.26	.68	34	206	950B1E103-	24
015	.14	.24	.63	15	126	950B1C153-	24	015	.22	.31	.68	52	273	950B1E153-	24
022	.18	.28	.63	22	167	950B1C223-	24	022	.17	.27	.95	36	255	950B1E223-	24
033	.17	.27	.78	33	214	950B1C333-	24	033	.22	.32	.95	54	332	950B1E333-	24
047	.21	.31	.78	28	209	950B1C473-	24	047	.27	.37	.95	76	418	950B1E473-	24
068	.21	.31	.88	41	287	950B1C683-	24	068	.23	.39	1.17	72	475	950B1E683-	24
082	.24	.34	.88	35	280	950B1C823-	24	082	.26	.42	1.17	87	535	950B1E823-	24
.10	.27	.37	.88	43	310	950B1C104-	24	.10	.29	.46	1.17	106	620	950B1E104-	22
.15	.29	.39	1.05	65	407	950B1C154-	22	.15	.38	.54	1.17	159	804	950B1E154-	20
.22	.26	.43	1.27	75	510	950B1C224-	22	.22	.47	.64	1.17	234	1077	950B1E224-	20
.33	.33	.50	1.27	78	620	950B1C334-	22	.33	.50	.67	1.45	260	1281	950B1E334-	20
.47	.41	.58	1.27	111	780	950B1C474-	20	.47	.48	.65	2.0	244	1430	950B1E474-	20
.68	.39	.56	1.80	160	1009	950B1C684-	20	.68	.60	.77	2.0	354	1855	950B1E684-	20
.82	.43	.60	1.80	192	1147	950B1C824-	20	.82	.67	.83	2.0	426	2084	950B1E824-	20
1.0	.49	.66	1.80	180	1221	950B1C105-	20	1.0	.75	.91	2.0	520	2408	950B1E105-	20
2.0	.66	.83	2.0	244	1744	950B1C205-	20	2.0	1.09	1.26	2.0	1041	4060	950B1E205-	20
5.0	1.09	1.26	2.0	611	3402	950B1C505-	20								

*Add suffix letter to part number for capacitance tolerance desired: $\pm 20\%$ = None $\pm 10\%$ = K $\pm 5\%$ = J $\pm 2\%$ = G $\pm 1\%$ = F.

**Higher voltages and other case styles (round wrap and fill, rectangular epoxy, round and rectangular metal hermetically sealed) are available.

***Peak Non-Repetitive Pulse

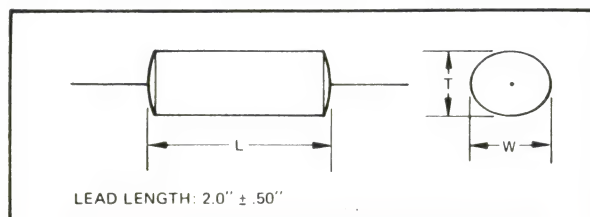

Metallized Polysulfone

100 VOLT 200 VOLT

MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)
	T ± .05"	W ± .05"	L ± .05"				T ± .05"	W ± .05"	L ± .05"		
.0010	.09	.18	.40	81081B102*	26	.0010	.09	.18	.40	81081C102*	26
.0012	.09	.18	.40	81081B122*	26	.0012	.09	.18	.40	81081C122*	26
.0015	.09	.18	.40	81081B152*	26	.0015	.09	.18	.40	81081C152*	26
.0018	.09	.18	.40	81081B182*	26	.0018	.09	.18	.40	81081C182*	26
.0022	.09	.18	.40	81081B222*	26	.0022	.09	.18	.40	81081C222*	26
.0027	.09	.18	.40	81081B272*	26	.0027	.09	.18	.40	81081C272*	26
.0033	.09	.18	.40	81081B332*	26	.0033	.09	.18	.40	81081C332*	26
.0039	.09	.18	.40	81081B392*	26	.0039	.09	.18	.40	81081C392*	26
.0047	.09	.18	.40	81081B472*	26	.0047	.09	.18	.40	81081C472*	26
.0056	.09	.18	.40	81081B562*	26	.0056	.09	.18	.40	81081C562*	26
.0068	.09	.18	.40	81081B682*	26	.0068	.09	.18	.40	81081C682*	26
.0082	.09	.18	.40	81081B822*	26	.0082	.09	.18	.40	81081C822*	26
.010	.09	.18	.40	81081B103	26	.010	.09	.18	.40	81081C103	26
.012	.09	.18	.40	81081B123	26	.012	.09	.18	.40	81081C123	26
.015	.09	.18	.40	81081B153	26	.015	.09	.18	.40	81081C153	24
.018	.09	.18	.40	81081B183	26	.018	.09	.18	.40	81081C183	24
.022	.09	.18	.40	81081B223	26	.022	.09	.18	.40	81081C223	24
.027	.09	.18	.40	81081B273	26	.027	.09	.18	.40	81081C273	24
.033	.09	.18	.40	81081B333	26	.033	.10	.20	.53	81081C333	24
.039	.10	.20	.40	81081B393	26	.039	.11	.21	.53	81081C393	24
.047	.12	.21	.40	81081B473	26	.047	.12	.22	.53	81081C473	24
.056	.18	.29	.53	81081B563	26	.056	.14	.24	.53	81081C563	24
.068	.18	.29	.53	81081B683	26	.068	.16	.26	.53	81081C683	24
.082	.10	.19	.53	81081B823	26	.082	.18	.27	.53	81081C823	24
.12	.11	.20	.53	81081B104	26	.10	.21	.30	.53	81081C104	24
.15	.12	.22	.53	81081B124	24	.12	.24	.32	.53	81081C124	24
.18	.14	.24	.53	81081B154	24	.15	.20	.29	.68	81081C154	24
.22	.16	.25	.53	81081B184	24	.18	.22	.32	.68	81081C184	24
.27	.18	.27	.53	81081B224	24	.22	.21	.30	.78	81081C224	22
.33	.20	.30	.53	81081B274	24	.27	.24	.33	.78	81081C274	22
.39	.22	.32	.53	81081B334	24	.33	.27	.36	.78	81081C334	22
.47	.24	.34	.53	81081B394	24	.47	.32	.42	.78	81081C474	22
.56	.26	.36	.53	81081B474	24	.56	.31	.41	.95	81081C564	22
.68	.22	.32	.78	81081B684	24	.68	.25	.42	1.17	81081C684	22
.82	.25	.34	.78	81081B824	22	.82	.28	.45	1.17	81081C824	22
1.0	.28	.38	.78	81081B105	22	1.0	.32	.49	1.17	81081C105	20
1.2	.32	.41	.78	81081B125	22	1.2	.32	.49	1.17	81081C125	20
1.5	.40	.50	.95	81081B155	22	1.5	.41	.58	1.17	81081C155	20
1.8	.31	.40	.78	81081B185	22	1.8	.46	.63	1.17	81081C185	20
2.0	.36	.45	.78	81081B205	22	2.0	.54	.71	1.30	81081C205	20
2.5	.30	.47	1.17	81081B255	20	2.5	.48	.64	1.45	81081C255	20
3.0	.34	.51	1.17	81081B305	20	3.0	.47	.63	1.70	81081C305	20
3.5	.37	.54	1.17	81081B355	20	3.5	.47	.63	1.90	81081C355	20
4.0	.41	.57	1.17	81081B405	20	4.0	.50	.67	1.90	81081C405	20
4.5	.43	.60	1.17	81081B455	20	4.5	.54	.71	1.90	81081C455	20
5.0	.46	.63	1.17	81081B505	20	5.0	.57	.74	1.90	81081C505	20
6.0	.46	.61	1.45	81081B605	20	6.0	.64	.80	1.90	81081C605	20
8.0	.46	.63	1.70	81081B805	20	8.0	.75	.92	1.90	81081C805	20
10.0	.48	.64	1.90	81081B106	20	10.0	.85	1.01	1.90	81081C106	20
12.0	.53	.70	1.90	81081B126	20						
15.0	.60	.77	1.90	81081B156	20						
20.0	.71	.88	1.90	81081B206	20						


Combination Film

100 VOLT 200 VOLT

MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)	MFD	DIMENSIONS			CATALOG PART NUMBER	LEAD SIZE (AWG)	
	T ± .05"	W ± .05"	L ± .05"				T ± .05"	W ± .05"	L ± .05"			
.0010	.09	.18	.40	73081B102*	26	.0010	.09	.18	.40	73081C102*	26	
.0012	.09	.18	.40	73081B122*	26	.0012	.09	.18	.40	73081C122*	26	
.0015	.09	.18	.40	73081B152*	26	.0015	.09	.18	.40	73081C152*	26	
.0018	.09	.18	.40	73081B182*	26	.0018	.09	.18	.40	73081C182*	26	
.0022	.09	.18	.40	73081B222*	26	.0022	.09	.18	.40	73081C222*	26	
.0027	.09	.18	.40	73081B272*	26	.0027	.09	.18	.40	73081C272*	26	
.0033	.09	.18	.40	73081B332*	26	.0033	.09	.18	.40	73081C332*	26	
.0039	.09	.18	.40	73081B392*	26	.0039	.09	.18	.40	73081C392*	26	
.0047	.09	.18	.40	73081B472*	26	.0047	.09	.18	.40	73081C472*	26	
.0056	.09	.18	.40	73081B562*	26	.0056	.09	.18	.40	73081C562*	26	
.0068	.09	.18	.40	73081B682*	26	.0068	.09	.18	.40	73081C682*	26	
.0082	.09	.18	.40	73081B822*	26	.0082	.09	.18	.40	73081C822*	26	
.010	.09	.18	.40	73081B103	26	.010	.09	.18	.40	73081C103	26	
.012	.09	.18	.40	73081B123	26	.012	.09	.18	.40	73081C123	26	
.015	.09	.18	.40	73081B153	26	.015	.09	.18	.40	73081C153	26	
.018	.09	.18	.40	73081B183	26	.018	.09	.18	.40	73081C183	26	
.022	.09	.18	.40	73081B223	26	.022	.11	.20	.40	73081C223	26	
.027	.09	.18	.40	73081B273	26	.027	.09	.18	.40	73081C273	26	
.033	.09	.18	.40	73081B333	26	.033	.09	.18	.40	73081C333	26	
.039	.09	.19	.40	73081B393	26	.039	.10	.20	.53	73081C393	26	
.047	.10	.20	.40	73081B473	26	.047	.11	.21	.53	73081C473	26	
.056	.11	.21	.40	73081B563	26	.056	.13	.22	.53	73081C563	24	
.068	.13	.23	.40	73081B683	24	.068	.15	.24	.53	73081C683	24	
.082	.11	.20	.53	73081B823	24	.082	.16	.26	.53	73081C823	24	
.10	.13	.23	.53	73081B104	24	.10	.18	.28	.53	73081C104	24	
.12	.14	.24	.53	73081B124	24	.12	.21	.30	.53	73081C124	24	
.15	.16	.26	.53	73081B154	24	.15	.23	.33	.53	73081C154	24	
.18	.18	.28	.53	73081B184	24	.18	.21	.30	.68	73081C184	24	
.22	.22	.31	.53	73081B224	24	.22	.23	.33	.68	73081C224	24	
.27	.24	.34	.53	73081B274	24	.27	.24	.33	.78	73081C274	24	
.33	.27	.37	.53	73081B334	24	.33	.27	.36	.78	73081C334	24	
.39	.30	.40	.53	73081B394	22	.39	.30	.40	.78	73081C394	24	
.47	.34	.44	.53	73081B474	22	.47	.33	.43	.78	73081C474	22	
.56	.36	.46	.53	73081B564	22	.56	.37	.47	.78	73081C564	22	
.68	.25	.34	.78	73081B684	22	.68	.25	.42	1.17	73081C684	22	
.82	.28	.38	.78	73081B824	22	.82	.28	.45	1.17	73081C824	22	
1.0	.31	.41	.78	73081B105	22	1.0	.32	.49	1.17	73081C105	22	
1.2	.35	.45	.78	73081B125	22	1.2	.36	.52	1.17	73081C125	20	
1.5	.42	.52	.95	73081B155	22	1.5	.41	.58	1.17	73081C155	20	
1.8	.39	.48	.95	73081B185	22	1.8	.48	.62	1.17	73081C185	20	
2.0	.46	.56	1.17	73081B205	22	2.0	.46	.65	1.17	73081C205	20	
2.5	.33	.50	.78	73081B255	22	2.5	.35	.47	.64	1.45	73081C255	20
3.0	.37	.53	.78	73081B305	20	3.0	.37	.49	.63	1.70	73081C305	20
3.5	.41	.57	.78	73081B355	20	3.5	.41	.53	.67	1.90	73081C355	20
4.0	.44	.62	.78	73081B405	20	4.0	.44	.56	.66	1.90	73081C405	20
4.5	.47	.64	.78	73081B455	20	4.5	.47	.59	.70	1.90	73081C455	20
5.0	.50	.67	.78	73081B505	20	5.0	.50	.67	.73	1.90	73081C505	20
6.0	.56	.73	.78	73081B605	20	6.0	.60	.74	.78	1.90	73081C605	20
8.0	.67	.84	1.45	73081B805	20	8.0	.74	.90	.78	1.90	73081C805	20
10.0	.81	.97	1.70	73081B106	20	10.0	.84	1.00	.78	1.90	73081C106	20
12.0	.91	.107	1.90	73081B126	20							
15.0	.95	.111	1.90	73081B156	20							
18.0	.95	.111	1.90	73081B186	20							
20.0	.95	.111	1.90	73081B206	20							


*Add suffix letter to part number for capacitance tolerance desired: $\pm 20\%$ = None $\pm 10\%$ = K $\pm 5\%$ = J $\pm 2\%$ = G $\pm 1\%$ = F.

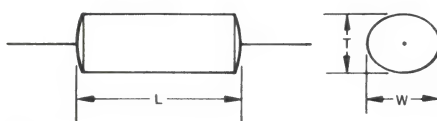**Higher voltages and other case styles (round wrap and fill, rectangular epoxy, round and rectangular metal hermetically sealed) are available.



LEAD LENGTH: 2.0" + .50"

Aluminum Foil Wound

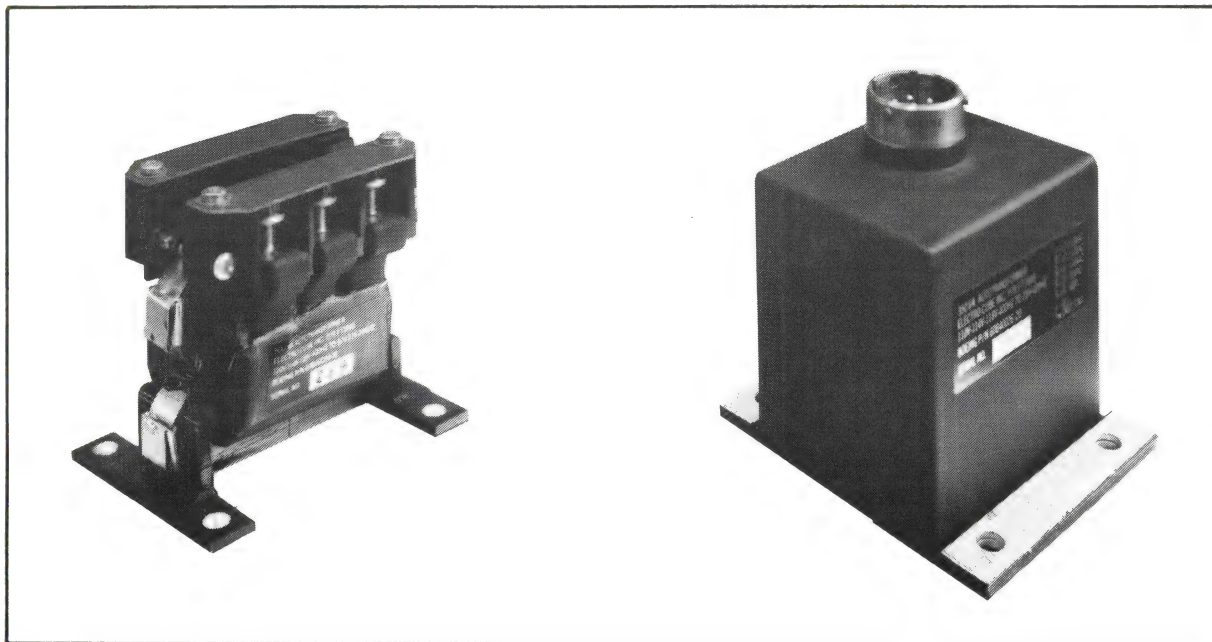

Electro Cube aluminum foil wound transformers are available in the standard models listed on the reverse and also to customer requirements as isolation or auto transformers for frequencies from 25 cycles into the kilocycle range. Units may be single or multi-phase. Open frame, shell enclosure and hermetically sealed configurations can be furnished.

Advantages of these foil wound transformers over conventional wire wound units include:

- higher operating efficiency
- reduced weight
- improved thermal efficiency
- higher temperature operation
- improved regulation
- internal losses
- improved volume efficiency

The ability of a transformer to dissipate heat affects its maximum rating. Electro Cube foil wound coils have the ability to dissipate large amount of heat because there is a direct metallic path to each end of the coil from any point within the coil. Special end treatment of the coil including attachment to a heat sink, can make possible significantly reduced operating temperatures.

Wire wound coils, by comparison, are more difficult to cool. As a result of a limited heat path a lower coefficient of heat transfer and increased resistance due to heat and vice versa, the heat is greatest in that part of the coil least capable of dissipating it. Heat generated by conductors deep within the coil must pass through many thermal barriers of the insulation between the wires.

In addition to thermal efficiency, the materials in Electro Cube foil transformers permit use with higher operating temperatures than are possible with wire coils with equivalent

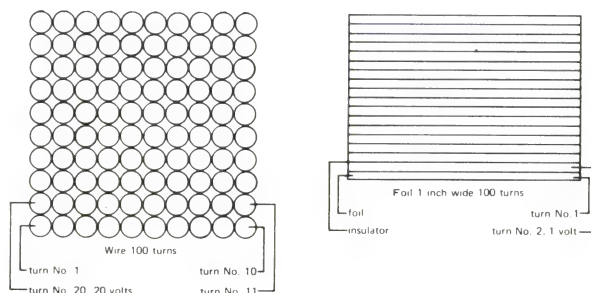


Figure 1. Typical coil sections with 100 volts excitation.

lent insulation ratings. This also contributes to reduced weight and volume.

Figure 1 shows the relative difference in volume required for a 100 turn wire coil and an equivalent foil coil, and the relative use of space for insulation and conductors. It also shows voltage stress and insulation requirements for the two configurations. At 1 volt per turn there would be 20 volts between the 20th and first turn of the wire coil. When the top layer is finished, the last turn may lay against one of the first, resulting in a voltage difference of up to 100 volts. The foil coil never has more than 1 volt between any two conductors, or a 100 to 1 advantage over the wire coil, in this example.


The physical arrangement of the foil windings promotes a lower leakage reactance or power loss in the transformer, which contributes to efficiency and regulation. Together with the lower I^2R loss of the windings, this allows the use of fewer circular mils of conductor area to meet required efficiency and regulation requirements.




UL Recognized



RC Networks

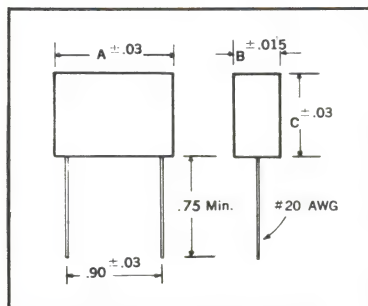


Capacity MFD	Resistance Ohms ±10%	Rated Voltage	Peak Pulse Voltage	Dimensions A in.	B in.	C in.	Electro Cube Part Number
0.5 ± 10%	22	200 VDC	300 V	1.00	.38	.63	RG 1780 — 1
0.5 ± 10%	33		300 V	1.00	.38	.63	RG 1780 — 2
0.5 ± 10%	47	OR	300 V	1.00	.38	.63	RG 1780 — 3
1.0 ± 10%	22		300 V	1.00	.50	.75	RG 1781 — 1
1.0 ± 10%	33	125 VAC	300 V	1.00	.50	.75	RG 1781 — 2
1.0 ± 10%	47		300 V	1.00	.50	.75	RG 1781 — 3
0.1 ± 20%	22	600 VDC	900 V	1.00	.38	.63	RG 1782 — 1
0.1 ± 20%	33		900 V	1.00	.38	.63	RG 1782 — 2
0.1 ± 20%	47	OR	900 V	1.00	.38	.63	RG 1782 — 3
0.25 ± 20%	22		900 V	1.00	.50	.75	RG 1783 — 1
0.25 ± 20%	33	250 VAC	900 V	1.00	.50	.75	RG 1783 — 2
0.25 ± 20%	47		900 V	1.00	.50	.75	RG 1783 — 3
0.5 ± 10%	22	250 VAC	900 V	1.25	.58	.83	RG 1784 — 1
0.5 ± 10%	33		900 V	1.25	.58	.83	RG 1784 — 2
0.5 ± 10%	47		900 V	1.25	.58	.83	RG 1784 — 3

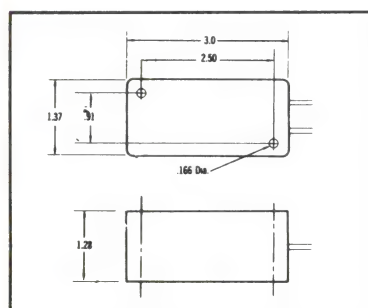


Part #	Resistance Ohms	Tolerance %	Power Watts	Capacity MFD	Tolerance %	VDC Volts	VAC Volts	Thyrector Part #	Lead Length Inches	Circuit #
RG 1676-1	100	10	10	1.0	10	1000	480	N/A	24	1
-148	100	10	10	1.0	10	1000	480	N/A	48	1
-2	100	10	10	.5	10	1000	480	N/A	24	1
-3	10	10	2	1.0	10	600	250	N/A	25	1
-10	220	10	5	2.0	10	600	250	N/A	25	1
-12	220	10	2	.5	10	1000	480	N/A	24	1
-13	220	10	1	.47	10	1000	480	N/A	24	1
-1848	220	10	5	.47	10	1000	480	N/A	48	1
-19	220	10	2	1.0	10	400	120	N/A	24	1
-20	100	10	2	2.0	20	600	250	N/A	18	1
-21	10	10	5	1.0	10	1000	480	N/A	24	1

Ballasts

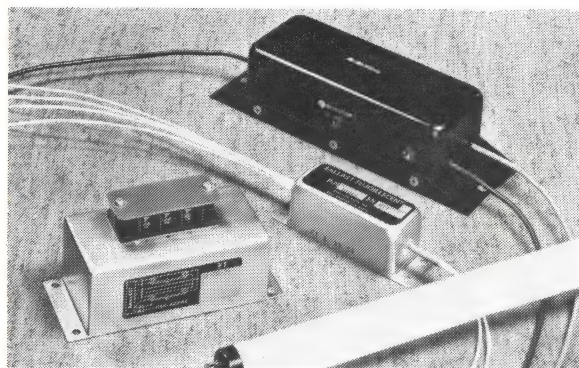


Electrocube has designed and produced a wide variety of fluorescent ballasts for airborne and ground systems installation, as well as selected commercial applications where size and weight are considerations. These lightweight units are offered in 60 Hz and 400 Hz versions, for operation on DC and to 15 KHz, for fixed or dimmable circuits. Either leading or lagging power factors may be specified, and burnout protection can be provided against tube rectification. For cold weather applications, ballasts have been designed for normal operation in temperatures to -10°C .

Filters

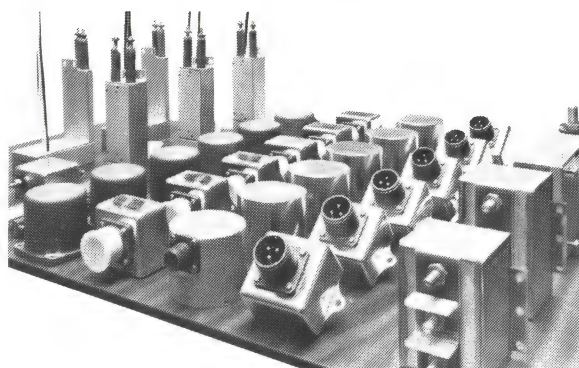


Electrocube has developed literally thousands of EMI filters, to meet military, aerospace and commercial applications. Versions have been designed with current carrying capacities from 0.1 to 500 amps, voltages to 5000 VDC and 600 VAC, and for DC to 1000 Hz and intermittent or continuous duty. Single and multi-circuit configurations are also offered, including L, Pi (also with feed-through capacitors) and T. Models include low pass, high reject, noise, interstage and line, screen room, and heavy duty industrial filters.

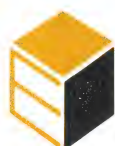

electrocube

1710 South Del Mar Avenue
San Gabriel, California 91776
Telephone: (213) 573-3300
TWX: 910-589-1609

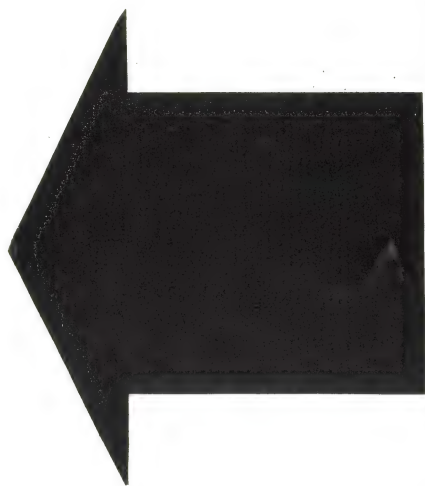**Remove
this
ELECTROCUBE
PRODUCT
SUMMARY
for future
reference!**



**(If someone
beat you to it,
circle the reader
service number
below and we'll
send you one.)**

ELECTROCUBE
1710 SOUTH DEL MAR AVE.
SAN GABRIEL, CA 91776
(213) 573-3300

For more information, Circle No 73

EDN APRIL 5, 1979



CAHNERS PUBLISHING COMPANY

The Cahners Magazine Division publishes the following specialized business magazines and directories:

- Appliance Manufacturer
- Brick & Clay Record
- Building Design & Construction
- Building Supply News
- Ceramic Industry
- Ceramic Data Book
- Construction Equipment
- Design News
- Design News Reference Editions
- EDN
- Electronic Business
- Foodservice Distributor Salesman
- Foodservice Equipment Specialist
- Institutions/VFM
- Mini-Micro Systems
- Modern Materials Handling
- Modern Railroads
- Package Engineering
- Plastics World
- Professional Builder/Apartment Business
- Purchasing
- Service World International
- Specifying Engineer
- Traffic Management
- U.S. Industrial Directory

The Cahners Exposition Group is the largest producer, operator and manager of trade and consumer shows in the United States... with 26 shows, 2,000,000 square feet of exhibition space and total annual attendance of over two million.

Cahners Publishing Company


221 Columbus Avenue
Boston, MA 02116
(617) 536-7780

**FREE! ALL NEW
NEWARK ELECTRONICS
CATALOG 104**


There's no other catalog like it...and there's no other distributor that gives you the kind of service Newark does.

- 756 pages!
- Over 100,000 items!
- 190 top brand name lines!

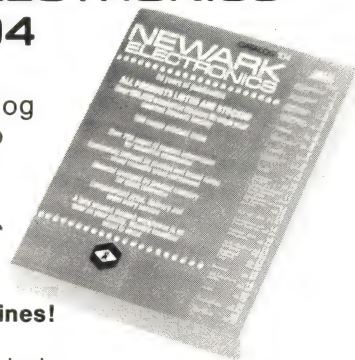Many new lines.
All products listed are stocked.



FEATURING BOURNS POTENTIOMETERS

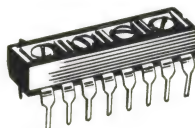

Full line of precision potentiometers, including the multi-function DIP trimmer—saves you manufacturing cost, board space, design time; improves circuit performance! Compatible with auto-insertion equipment, too. Stocked regionally for quick delivery.

Write or phone today for your personal copy!



NEWARK ELECTRONICS

500 N. PULASKI • CHICAGO, IL 60624
PHONE (312) 638-4411 • TELEX 25:3218

For more information, Circle No 120

Design Entry Blank

\$25 Cash Award for all entries selected by editors. An additional \$50 U.S. Savings Bond Award for winning design each issue, determined by vote of readers. Additional \$1000 Bond Award for annual Grand Prize Design, selected among semimonthly winners by vote of editors.

To: Design Ideas Editor
EDN
Cahners Publishing Co.
221 Columbus Ave., Boston, MA 02116

I hereby submit my entry for
EDN's DESIGN IDEAS PROGRAM.

Name _____

Title _____ Phone _____

Company _____

Division (if any) _____

Street _____

City _____ State _____ Zip _____

Design Title _____

Print full name (no initials) and home address on lines below for mailing of your bond if chosen monthly issue winner. Also, please include your Social Security number.

Social Security No. _____

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co. unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed _____

Date _____

Your vote determines this issue's winner. All designs published win \$25 cash. All issue winners receive an additional \$50 U.S. Savings Bond and become eligible for the annual \$1000 U.S. Savings Bond Grand Prize.

Vote now, by circling the appropriate number on the reader inquiry card.

Submit your own design, too. Mail entries to Design Ideas Editor, EDN, 221 Columbus Ave., Boston, MA 02116.

Flip flop provides long delay

Haresh Shah

Bunting Steri System, Bridgeport, CT


You can extend the delay of a D flip flop with the 3-transistor circuit shown in the figure. The unijunction transistor (Q_1) remains OFF until the voltage across C_1 exceeds its threshold voltage. This hold-off time can be determined from

$$T = R_1 C_1 \ln(1/(1 - (V_T + 0.6)/V_{DD}))$$

and ranges from a few milliseconds to a few minutes.

EDN

To Vote For This Design, Circle No 454

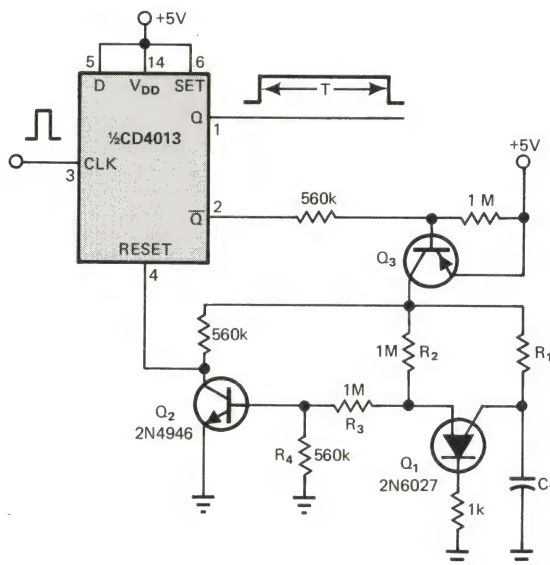

Delay circuitry stretches an output pulse to a length dependent on the charge rate of C_1 through R_1 . For the component values shown, the pulse period T is $0.8R_1C_1$.

JOB SHOPPING?


Check EDN's Career Opportunities

EDN: Everything Designers Need


MORE PULL in a smaller package?




Check these curves.

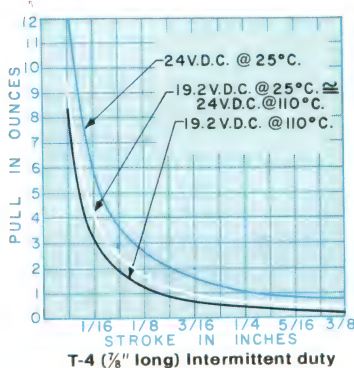

T-4 (1/8" long) Intermittent duty

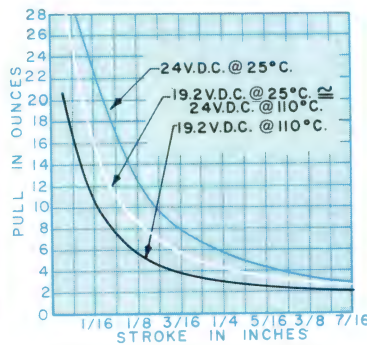

T-8 (1 1/8" long) Continuous Duty

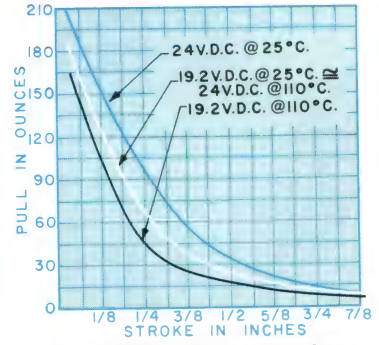

T-12 (1 1/2" long) Intermittent Duty


Ounce-for ounce, inch-for-inch Guardian Tubular Solenoids pack more power... because our tubular designs assure total magnetic field enclosure and result in efficient, powerful operation. More efficient than other DC solenoids. They give you more power in less space, plus U/L and CSA recognition.

Easy to design-in. Easy to install. By design.

Guardian Tubulars work in any position. Close tolerance between plunger and bobbin means no possibility of double seating. So they work in your product just the way you want them to work.

Mount them directly into panel by inserting threaded bushing thru installation hole and tightening nut on lock washer. Or, mount with standard bracket.

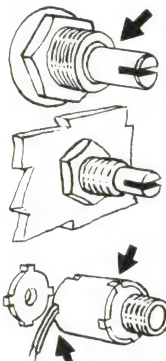Either way, Guardian Tubulars install without damage to the solenoid. Look how the



notched tube-steel shell mates with notched end plate. Result? A stronger assembly that takes more torque when installing...with no chance of damage. The leads emerge thru a notch in the steel shell, so they *will* not, *can* not be sheared by rotation during installation.

Once you put a Guardian Tubular in your product...forget it. Typical mechanical life is 20 million. That's probably longer than your product's life expectancy...due primarily to the unique Valox® 420 molded bobbin.

Variations and specials? Guardian's got 'em. Any DC voltage from 6 to 240. Push type or pull type operation. Return springs, silencers, termination variations, special mountings... you name it and we'll deliver it with the high quality craftsmanship and low prices that have made Guardian Number 1 in Solenoids—and that keeps us here on top.

Let the Guardian Angel reveal all the pull charts and curves in full size. Send for your free copy of our 72 page catalog.



This mark indicates recognition under the component program of Underwriters Laboratories, Inc.



GUARDIAN®


See us at Booth # 1310
Design Engineering Show

GUARDIAN ELECTRIC MANUFACTURING CO. 1550 West Carroll Avenue—Chicago, Illinois 60607 • 312/243-1100

For more information, Circle No 74




1.

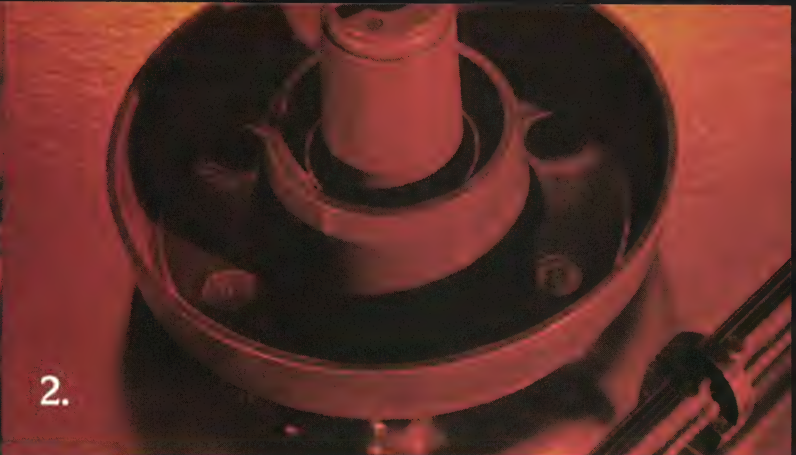

2.

5 ways to make a better product— and Ryton® does them all.

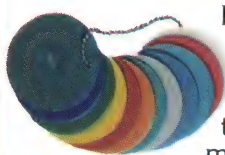1. **Keep it heat-resistant**—Ryton® polyphenylene sulfide resins have UL 94 V-O and 5V flammability ratings, without additives.
2. **Keep it stable**—Ryton engineering plastics have excellent dimensional stability—the only thermoplastic molding compounds with a UL Temperature Index as high as 240°C. (and documented performance in temperatures to 260°C.).
3. **Keep it arc-resistant**—Where high voltages are a requirement, Ryton resins with high arc resistance and low tracking rate are available.
4. **Keep it chemical resistant**—Ryton has no known solvents under 200°C.
5. **Keep it all**—There is no waste to Ryton. Simply recycle your sprues and runners. You save many dollars in raw materials costs. Dollars you can reinvest in R&D or further product refinements.



Ryton engineering plastics are available in 5 standard colors and an unlimited number of custom variations. And, as always, Ryton technicians stand ready to help you make the most out of your Ryton applications. For quick action from the Ryton Sales Engineer nearest you call our Phillips Engineering Plastics Office toll free ... 800 231-3630 (In Texas 800 392-3716).


Ryton® engineering plastics perform.

Phillips also produces K-Resin® butadiene styrene polymers and Marlex® polyolefin resins. Call toll free 800 231-1212 (In Texas 800 392-2078).


PHILLIPS CHEMICAL COMPANY
A DIVISION OF PHILLIPS PETROLEUM COMPANY



For more information, Circle No 75

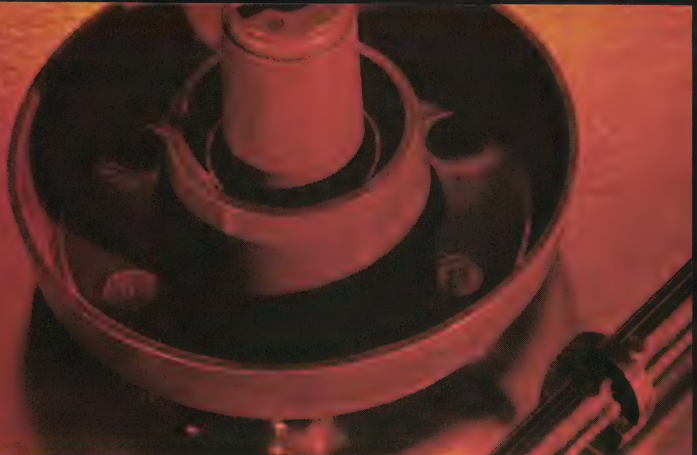


3.

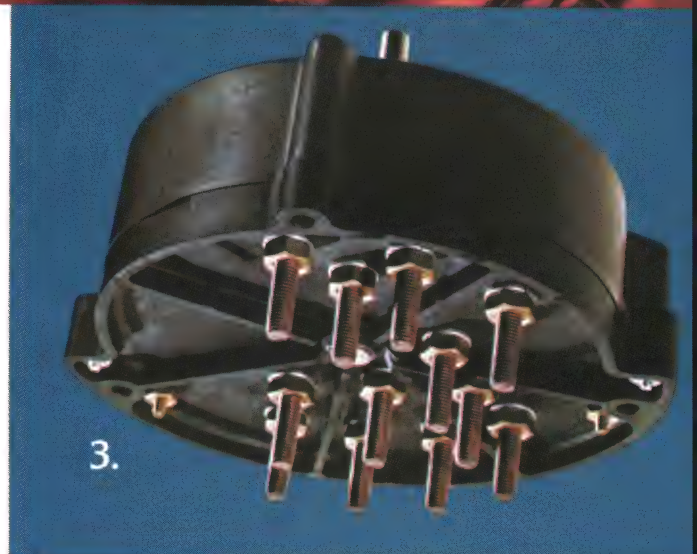

4.



5.

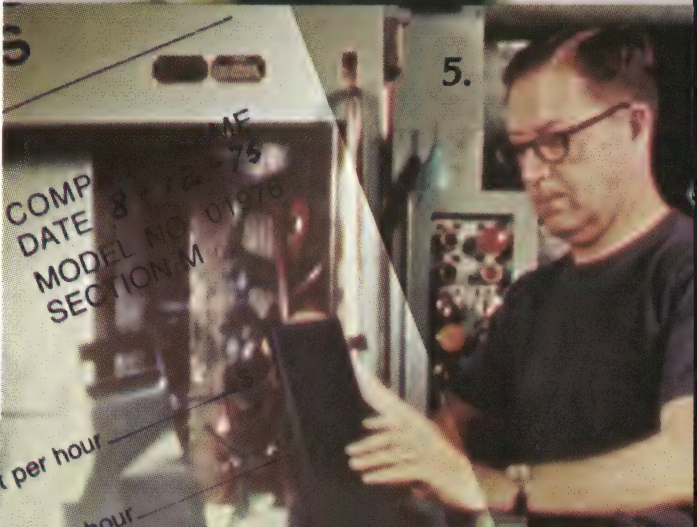

Feature Products

Electronic load handles 300A, features no-guess digital readout

Power supplies are getting bigger and bigger, and whether you build them or buy them, you must also be able to test them. Lectra-Load II meets this need; it's programmable, dissipates up to 1250W, specs a 0 to 300A constant-current capability and a 0.01 to 100 Ω constant-resistance range, and accepts inputs ranging from 1.5 to 50V dc.

Unlike its competitors, the instrument sports a 4-digit readout and a *true* short-circuit test, controlled by a pushbutton. Its flexibility is further enhanced by a built-in pulse generator that can simulate dynamic loads. And for direct, constant sampling of these tests, the unit provides a front-panel 1-mV/A scope output.

Varied uses

If you're not familiar with electronic loads, you might not appreciate the Lectra-Load II's full capabilities. So consider the following potential applications of the device:

- In its constant-current mode, you can connect it in series with a constant-voltage dc power supply to form a variable constant-current source.
- It can test capacitor banks and batteries by acting as a constant-current discharge; it also tests dc voltage regulators.



Programmable from front-panel controls or remotely via resistance or voltage inputs (IEEE-488 capability is optional), the portable Lectra-Load II operates over 0 to 40°C. Its dynamic loading capability permits switching between two current levels, and its built-in pulse generator provides both amplitude and duty-factor adjustment over a 1- to 1000-Hz range.

- Because its voltage range extends down to 1.5V, it can test ECL power supplies.
- In its constant-resistance mode, the wide range frees you from the need to stock power rheostats among your test components.
- By using its built-in pulse generator, you can create many useful tests. For example, with duty factor set at 100%, you can program the unit to exercise a power supply at three levels—no load plus two preprogrammed values.

Human engineering

To make the Lectra-Load II easier to operate, designers engineered its front

panel with well-spaced vernier controls and smooth push-push mode and range switches. They also added a built-in bale that tilts the instrument to the desired viewing angle.

Inside the electronic load's 5×10×16-in. case, all-copper heat sinks and bus bars attest to quality construction. Service problems are further minimized by the use of plug-in-type pc boards and cables, socket-mounted heat-dissipating elements and hermetically sealed semiconductors. Two 4-in. cooling fans eliminate hot spots. \$1100; available in August.

Power/Mate Corp, 514 S River St, Hackensack, NJ 07601. Phone (201) 343-6294. Circle No 455

Centigrid II: Never before a relay this sensitive at this size



We told you that our Centigrid® was the ultimate sub-miniature relay — and it is. Centigrid II is not a replacement, but a companion developed for applications that demand ultra-small size *plus* ultra-high sensitivity. Centigrid II dissipates 65% less power than the .150 grid relay, and 75% less than the 1/2 crystal can. And it still features .100" grid spaced pinout for optimum pc board layouts and occupies only .14 sq. in. of board space.

Like the TO-5, the Centigrid II makes an ideal subminiature RF switch, providing high isolation and low insertion loss up through UHF frequencies. And the low coil power requirement means extended battery life for hand-held transceivers.

Centigrid II meets all requirements of MIL-R-39016, and is available with internal diode suppression. Call or write us today for complete specification data.

 **TELEDYNE RELAYS**

12525 Daphne Avenue, Hawthorne, California 90250 • (213) 777-0077


U.K. Sales Office: Heathrow House, Bath Rd. MX, TW5 9QQ • 01-897-2501

European Hqtrs.: Abraham Lincoln Strasse 38-42 • 62 Wiesbaden, W. Germany • 6121-700811

For more information, Circle No 76


New Products

COMPUTER-SYSTEM SUBASSEMBLIES

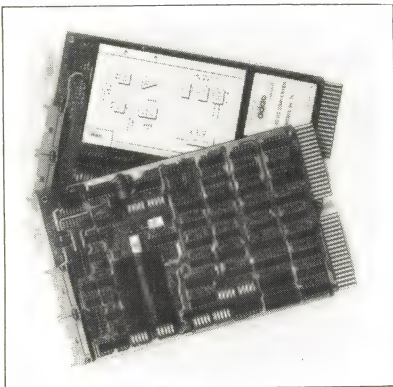

I/O CARDS. These two dual-width boards furnish I/O capabilities to DEC LSI-11, LSI-11/2 and PDP-11/03 μ Cs, as well as the manufacturer's Series 1000 and 2000 systems. One of the boards, the Model 1750 asynchronous serial-line I/O card, contains sockets for 512 \times 16 bits of PROM. Each of this dual-port board's I/O channels performs serial to parallel (and vice versa) conversion in 5-, 6-, 7- or 8-bit format.

The other board, the Model 1014 A/D converter, features 14-bit resolution and a 10-kHz throughput rate. This unit allows random- or sequential-mode access, vector addressing, and selection of full-scale ranges and register addressing. You can increase its 16-channel capacity to 64 channels with a Model 1012-EX expander board. Model 1750, \$395; Model 1014, \$1195. Delivery, 30 days ARO. **ADAC Corp.**, 70 Tower Office Park, Woburn, MA 01801. Phone (617) 935-6668. **Circle No 166**

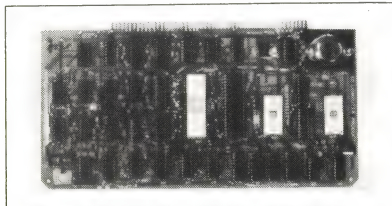


VIDEO-DISPLAY BOARD. The Z80 μ P-based VDB-8024 offers 80-character \times 24-line display (7 \times 10-dot character matrix), composite video output (in addition to separate TTL-level sync and video outputs), 2k bytes of RAM and an I/O-mapped interface. Display features include full cursor control, forward and reverse scrolling, variable-speed display rate and enhancements such as blinking

and underlining. \$499 (\$349, kit). **SD Systems**, Box 28810, Dallas, TX 75228. Phone (214) 271-4667. **Circle No 167**

ANALOG I/O BOARDS. Compatible with PDP-11 Unibus systems, the DT1711 Series of 1-card analog-I/O and input systems offers four hex-height models. Standard features of units in this family include a channel capacity of up to 64 analog inputs and a choice of high- or low-level signal capability with 12-bit A/D conversion. These boards can also perform logic-controlled 3-axis point plotting via high-current outputs from two 12-bit DACs and an on-board Z-axis pulse generator. From \$1240. **Data Translation Inc.**, 4 Strathmore Rd, Natick, MA 01760. Phone (617) 655-5300. **Circle No 168**

PRINTER INTERFACE. Containing two separate interfaces, the PRI card handles either dot-matrix or daisy-wheel printers. One interface utilizes the "Centronics parallel" convention for dot-matrix operation, the other employs the "daisy-wheel parallel" convention and includes ribbon-lift and ribbon-lowering circuitry. \$195. **Cromemco Inc.**, 280 Bernardo Ave, Mt View, CA 94043. Phone (415) 964-7400. **Circle No 169**

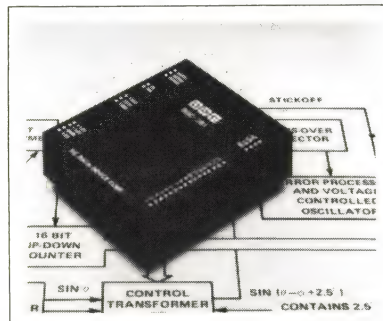

S/D CONVERTER MODULE. Featuring internal transformer isolation, the SDC-361 synchro-to-digital converter module operates over a 47-to-1000-Hz range. This 2-speed (1:36 ratio) converter provides accuracy to within 20 seconds of angle and accommodates all standard synchro and resolver input formats. Tracking rates are 1000°/sec for 400 Hz and 250°/sec for 60 Hz. \$695. **ILC Data Device Corp.**, Airport International Plaza, Bohemia, NY 11716. Phone (516) 567-5600. **Circle No 170**



Cahners Publishing Company


The Cahners Magazine Division publishes the following business magazines and directories:

- Appliance Manufacturer
- Brick & Clay Record
- Building Design & Construction
- Building Supply News
- Ceramic Industry
- Ceramic Data Book
- Construction Equipment
- Design News
- Design News Directories
- EDN
- Electronic Business
- Foodservice Distributor Salesman
- Foodservice Equipment Specialist
- Institutions
- Mini-Micro Systems
- Modern Materials Handling
- Modern Railroads
- Package Engineering
- Plastics World
- Professional Builder/ Apartment Business
- Purchasing
- Service World International
- Specifying Engineer
- Traffic Management
- U.S. Industrial Directory

The Cahners Exposition Group is the largest producer, operator and manager of trade and consumer shows in the United States...with 28 shows, 2,000,000 square feet of exhibition space and total annual attendance of over two million.

Cahners Publishing Company
221 Columbus Avenue
Boston, MA 02116
(617) 536-7780

New Products

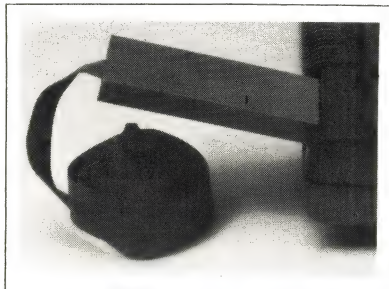

PRINTER INTERFACE. Plugging directly into the back of a TRS-80 computer keyboard, the Print Module eliminates the need for an expansion interface when driving printers such as Centronics (P1, 779, 703), Telpar and Axiom models. This parallel line-printer interface is compatible with line-print commands in Level II BASIC. \$99.95. **American Micro Products**, 6550 Tarnef, MS 11, Houston, TX

77074. Phone (713) 777-2759.

Circle No 171

UNIBUS I/O BOARD. Acting as a general-purpose interface, the DUAL I/O board provides the logic for program-controlled parallel transfers of 16-bit data between two external devices and a Unibus system. The quad-height unit is the hardware and software equivalent of two DR11-C interfaces. \$900. **Able Computer Technology Inc.**, Box 18162, Irvine, CA 92714. Phone (714) 979-7030.

Circle No 172

Micro upgrades its *new* ELECTRONIC READ/WRITE TAPE SYSTEM.


MICRO COMMUNICATIONS has been delivering its new ELECTRONIC READ/WRITE Tape Transport System to a number of customers in such application areas as Program Loading, Data Logging, Point of Sale and Personal / Small Computers.

Since introduction, Micro has upgraded the capability of the system to include such features as a 4800 baud transfer rate and *double density* (3200 fci). Mainly based upon the size and weight of the system (less than 6" in length; less than 6 ounces in weight), the system is a natural for microprocessor integration.

The READ/WRITE System includes such features as: TTL and CMOS compatability, START/STOP TIME of 30/40 milliseconds, a block construction of *die cast aluminum*, a *read/write* speed of 3 ips and a fast forward speed of 6 ips and a data capacity of 120K bytes (using a 50' wafer cartridge).

In OEM quantities, the READ/WRITE System is \$69.00. Delivery is two weeks ARO. Micro supplies mechanical transports at \$25.00 per unit in 1000 unit quantities. Data sheets and system documentation are available upon request.

Call or write today for details.

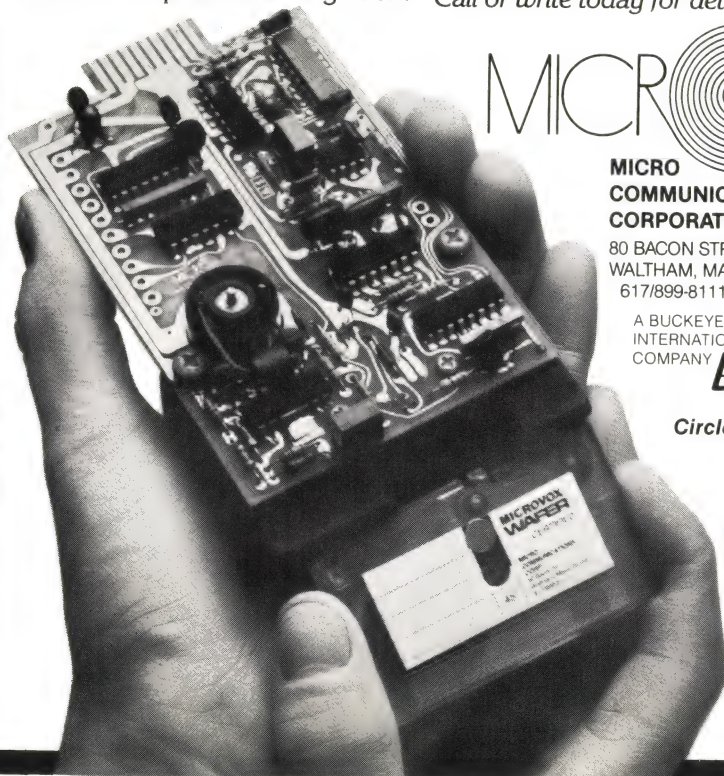

MICRO COMMUNICATIONS CORPORATION


80 BACON STREET
WALTHAM, MASS. 02154
617/899-8111

A BUCKEYE
INTERNATIONAL
COMPANY



Circle No 78

DAC BOARD FOR LSI-11. Residing on a half-quad-size board, the ST-LSI-DA4 4-channel DAC interfaces with LSI-11 μ Cs. Jumper-selectable addressing allows you to cascade any number of boards. These 12-bit units offer 4- μ sec settling time, $\pm 1/2$ -LSB max nonlinearity and a choice of four full-scale output-voltage ranges: 0 to +5, 0 to +10, -5 to +5 and -10 to +10V. \$535; \$475 without dc/dc converter. **Datel Systems Inc.**, 11 Cabot Blvd, Mansfield, MA 02048. Phone (617) 828-8000. **Circle No 173**

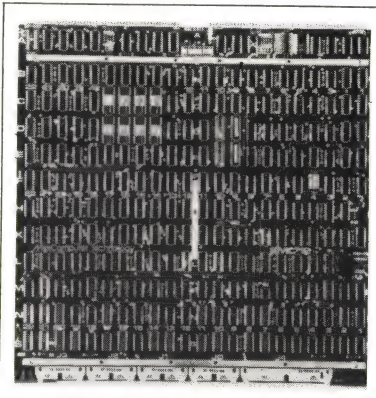


DISC CONTROLLER. With a transfer rate up to 1.2M bytes/sec, the SM12 interfaces Data General minicomputers to as many as four storage-module disc drives in any mix of capacities up to 1200M bytes. Two computers with these controllers can share dual-ported drives. Dual, full-sector RAM buffers allow single-command contiguous-sector transfers up to 64k words. \$3580. Delivery, 45 days ARO. **Minicomputer Technology**, 2470 Embarcadero Way, Palo Alto, CA 94303. Phone (415) 321-7400.

Circle No 174

GROWING UP TOGETHER

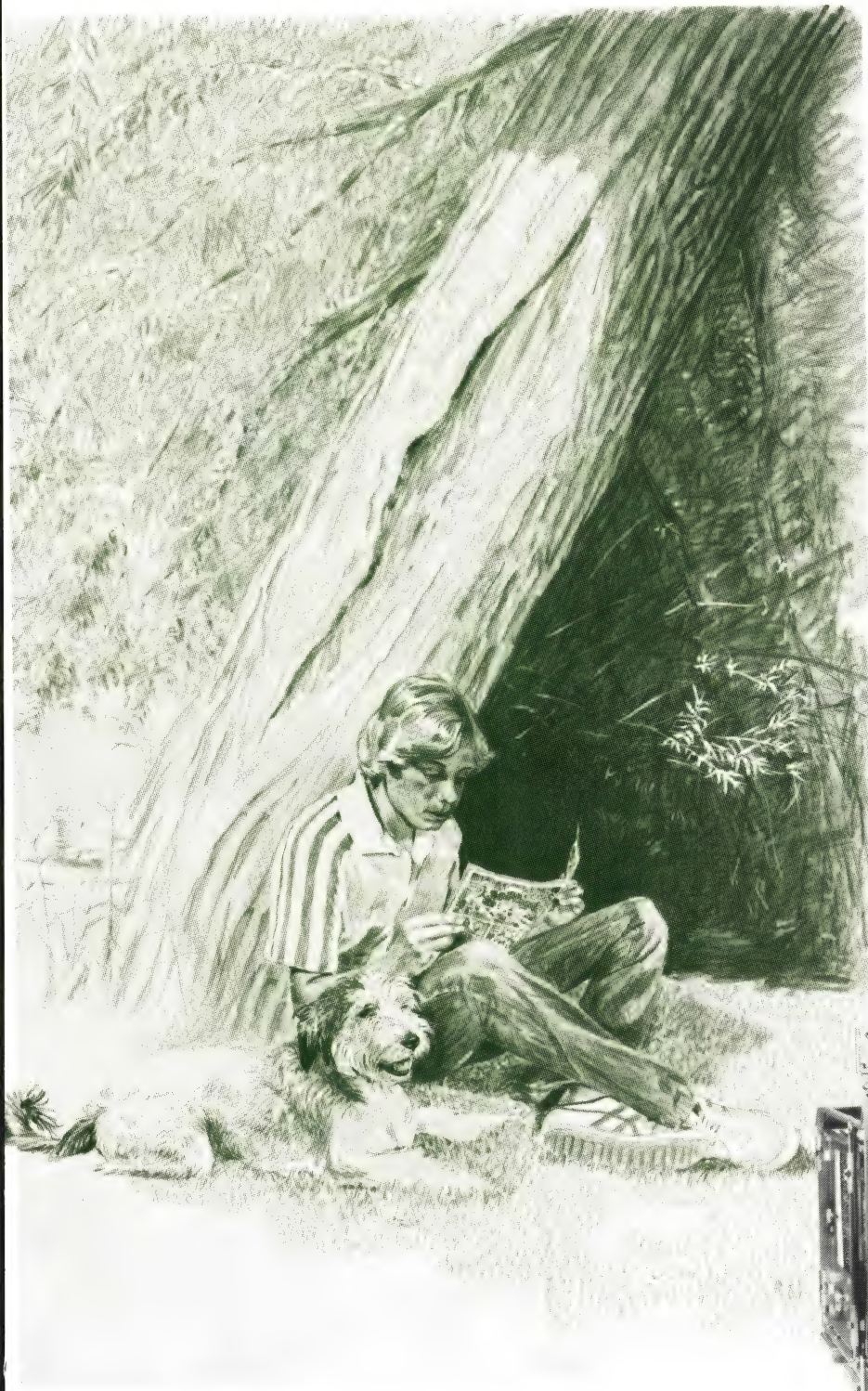... there's no more certain path to understanding



The years we've spent growing up with the alphanumeric terminal industry—years of working closely with the designers and makers of the final product—have given us the insight and understanding of the industry's needs that could have come no other way.


This relationship has helped Motorola grow to be a leading supplier of CRT display modules to the industry. Leading not only in terms of sales, but also in terms of quality, reliability and technology; leading in terms of performance vs. price.

When you're considering the single most important hardware item in your terminal design, you'll want the supplier that can put all those years of experience, understanding and leadership to your best benefit.

Call the sales office in your area:

Sunnyvale, California (408) 744-1277
Tustin, California (714) 838-5621
West Chicago, Illinois (312) 231-4400
Dallas, Texas (214) 233-2006
Salem, New Hampshire (603) 898-5921
Shrewsbury, New Jersey (201) 544-9541
Baltimore, Maryland (301) 821-0062

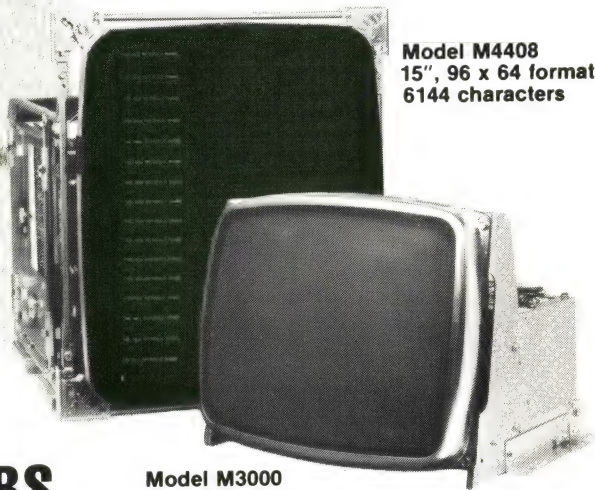*Overseas, ask for International Sales Manager, West Chicago, Illinois (312) 231-4400
TWX: 910-230-3117*



Model M4408
15", 96 x 64 format
6144 characters

Model M3000
12", 80 x 24 format
1920 characters


BENEFIT FROM EXPERIENCE ... OURS



MOTOROLA INC.

Display Systems 1155 Harvester Rd., West Chicago, IL 60185

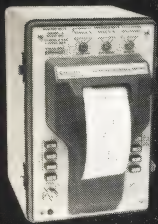Now—Analyze, Monitor, & Record Disturbances on both the AC Line and 2 DC Levels simultaneously



Fantastic new version of the original Series 606 micro-programmed line-disturbance monitor, the Series 616 senses impulses, sags/surges, and slow-average variations in one AC and two DC levels, simultaneously. Internal processor prints out all data on each type of disturbance, with time signature; also summaries, daily and on demand. Performs all tests required to verify static and transient behavior of power-supply systems, especially UPS, at the factory and on-site.

...or on 3 AC Lines plus Frequency simultaneously




The proven, industry-standard way to analyze power-line behavior now adds over/under frequency monitoring to its 1, 2, or 3-phase voltage monitoring — Series 606 with Option 101... a must for power-line-critical installations!

Come see the complete Dranetz Line of Power System Instruments at PowerCon 6

We'll be on the exhibit floor, and participating in the technical program, too!

or send for full data

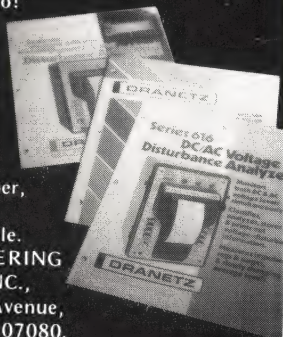Use the inquiry number, call, or write for comprehensive data file. DRANETZ ENGINEERING LABORATORIES, INC., 2385 South Clinton Avenue, South Plainfield, N.J. 07080. (201) 755-7080.




DRANETZ


For more information, Circle No 113

New Products

COMPUTERS & PERIPHERALS

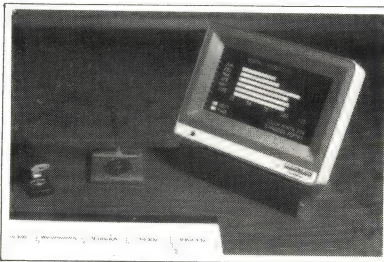


TOUCH PANEL. Communicating at 300 to 19,200 baud over an RS-232 interface, Vuepoint serves as a direct replacement for a CRT terminal. Only 2.5 in. thick, the unit's 12-line×40-character panel accepts touch input. Wall-mount, rack-mount, printer and keyboard options configure the panel for a variety of applications. \$3500. **General Digital Corp.**, 700 Burnside Ave, East Hartford, CT 06108. Phone (203) 289-7391. **Circle No 211**

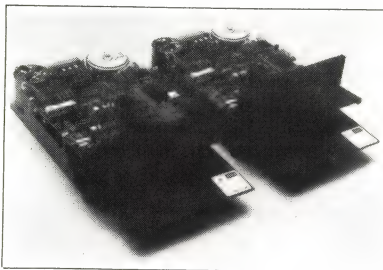

MINI-FLOPPY DRIVE. Offering 40-track capacity in a small package, Model 6106 5.25-in. floppy drive furnishes track-to-track access time of 12 msec. The drive operates in both FM and MFM recording modes, providing up to 250k bytes (unformatted) storage on one side of a diskette. \$450; \$225 (500). **BASF Systems**, Crosby Dr, Bedford, MA 01730. Phone (617) 271-4064. **Circle No 212**

MODULAR TERMINALS. By combining the separately packaged display screens, keyboards, printers, magnetic card readers and memory subsystems included in BMT Series electronic terminals, you can tailor them to specific applications. Each terminal furnishes its own intelligence, eliminating the need for separate terminal controllers. From \$2500. **Burroughs Corp.**, Box 418, Detroit, MI 48232. Phone (313) 972-7267. **Circle No 213**

FLOPPY-DISC EXECUTIVE. Suitable for most popular 6800 systems, INDEX (interrupt-driven executive) services the console and I/O devices by interrupt requests rather than polling. You can write your own utility commands and driver routines to expand the versatility of the operating system. The software comes on two mini diskettes. \$99.95. **Percom Data Company**, 318 Barnes, Garland, TX 75042. Phone (214) 272-3421. **Circle No 214**

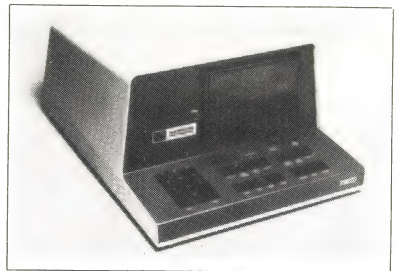


COMMUNICATIONS DISC. Designed to efficiently replace paper-tape, cassette or magnetic-tape units, Model AJ 460 diskette system operates at higher transmission rates than those devices and furnishes over 204k of storage. You can record data in binary, which allows the system to be transparent to control characters, or in packed mode for maximum storage efficiency. \$1995. **Anderson Jacobson Inc.**, 521 Charcot Ave, San Jose, CA 95131. Phone (408) 263-8520. **Circle No 215**

MODEM MULTIPLIER. MM-4 is designed to replace multiple modems interfaced to individual terminals in polled communications systems. The multiplier supports four terminals and each terminal can be located up to 50 ft from the unit. The units can also be linked to support more than four terminals. \$450. **Wizard Associates**, 1019 S Noel, Wheeling, IL 60090. Phone (312) 541-6803. **Circle No 216**

CRT TERMINAL. Offering switch-selectable software compatibility with four leading terminals, Act-V provides a separate numeric keypad, and software-selectable screen formats of 80×24 or 48×39. \$865. **Micro-Term Inc.**, 1314 Hanley Industrial Ct, St Louis, MO 63144. Phone (314) 968-8151. **Circle No 217**

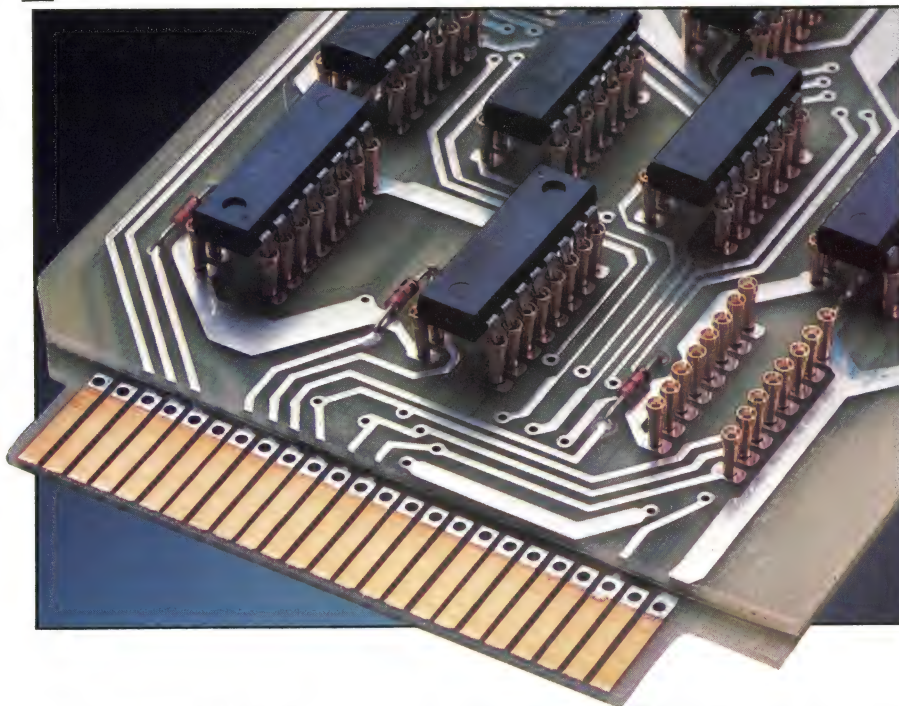Expanding the parameters of press-fit technology



New press-fit I.C. socket offers lower cost, higher density and cooler operation.


Low Cost

Using a conventional precision screw machine contact, press-fit into the circuit board, this new socket is a major improvement over time-proven packaging methods. This innovative conversion to press-fit techniques greatly increases cost effectiveness by reducing need for external wiring and the elimination of soldering.

Characteristics of the new socket allow us to selectively plate a portion of the tails with significant savings in gold plating.

High Density—Greater Design Freedom
The new socket stands rather high on the board (.190")—but with good reason.

The .062 pad now allows a trace to be run between contact holes for greater circuit density. This should allow a drop from a 3-wrap tail to a 2-wrap—or no tail at all. The 2-wrap offers about the same spacing as a conventional low profile socket with 3-wrap tail. Used in an Elfab Multi-Pac® system, you can get up to six planes of circuitry on a modular daughter board or backpanel. You eliminate the need for

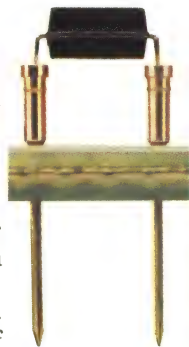

complex and expensive multilayered boards.

Cooler Operation

Since the socket stands up off the board, air flow aids in heat dissipation giving you much cooler operating temperatures. This is especially significant with higher pin count IC's.

Oriented Contact — both clip and contact tail.

Clip is so oriented that the four contact tines are in perfect alignment with the IC lead. Each tail is oriented square and parallel with the others to accept a mating connector when desired. An Elfab exclusive!

For additional information contact:




ELFAB

The Leader in Press-fit Technology

P. O. Box 34555 • Dallas, Texas 75234 • 214-233-3033

For more information, Circle No 80

IN A WORLD OF NOISE...

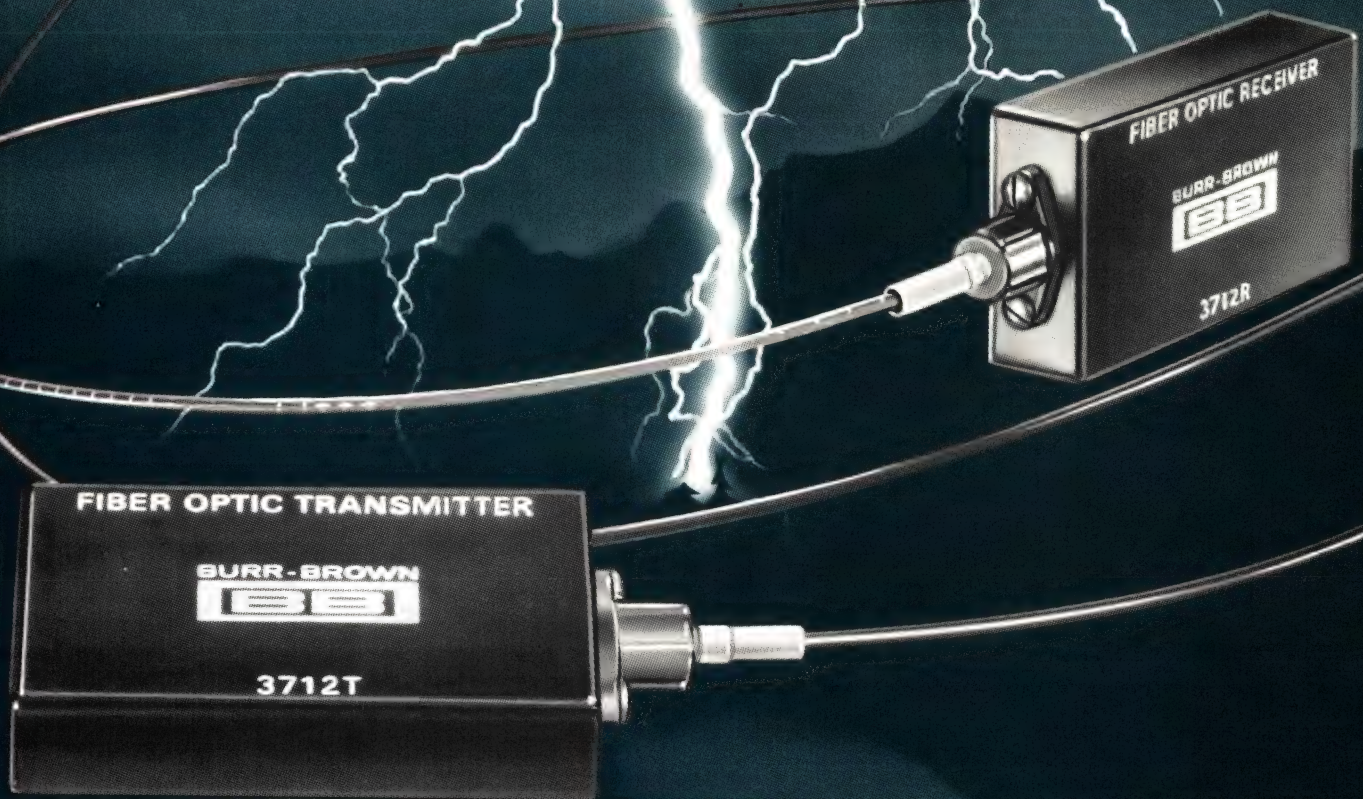

* 100's, cable not included.

HERE'S A \$99* LINK TO ISOLATED, ERROR-FREE TTL DATA TRANSMISSION

This fiber optic data link offers the lowest cost alternative to achieve total electrical isolation and noise immunity. 3712T transmitter (TTL In/Light Out) and 3712R receiver (Light In/TTL Out), coupled by fiber optic cable, form a simplex data link. You're assured of reliable, error-free 20k bit data transmission through hostile, noisy environments.

Maximum transmission length depends on the type of fiber optic cable you select. Lengths exceed 1.5km with 10^{-9} BER when low loss 200 μ m silica fiber is used. Units use the popular AMP single fiber connector.

DC coupled, 3712R is designed for low noise, low drift and maximum sensitivity. It requires only 5nW optical power and ± 15 VDC (± 20 mA). 3712T requires +5VDC (+60mA max) and launches 3.5 μ W of optical power into a 40mil, 0.53 N.A. fiber.

Metal packages (1.6" x 3.0" x 0.6") increase noise immunity and are suitable for PC board or connector mounting. Link operating temperature is 0 to +70°C.


Burr-Brown, Box 11400, Tucson, Arizona 85734.
(602) 746-1111.



Putting Technology
To Work For You

AMSTERDAM, BOSTON, CHICAGO, LONDON, LOS ANGELES, NEW YORK, PARIS, SAN FRANCISCO, STUTTGART, TOKYO, TUCSON, ZURICH

For more information, Circle No 81

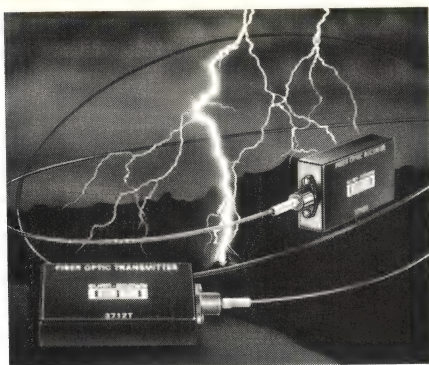

New Products

SPECIAL FIBER OPTIC DATA LINK OFFER: A Complete Link Just \$99.00

3712T Transmitter and 3712R Receiver

20-foot fiber optic cable
(with connectors)

Two electrical connectors

A \$166.70 value ...
you save \$67.70

Get everything you need
(except +5VDC and ± 15 VDC
supply) to test the exciting
isolation/transmission benefits
of fiber optics!

To take advantage of
this special offer specify
Burr-Brown
Part No.
FODL-K1

\$99 price effective until
May 31, 1979


Offer good in USA and Canada only




P.O. Box 11400
Tucson, AZ 85734
(602)746-1111

For more information, Circle No 81

EDN APRIL 5, 1979

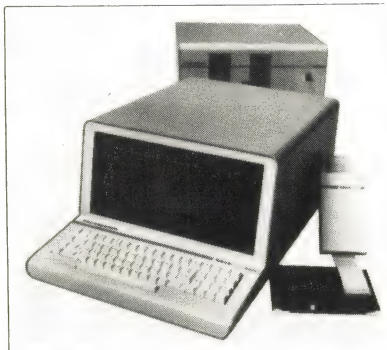

DEVELOPMENT SYSTEM. Providing the necessary tools for developing 8080-, 8085-, 6800-, 6802- or Z80-based products, the AMDS system furnishes real-time, in-circuit emulation up to 5 MHz. A 48-channel logic analyzer provides three hardware-break registers and a 256-state trace buffer. Software includes a screen-based editor and macro assembler. \$16,500, with choice of CPU. **Future-data Computer Corp.**, 11205 S La Cienega Blvd, Los Angeles, CA 90045. Phone (213) 641-7700. **Circle No 218**

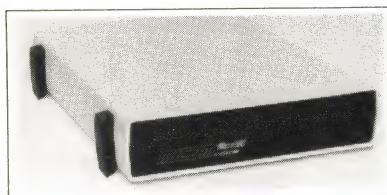

ERROR CONTROLLER. Eliminating the risk of undetected transmission errors by providing retransmission on error, Micro500 suits data communications over dial-up or dedicated lines at speeds up to 9600 bps. The unit also furnishes asynchronous to synchronous conversion. \$895. Delivery, 45 days ARO. **Micom Systems Inc.**, 9551 Irondale Ave, Chatsworth, CA 91311. Phone (213) 882-6890. **Circle No 219**

PRINT MECHANISM. Model AP-20M provides up to 20 columns of nonimpact thermal printing. The 5x7 alphanumeric characters output at 2.5 lines per sec, and the unit's fixed-head design requires only one moving part—the paper-roll drive. \$275. **Gulton Industries Inc.**, Gulton Industrial Park, East Greenwich, RI 02818. Phone (401) 884-6800. **Circle No 220**

MULTIUSER MICRO. Based on an 8085A computer, Microstar adds a floppy-disc operating system with interactive BASIC, multiuser and multitasking capability and a report writer to furnish complete software support. File access methods supported include direct, sequential and index sequential (ISAM). **Micro V Corp.**, 17777 S E Main St, Irvine, CA 92714. Phone (714) 957-1517.

Circle No 221




μ C SYSTEM. Configured around the Z80 μ P and a 12-in. Mindless terminal, System B utilizes both the manufacturer's disc operating system and CP/M. The system incorporates a 48k dynamic-RAM board; a Flashwriter video board displays 80x24 characters in an 8x10 matrix. \$4750. **Vector Graphic Inc.**, 31364 Via Colinas, Westlake Village, CA 91361. Phone (213) 991-2302. **Circle No 222**

JOB SHOPPING?

Check EDN's Career Opportunities

EDN: Everything Designers Need

FLEXIBILITY

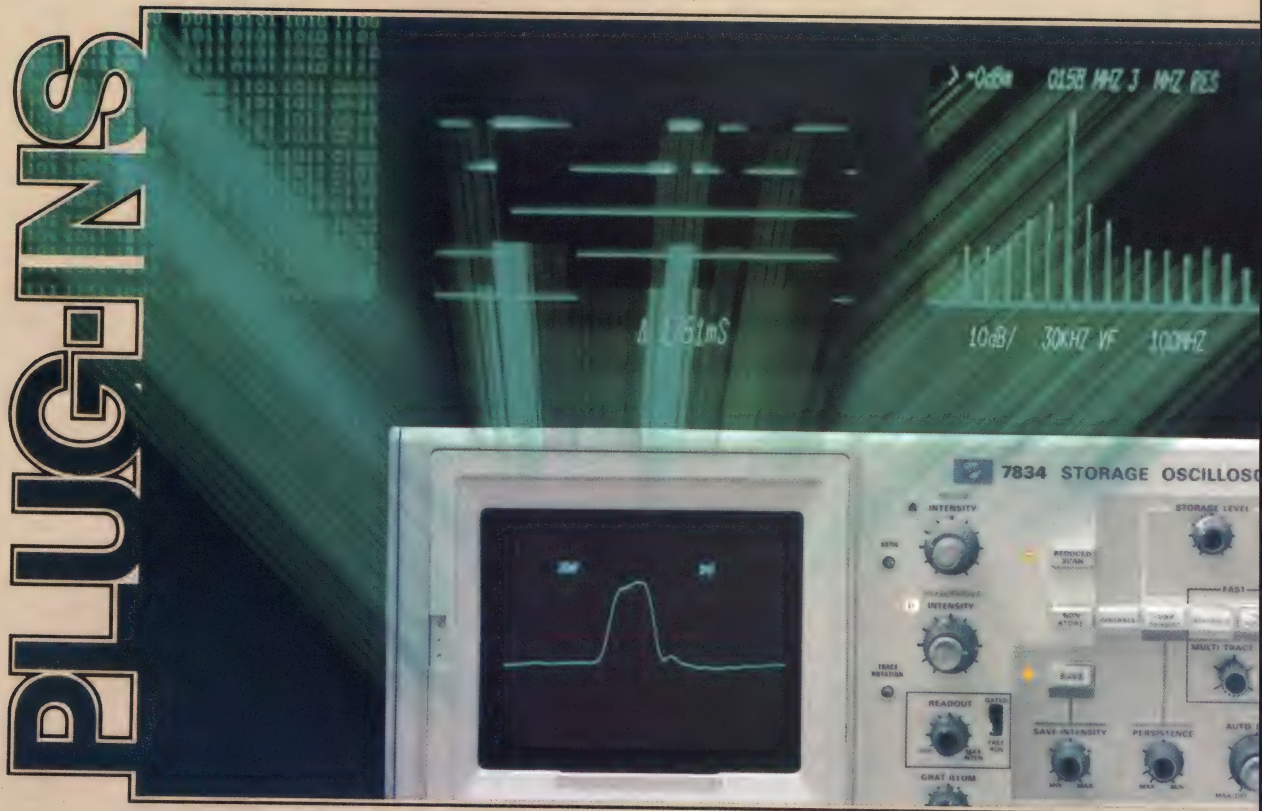

One instrument. Multiple measurements.

Tektronix Plug-In oscilloscopes combine a number of diverse measurement functions in the same instrument. And in combinations you require. One instrument takes the place of many. You get maximum measuring power with a minimum of instruments.

How? By choosing from the continually evolving 5000 and 7000 families of Plug-Ins. Already there are 14 mainframes and 21 plug-ins in the 5000-Series; 19 mainframes and 35 plug-ins in the 7000-Series. (With them, you can also use compatible logic and spectrum analyzers plus other special purpose plug-ins.) Choose from a family providing up to 8 input display channels. Analog and digital delayed sweeps. Sampling displays. Digital interconnections. And differential inputs. Just to name a few.

No matter what your test and measurement situation, we offer a Plug-In oscilloscope that fits. From circuit design to plasma physics research. From balancing rotating machinery to measuring the accuracy of D to A converters. With every scope representing the same superior research and engineering you expect from Tektronix.

What about your own particular situation? Are your measurement capabilities confined by monolithics? Contact the Tektronix Field Office near you and get your hands on the kind of flexibility that only a Plug-In scope can deliver.


Tektronix®
COMMITTED TO EXCELLENCE

For literature, call (800) 547-1512 toll free.

For technical data Circle no 13
For demonstration Circle no 14

New Products

INSTRUMENTATION & POWER SOURCES

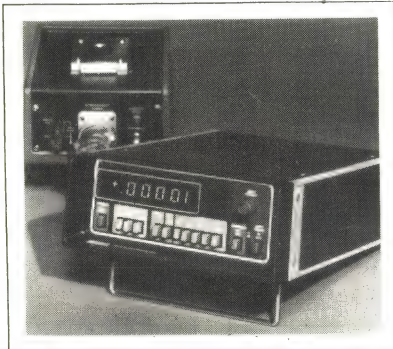


10⁻¹⁷A ELECTROMETER. In Model 642, MOSFET technology enables you to make measurements to 60 electrons/sec. Resolution approaches 0.005% of the input signal, so one range covers 200× the span of an equivalent analog instrument's—one range thus replaces six analog ranges.

The instrument provides direct readings of voltage, current or charge, spanning 10 μ V to 10V (10¹⁶ Ω input resistance), 10⁻¹³ to 10⁻⁷A FS (4-1/2-digit resolution) and 10⁻¹¹ coulombs (0.1, 1 or 10 ranges).


Innovations in the electrometer's design include a drift-compensated input stage; a lead(PB)-free input-terminal that minimizes surrounding air volume and thus reduces ionization; elimination of the need for switching devices with OFF resistances in the order of 10¹⁷ Ω ; and minimized-insulation contact points, guarded and made of sapphire to reduce their contribution to leakage currents.

Analog inputs permit recording of large signals and allow high-gain observation of low signals. Dessicant paper, BCD output, BNC input connector, an air-line input connector, a test box and a battery adapter (to allow external 12V powering) are available as accessories. \$3395. Delivery, 60 to 90 days ARO. **Keithley Instruments Inc.**, 28775 Aurora Rd, Cleveland, OH 44139. Phone (216) 248-0400. **Circle No 175**

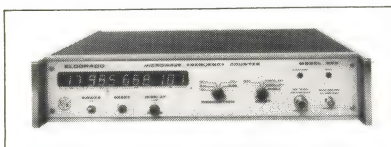


μ WAVE FREQUENCY COUNTER. Model 990 performs completely auto-


matic measurements under μ P control. A frequency-only device, it utilizes automatic heterodyning to cover from 20 Hz to 18 GHz in two ranges. Sensitivity specs at -25 dBm; overload at +25 dBm. Options provide -30-dBm sensitivity, 26-GHz response, GPIB (IEEE 488-1975) interface and 2W input protection. \$3800. **Eldorado Instruments Co.**, 2945 Estand Way, Pleasant Hill, CA 94523. Phone (415) 682-2100. **Circle No 176**

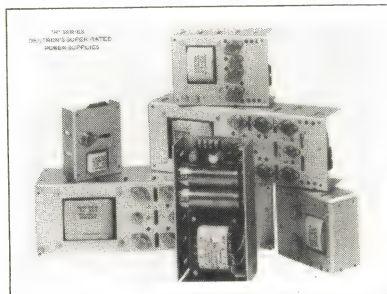


OPEN FRAMES. Claimed to deliver 25% more output than competitive units with the same case size, R Series supplies feature socketed semis and protection against reversed voltage or loss of sense. Forty two single-output models span 5 to 24V at 1.5 to 33.7A. All have a shielded split primary, 0.1% regulation and 1.5-mV rms noise. OVP comes as an option. From \$37. **Deltron Inc.**, Wissahickon Ave, North Wales, PA 19454. Phone (215) 699-9261. **Circle No 177**

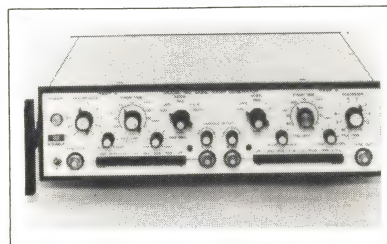

DUAL RAMP GENERATOR. Model 180 effectively combines dual-ramp raster and delay generation. Its two complete 1- μ sec to 1000-sec ramp generators (independently operable) can be synchronized for 1:1, 2:1 and 4:1 interlace. Rasters can easily be generated by using the unit's position and size controls, reverse sweeps, single-shot frames and fields, composite blanking pulses and 2:1 and 4:1 vertical sweeps for interlace. \$995. **Exact Electronics Inc.**, Box 347, Tillamook, OR 97141. Phone (503) 842-8441. **Circle No 178**

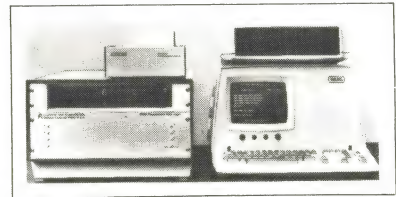

DAS. Included in Model 7251B are a BASIC-language computer with CRT, printer and mini-floppy disc; 8k of RAM (in addition to 42k of BASIC ROM); a scanner/mainframe with capacity for 14 I/O cards; a 4-1/2-digit DVM and a 10-channel low-level MUX. You can display bar charts and quasi-graphics on the CRT. Little or no programming experience is required of system users. \$12,700, including the computer. **FI Electronics**, 968 Piner Rd, Santa Rosa, CA 95401. Phone (707) 527-0410. **Circle No 179**

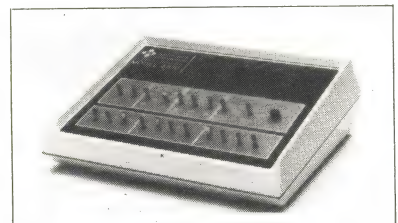

BUS-FAULT ANALYZER. Using the portable Model 4810 you can view or control IEEE-488-bus data, handshake and control lines. The analyzer acts as a manual bus driver, controlled either from front-panel switches or the switch-programmed memory. For fault analysis, an internal memory permits review of up to 100 characters of bus transmissions; a memory loop bypasses unused memory space and repeats only the programmed segment. \$1595. **ICS Electronics Corp.**, 1450 Koll Circle, Suite 105, San Jose, CA 95112. Phone (408) 298-4844. **Circle No 180**

DIGITAL PATTERN GEN. Model 710A's hex keypad and display permit easy data entry. The unit generates patterns from 8 to 64 bits wide and 1024 bits deep, at a 10-MHz rate. It features programmability through keyboard or IEEE-488 controller, nonvolatile storage of digital patterns and expansion to 64-channel \times 1024-bit capability. \$2400. Delivery, 60 days ARO. **Moxon Inc.**, 2222 Michelson Dr, Irvine, CA 92715. Phone (714) 833-2000. **Circle No 181**

Product Managers: The best things in life are **FREE**

And that includes the exposure your newest products receive in EDN's Product Showcase. Twice yearly, in December and July, EDN's editors screen the previous six months' product introductions and publish the cream of the crop. Our over 200,000 readers save and constantly use this valuable reference issue, which in July will be organized into six comprehensive product categories. Reader

service cards are valid for six months, so this issue keeps working for you.

Send us your candidates for this July Product Showcase **NOW**. Deadline is May 14, 1979. To qualify for initial consideration, an input

- **Must** have been introduced or be slated for introduction between January 1, 1979 and July 20, 1979. (Naturally, we pledge to

keep any information about products not yet introduced *strictly confidential*.)

- **Must** be accompanied by a black-and-white photo and full pricing and availability information.
- **Must** be fully spec'd. Please tell us *why* the product is noteworthy. Brag about it. Give us enough information on which to adequately judge its merits.

Don't delay! Send us your inputs NOW! Clearly mark the envelope "PRODUCT SHOWCASE" and, depending on product category, mail to one of the following addresses:

1.

EDN Product Showcase
221 Columbus Avenue
Boston, MA 02116

Inputs in these categories:

- Components — Relays, pots, switches, keyboards, displays, all function *modules* (V/F, A/D, D/A, D/S), capacitors, indicator lamps, resistors, materials, etc
- Computers and peripherals — all computer equipment, packaged and board level, including interfaces and software

- Power sources — All types of power supplies, including batteries
- Hardware and interconnect devices — wire, cable, connectors, pc boards, enclosures, fiber-optic links, etc
- ICs and semiconductors — All types of solid-state devices, discrete to LSI, hybrid and monolithic, that come in DIPs or smaller packages. Includes μ Ps, RAMs, ROMs, power transistors, all function *chips* (A/D, D/A, V/F), fiber-optic sources and detectors, etc

2.

EDN Product Showcase
(Instrument Section)
3771 20th Street
San Francisco, CA 94110

Inputs in this category:


- Instruments — Generating, measuring and viewing instruments as well as testing devices

Don't miss this **FREE** opportunity to reach over 200,000 design engineers and engineering managers in electronics. Send your inputs today!


EDN

Everything Designers Need

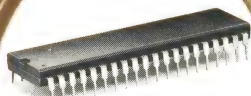Standard Microsystems' Family of MOS/LSI circuits.



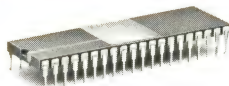
Floppy Disc
Hard-Sector Floppy Disc
Data Handler
FDC3400




Cassette
Cassette/Cartridge
Data Handler
CCC3500



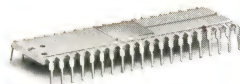
Printer
Character Generator
CG4103
Static Shift Register
SR5015
Shift-Right/Shift-Left
Shift Register SR5017/18



Keyboard
Keyboard Encoders
KR2376
KR3600

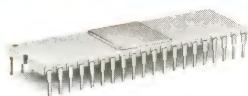

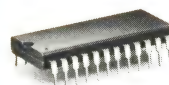
**Custom LSI & Dedicated
Microprocessors**
N Channel Silicon Gate
COPLAMOS®/CLASP®
P Channel Metal Gate



Memory ROM
32KBROM/ROM 4732



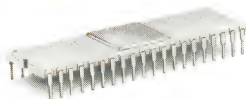**Programmable
Frequency
Synthesizers**
Baud Rate Generators
COM5016/5026/5036/5046
COM8046/8116/8126/
8136/8146



CRT
CRT Controller VTAC® CRT5027
CRT Controller CRT96364
Character Generator CG7004
VDAC™ CRT8002




Communications
UART COM2017/2502/
COM8017/8502
USRT COM2601
Multi-Protocol USRT
COM5025
ASTRO COM1671


STANDARD MICROSYSTEMS CORPORATION
35 Marcus Boulevard, Hauppauge, New York 11787 (516) 273-3100 TWX 510-227-8898
We keep ahead of our competition so you can keep ahead of yours.

For more information, Circle No 82

New Products

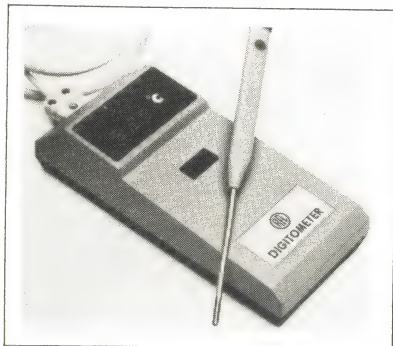

DIGITAL THERMOMETERS. Unlike many competitive units, LED-readout Digitimeters come complete with probe and batteries. The standard Type-K liquid-immersible thermocouple probe covers -25 to $+250^{\circ}\text{C}$ (Model BDK-450) or -25 to $+482^{\circ}\text{F}$ (Model BDK-1000), with accuracy of $\pm 0.2\%$ of reading ± 1 digit; optional probes extend these ranges. An internal element provides cold-junction compensation. Four 1.5V AA alkaline cells give 10 hrs of continuous operation or 10,000 readings. \$340 for either model. **RFL Industries Inc.**, Boonton, NJ 07005. Phone (201) 334-3100. **Circle No 182**

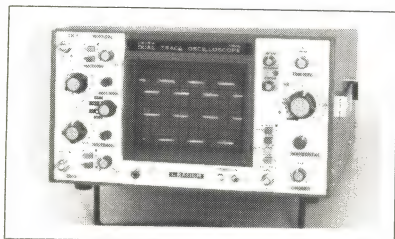


10-MHz SCOPES. Both the single-trace Model LBO-53 and the dual-trace Model LBO-514 furnish 8×10 -cm display, Z-axis modulation, $\times 5$ magnifier and complete trigger controls. Sensitivity reaches 1 mV on both units. Extensive use of ICs reduces instrument parts count and permits design simplification. Model LBO-514 also features X-Y operation, CH-1/CH-2 trigger selection and alternate or chopped display modes. \$499 for LBO-53; \$649 for LBO-514. **Leader Instruments Corp.**, 151 Dupont St, Plainview, NY 11803. Phone (516) 822-9300. **Circle No 183**


TINY SWITCHERS. Able to hide under a penny, units in the $0.5 \times 0.5 \times 0.5$ -in. $\mu\text{S-A}$ Series of switching-mode power supplies deliver up to 30 mW of output. Available models output 1.5 to

15V, regulated or unregulated, and operate from 47- to 440-Hz input. Full-output models accept either 120 or 240V input, while a reduced-output version operates from 90 to 255V without switching. I/O isolation specs at 2500V. \$2.86 (100). **Microsource Corp.**, 7330 Rogers Ave, Chicago, IL 60626. Phone (312) 465-8420.

Circle No 184

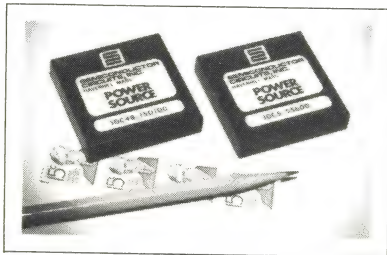


DC-DC CONVERTERS. Series 30 units' low output noise (5 mV p-p max for dual-output models, 8 mV p-p max for single-output models) fits them for demanding applications. Common specs for the 12 devices in the line show full output to 71°C ambient, $< 1\%$ reflected input ripple, 55 to 75% efficiency, a $2 \times 2 \times 0.4$ -in. case and 300V I/O isolation. Available input can be 4.5 to 5.5, 10.8 to 15, 21.6 to 30 or 42 to 56V dc; output, 5V/600 mA, $\pm 12\text{V}/125$ mA or $\pm 15\text{V}/100$ mA. \$74.75. **Semiconductor Circuits Inc.**, 218 River St, Haverhill, MA 01830. Phone (617) 373-9104. **Circle No 185**

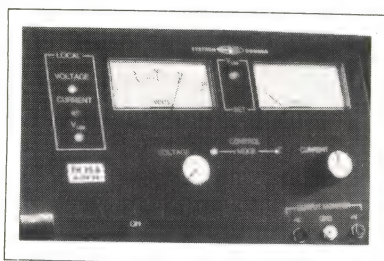

PROGRAMMABLE SUPPLIES. Four quarter-rack models (10V/3A, 20V/2A, 50V/1A, 100V/0.5A) and four half-rack 150W models (10V/10A, 20V/6A, 50V/3A and 100V/1.5A) make up the series. Each unit can have its output voltage, current and voltage limit controlled by IEEE-488 bus, external analog signals or manually. Outputs respond to programmed changes in 1 to 2 msec; current-sink circuitry discharges load capacitance. \$495 to \$625. **Systron-Donner**, 10 Systron Dr, Concord, CA 94518. Phone (415) 676-5000. **Circle No 186**

COMPONENTS & PACKAGING

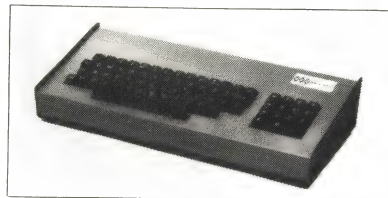

KEYBOARD. Designed specifically for personal, business and educational μC systems, Model 771 includes 56 alphanumeric keys which provide the full ASCII set (including lower case) and a separate 15-key numeric/cursor control keypad.

Four encoding modes, including an upper-case-only mode, combine convenient entry of data with high throughput. Standard features include auto-repeat, 2-key rollover and fully buffered outputs. The unit is equipped with a parallel interface and D-series connector for easy interconnection.

The options allow users to tailor the keyboard to their specific application. Four power-supply options suit almost any available voltage source. A versatile interface permits user selection of data, strobe and parity sense. An optional adapter converts the keyboard to a self-contained transmitter with 110 to 9600 baud RS-232 or current-loop serial-data output. From \$150. **George Risk Industries Inc.**, GRI Plaza, Kimball, NB 69145. Phone (308) 235-4645. **Circle No 187**



R NETWORKS. Designed for precision linear, digital and microwave circuits, this line of thin-film-on-ceramic chip resistors provides 20Ω to 500-k Ω resistance and 15- to 400-mW power ratings. The chips range in size from 0.02×0.04 to 0.1×0.1 in. and are laser-trimmed to standard tolerances of 1 and 5% (0.05% on special order). Long-term stability is typically 0.1%/1000 hrs at 125°C . The standard terminations are gold, nickel-gold or nickel-solder. **Electro Films Inc.**, 100 Meadow St, Warwick, RI 02886. Phone (401) 738-9150. **Circle No 188**



Gain huge savings—in dollars and inches—by replacing bulky conventional oscillators with tiny IC circuits.

WHILE CONVENTIONAL OSCILLATORS (FUNCTION GENERATORS, WAVEFORM GENERATORS, VCO'S, ETC.) COST UP TO SEVERAL HUNDRED DOLLARS, A SINGLE-CHIP IC OSCILLATOR CAN LITERALLY DO THE SAME JOB...AND FOR AS LITTLE AS \$1.72. All you give up for this tremendous reduction in cost and size is a certain degree of regulation in the output, and a variety of knobs and controls. But let's be realistic—for most applications, the IC oscillator is perfectly adequate. Its small size and low price makes the alternate approach quite impractical.

Nothing left out in the process.

Despite its small size, an IC chip really does contain every operating section of a traditional function generator. Consider a typical semiconductor oscillator, the XR-2206. On-chip you find the oscillator circuit (to generate the basic periodic waveform); the wave shaper to give you a clean sinewave; the modulator section (for AM capability); and an output drive amplifier. Basically the selfsame circuitry you'd receive if you bought a standard oscillator or benchtop function generator hundreds, even thousands of times as big as the IC.

But the real payoff comes in the outputs of these oscillators, and here too you lose nothing by going solid-state. The IC

oscillator will generate a combination of eight different types of output waveforms: triangle, ramp, sawtooth, squarewave, sinewave, pulse and FSK (frequency-shift keying) outputs, each with its own appropriate range of applications.

Just the item for sweep generators and sweep modulators.

The sweep generator, with its output hodgepodge of frequencies, can be a complex device. Yet it's a circuit easily built with ICs. A triangle-, ramp- or sawtooth-wave generator (XR-2207) modulates another oscillator (XR-2206) set up for voltage-to-frequency conversions. And presto! You have a functioning pocket-size sweeper.

Digital test equipment and stable phase-locked loop design.

Where space is at a premium, the solid-state precision voltage-controlled oscillator (XR-2209) comes to the rescue with banners flying. It more than meets the functional accuracies required, saves pounds and inches, and shaves dollars too.

Audio test equipment too.

Low cost is the prime requisite here, and once again the IC oscillator comes through for the design engineer. Solid-state sinewave generators (XR-2206 or XR-8038) are ideal, low-cost, simple solutions that often can offer a size and power advantage perfect for the test or hobby market.

Digital communications, including data-interface or acoustical-coupled MODEMS.

The FSK oscillator is tailor made to solve this design dilemma. Modern designers, particularly those dealing with computer and data-processing systems, are continually put upon to squeeze more capability into ever decreasing amounts of space. Where board space is tight, the IC FSK oscillator (XR-2206 or XR-2207) is magnificently effective in compressing a complex function into a nutshell. You wind

up with inches of real estate for really important things such as more memory.

Digital testers, logic circuits, on/off gating.

Naturally, there's an IC oscillator for the purpose. This time one with a pulse output (XR-

2206 or XR-2207). All the same advantages you find in other applications—size, cost, low power requirements—apply here as well. In short, regardless of where you need to use an oscillator or function generator, there's an outstanding chance you can find a solid-state device to do the job and make you a hero in the bargain.

Beware. Only one company produces a complete line of IC oscillators.

With a stable of five different circuits, Exar boasts by far the industry's broadest choice of IC oscillators. From low cost, easy-to-use devices to high performance function generators, the line is summarized in Table 1. Check them out, find the one best suited for your use, then make the shrewd move to solid state.

Exar's Function Generator Data Book contains technical articles and application notes. To request your copy, write on your company letterhead to your nearest Exar representative or to Exar, 750 Palomar Avenue, Sunnyvale, California 94086.




Electrical Characteristics	EXAR Device Type				
	205	8038	2206	2207	2209
Output Waveforms	Triangle, Square, Sine			Triangle, Square	
Upper freq. limit (MHz)	4	1	1	1	1
Sweep range	7:1	1000:1	2000:1	2000:1	2000:1
Typ. temp. Drift (PPM/°C)	300	50	20	20	20
Typ. sinewave distortion	2.5	0.5	0.5	—	—

Table 1. Exar's line of IC Oscillators.


FOR THE EXAR DISTRIBUTOR OR REP NEAREST YOU, CALL EXAR AT (408) 732-7970.

New Products

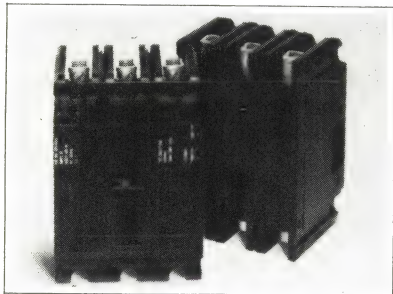

CIRCUIT BREAKERS. Accommodating 250V at each pole, GH Series units feature three time-delay choices, ratings of 15 to 100A and a 10,000A interrupt capacity. These fully magnetic breakers carry 100% of rated load without derating; changes in temperature have no effect on current rating, must-trip point (125% rated load) or instantaneous-trip point. An inverse time delay protects against nuisance

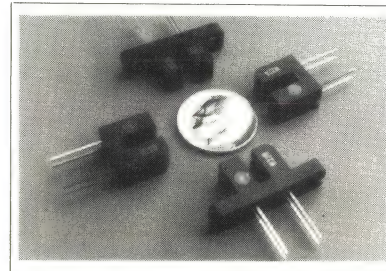trips caused by normal starting surges. **Heinemann Electric Co.**, Magnetic Dr., Trenton, NJ 08650. Phone (609) 882-4800. **Circle No 189**



INTERRUPTER MODULES. H21/H22 Series devices are compatible with logic systems from CMOS to relays. The units provide a consistent light beam with maximum dimensions of 1×1.5 mm, up to 25-mA minimum output and 55V blocking capability. The line includes 24 types: 12 transistor detectors feature low saturation voltage (<0.4V at 1.8 mA), and 12 darlingtontons feature high output current (≥50 mA at 1.5V). **General Electric Co.**, W Genesee St., Auburn, NY 13021. Phone (315) 253-7321.

Circle No 190

MIXERS. Model MHP-106 operates over a 1- to 2500-MHz range with an IF of 1 to 2000 MHz. This medium-power-level device (17-dBm LO power) has a 1-dB compression point of 10 dBm min from 1 to 1000 MHz and 8 dBm min from 1000 to 2500 MHz. Full MIL-STD-202E performance is guaranteed. Contained in a hermetically-sealed 8-pin plug-in or solder-pin package, the MHP-106 measures 0.4×0.4×0.8 in. \$50. **Engelmann Microwave Co.**, Skyline Dr., Montville, NJ 07045. Phone (201) 334-5700.


Circle No 191

MIXER. Model MD-159 is a 5- to 1000-MHz double-balanced mixer that provides a typical VSWR of 1.1:1. Other typical specs include 45-dB LO-to-RF isolation, 6-dB midband conversion loss and SSB NF within 1 dB of conversion loss. Typical two-tone IM ratio (with a -10-dBm input for each tone at 10-MHz separation) is 50 dB at 500 MHz. All specs apply with 50Ω source and local impedance and 7-dBm available LO power. \$55. **Anzac Electronics**, 39 Green St., Waltham, MA 02154. Phone (617) 899-1900.

Circle No 192



**SOLID
STATE
SCIENTIFIC INC.**

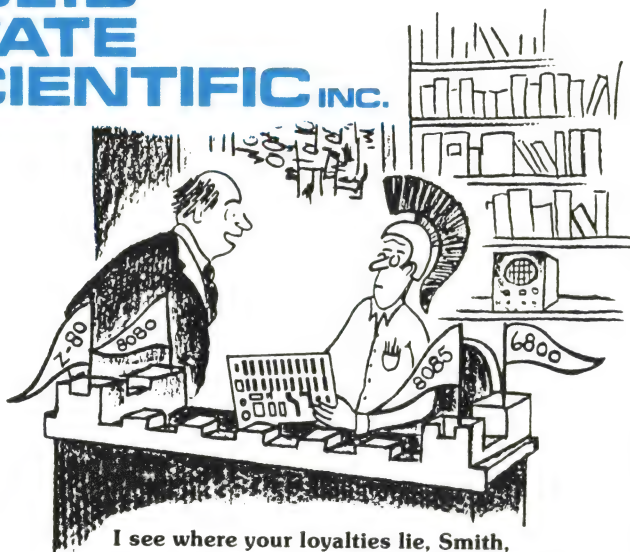

I see where your loyalties lie, Smith,
but your data isn't complete if you don't
have information about SOLID STATE
SCIENTIFIC'S 1802 MICROPROCESSOR.

**Get the FACTS on our
MICROPROCESSORS.**

Cut out coupon below or photocopy and attach to your letterhead. Mail to: **SOLID STATE SCIENTIFIC**, Montgomeryville, Pa. USA 18936. Attn: L. Rocco. Or call 215-855-8400.

Send me Facts about your μ MOS families. **N 3**

Name _____

Position _____

Company _____

Street _____

City _____

State _____

Zip _____

Phone _____

Also send information about
THE MANY SIDES OF
SOLID STATE SCIENTIFIC:

- ☐ DT/ μ MOS Systems
- ☐ μ MOS Memories
- ☐ Custom MOS ICs
- ☐ Hi Rel MOS
- ☐ Data Communications
- ☐ Display Drivers
- ☐ Security ICs
- ☒ 4000 Series
- ☐ Timekeeping
- ☐ RF Transistors



**SOLID
STATE
SCIENTIFIC INC.**

For more information, Circle No 84

Relax!

We can get Microprocessor Development Systems from Zilog, Intel or Tektronix on their way to you in minutes.

Whether your requirement is for a week, a month, a year or longer, there's one way to get the latest in microprocessor development systems from Zilog, Intel or Tektronix without waiting. Rent it from Leasametric.

Instantly, AUTEX, our nationwide computerized inventory system, will check our dozens of regional inventory centers to pinpoint the unit closest to you. Within minutes, your order will be processed and moving on its way. In most cases, your development system will be in your hands in less than 24 hours.

Need more than one system? Don't waste time and energy calling everyone in the book. One phone call to Leasametric is the fast, simple way to end your equipment worries and start relaxing. And, rental means more than immediate possession.



It's the one effective way to get the new equipment you need without going back to management for more money. There's no major capital investment with a Leasametric rental.

Leasametric, of course, means more than development systems. We stock the latest terminals, acoustic couplers, modems, communications and general-purpose test equipment . . . just about anything you might conceivably need.

Our growing inventory includes over 23,000 items from 500 of the top electronic manufacturers — including almost the entire HP catalog.

Need it now? Why wait? To order, or for our latest rental catalog, pick up the phone and call one of the relaxing, nationwide numbers shown below.

They're toll free. Or call your local Leasametric office. There's one in every major city.

Leasametric/Rent it and relax.

In the West

Call 800-227-0280

In California, call (415) 574-4441

In the Central U.S.

Call 800-323-2513

In Illinois, call (312) 595-2700


In the East

Call 800-638-4009

In Maryland, call (301) 948-9700

A Trans Union Company
1164 Triton Drive, Foster City, CA 94404

For more information, Circle No 85

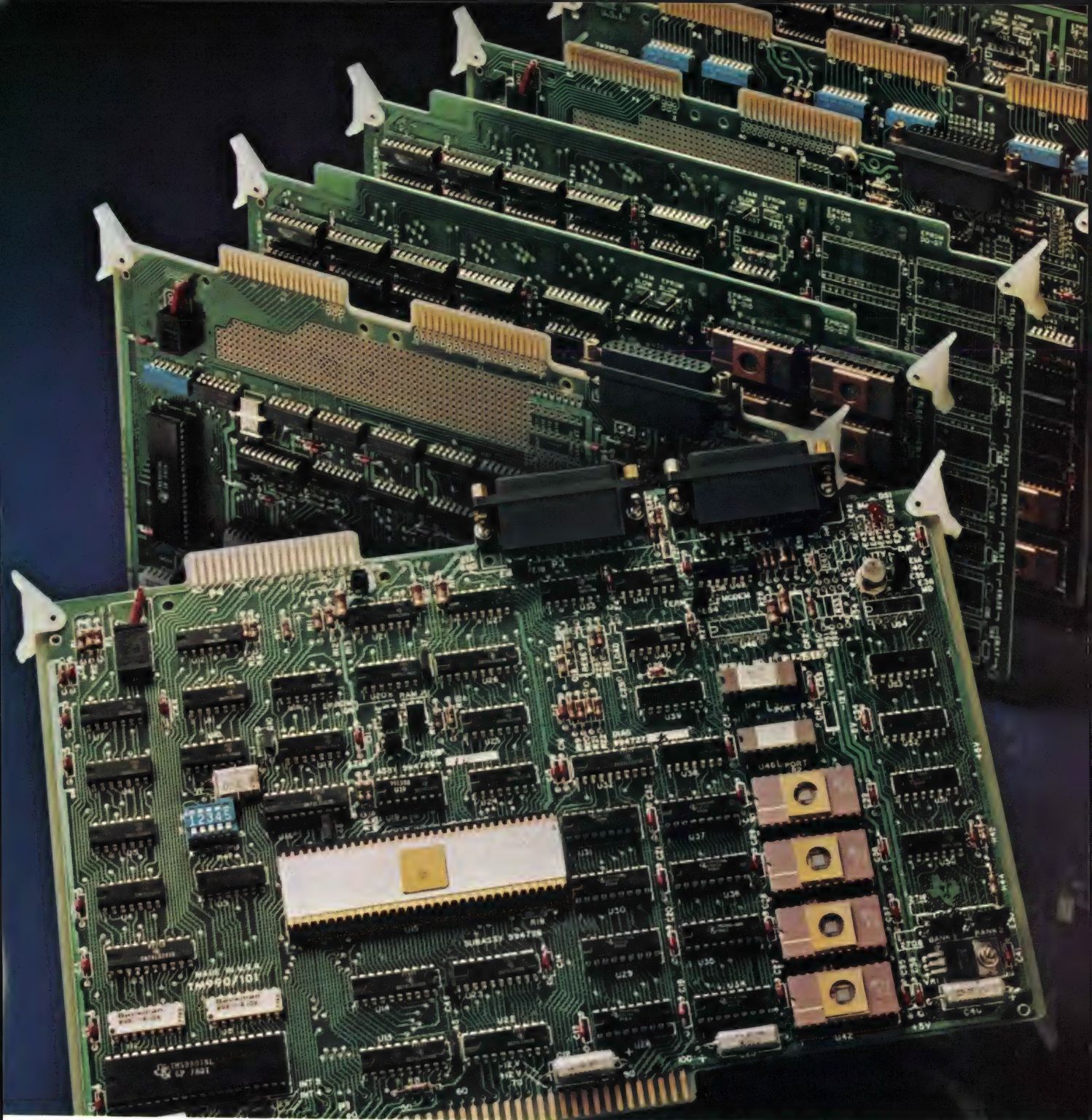

Joining the growing 990/9900 Family:

First 16-bit microcomputer with BASIC. Easier to program. More capability to store. Remember. Communicate.

Now available from your local TI distributor, true single-board computers. TI's new TM 990/101M microcomputer modules. More memory than ever before. Simultaneous dual communication. With

communication protocol on the board and POWER BASIC* high-level language on the TM 990/101M-10 to make programming faster, easier.

These new modules from TI save

you design and development time. Cut the number of system components. Reduce costs and improve reliability.

They're preassembled. Pre-tested. Ready to plug in.

Four times the memory

The TM 990/101M microcomputers come with as much as four times the static RAM on board: up to 2K by 16 bits. The EPROM is either 2K by 16 bits or 4K by 16 bits.

Double the communication capability

Also on board: two serial communication ports. One for "remote" usage such as a terminal or modem. The other for "local" usage with an EIA terminal, a teletype, or TI's TM 990/301 microterminal.

The most in microcomputers

In TI's TM 990 Series, you have the widest available choice of cost-effective, 16-bit microcomputers to meet your system needs. Ideal for microprocessor evaluation. To speed your microprocessor-based design to market. Or as a production alternative. And all are instruction-set compatible with other members of TI's 990/9900 First Family.

For evaluation and OEM applications:

- TM 990/100M — Utilizes TI's NMOS 16-bit TMS 9900 microprocessor. Includes 1024 bytes of static RAM, 2K bytes of EPROM, and programmable serial and parallel I/O to form a powerful, single-board microcomputer.
- TM 990/180M — Provides 2.5 MHz operation. Incorporates an 8-bit memory interface.
- TM 990/189M — A self-contained, assembled, single-board 16-Bit Microcomputer System complete with integral keyboard, system monitor, symbolic assembler, 500 page Tutorial Text and 200 page User's Guide.

For memory expansion:

- TM 990/201 — 8K bytes of EPROM and 4K bytes of static RAM. Expandable to 32K bytes of EPROM and 16K bytes of RAM.
- TM 990/203 — Dynamic memory module with up to 64K bytes capacity with parity.
- TM 990/206 — 8K bytes of RAM expandable to 16K bytes.

For data entry and display:

- TM 990/301 — Provides hexadecimal entry of program data, as

well as display and modification of internal registers and memory under software (TIBUG*) control.

For I/O expansion:

- TM 990/310 — A 48-bit input/output expansion module.
- TM 990/305 — Up to 32K bytes memory capacity using pin compatible static RAMS and/or EPROMS. Plus 32 optically isolated I/O lines, 16 dedicated parallel input lines and 16 user-configurable parallel I/O lines.

For A/D, D/A and digital I/O industrial interfaces:

- 16 new TM 990 Bus Compatible Modules — 7 A/D and D/A modules — 9 AC and DC input and output modules.

For development and production:

- TM 990/302 Software Development Module — Includes ROM resident symbolic assembler, text editor, loader, debug package. EPROM programming, dual audio cassette interface, and POWER BASIC development options.
- TM 990/401 — Interactive debug monitor (TIBUG) preprogrammed into EPROM.
- TM 990/402 — Line-by-line assembler preprogrammed into the EPROM.
- TM 990/450 — 8K POWER BASIC preprogrammed into ROM.
- TM 990/451 — 12K POWER BASIC preprogrammed into ROM.
- TM 990/452 — POWER BASIC option — EPROM programming and audio cassette interface.
- Configurable Basic — TMS W510F floppy based Industrial Basic allowing minimum memory configuration.

OEM card cages, cables, connectors, extender and prototyping boards are available.


Time-saving software support

The TM 990 microcomputers are fully supported by TI's Advanced Microprocessor Prototyping Laboratory. AMPL* features 10 MHz trace capability and universal emulation for the TMS 9900, SBP 9900, TMS 9980, and TMS 9940 microprocessors as well as others to come.

*Trademark Texas Instruments Incorporated

AMPL is available as a floppy diskette system or as a disk system that accommodates multiple users. Programs can be edited, assembled, linked, loaded, and executed much faster than conventional paper tape or cassette based systems.

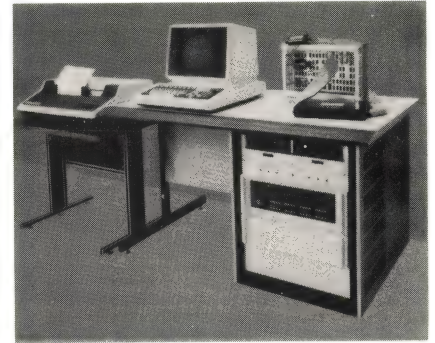The 9900/9980 emulation allows development and debugging of software directly on a TM 990 module while monitoring and controlling the operation from the AMPL prototyping system.



For today and tomorrow: the 16-bit First Family

The TM 990 Series microcomputers and AMPL are integral members of TI's pace-setting 990/9900 First Family. A mature, proven family already providing the power and performance of 16 bits that many others are just beginning to imitate.

It's a broad, readily available selection of compatible microprocessors, microcomputers and minicomputers using the same advanced memory-to-memory architecture. Same instruction set. Same development system. All software supported and software compatible.

The 990/9900 Family gives you flexibility and economy to meet today's specific needs. And provides the base to improve and innovate as your needs change while protecting both your hardware and software investments.

For technical assistance on the TM 990 Series microcomputers, call your TI Field Sales Office. For more information, call your TI distributor or write: Texas Instruments, P.O. Box 1443, M/S 6404, Houston, Texas 77001.


**TEXAS INSTRUMENTS
MOVING AHEAD
IN MICROCOMPUTERS**



TEXAS INSTRUMENTS
INCORPORATED


For more information, Circle No 86

New Products

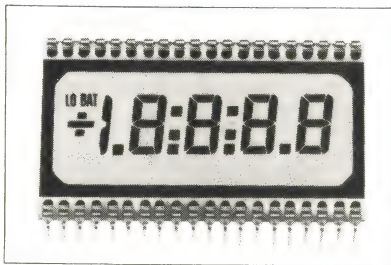

DISPLAY. The 4-1/2-digit Model FE0206 liquid-crystal display features a 0.4-in. digit height, four decimal points, "low-battery" annunciator, +/— sign and two colons. The unit is available in transmissive, reflective and transreflective modes and can be purchased with DIP pins or in a leadless version for use with elastomeric connectors. Crystal materials are available in two operating ranges: -10 to +55°C and -5 to +90°C. Red, blue and green readouts are available on special order. \$11.25 (100). **AND**, 770 Airport Blvd, Burlingame, CA 94010. Phone (415) 347-9916.

Circle No 193

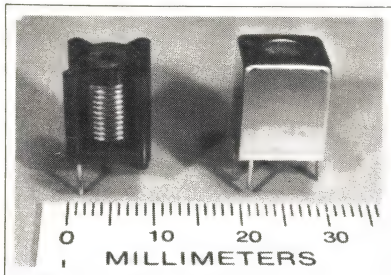

COILS. Tuneable Uni-10 devices employ a precision winding in a single molded piece of polypropylene plastic to assure mechanical and electrical stability. Nominal inductance for a 1-1/2-turn coil with a 0.25-in.-long carbonyl E core is 0.059 μ H; a 10-1/2-turn unit yields 0.429 μ H. Typical Q for the latter is 100 at 40 MHz. The coils' hex-hole core tunes more easily than slotted cores. \$0.10 (5000). **Coilcraft**, 1102 Silver Lake Rd, Cary, IL 60013. Phone (312) 639-2361.

Circle No 194

SWITCHES. Series TH lighted push-buttons convert from alternate to momentary action through movement of a lever accessible through a window in the switch body. Three available models include: TH01 with tapered bezel, TH31 with straight bezel and TH42 with covered bezel. Wipe-and-roll gold-plated-silver con-

tacts handle loads to 5A at 250V ac. Most units come with round, square or rectangular lenses (translucent or transparent) and up to 4-pole switching capability. \$3.55 (1000) for TH01.

Unimax Switch Corp, Ives Rd, Wallingford, CT 06492. Phone (203) 269-8701.

Circle No 195


POSITION SENSORS. This line of contactless linear and rotary sensors serves industrial applications; the linear units have two ferrite-tube inductors connected in series and mounted between a movable plunger assembly containing two ceramic permanent magnets. When a unit is driven with an ac signal, its output is an ac voltage with amplitude proportional to the plunger position. Output of the similarly constructed rotary units varies linearly with shaft angle. Approx \$20. **Licon Div/ITW Inc**, 6615 W Irving Park Rd, Chicago, IL 60634. Phone (312) 282-4040. **Circle No 196**

ASSEMBLY PANELS. Mountable on 0.5-in. centers, W9302 hex wire-wrapping modules accommodate up to 96 DIP ICs or sockets; 55 positions are dedicated to 16-pin devices and 11 to 20-pin units. These dedicated positions are prewired for ground and power. In addition, power and ground pads accommodate ceramic decoupling capacitors at 55 locations. Two I/O positions serve ribbon-cable edge connectors with up to 50 conductors, and 2-level wrapping posts are installed on the boards' component side. **MDB Systems Inc**, 1995 N Batavia St, Orange, CA 92665. Phone (714) 998-6900. **Circle No 197**

SOCKET BOARDS. The metric DMPS series of packaging panels offers a 160×233-mm board with an I/O area compatible with European right-angle wire-wrappable, 96-pin connectors. The Schottky-TTL construction combines two outside ground planes with a sandwiched V_{CC} plane. Socket/terminals have brass sleeves with gold-plate over nickel or a 200- μ in. electro-tin finish. The four-tine spring-socket members are gold-plated beryllium copper and are available with three lengths of wire-wrapping or rectangular-post terminations. \$150 to \$350. Delivery, 4 to 6 wks ARO. **Garry Mfg Co**, 1010 Jersey Ave, New Brunswick, NJ 08902. Phone (201) 545-2424. **Circle No 198**

HEAT SINKS. Series 6075 components feature a universal hole pattern for 2-, 3- and 4-lead TO-3, TO-127 and TO-220 plastic power devices. For a 75° rise, thermal resistance specs at 6.25 (6077B), 7.4 (6076PB) and 11 (6075PB) °C/W. The sinks' U-shaped stampings require little board space; the components are a good choice in applications where vertical space is plentiful. The heat sinks come in pre-black-anodized aluminum material. \$0.08 to \$0.15 (1000). **Thermalloy Inc**, Box 34829, Dallas, TX 75234. Phone (214) 243-4321. **Circle No 199**

SWITCHES. 39000 Series thumbwheels are only 0.315 in. wide and include an isolated switching chamber for extra protection against dust and debris. Units are available with 10, 11, 12 or 16 positions (with field-installable dial stops) in a wide variety of output codes. The front-mounted modules feature 0.2-in.-high characters, a gold contact system and G-10 circuit board. The units assemble without tools and come with solder or optional pin terminations. \$3.15/module (100). **Digitran Co**, 855 S Arroyo Parkway, Pasadena, CA 91105. Phone (213) 449-3110. **Circle No 201**

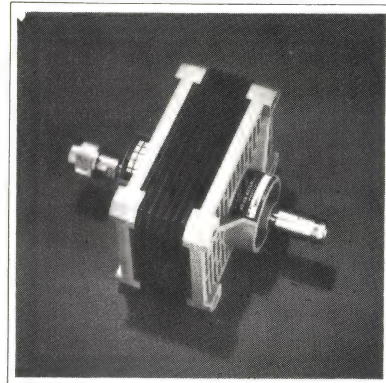

ATTENUATOR. Intended for broadband coaxial measurements at medium power, the 8498A offers 30-dB attenuation and covers a dc to 18-GHz range. It has a standing wave ratio of 1.3 at 18 GHz, and its attenuator pad is bilateral so that either end accepts 25W inputs. No adapters are needed because the standard connector configuration uses one Type-N male and one Type-N female. \$475. Delivery, 8 wks ARO. **Hewlett-Packard Co**, 1507 Page Mill Rd, Palo Alto, CA 94304. Phone (415) 493-1501.

Circle No 202

Ampex non-volatile RAM for 8080. 16K bytes \$885.

Now Ampex gives you proven, non-volatile RAM in a single-board, 16K byte module: the MCM-8080. It'll work with Intel SBC 80/05, 80/10 and 80/20, System 80, the MDS-800 Microcomputer Development System, and the 888 System Development Center.

MCM-8080 is pin compatible with the Multibus*, fits in a single card slot, has data save for out-of-tolerance power supplies,

and won't lose data when the power goes off.

Remember, a system is only as reliable as the memory, and Ampex non-volatile core RAM is the most reliable memory you can use. Write Ampex Memory Products Division, 200 North Nash Street, El Segundo, California 90245. Or call Ted Conant at 213/640-0150. Try 16K bytes of reliable memory for only \$885.

AMPEX

*Trademark, Intel Corporation

For more information, Circle No 87

We Protect Your Reputation

The hefty power supply module will power two duplicators simultaneously. Load one unit while the other is duplicating.

Tests and Duplicates 1 to 16 EPROMS simultaneously.

Reliable single board construction and LSI components.

Solid state audio transducer informs the operator of incorrectly inserted devices or test failures.

AUTO PROG-single key automated test-program-verify sequence.

40 pin Personality Module contains the programming algorithm and reference voltages for a complete generic EPROM family.

Fast 8048 processor performs comprehensive diagnostics in seconds, not minutes!

Put an end to costly and embarrassing field failures caused by marginal EPROMS with the first Production Duplicator that "tests" your EPROMS both *before* and *after* programming!

Whether you are programming 1 or 100 EPROMS a day, you can't afford a marginal EPROM in your end product. OAE's new Programmer includes an exclusive set of "test" routines designed to detect poorly erased or static damaged EPROMS which would otherwise pass a Verify test.

And it's so easy to use — simply touch the AUTO PROG key and the UPP-2700 will automatically test and program 1 to 16 EPROMS. Or, use the other 15 keys to access the individual test routines.

A small 40 pin Personality Module contains the test and programming algorithms for a specific generic EPROM family. This open-ended design does not limit the UPP-2700 to current or "projected" EPROMS. Personality Modules are currently available to handle all of the following EPROMS:

PM-1: 2704, 2708, 27L08; **PM-2:** TMS-2716; **PM-3:** 12758, 12716, TMS-2516; **PM-4:** TMS-2532.

The UPP-2700 could pay for itself in its first week of operation. Can you afford to be without it?

Protect your profits . . . Call us today!

UPP-2700 PROGRAMMING SYSTEM includes power supply and one Personality Module (please specify) . . . \$2450.00


Second UPP-2700 Programmer (please specify Personality Module) . . . \$1995.00

For more information, Circle No 89




Oliver Advanced Engineering Division
676 West Wilson Avenue
Glendale • Ca. • 91203
(213) 240-0080

DPM. Model 3362 features a full-scale capability of ± 5999 counts with a bright 0.55-in. gas-discharge display. External control signals include hold, trigger, blank, read-rate and decimal point. Output signals include polarity and overrange; read-rates to 8 samples/sec are available. Options include parallel BCD output and offset for process applications. The unit is housed in a standard NEMA-size case. \$118 (OEM qty). **Data Tech**, 2700 S Fairview, Santa Ana, CA 92704. Phone (714) 546-7160. **Circle No 206**

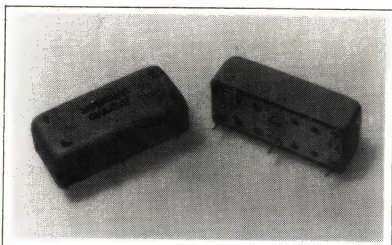

HYBRIDS. Series QHS-6 quadrature 90° hybrids are aimed at amplifier-combining, SSB-generator, image-reject mixer and radio direction-

finding applications. Three units make up the line: QHS-6-17, 2 to 32 MHz; QHS-6-42, 3.5 to 80 MHz; and QHS-6-225, 50 to 400 MHz. All units have a 3-dB coupling loss, 20-dB isolation (15 dB for the -225), 1-dB amplitude balance and 1.5-dB insertion loss. VSWRs are 1.3, 1.35 and 1.5, respectively. The units are housed in a miniature pc-board plug-in package. \$195 to \$245. **Merrimac Industries Inc.**, 41 Fairfield Pl, West Caldwell, NJ 07006. Phone (201) 575-1300. **Circle No 207**

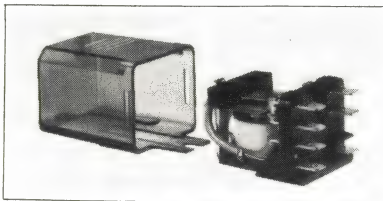

RELAYS. Type 188 relays are rated for 30A at 28V dc, 120/240V ac (80% power factor) and 1 hp at 120V ac. They are available in Form X, Y and Z contact arrangements. Standard input-coil voltages range from 6 to

100V dc and 6 to 220V ac. The relays provide 0.25-in. combination quick-connect/solder terminals and are offered with either a standard or open-style, stud-mounted, plastic-flanged dust cover. \$3.56 (2500) for Form Z, 120V-ac-coil unit. Delivery, stock to 6 wks ARO. **MidTex Inc.**, 1650 Tower Blvd, North Mankato, MN 56001. Phone (507) 625-6521.

Circle No 208

I/O SWITCHES. S442 and S443 solid-state ac-output switches provide an electrically clean, photoisolated, noise-free interface between sensitive controls and their load-field elements. Both units have a load-current rating of 2A at 40°C and 1.3A at 70°C. The S442 features a 30 to 140V-ac rms range, while the S443 is rated at 60 to 280V-ac rms. The devices are fully potted and have an internal heat spreader for optimum thermal management. S442, \$12.25 (50); S443, \$12.85. Delivery, stock to 6 wks. **International Rectifier Corp.**, 1521 E Grand Ave, El Segundo, CA 90245. Phone (213) 322-3331. **Circle No 209**

The NEW GENERATION of PHI-DECK® Cassette Transports

- Cast Chassis
- Four Motors
- Fully Remote Controllable


FIXED SPEED DECK with AC CAPSTAN MOTOR - Single speed transport. Excellent speed regulation from synchronous AC capstan motor. $1\frac{3}{16}$, $1\frac{1}{8}$, $3\frac{3}{4}$, 5, 6, 7, 8, or 10 ips.

FIXED SPEED DECK with DC CAPSTAN MOTOR - Lowest cost, single speed transport. $1\frac{1}{8}$, 2, $3\frac{3}{4}$, 5, or 6 ips.

OPTO-TACH TRANSPORT - Precise speed control. Optical tachometer allows digital selection of 2 speeds.

SELECTO-SYNC SYSTEM - Our most advanced synchronous drive system. Any of 15 speeds selected by digital code. Includes transport, motion control, and speed selection circuitry. Optional ULTRA-SYNC board provides crystal-controlled tape signal synchronization for the ultimate in precision tape movement.

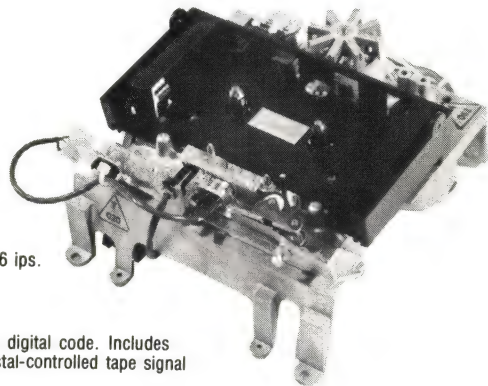HI-PHI-DECK - Designed for high quality audio applications. Precision components provide typical 0.05% wrms Wow and Flutter.



and ELECTRONICS developed exclusively for PHI-DECK

MOTION CONTROL BOARDS for DC, AC, OPTO-TACH - Accepts 5 volt CMOS signals to initiate Run, Stop, Fast Forward, and Fast Rewind. Tape tension, braking, and motion sensing are automatically controlled.

UNIVERSAL MOTION CONTROL BOARDS - Provides complete deck control for all models of PHI-DECK. Provisions for plug-in boards for bi-directional operation and solenoid controlled pinch roller operation.

COMBINED MOTION CONTROL and RECORD/PLAY AMPLIFIER - Stereo R/P operates from a single 12 volt supply. Line and microphone inputs, line and speaker outputs. Record/Play electronics available separately.

COMBINED MOTION CONTROL and READ/WRITE AMPLIFIER - For saturated digital recording and reading. TTL level data interface logic. Recording density up to 1600 FRPI. Read/Write electronics available separately.

ADDRESSABLE SEARCH SYSTEM BOARD - Zeros in on precise address with average access speed of 120 ips. Location is accurate within one audio word. Provisions for either keypad or computer entry of desired tape position.

- The exciting new **TEAC MT-2** series of Digital Cassette Transports is distributed in the U.S. exclusively by Triple I, Inc. Contact us for complete details.



4605 North Stiles
P.O. Box 18209
Oklahoma City, OK 73154
(405) 521-9000 TWX: 910-831-3286

Designer's Guide to FIBER OPTICS

A Designer's Guide to FIBER OPTICS

This comprehensive, authoritative guide covers all aspects of fiber-optic systems. Totalling 60 pages, it provides full understanding of the components, their key parameters and how they relate to fiber-optic system design.

- **Part 1** — Understanding glass fibers and their parameters
- **Part 2** — Matching sources and detectors to the fibers
- **Part 3** — System-design considerations
- **Part 4** — Building a fiber-optic system
- **Part 5** — What's available today: Fibers, connectors, sources and detectors

Send to:

Fiber Optic Reprints

EDN Magazine
221 Columbus Ave
Boston, MA 02116

Please send _____ copies of
Designer's Guide to Fiber Optics
— \$4.00 (\$5.00 Non-USA)

Check or money order must accompany each order. No COD. MA residents add 5% sales tax.

Send to:

Name _____

Title _____


Company _____

Address _____

City _____


State _____ Zip _____

New Products

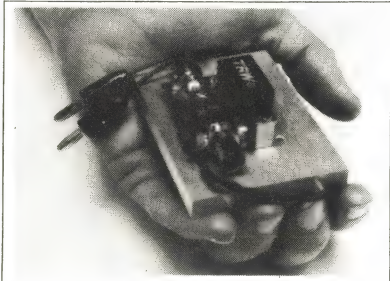

TEST PACKAGE. The Demonstrator consists of an evaluation fixture and one high-power hybrid amplifier. Two amplifiers—both having a 30-dB gain and operating over a 1- to 520-MHz range with ± 1 -dB flatness—are offered: CA2820 which operates on 16 to 28V and delivers 0.5W, and CA2812 which operates on 8 to 15V and outputs 0.3W. The test fixture includes a base plate for the heat sink, pc board with BNC connectors, banana jacks for connecting a power supply and gold-plated pin sockets for terminating the amplifier. **TRW Semiconductors**, 14520 Aviation Blvd, Lawndale, CA 90260. Phone (213) 679-4561. **Circle No 210**

ICs & SEMI-CONDUCTORS

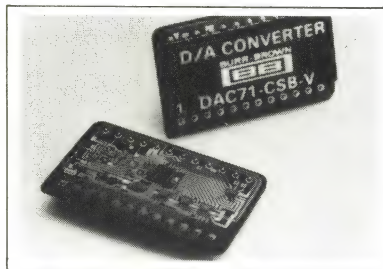

16-BIT DAC. Offering 16-bit, 4-digit resolution and $\pm 0.003\%$ linearity error, Model DAC71 settles in 10 μ sec to $\pm 0.003\%$ FS. Six models give a choice of complementary straight-binary, complementary offset-binary and complementary decimal input codes, as well as voltage (0 to 10V or ± 10 V) or current (0 to -2 -mA or ± 1 -mA) outputs. Gain drift is limited to ± 15 ppm/ $^{\circ}$ C over 0 to 70 $^{\circ}$ C. The 24-pin ceramic hybrid DIP requires ± 15 and ± 5 V supplies. \$39 (100). **Burr-Brown**, Box 11400, Tucson, AZ 85734. Phone (602) 746-1111. **Circle No 223**

DC-MOTOR SPEED CONTROL. Essentially a phased-locked-loop IC, the CS-175 is intended primarily for use with ac tachometer signals from dc motors. With this circuit in operation, the external compensation required to ensure motor stability dominates motor-speed errors. For multiple-speed requirements, pin-programmed speed ratios of 1.333:1, 1.5:1 and 2:1 are included. The 14-pin DIP contains a tachometer input comparator, a voltage-controlled one-shot, a phase comparator, a current-limited output amp and a reference voltage. Nominal supply voltage equals 6V dc. \$0.79 (1000). **Cherry Semiconductor Corp.**, 99 Bald Hill Rd, Cranston, RI 02920. Phone (401) 463-6000. **Circle No 224**

4-1/2-DIGIT COUNTER/DRIVERS. Featuring guaranteed counting up to 15 MHz (25 MHz typ), ICM7224 and 7225 use CMOS technology to achieve low-power operation (1 μ A at 10 kHz, 2 mA at 20 MHz). The devices operate as decade counters to 19999 or as timers



WIRE FOR WIRE-WRAPPING



CUT TO LENGTH AND PRE-STRIPPED ON BOTH ENDS

AWG 30 (0.25MM) KYNAR WIRE					AWG 28 (0.32MM) KYNAR WIRE					AWG 26 (0.40MM) KYNAR WIRE				
INSULATION DIAMETER: 0.195 INCH (0.50MM) STRIP-OFF LENGTH BOTH ENDS 1 INCH (25MM) 500 WIRES PER PACKAGE					INSULATION DIAMETER: 0.23 INCH (0.59MM) STRIP-OFF LENGTH BOTH ENDS 1 INCH (25MM) 500 WIRES PER PACKAGE					INSULATION DIAMETER: 0.27 INCH (0.69MM) STRIP-OFF LENGTH BOTH ENDS 1 INCH (25MM) 500 WIRES PER PACKAGE				
LENGTH "L" INCH	BLUE PART NO.	WHITE PART NO.	YELLOW PART NO.	PRICE PER 500	BLUE PART NO.	WHITE PART NO.	YELLOW PART NO.	PRICE PER 500		BLUE PART NO.	WHITE PART NO.	YELLOW PART NO.	PRICE PER 500	
1	30B-010	30W-010	30Y-010	\$4.88	28B-010	28W-010	28Y-010	\$5.25		26B-010	26W-010	26Y-010	\$5.75	
1.5	30B-015	30W-015	30Y-015	5.19	28B-015	28W-015	28Y-015	5.63		26B-015	26W-015	26Y-015	6.23	
2	30B-020	30W-020	30Y-020	5.50	28B-020	28W-020	28Y-020	6.00		26B-020	26W-020	26Y-020	6.68	
2.5	30B-025	30W-025	30Y-025	5.82	28B-025	28W-025	28Y-025	6.38		26B-025	26W-025	26Y-025	7.13	
3	30B-030	30W-030	30Y-030	6.13	28B-030	28W-030	28Y-030	6.75		26B-030	26W-030	26Y-030	7.60	
3.5	30B-035	30W-035	30Y-035	6.44	28B-035	28W-035	28Y-035	7.13		26B-035	26W-035	26Y-035	8.05	
4	30B-040	30W-040	30Y-040	6.75	28B-040	28W-040	28Y-040	7.50		26B-040	26W-040	26Y-040	8.50	
4.5	30B-045	30W-045	30Y-045	7.07	28B-045	28W-045	28Y-045	7.87		26B-045	26W-045	26Y-045	8.98	
5	30B-050	30W-050	30Y-050	7.38	28B-050	28W-050	28Y-050	8.25		26B-050	26W-050	26Y-050	9.43	
6	30B-060	30W-060	30Y-060	8.00	28B-060	28W-060	28Y-060	9.00		26B-060	26W-060	26Y-060	10.35	
7	30B-070	30W-070	30Y-070	8.63	28B-070	28W-070	28Y-070	9.75		26B-070	26W-070	26Y-070	11.25	
8	30B-080	30W-080	30Y-080	9.25	28B-080	28W-080	28Y-080	10.50		26B-080	26W-080	26Y-080	12.18	
9	30B-090	30W-090	30Y-090	9.88	28B-090	28W-090	28Y-090	11.25		26B-090	26W-090	26Y-090	13.55	
10	30B-100	30W-100	30Y-100	10.50	28B-100	28W-100	28Y-100	12.00		26B-100	26W-100	26Y-100	14.00	

ROLLS OF WIRE

100 ft. roll	R30B-0100	R30W-0100	R30Y-0100	\$3.65	R28B-0100	R28W-0100	R28Y-0100	\$4.05	R26B-0100	R26W-0100	R26Y-0100	\$4.35
500 ft. roll	R30B-0500	R30W-0500	R30Y-0500	10.40	R28B-0500	R28W-0500	R28Y-0500	12.85	R26B-0500	R26W-0500	R26Y-0500	13.80
1000 ft. roll	R30B-1000	R30W-1000	R30Y-1000	16.82	R28B-1000	R28W-1000	R28Y-1000	21.10	R26B-1000	R26W-1000	R26Y-1000	23.15

© KYNAR - PENNALT

MINIMUM BILLING \$25.00.

ADD SHIPPING CHARGE \$1.00.


NEW YORK RESIDENTS ADD APPLICABLE TAX.

OK MACHINE & TOOL CORPORATION

3455 CONNER STREET, BRONX, N.Y. 10475 (212) 994-6600 Telex 125091

New Products

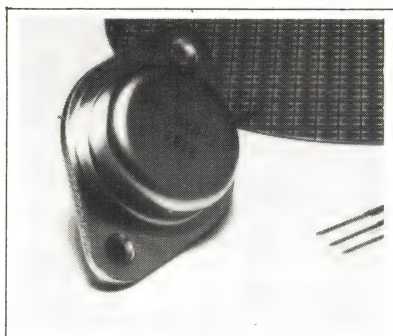
to 15959; Schmitt-trigger input assures accurate counting. The 7225 LED-driver has direct, nonmultiplexed, common-anode 8-mA segment drivers. The 7224 LCD version has an on-board backplane RC oscillator. Minimum operating voltages are 3V (7224) and 4V (7225). ICM7224, \$7 (100); ICM7225, \$5.30. **Intersil Inc.**, 10710 N Tantau Ave, Cupertino, CA 95014. Phone (408) 996-5000. **Circle No 225**



POWER MOSFETs. VN12 n-channel devices come with 40, 60, 80 and 90V ratings. Housed in a TO-3 package, the transistors supply 16A continuously or 32A pulsed. ON resistance of 0.25Ω and switching speed of <50 nsec make these devices interchangeable with IRF 100 units, and a gate threshold-voltage range of 0.8 to 2.5V simplifies TTL or MOS interfacing. A companion p-channel series, the VP12, offers the same voltage ratings. Units in this family supply 10A continuously or 30A pulsed; gate threshold voltage ranges from 1.0 to 3.0V. 80V VN12, \$12 (1000); 80V VP12, \$15. **Supertex Inc.**, 1225 Bordeaux Dr, Sunnyvale, CA 94086. Phone (408) 744-0100. **Circle No 226**

10-BIT DAC IC. Accepting TTL-compatible inputs, the DAC-IC10B features $\pm 1/2$ -LSB worst-case linearity error. An external reference current programs the device's scale factor and can be varied over a 4:1 range for multiplying operation. Output currents of 0 to 4 mA settle in 250 nsec to $1/2$ LSB. Output compliance is -2.5 V to $+0.2$ V, and gain TC is 20 ppm/ $^{\circ}$ C. The 16-pin ceramic DIP requires $+5$ V at 18 mA and -15 V at 20 mA. From \$14.50. Delivery, 4 wks. **Datel Systems Inc.**, 11 Cabot Rd, Mansfield, MA 02048. Phone (617) 828-8000, Ext 124. **Circle No 227**

LOW-EMI SWITCHING NPNs. Combining the economy of the TO-3 package with the versatility of an isolated-collector design, this family of transistors addresses problems encountered in high-voltage switching circuits. A reduction of collector-to-base capacitance reduces conducted interference by 20 to 30 dB; other benefits include reduced ground-loop currents, lowered assembly costs (no insulators required) and reduced shock hazards. V_{CE0} specs range from 200 to 450V; I_{CS} from 10 to 30A. \$7.10 to \$18.40 (100). **General Semiconductor Industries Inc.**, Box 3078, Tempe, AZ 85281. Phone (602) 968-3101. **Circle No 228**

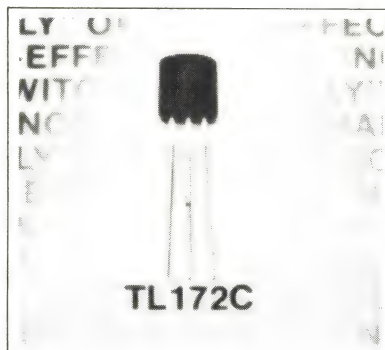


HALL-EFFECT SWITCH. Containing a Hall-effect sensor, signal-conditioning and hysteresis functions and an output transistor, the TL172C senses the presence of a magnetic field. A field of sufficient strength causes the output to switch from a high-impedance to a low-impedance state. \$0.43 (100). **Texas Instruments Inc.**, Box 225012, MS 308, Dallas, TX 75265. Phone (214) 238-5908. **Circle No 229**

LOW-COST ADC. For use with TMS-1000-type μ Cs, the TL507C contains a 7-bit synchronous counter, a binary-weighted resistor ladder, a summing amp, two comparators, a buffer amp, an internal regulator and logic circuitry. Using a single-slope conversion technique, the 7-bit-resolution, 8-pin DIP outputs a pulse whose duration is proportional to the analog input. Conversion speed equals about 1 msec. The unit operates on 8 to 18V from unregulated supplies or 3.5 to 6V from regulated supplies. \$0.65 (100). **Texas Instruments Inc.**, Box 225012, MS 308, Dallas, TX 75265. Phone (214) 238-5908. **Circle No 230**

SIEMENS

Economy DIP Tantalum Capacitors

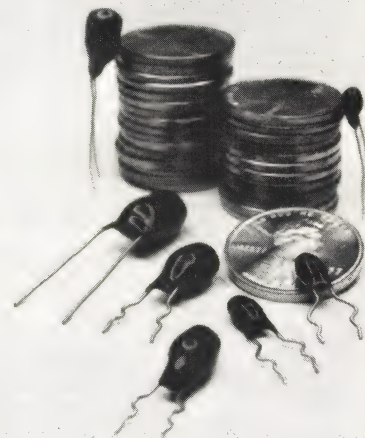


Siemens new ST841 and ST842 Sub-miniature Epoxy Coated Solid Tantalum Capacitors are the economical answer to Tantalum Capacitor applications.

Features:

- Capacity Ranges from 0.1μ F thru 680μ F
- Tolerances of 5, 10, or 20%
- Eight categories from 3 to 50 Volt
- Lead Styles of straight or "Lock-in" crimp
- Lead Spacings of 0.1 or 0.2 inch are available
- Manufactured in U.S.


Typical Impedance vs. Frequency @ 25°C.

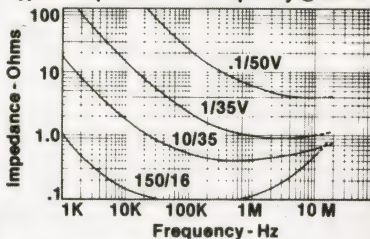

Siemens Corporation
Components Group
186 Wood Avenue South
Iselin, New Jersey 08830

Fluke Sponsors New Series:

"One Great Family"

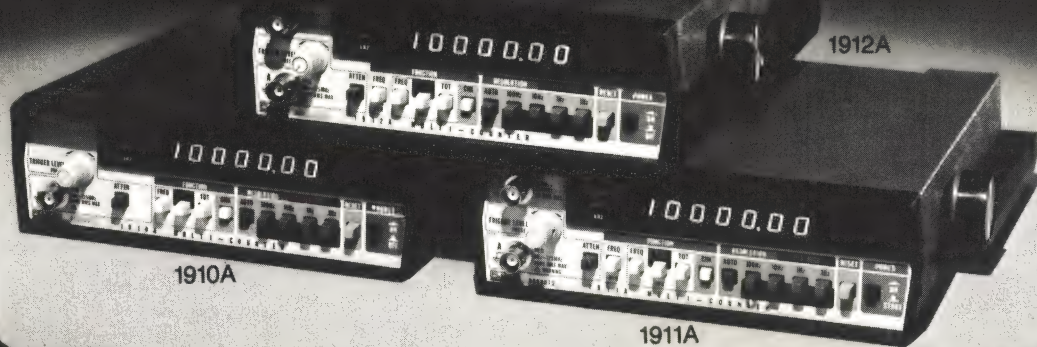

Tired of Reruns?

Fluke counters with a new series in the 5 Hz-520 MHz/time slot.

If you're paying over \$345 for a counter and getting frequency only, tune in on our new 1900-series of priced-right multicounters.

Five different models offer both time *and* frequency, with award-worthy performance and features; the ratings are terrific!

New Time and Frequency.


Last year's hit, the model 1900A, set the stage for this new series of multicounters by offering frequency, period, period average and totalize *standard* in one great counter.

Now all models in the series offer comparable features and value, with autoranging and autoreset as well.

Most models feature a trigger level control and battery option for reliable field use or line-cord-free bench operation. All typically have a 15 mV sensitivity (guaranteed on most!), plus a 0.5 ppm/month time base for long-term stability.

The Price is Right.

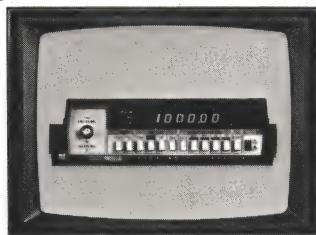From this shared base of solid performance features,



1900A

we've built a series of counters with one model just right for your needs.

The new **1912A**, with a 520 MHz range and an extensive package of standard features, offers more capability for \$620 than you're likely to find anywhere. For 250 MHz measurement perfection, the **1911A** multicounter is a best-buy for only \$495.

For lower frequency (125 MHz) applications, specify the **1910A** for \$395. The **1900A**, years ahead in value, has been reduced to \$345 for even more cost-effective 80 MHz measurement.

All models include true ± 1 count for improved resolution, and the 1911A and 1912A have "clean drop-out" implemented on the high frequency inputs. Most models include internal RFI shielding.

Tune In and Count.

Call (800) 426-0361*, toll free, for the location of the closest office or for complete technical literature. Then stop in for the great family picture, and review the extensive option list for better TCXOs, data outputs, and more. John Fluke Mfg. Co., Inc., P.O. Box 43210, Mountlake Terrace, WA 98043.

Prices U.S. only.

* Alaska, Hawaii and Washington residents please call (206) 774-2481.

Command Performance: Demand Fluke Multicounters.



7501-1900S

For literature Circle no 94
For demonstration Circle no 119

LAMBDA ANNOUNCES THE WORLD'S ONLY 8 AMP MONOLITHIC VOLTAGE REGULATOR

**LSI REGULATOR WITH
OVER 1000 CIRCUITS.**



**A COMPLETE LINE OF VOLTAGE REGULATORS
1.5a, 2a, 3a, 5a AND NOW 8a.**

△ LAMBDA SEMICONDUCTORS

LAMBDA LAS 3905, 8 AMP, 80 WATT MONOLITHIC POSITIVE VOLTAGE REGULATORS

ABSOLUTE MAXIMUM RATINGS

PARAMETER	SYMBOL	MINI-MUM	MAXI-MUM	UNITS
Input Voltage	V_{IN}	0	25 (1)	VOLTS
Input/Output Differential	$V_{IN}-V_{OUT}$	0	20 (1)	VOLTS
Power Dissipation @ $T_C \leq 94^\circ\text{C}$	P_D		80 (1) (2) (3)	WATTS
Thermal Resistance Junction To Case	θ_{JC}		0.7	$^\circ\text{C/WATT}$
Operating Junction Temperature Range	T_J	-55	150	$^\circ\text{C}$
Storage Temperature Range	T_{STG}	-65	150	$^\circ\text{C}$
Lead Temperature (Soldering, 60 Seconds Time Limit)	T_{LEAD}		300	$^\circ\text{C}$

Description

8 amp positive regulator

The LAS-3900 series voltage regulators are monolithic integrated circuits designed for use in applications requiring a well regulated positive output voltage. Outstanding features include full power usage up to 8.0 amperes of load variation, internal current limiting, thermal shutdown, and safe area protection on the chip, providing protection of the series pass Darlington, under most operating conditions. In addition, a sense terminal is provided for elimination of voltage drop problems at high currents. Hermetically sealed copper TO-3 packages are utilized for high reliability and low thermal resistance when used with an appropriate heat sink. A low-noise temperature-stable diode reference is the key design factor insuring excellent temperature regulation of the LAS-3900 series. This coupled to a very low output impedance insures superior performance and load regulation.

The LAS-3900 series of four terminal regulators is available in a fixed output voltage tolerance of $\pm 5\%$ with a nominal output voltage of +5 volts.

- (1) The maximum input voltage of the LAS-3900 Series is limited by the maximum input-output differential, maximum power dissipation, or the maximum current limit safe operating area, whichever is less.
- (2) For operation above 94°C T_{CASE} , derate @ $1.42 \text{ watt}/^\circ\text{C}$.
- (3) In case of a short circuit, the second breakdown protection designed in this regulator may require the removal of the input voltage to re-start the regulator.

Regulator Performance Specifications

Input voltage test condions are as follows: $V_1 = V_o + 3 \text{ Volts}$, $V_2 = V_o + 10 \text{ Volts}$, $V_3 = V_o + 150 \text{ volts}$, or the maximum input whichever is less.

TEST CONDITIONS

PARAMETER	SYMBOL	V_{IN}	I_o	T_J	MIN	MAX	UNITS
Input Voltage	V_{IN}		10MA.		$V_o+2.6$	25(5)	.Volts
Output Voltage	V_o	V_1 to V_2	10MA to 8.0 Amp	25°C	$0.95[V_o]$ (1)	$1.05[V_o]$.Volts
Input-Output Differential	$V_{IN}-V_o$		8.0 Amp	0°C to $+125^\circ\text{C}$	2.6		.Volts
Output Current	I_o	V_1	0.5 Amp	0°C to $+125^\circ\text{C}$		20.	.Volts
Line Regulation (2)	$\text{REG}(\text{LINE})$	V_1 to V_3	5A	25°C	0	8.0	.Amps
Load Regulation (2)	$\text{REG}(\text{LOAD})$	V_1	10MA to 8.0 Amp	25°C		2.0	$\%V_o$
Quiescent Current	I_Q	V_1	Output/Open	25°C		0.6	$\%V_o$
Quiescent Current Line	$I_Q(\text{LINE})$	V_1 to V_2	10MA.	25°C		20.	.MA
Quiescent Current Load	$I_Q(\text{LOAD})$	V_1	10MA to 8.0 Amp	25°C		5.	.MA
Current Limit	I_{LIM}	V_o+5V		25°C		14.	.Amps
Short Circuit Current	I_S	V_o+5V		25°C		14.	.Amps
Temperature Coefficient	T_C	V_1	0.1 Amp	0°C to $+125^\circ\text{C}$		0.03	$\%V_o/^\circ\text{C}$
Output Noise Voltage	V_N	V_1	0.1 Amp	0°C to $+125^\circ\text{C}$		10(3)	$\mu\text{Vrms}/V$
Ripple Attenuation	RA	V_1	2.0 Amp	0°C to $+125^\circ\text{C}$	60(4)		.dB

- (1) Nominal output voltages are specified under ordering information.
- (2) Instantaneous regulation, average chip temperature changes must be accounted for separately.
- (3) $BW=10\text{Hz} - 100 \text{ Hz}$.


- (4) Ripple attenuation is specified for a 1 VRMS, 120 Hz input ripple. Ripple attenuation is a minimum of 60 dB at a 5 volt output.
- (5) The maximum input voltage of the LAS-3900 series is limited by maximum input-output differential voltage, maximum power dissipation, or the current limit-SOA, whichever is less.

Price List


NOMINAL V_o VOLTS	DEVICE PART NO.	QTY 1-24	QTY 25-49	QTY 50-99	QTY 100-249	QTY 250-499	QTY 500-999	QTY 1000-2499	QTY 2500-4999
5	LAS-3905	\$18.00	\$16.50	\$15.75	\$14.75	\$13.00	\$11.90	\$10.65	\$10.00

CONTACT THE FACTORY FOR HIGHER QUANTITY PRICES. DEVICE CONFIGURATIONS, SPECIFICATIONS, AND PRICES SUBJECT TO CHANGE WITHOUT NOTICE


Operational Data

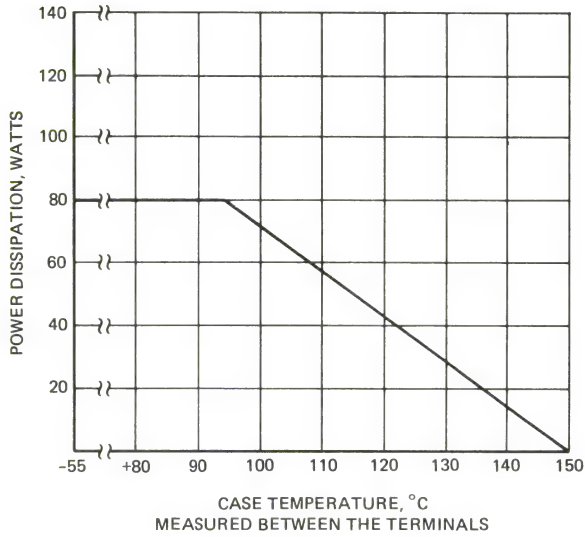


POWER DERATING

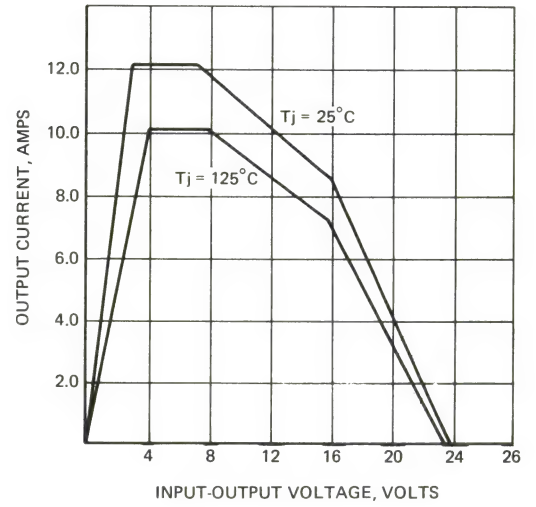

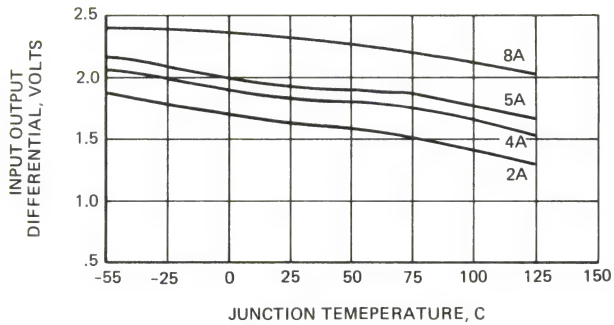
TYPICAL CURRENT LIMIT
VS INPUT OUTPUT
VOLTAGE DIFFERENTIAL



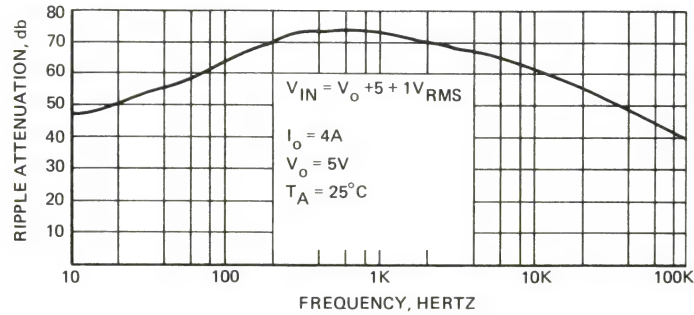TYPICAL INPUT-OUTPUT
DIFFERENTIAL VOLTAGE vs
JUNCTION TEMPERATURE




TYPICAL RIPPLE ATTENUATION
vs FREQUENCY

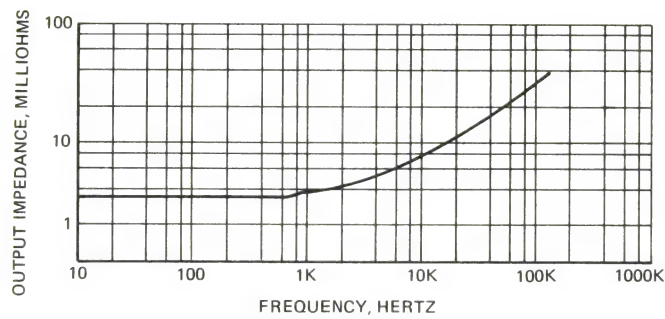


TYPICAL OUTPUT IMPEDANCE
vs FREQUENCY



Outline Drawing

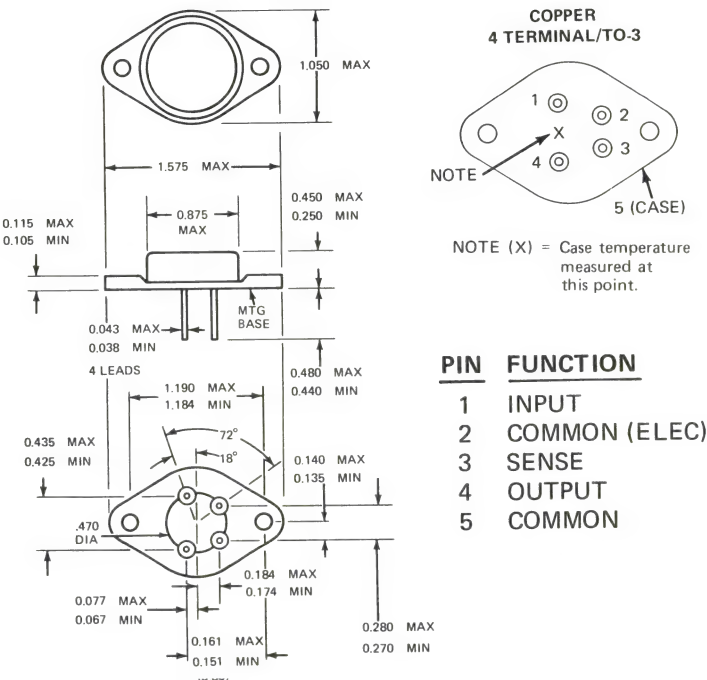

Functional Block Diagram

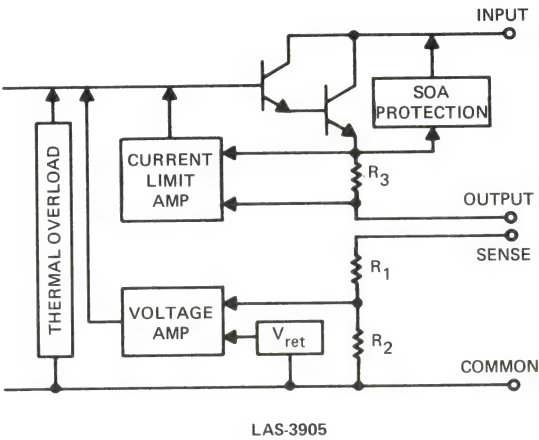

Typical Applications

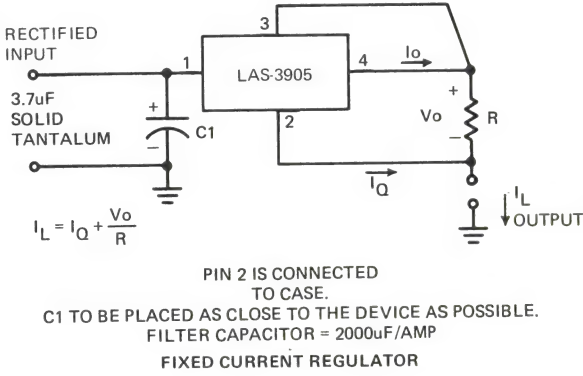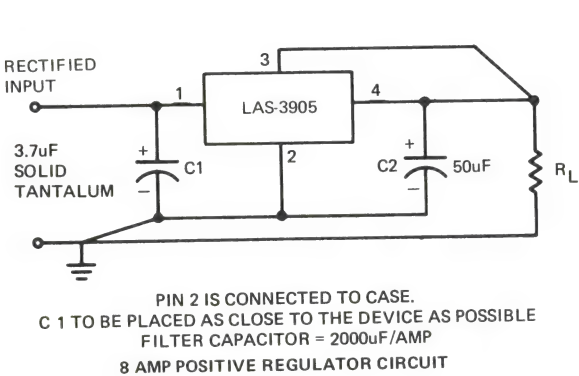


Lambda staffed sales and service offices

POWER SEMICONDUCTORS
DESIGNED, DEVELOPED
AND MANUFACTURED BY

ATLANTIC REGION
Melville, New York 11747
515 Broad Hollow Road
Tel. 516-694-4200
TWX: 510-224-6484

SOUTH-WESTERN REGION
Corpus Christi, Texas 78410
121 International Drive
Tel. 512-883-6251

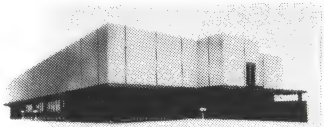FAR-WESTERN REGION
Cerritos, Ca 90701
12607 Hidden Creek Way Suite J
Tel. 213-926-0941
TWX: 910-346-7649




LAMBDA ELECTRONICS
DIVISION of **Veeco** INSTRUMENTS INC.

NORTH-EASTERN REGION
Lexington, Massachusetts 02173
2 Militia Drive
Tel. 617-861-8585
TWX: 710-326-7558

MID-WESTERN REGION
Arlington Heights, Ill. 60005
2420 East Oakton St., Unit Q
Tel. 312-593-2550
TWX: 910-222-2856


NORTH-WESTERN REGION
Sunnyvale, Ca 94086
599 N. Mathilda Ave.
Tel. 408-738-2514
TWX: 910-339-9243

New Products

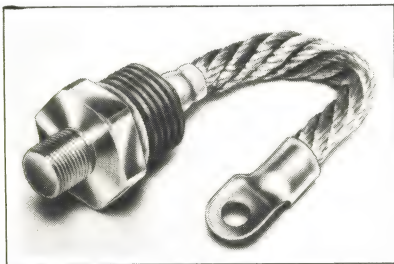

HIGH-POWER RECTIFIER. Capable of withstanding a single-cycle surge current of 9000A, Model SKN-40 also passes an average forward current of 400A (900A max). The unit features a reverse voltage in the 1800 to 3000V range and a V_f of 1.45V max. Each part comes with a ribbed isolator, which allows fault-free operation in high-pollution atmospheres. Junction-to-case thermal resistance equals 0.11 °C/W. **Semikron International Inc.**, Box 83, Hudson, NH 03051. Phone (603) 883-8102. **Circle No 231**


SEVEN-SEGMENT DRIVER. Pin compatible with 7447, 9374 and 8674 drivers, the NE 586 common-anode LED decoder/driver features 25-mA constant-current outputs; LOW-loading, bus-compatible, latched BCD inputs; and ripple blanking on leading/trailing zeros. You can specify alternative fonts because ROM implements the segment decoding. The chip requires a 4.75 to 5.25V (7V max) supply, but its inputs withstand 15V. \$1.78 (100). **Signetics**, Box 9052, Sunnyvale, CA 94086. Phone (408) 739-7700. **Circle No 232**

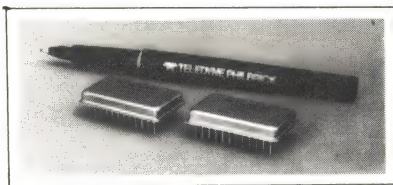

HI-REL V/F CONVERTERS. Processed to MIL-STD-883, Models 4731 (10 kHz) and 4733 (100 kHz) have a full-scale nonlinearity of less than $\pm 0.005\%$ over the -25 to $+125^\circ\text{C}$ range. These hybrid units handle positive, negative and differential input signals, using ± 9 to $\pm 18\text{V}$ supplies. Guaranteed specs include TC of ± 50 ppm/°C, V_{OS} TC of ± 100 $\mu\text{V}/^\circ\text{C}$ and 100-dB dynamic range. A current input resolves levels as low as 1 nA, making possible operation with full-scale V_{in} s of <250 mV to $>100\text{V}$.

For more information, Circle No 95

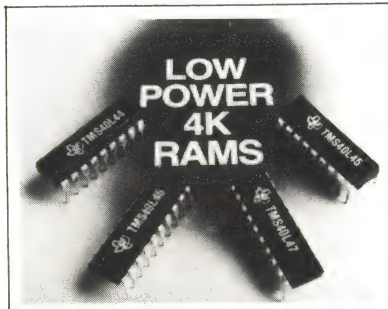4731, \$125; 4733, \$135. **Teledyne Philbrick**, Allied Dr at Rte 128, Dedham, MA 02026. Phone (617) 329-1600. **Circle No 233**




LOW-POWER RAMS. Models TMS40L44 and TMS40L46 ($4\text{k} \times 1$) and TMS40L45 and TMS40L47 ($1\text{k} \times 4$) come in three speed ranges—450-, 250- and 200-nsec maximum access times. Fully static units, they operate from single +5V supplies and are TTL compatible. Typical power dissipations for the 200-nsec 40L44 and 40L45 units are 200 and 250 mW, respectively. The 40L46 and 40L47 units have a power-down feature providing 6-mW typical dissipation. The 40L44 and 40L45 units come in 18-pin DIPs, the others in 20-pin packages. 200-nsec units, \$11.40 (100); 450-nsec units, \$6.90. **Texas Instruments Inc.**, Box 1443, MS 669, Houston, TX 77001. Phone (713) 494-5115. **Circle No 234**

TEMPERATURE CONTROLLER. Accepting inputs directly from a thermistor, the AY-3-1270 measures temperatures arising in domestic and commercial equipment and displays them on either LED or LCD panels. Its 40-pin DIP includes a power-failure detector and warning indicator for out-of-range conditions. Two control outputs can be used for external alarm circuitry or compressor control. One output operates at the temperature setpoint plus hysteresis (0, 0.2, 0.4, 0.8, 2, 4 or 8°C), the other at setpoint minus hysteresis. Accuracy of temperature sensing is $\pm 1^\circ\text{C}$, while the temperature range depends on the thermistor chosen. The chip requires one supply voltage between 7.2 and 10.8V. \$8 (100). **General Instrument Corp.**, 600 W John St, Hicksville, NY 11802. Phone (516) 733-3606. **Circle No 235**

SIEMENS

New Zener Wall Chart

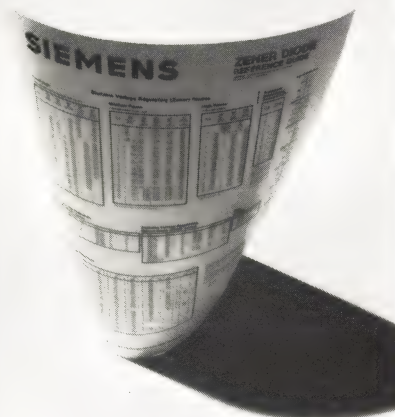A "must" for all up-to-date files...yours for the asking from Siemens.



To see at a glance the full line of Siemens Zener Diodes manufactured in Scottsdale, Arizona...you should have this new chart. It's a real time-saver.

Siemens is the world's leading supplier of Hi-Rel Zener Diodes. Almost without exception, every major U.S. military and space program used Siemens Zeners for the reliability they provide in critical environments.

In addition to the Hi-Rel Zeners, Siemens supplies a full line of commercial zeners, rectifiers and transient suppression zeners.

To have our Zener wall chart sent to you without charge, just circle the reader service number below or write to:

Siemens Corporation
Components Group
186 Wood Avenue South
Iselin, New Jersey 08830

For more information, Circle No 96

25 MHz or 100 MHz? What Makes the Difference?

At Philips it's bandwidth and bandwidth alone. All of the most important standard features on our 100MHz scope are standard on our 25MHz. In fact we often talk 100MHz-customers into buying our 25MHz scope because they need our standard features, not our expanded bandwidth-which costs a mere \$1,000 extra.

Aside from costing \$1,000 less, the Philips PM3214 25MHz/2mV dual trace alternate time base scope gives you more for your money than any other 25MHz scope on the market.

Although its vertical bandwidth is 25MHz, it typically triggers to 40MHz or more. And it does so in the quick, convenient Auto mode.

When this Auto button is depressed the trigger level is automa-

tically held within peak to peak amplitude of the signal. If there's no signal a zero line is displayed. Triggering is instant and unambiguous for a wide variety of measurement conditions. For phase measurements the level can still be adjusted between the extremes of the signal amplitude. TV trigger is also fully automatic.

Fully calibrated delayed sweep shows the PM3214's comprehensive time base facilities. There is independent triggering for each time base, separate source selection and DC coupling for both sweeps, plus an

alternate time base mode. Good reasons the PM3214 can take the place of larger, more expensive scopes in the lab or field.

Priced at under \$1500*, the Philips PM3214 gives you more for your money- and no more than you need.



For More Facts or a Convincing Hands-On Demonstration,
use our toll-free number, (800) 631-7172 in the continental U.S. In New Jersey, please call collect, (201) 529-3800. Or contact Philips Test & Measuring Instruments, Inc., 85 McKee Drive, Mahwah, New Jersey 07430.


*U.S. Domestic Price Only.



Test & Measuring
Instruments

PHILIPS

Literature

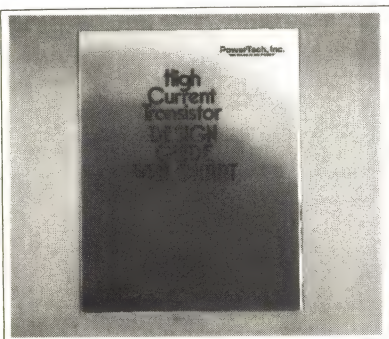

Power-transistor wall chart

This design-guide chart unfolds to colorfully illustrate the performance of 53 of the company's high-current power transistors. The chart depicts power-transistor and module anatomy, along with package options. It also provides specs and a list of applications. **PowerTech Inc.**, 0-02 Fair Lawn Ave, Fair Lawn, NJ 07410.

Circle No 236

New products highlight data-comm catalog

This latest "Black Box" edition features descriptions of the company's data communication devices including test sets, switches, interfaces, converters, stunt boxes, modems and modem eliminators, as well as cables and connectors. Along with coverage of 25 new products, the catalog presents specs, features, applications and prices of each device listed. **Expandor Inc.**, 400 Sainte Claire Plaza, Upper Saint Clair, PA 15241.

Circle No 237




Winchester-disc-drive technology primer

"Who's Selling Rifles to the Indians?" explains the evolution of the Winchester disc drive and covers the

differences between that technology and earlier innovations. A brief history traces development from IBM's RAMAC 305, with its 50 discs and 5M-byte capacity to today's single-disc Winchester drives having as much as 33M bytes of data storage. The pamphlet describes both track-and bit-density gains and improvements to disc-drive reliability. **Priam Corp.**, 20730 Valley Green Dr, Cupertino, CA 95014.

Circle No 238

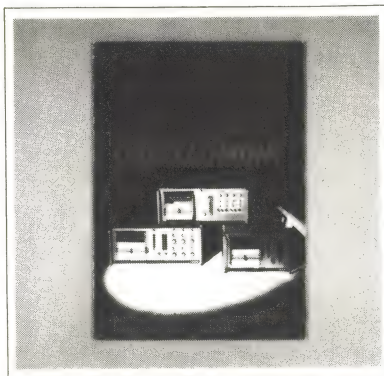

Liquid-jet oscillographs: Principles, applications

Through diagrams, photos and text, this 24-pg booklet explains the liquid-ink-jet printing principle used in the company's line of portable and benchtop oscillographs. Comprehensive specs for instruments employed in industrial maintenance and monitoring applications complete the brochure. **Siemens Corp.**, Measuring & Scientific Instruments Div, 2 Pin Oak Lane, Cherry Hill, NJ 08034.

Circle No 239


Note describes resistor pulse-handling capabilities

"Pulse Handling Capability of Wirewound Resistors," a 24-pg application booklet, explains how to pick the right wirewound resistor to withstand short-duration pulses. For pulses from 0.5 to 5 sec long, the pamphlet explains how to calculate the maximum energy that can be safely applied to the resistor. For pulses lasting less than 0.5 sec, the brochure offers a series of charts to help you determine if the calculated pulse energy is greater or less than a given resistor's rated energy. **TRW/IRC Resistors**, Box 1860, Boone, NC 28607.

Circle No 240

SIEMENS

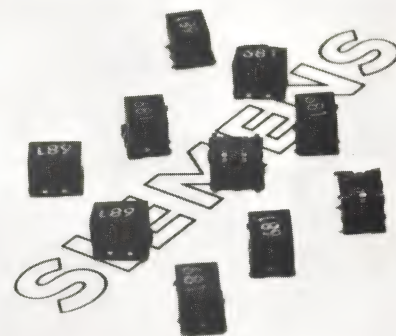Chip Inductors for thick or thin film circuits



Intended for use as D.C. Chokes in RFI filtering circuits.

Features and specs:

- Much smaller than comparable DC chokes
- Reduces labor costs-eliminates need for lead bending or clipping
- Compatible with reflow soldering techniques
- Inductance range from .1 μH to 470 μH
- Minimum Q of 40 for .1 μH to 50 for 470 μH
- Self resonant frequency to over 250 MHz
- DC current capability to 1 1/4 amps
- DC resistance as low as 60 m Ω

For further information on Siemens full line of Ferrites that offer a wide range of applications, write:

Siemens Corporation
Components Group
186 Wood Avenue South
Iselin, New Jersey 08830

For more information, Circle No 98

Literature



A potpourri of offerings for kit builders

The 96-pg Winter 1979 Heathkit catalog describes a variety of electronic kits in such areas as color TV, hi-fi components, amateur radio, test instruments, personal computers and weather instruments. New products in this issue include a dc to 35-MHz dual-trace, delayed-sweep scope; a rack-mounted AM/FM stereo tuner;


and a solid-state heat/cool setback unit for home energy saving. **Heath Co**, Benton Harbor, MI 49022.

Circle No 241

Extend storage capability with digital scopes

Bulletin 449-5 illustrates the advantages of digital-storage oscilloscopes compared with storage-tube models. The 6-pg publication presents specs on two of the company's portable dual-trace units, which are designed for flicker- and fade-free viewing of both long-term events and transients. **Gould Inc**, Instruments Div, 3631 Perkins Ave, Cleveland, OH 44114.

Circle No 242

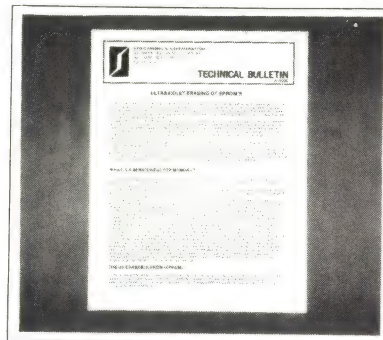

EPROM bulletin shows erase times

Spectronics Corp's "Ultraviolet Erasing of EPROMs" (A-78286) offers an in-depth discussion of erase times and contains tables listing the nominal erasing energy required for various popular EPROM types. A pair of charts show the erasing times required for simultaneous erasure of several EPROMs using the company's UV sources. Also described are the advantages of EPROMs and how they work. **Adco Electronics**, 2182 DuPont, Suite 222, Irvine, CA 92715.

Circle No 243

Learn what's new in electrical contacts

In addition to describing the company's electrical contacts, this 21-pg brochure lists properties of powder-metal contact materials, copper-base contact-support materials and the silver-braze alloys used for attaching contact tips to contact supports. Publication P102 also relates the particle sizes of tungsten and



OUR CRYSTALS AGE GRACEFULLY... AND PREDICTABLY.

Superior frequency control from the XTAL XPERTS • For example, at 65°C, many Reeves-Hoffman quartz crystal units change only 5 parts per hundred million per day. Many others hold the line at an even better figure. Or we can provide them merely to Mil spec. That's graceful aging.

Frequency stability for the long haul is one of the main reasons for crystal control...and one of the reasons for Reeves-Hoffman's leadership in crystal technology for over 35 years. The same meticulous care that we give our hi-rel crystals also goes into our commercial products—and only Reeves-Hoffman assures you in-house control of every manufacturing step. That's why we can offer coldweld sealing as a standard at no extra cost.

Call or write today for information on our complete line, including monolithic and discrete filter networks.

REEVES-HOFFMAN

DIVISION, DYNAMICS CORPORATION OF AMERICA

400 W. North St., Carlisle, PA 17013 U.S.A. Phone (717) 243-5929 • TWX 510-650-3510

© R-H


7205

For more information, Circle No 101

Literature

tungsten-carbide powders to the wear characteristics of silver-tungsten and silver-tungsten carbide contacts. The brochure provides weight-system conversion factors (troy, avoirdupois and metric), a table of crown heights for given contact diameters and face radii, application factors and an explanation of how order prices are adjusted to the market price of silver. **Advanced Metallurgy Inc.**, 1011 E Smithfield St, McKeesport, PA 15135.

Circle No 244

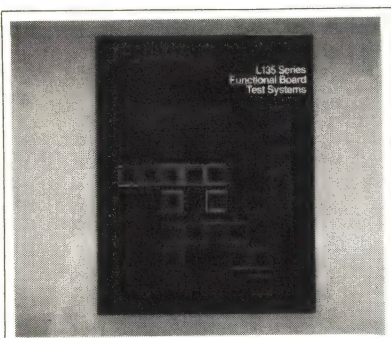

System expands into a series of board testers

A 4-pg brochure illustrates the L135 functional board-test systems, which serve a variety of production-line testing needs. The folder details the family's modular system architecture that permits users to move up to larger configurations and increase the number of testing modes with virtually no production-schedule disruptions. **Teradyne Inc.**, 183 Essex St, Boston, MA 02111.


Circle No 245

You can specify and order with instrumentation note

Catalog I highlights a line of instrumentation for the measurement, analysis and/or recording of power-line disturbances and power-system parameters. Other general-purpose instruments measure phase/gain, impedance, current voltage, Q and time/frequency. The brochure also describes the company's SERs (Sequence-of-Event recorders). Each product section lists features, supplies comprehensive details of the instruments and plug-ins, and, where applicable, performance curves. The last page lists company technical literature available upon request.

Dragnet Engineering Laboratories Inc., 2385 S Clinton Ave, South Plainfield, NJ 07080. Circle No 246

E-Z-HOOK® PROBLEM SOLVER NO. 5

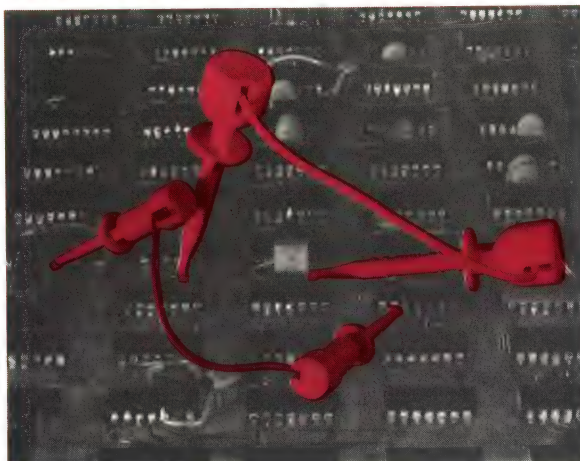

JUMPERS . . . OVER 65 CONFIGURATIONS EACH IN A WIDE VARIETY OF LENGTHS.

Construction: Most have One-Piece Conductor and Hook, either of Gold Plated BeCu or Nickel Silver are insulated to a single contact point to assure true meter readings. Heat and Chemical Resistant Nylon Bodies. Stainless Steel Springs. All units are field serviceable. **Lead Wires:** Insulated and matched to meet your testing needs. **Colors:** Blk, Brwn, Red, Orng, Yello, Green, Blue, Violet, Gray, White.

SEND FOR COMPLETE CATALOG AND PRICE LIST

E-Z-HOOK®
A DIVISION OF TEKTEST, INC.

MAILING ADDRESS: P.O. BOX 450
ARCADIA, CALIFORNIA 91006
(213) 446-6175 / TWX 910 582 1614


For more information, Circle No 102

325 ways to keep ahead of the game.

You need 24 enclosures. You phone your local source. They'll make them. But, it's all going to take a while. You live with it because you've always done it that way.

There's a better way. Bud. We have 325 distributors. There's one near you. He stocks Bud standard enclosures. If he shouldn't have what you want, no problem. We'll ship immediately from our warehouses in Willoughby or Phoenix.

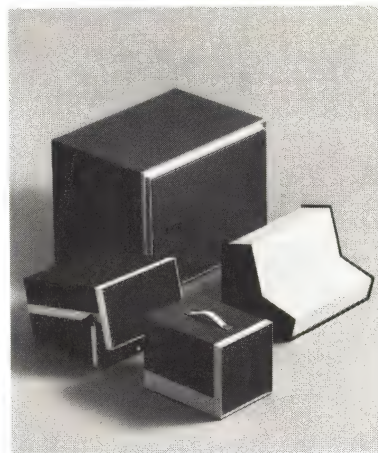We're the industry's largest. Why? The people we deal with realize the value of service. The service they get from Bud. Get the name of your local Bud distributor and with it, some service for a change. Bud Industries, Inc., 4605 E. 355th St., Willoughby, Ohio 44094. Phone: 216/946-3200. Bud West, Inc., 3838 N. 36th Ave., Phoenix, Arizona 85019. Phone: 602/269-3151.





Our small enclosures come in 31 designs, 181 sizes, 19 colors. And they're in stock.

Service. **BUD**

For more information, Circle No 103

Only from CPT

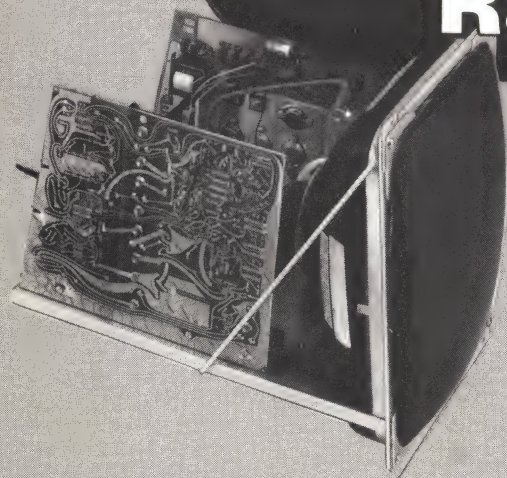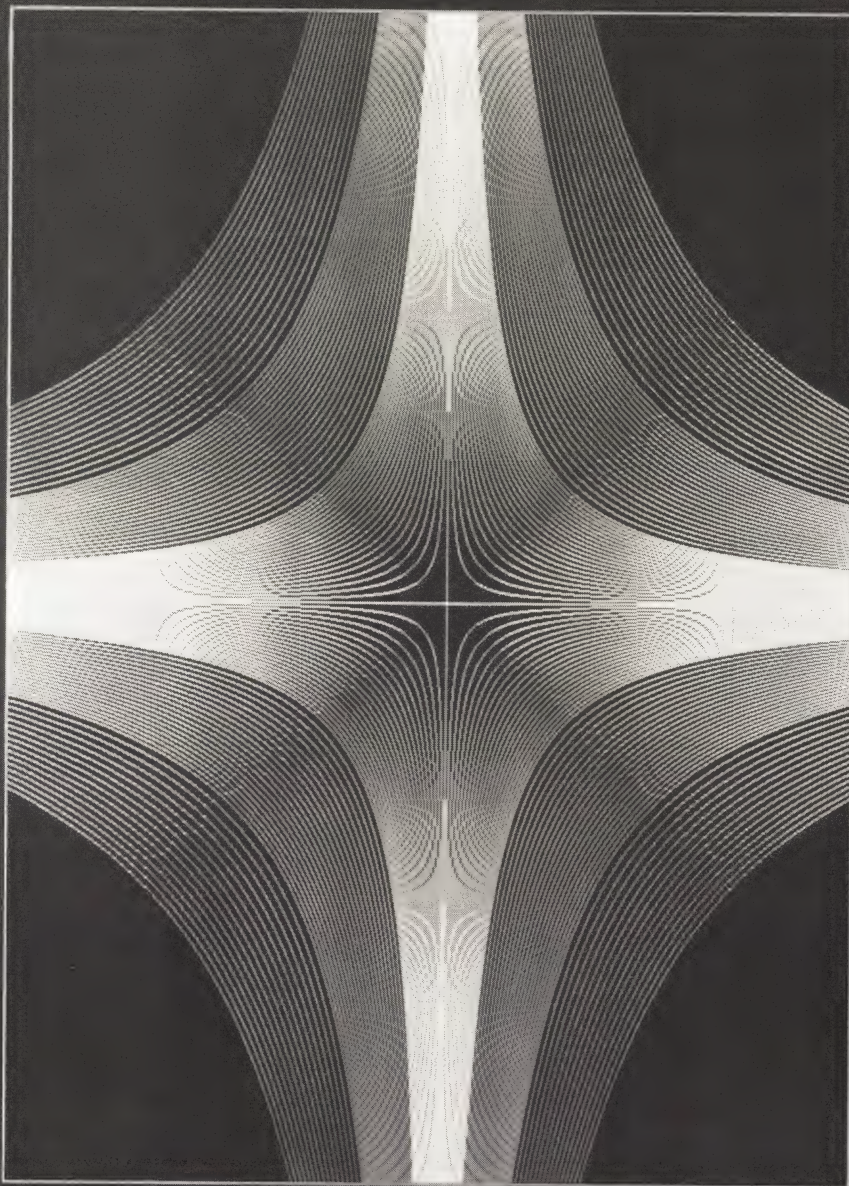

Raster-scan graphics as pretty as this picture.

But it's not just another pretty OEM data display module.

Consider:

- generates 1,024 X 768 pixel raster

- 105 megahertz band-width

- mono-chromatic

- non-interlaced raster scan




OEM SALES MANAGER
1001 SECOND STREET SOUTH
HOPKINS, MINNESOTA 55434
OR PHONE: (612) 935-0381

FOR MORE INFORMATION
OR A DEMONSTRATION WRITE:

WORD'S GETTING AROUND...FAST!

For more information, Circle No 115

Literature

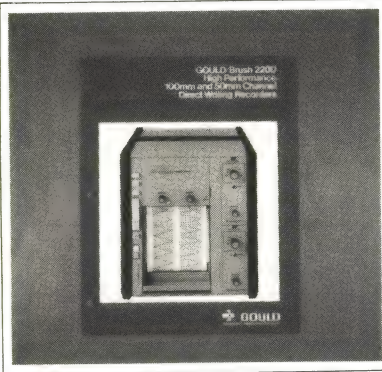

One- and 2-channel high-performance recorders

A photo in this 6-pg bulletin points out the major features of the 2200 Series of direct-writing recorders, and an actual chart sample depicts the recorders' resolution and trace fidelity. The brochure also supplies complete specs and options for the series. **Gould Inc.**, Instruments Div, 3631 Perkins Ave, Cleveland, OH 44114. **Circle No 247**


Low-pass filter offers 230 dB per octave

Providing information on the Model 752 programmable, dual low-pass anti-aliasing filter, this 4-pg data sheet describes the device as the closest approach to the ideal "brickwall" filter allowable by the present state of the art. Listed features include a rolloff rate, in each of two identical channels, of better than 115 db/octave (cascading permits 230 db/octave)—illustrated by three CRT traces. The brochure briefly describes such typical applications as band-limiting of analog signals before A/D conversion; signal conditioning; waveform analysis; noise studies; distortion measurement and data recording and playback. **Rockland Systems Corp.**, Rockleigh Industrial Park, Rockleigh, NJ 07647. **Circle No 248**

Varied applications for telemetry products

Twenty data sheets constitute this package, which details a complete line of receivers, transmitters, amplifiers, multiplexers and synthesizers. Each sheet begins with a short description of a product and its typical applications, then lists complete specs. **Communitronics Ltd.**, 1324 Motor Parkway, Hauppauge, NY 11787. **Circle No 249**

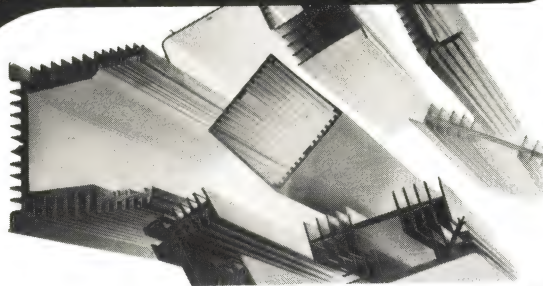Big Al sez: It's Precision Extrusions For HEAT SINKS



In this age of computers and computer oriented production machinery, the demand for fast, efficient, dependable dissipation of heat will continue to grow. Accordingly, designers will want to put more "custom" into custom extruded heat sinks. To the extent that the housing for this component will be the heat sink itself, Precision Extrusions not only extrudes, but also fabricates and anodizes heat sinks, and offers professional assistance in the design and engineering to suit each customer's individual requirements.

PE extrusion specialists pursue the most cost-effective way to meet each customer's requirements. This is the PLUS you get with PE heat sink extrusions.



Write or phone:

PRECISION EXTRUSIONS, INC.
721 East Green Street Bensenville, IL 60106
(312) 766-0340

Other offices in:
William, Walker & Assoc.
Minneapolis, Minn.
612-566-9880

Tom Hughes & Assoc.
Indianapolis, Ind.
317-846-5156

Jack Mossong & Assoc.
Nashville, Tenn.
615-834-5497


For more information, Circle No 104

98 ways to save some embarrassment.

You need enclosures for a new system. You explain everything to your local source. Their prototypes miss the mark. You explain again. Hope it works. If not, embarrassment will be the least of your worries.

There's a better way. Bud. To the point, our 98 sales representatives. They will give you experienced guidance on what standard Bud enclosure will house your system. Advise you on new products, for example, see-thru plexiglass doors for upright racks. Counsel you on how Bud accessories help make systems even more effective.

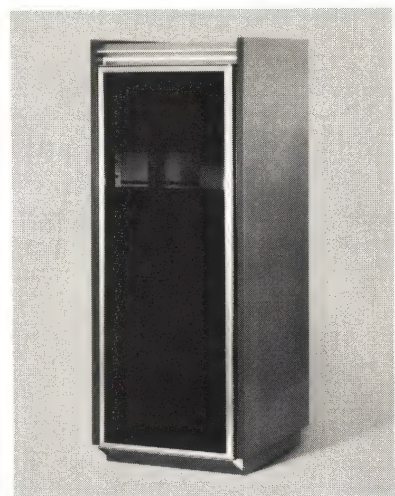
Get the name of your Bud sales representative and get some correct advice for a change. Bud Industries, Inc., 4605 E. 355th St., Willoughby, Ohio 44094. Phone: 216/946-3200. Bud West, Inc., 3838 N. 36th Ave., Phoenix, Arizona 85019. Phone: 602/269-3151.



Write for clear-cut facts on the new Bud plexiglass doors.


Dependability. BUD

For more information, Circle No 105

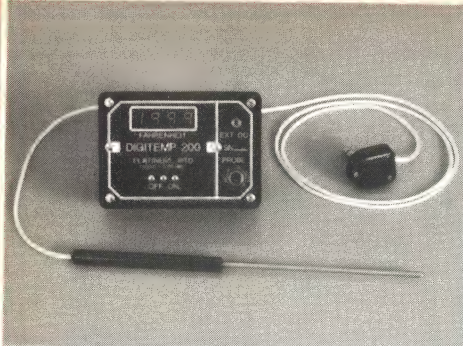

DIGITEMP 200 PLATINUM RTD DIGITAL THERMOMETER spans -328°F to $+1562^{\circ}\text{F}$ with 0.2% accuracy and 1°F resolution. Also available is the **DIGITEMP 100** digital meter which uses a Semiconductor Type sensor and spans -55°C to $+150^{\circ}\text{C}$ with 0.5°C accuracy and 0.1°C resolution. A variety of probes are available for either meter, and both may be ordered in either Fahrenheit or Centigrade. Prices start at \$155. **MID-CONTINENT COMMUNICATIONS CORP.**, 3618A Noland Court, Independence, Mo. 64055. (816) 461-1334.

For more information, Circle No 106

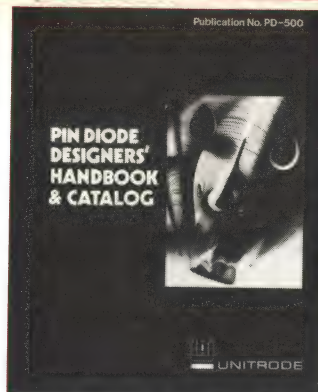

PIN Diode Handbook and Catalog For RF Engineers

Complete catalog of Unitrode's PIN Diode data. Including selection guide relating PIN Diode types to applications such as: common RF switches, attenuators, transmit-receive switches, and phase shifters. Bias, thermal conditions, and distortion are discussed. For your copy: contact Unitrode Corporation, 580 Pleasant St., Watertown, MA 02172, (617) 926-0404.

For more information, Circle No 107

RENT THIS SPACE

- EDN 1/9-page ads feature:
- Color border highlighting
 - Always next to editorial
 - Rate: \$350 per insertion
 - Reaches over 100,000 engineers
- For details contact:
Donna DiChiara
EDN
221 Columbus Ave.
Boston, MA 02116

Literature

Handbook explains workings of mag-tape recorders

"Modern Instrumentation Tape Recording" discusses: the physics of magnetic-tape recording; media, means and mechanisms for recording and reproduction; direct, FM and digital recording of analog signals; tape-movement systems; tape and tape heads; and selection and specification of instrumentation tape recorders. The last chapter of the 140-pg opus highlights comprehensive applications. \$6. **EMI Technology Inc.**, 100 Research Dr, Stamford, CT 06906.

INQUIRE DIRECT

Catalog chock full of test accessories


New product descriptions combine with details of previously offered electronic-test-accessory families in this 100-pg document. Accessories described include molded patch cords, cable assemblies, test-socket adapters, molded test leads, plugs, connecting cords, probes and holders. Photographs and drawings accompany ordering information, BNC- and triaxial-cable assembly procedures and two tables for metric and temperature conversions. **ITT Pomona Electronics**, 1500 E Ninth St, Pomona, CA 91766.

Circle No 250

A power supply for every need


Containing 32 pages of helpful application hints and a design tutorial, this 144-pg catalog also describes the company's power supply line. The booklet groups the products by shared characteristics: modular/linear, modular/ferroresonant, modular/switching, laboratory/systems, high speed/unipolar, high speed/bipolar, and programmer and interfaces. It lists accessories and hardware, and also offers a glossary of power-supply terms. **Kepeco Inc.**, 131-38 Sanford Ave, Flushing, NY 11352.

Circle No 251

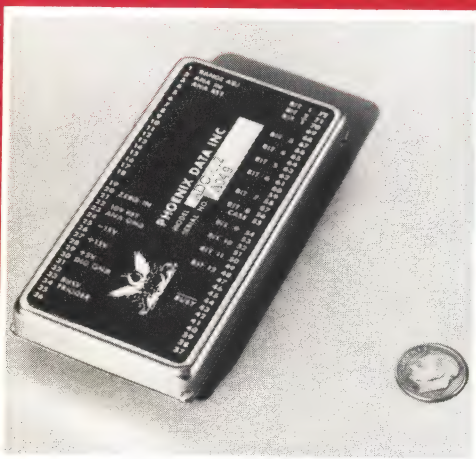

ALL 6 NEW SERIES OF ENCASED A/D CONVERTERS—ADC 1300 thru ADC 1800—employ the highly reliable and stable voltage switching successive approximation techniques. Features include 8 thru 14 bit resolution; conversion time: 2 μsec : 8 bits; 4 μsec : 12 bits; 10 μsec : 14 bits. All are RFI and EMI shielded with guaranteed monotonicity. No adjustments necessary over 10°C to 40°C range with optional temp. ranges from -55°C to 90°C ambient. **Phoenix Data, Inc.**, 3384 W. Osborn, Phoenix, AZ 85017. PH 602/278-8528 TWX 910-951-1364

For more information, Circle No 108

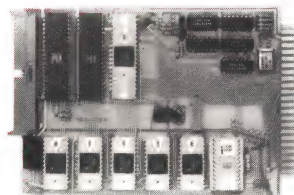

SINGLE BOARD COMPUTER \$99.50*

with 6800 MPU, 6850 serial I/O, 2 6820 parallel I/O (32 lines), 512 RAM, socket for 2708, 2716, EPROM. Interface modules for industrial control, data acquisition, lab instrumentation, on 44 pin $4\frac{1}{2}'' \times 6\frac{1}{2}''$ PCB's. RAM, ROM, CMOS RAM/battery, A/D, D/A, Driver/Sensor, Serial I/O, Parallel I/O, Counter/Timer, IEEE 488 GPIB, floppy controller.

*OEM (500 piece) price

WINTER Corp.
902 N. 9th Street
Lafayette, IN 47904
Phone (317) 742-6802

For more information, Circle No 109

"AIR POLLUTION ATTACKS US ALL"

AMERICAN LUNG ASSOCIATION
The "Christmas Seal" People
GPO Box 596, NY, NY 10001

Space contributed by the publisher as a public service

Sales Offices

H Victor Drumm

Executive Vice President
and Publisher
Boston, MA 02116
(617) 536-7780

NEW YORK CITY 10017

Bill Segallis, Regional Manager
205 E 42nd St
(212) 949-4423

BOSTON 02116

Richard Parker, Regional Manager
Hal Short, Regional Manager
221 Columbus Ave
(617) 536-7780

PHILADELPHIA 19087

Steve Farkas, Regional Manager
999 Old Eagle School Rd
Wayne, PA 19087
(215) 293-1212

CHICAGO 60521

Clayton Ryder, Regional Manager
Charles Durham, Jr
Regional Manager
15 Spinning Wheel Rd
Hinsdale, IL 60521
(312) 654-2390

CLEVELAND 44115

Charles Durham, Jr
Regional Manager
1621 Euclid Ave
(216) 696-1800

DENVER 80206

John Huff, Regional Manager
270 St Paul St
(303) 388-4511

SAN FRANCISCO 95008

Hugh R Roome, Vice President,
Northwest Regional Manager
Pruneyard Towers
1901 S Bascom St, Suite 1100
Campbell, CA 95008
(408) 377-6777

LOS ANGELES 90036

Ed Schrader, Regional Manager
Charles J Stillman, Jr
Regional Manager
5670 Wilshire Blvd
(213) 933-9525

TOKYO 106 JAPAN

Tomoyuki Inatsuki
TRADE MEDIA JAPAN INC
R212, Azabu Heights
1-5-10 Roppongi, Minato-ku
Tel: (03) 585-0581
Telex: J28208 MEDIAHS

CAREER OPPORTUNITIES

Eastern US

Nancy Muenchinger
221 Columbus Ave, Boston,
MA 02116 (617) 536-7780

Western US

Diane Smith
5670 Wilshire Blvd
Los Angeles, CA 90036
(213) 933-9525

ADVANCED 6800 SOFTWARE

CP/68™ OPERATING SYSTEM

- PIP Peripheral Interchange Program Transfers Data Between Physical Devices
- Wildcard Filenames and Extensions
- Relocatable Anywhere in Memory
- Extended Instruction Set Includes 6809-type Instructions (PSHX, PULX, etc)
- Complete Device-Independent I/O
- Random and Sequential Files
- Fits in Less Than 8k
- Chaining and Overlaying
- Single Supervisor Call Furnishes All DOS Services
- Easily Interfaced to New Devices and Peripherals
- Dynamic File Allocation

STRUCTURED BASIC Language (STRUBAL +™) COMPILER for both business and science uses

- Variable Precision From 4 to 14 Digits
- Structured Programming Forms
- Produces Relocatable and Linkable Code
- COMMON and DUMMY Sections
- Extensibility
- String Handling
- Full Scientific Package
- Data Structures with Mixed Data Types

LNKEDT68™ LINKAGE EDITOR

- Links and Relocated Files Produced by STRUBAL + or RA6800ML Macro Assembler
- Two-Pass Disk-to-Disk
- Libraries of Relocatable Files Can be Searched
- Extensive Listing Outputs

XREF68™

- Produces a Cross-Reference Listing of the XREF File Produced by STRUBAL + or RA6800ML Macro Assembler
- Alphabetic Listing of Every Symbol in a Source Program Followed by the Line Number of Every Reference

RA6800MLD™ MACRO LINKING ASSEMBLER

- Full Macro Facilities
- COMMON Section for the Production of ROMable Code
- Conditional Assembly
- Generates Linkable and Relocatable Code
- Sorted Symbol Table Listing
- Hash-coded Symbol Table for Speed

EDIT68™ TEXT EDITOR

- Change, Delete, Replace Text Globally
- Powerful Macro Facilities
- Supports Horizontal Tabs
- Disk-to-disk Edit Accommodates File of any Length
- Find a Character or Character String
- Block Moves of a Line or Lines

Versions are available for Percom, ICOM, MSI, Smoke Signal and SWTPC systems.

HEMENWAY ASSOCIATES, INC.

101 Tremont St., Suite 208
Boston, MA 02108
(617) 426-1931


For more information, Circle No 110

56 ways to break an old habit.

You need enclosures. You go to a fabricator across town. They'll make some metal "boxes". You may have to guide them. You may get sporadic delivery and maybe their "boxes" are sometimes off the mark in size, color, quality. But you live with it because you've always done it that way.

There's a better way. Bud. Bud standard enclosures: small, medium, large; 56 styles, 326 sizes. The broadest line of standard enclosures in the industry. Available from any one of 325 stocking distributors.

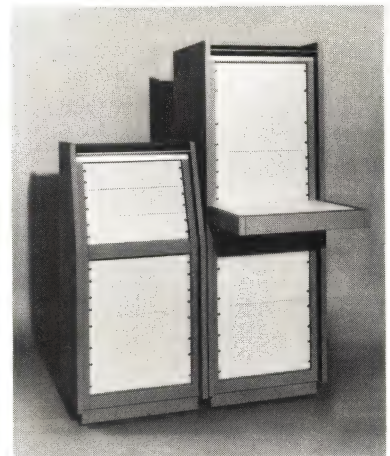We're the industry's largest. Why? The people we deal with realize the value of a dollar. The value they get from Bud. Get our catalog and with it, a choice for a change. Bud Industries, Inc., 4605 E. 355th St., Willoughby, Ohio 44094. Phone: 216/946-3200. Bud West, Inc., 3838 N. 36th Ave., Phoenix, Arizona 85019. Phone: 602/269-3151.



Our racks come in eight designs, 81 sizes, 19 colors. Shipped fully assembled. And they're in stock.

Value. **BUD**

For more information, Circle No 103

EDN CAREER OPPORTUNITIES

To place an advertisement in this section contact:

BOSTON

Nancy Muenchinger
(617) 536-7780
Telecopier: (617) 536-7780 Ext. 282

LOS ANGELES

Diane Smith
(213) 933-9525

The Optimum System Approach.

It's the concept that we base our engineering on at the Space Information Systems Operation...a dynamic approach to design that allows us to build in specific capabilities and maximize flexibility and cost efficiency. Within the Space Information Systems Operation we have all the necessary resources to build and deliver an optimum system. We can provide requirements analyses, system design and engineering, hardware and software design and development, manufacturing, procurement, logistics support, system maintenance, system operation, maintenance and user documentation, and programmer, operator and analyst training.

We have this same attitude toward our employees, giving them maximum responsibilities across the entire development cycle, in a growth oriented environment. Additionally, we offer highly competitive salaries, outstanding benefits, and an uncongested working community...the optimum employment opportunity. What's more, Texas does not have a state income tax. Our current openings are for experienced Digital and Analog Design engineers and Minicomputer Systems engineers. For more information CALL COLLECT or send a resume to: John Brown, Space Information Systems Operation, P.O. Box 58487, Houston, Texas 77058, (713) 488-1270.

We are an equal opportunity employer, m/f.



Ford Aerospace & Communications Corporation

WHAT HAPPENED TO YOUR LAST BIG IDEA?


SOFTWARE ENGINEERS

Was it lost? Stolen? Or simply stifled?

If you want your ideas to get beyond the idea stage, come to GenRad. Because we use all the big ideas we can get—from applications software to systems development to microcode. In fact, thinking big is what's made us number one in the automatic test equipment industry.


And maybe your ideas can help keep us there.

To discuss the job, salary, and benefits, call Norm Schwartz, collect, at (617) 369-4400, Ext. 329, between 9:00 am and 4:00 pm EST. Or write GenRad, Dept. 29, Concord, MA 01742.

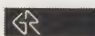 **GenRad**

Put our leadership to the test.

An equal opportunity employer M/F.

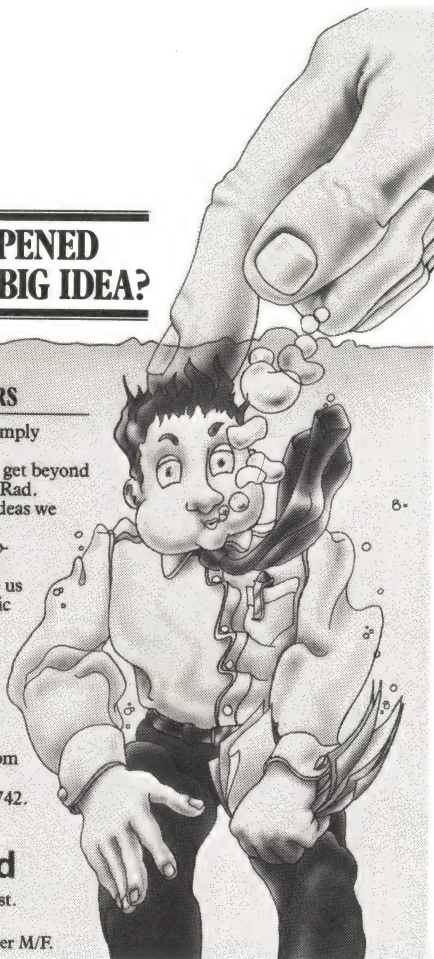

THE BEST & THE BRIGHTEST ENGINEERS SCIENTISTS

\$18-35K


The best and the brightest choose P'nB to market them to the best and the brightest companies in the United States, — Because I'm an engineer who talks your language.

I know what you want—I was there myself for 25 years as a design specialist, systems engineer, project manager, operations researcher, program manager. I am an engineer out of M.I.T. many years ago. It was lots of fun and worth every minute of it. So let me find you what you really want. For starters...

Just send your resume or write me about yourself. I'll be in touch with you about unadvertised positions for degreed engineers, computer scientists, physicists in the Electronics, Computer and Aerospace Industries.

YOU are our client, but the companies pay all fees and expenses. Please include present salary.

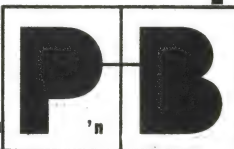Monarch L. Cutler, Chief Executive
P 'n B CONSULTANTS
Box 494-7, Wayne, Pa. 19087
(215) 687-4056



Your Career Path Leads To Honeywell-Phoenix

Located in the heart of Arizona, not only will you have the opportunity to join the staff of a company that is the nucleus of tomorrow's computer technology, but you will also have the chance to live in an area that has everything to offer in recreational facilities

with perfect weather in which to enjoy them.

Therefore, the people we're looking for must be familiar with today's processes and still be innovative enough to develop tomorrow's systems.

Hardware positions are currently available in the following areas:

- Systems Availability Engineering
- Large Scale Computer Systems Design and Testing
- Micropackaging Engineering — Thin Film or Thick Film Hybrid
- Large Scale CPU and I/O Logic — Digital Design
- Process Control Engineering
- Sr. Diagnostic Engineers Conversant with Fault Simulation Techniques
- Distributed Processing and Networking
- Computer Systems Performance Analysis
- LSI Bipolar Circuit Chips Design and Development
- Computer Hardware & System Qualification Engineering

The roads lead in many directions in today's world. If you're ready to take one that will be the most beneficial to you, send your resume with salary requirements in complete confidence to:

HONEYWELL LARGE INFORMATION SYSTEMS
Manager, Recruitment & Placement
P.O. Box 6000
Mail Station Y12
Phoenix, AZ 85005



Honeywell

A Equal Opportunity Employer M/F/H

NORTHROP

engineers

challenge... research... discovery... ...it's the world of ECM

It's our world here at Northrop Defense Systems Division. And it's a world to which you should aspire.

If you're intrigued and inspired by the new, the innovative, the state-of-the-art...you'll want to know that we at Northrop have committed ourselves to these ideals for the past twenty-five years. They've led us to our position as a renowned leader in the research, design and manufacture of sophisticated electronic countermeasure (ECM) systems.

By maintaining an environment that encourages creative freedom, coupled with our consistent procurement of long-term contracts and outstanding financial compensation - we've succeeded in building one of the finest engineering teams in the world.

But we need YOU. If you're trained and experienced in one of the following areas, investigate the potential at Northrop:

ENGINEERS

PRODUCT DESIGN SOFTWARE

Senior Engineers
Project Engineers
Engineers

Engineers
Analysts
Programmers

AUTOMATIC TEST ENGINEERS

Digital Test
Analog Test

RF (Microwave Test)

PRODUCT
ASSURANCE
Reliability
Maintainability

SYSTEMS
Senior Engineers
Project Engineers
Engineers

We offer outstanding compensation packages including complete benefits, unlimited growth potential and the opportunity to combine the career of a lifetime with off-hours enjoyment in Chicago, one of the most exciting, culturally alive and highly liveable areas in the nation. For further information, please forward your resume stating salary history and requirements, in confidence, to:

Employment Manager, Dept EDN479
NORTHROP CORPORATION
Defense Systems Division
600 Hicks Rd., Rolling Meadows, IL 60008
an equal opportunity employer m/f



ENGINEERS—Mini-Computers, Microprocessors, Analog & Digital, RF, Communications or Microwaves. Wash., D.C. area. Sal. to \$34,000. Replies kept confidential. Feed Pd. Agcy. Contact:

D. Jones
TECH-PROF EMPL. (Estab. 1967)
3610 Milford Mill Rd.
Baltimore, Md. 21207

Fresh!

The openings you'll see in our Career Opportunities section were alive and waiting just 5 days before we mailed to you! A fresh look at who's expanding, growing, looking for electronic design engineers and managers. You couldn't pick a better spot to look. Exclusively yours. EDN.

EDN



We put the future in your hands when you become a TI design engineer.

Electronic engineers come to TI to get in on the future of technology. They stay because they find a future for themselves.

You don't start at ground-zero when you join TI, because everyone works on equal footing. Of course, there are differences in rank and responsibility. But everyone is on a first-name basis, right up to the president of the company.

So, if you have a good idea your first week on the job, you speak your mind. And you get heard. Or, if you need to ask your department head some questions, you ask. And you get answers.

There's nothing to slow down your initiative at TI. We've got a

move-up environment that lets you prove how good you are fast. Everybody is evaluated regularly. And if you're good, you advance. No matter how new you are.

TI has developed a solid reputation for technological leadership through work in more than 15 major fields of science and engineering. So you'll have an infinite variety of mind-broadening projects to work on. And grow with.

And because TI is headquartered in Dallas, you'll work in one of the most progressive cities in the nation. You'll have a sunny, relaxed lifestyle at a cost way below the national urban average, with no state or city income tax whatsoever.

Right now, we are looking for some free thinking design engineers that have experience designing automatic semiconductor test systems and real time microcomputer-based machine control systems.

- Circuit designer (Analog & Digital)
- S/C test system designer
- Equipment controls designer
- Software specialist
- Test system application specialist
- Computer system designer

Contact Bill Rigsby
Staffing Manager
Dept. D2
Box 225012, M.S. 11
Dallas, Texas 75265



TEXAS INSTRUMENTS
INCORPORATED

An Equal Opportunity Employer

ENGINEERS...

... MAKE IT
HAPPEN
AT
LITTON
DATA
SYSTEMS

NOW more than ever before we're involved with the kind of technology that will interest even the most challenged engineer. Add this to the Southern California climate and lifestyle and you've got Litton Data Systems, a highly respected leader in Communications, Displays, Command and Control Systems, Radar Signal Processing and Software.

Current openings NOW include:

COMMUNICATIONS SYSTEMS
AND DESIGN ENGINEERS
AIR DEFENSE SYSTEM ENGINEERS
RADAR SIGNAL PROCESSING ENGINEERS
MECHANICAL ENGINEER & DESIGNERS
ANALOG DESIGN ENGINEERS
POWER SUPPLY ENGINEERS
SR. DISPLAY SYSTEMS ENGINEER
DISPLAY CIRCUIT DESIGNER
LOGIC/FIRMWARE DESIGNERS
MEMORY DESIGN ENGINEERS
AIRCRAFT TRACKING SPECIALISTS

Make it happen NOW! Call or send resume to:

Tom Bradford
Professional Employment
8000 Woodley Ave., (43-01)
Van Nuys, CA 91409



Litton

DATA SYSTEMS

Equal Opportunity/Affirmative Action Employer

Advertisers Index

Airpax/Cheshire Div	95	Mostek	8-9, 45, 96-97, 98
Allen-Bradley Co	47	Motorola	123
AMP Incorporated	18A, 50A	Mueller Electric	92
Ampex MPD	139	National Semiconductor Corp	10-11
AVX	84-85	Newark Electronics	115
Beckman Instruments Inc	30	Northern Engineering Labs	77
Berg Electronics	14-15	OK Machine & Tool	144
Bud Industries	151, 153, 155	Oliver Applied Engineering	141
Burr-Brown Research Corp	126-127	Philips Test & Measuring Instruments Inc	148
Computer Automation-NMD	70	Phillips Chemical Co	118
CPT Corp	152	Phoenix Data Inc	154
Deltron Inc	108	Piezo Technology Inc	32
Dialight, a North American Philips Co	83	Pioneer Magnetics Inc	C3
Dranetz Engineering Labs	124	Polymer Corp	28-29
Dynamic Sciences	35	Powercon Conference & Seminars	26-27
EDN	34, 143	Powercube Corp	17
EDN Product Showcase	130	Power/Mate Corp	75
Electrocube	114A, 115	Precision Extrusions Inc	153
Elfab	125	Process Computer Systems Inc	91
Exar Integrated Systems Inc	133	RCA Solid State Div	C4
E-Z Hook	151	Reeves-Hoffman	150
John Fluke Mfg Co Inc	19, 60, 146	Relational Memory Systems	140
Forth Inc	113	Republic Electronics	94
Frequency Devices	59	SD Systems Inc	4
Futuredata Computer Corp	61	Security Research Laboratories Inc	16
Garry Manufacturing Co	49	Siemens Corp	145, 147, 149
GenRad Inc	20-21	Signetics Corp	53
Gould Inc/Electronic Components Div	36	Sinclair Radionics	76
Guardian Electric Mfg Co	117	Solid State Scientific	134
Harris Semiconductor	43	Sprague Electric Co	109
Hemenway Associates Inc	155	Standard Microsystems	131
Hollingsworth Solderless Terminals	C2	Tektronix Inc	12-13, 69, 128
Hulltronics	32	Teledyne Relays	120
Hycom Inc	32	Texas Instruments Inc	136-137
Hybrid Systems	33	Triple-I Inc	142
Instrument Rental	82A	TRW/IRC Resistors	54-55
Intel Corp	6-7, 24	United Chemicon	110
International Crystal Mfg Co Inc	18	Unitrode Corp	154
Kepco Inc	107	US Instrumental Rentals	82A
Lambda Electronics Corp	146A	Wintek	154
Leasametric	135	Zilog Inc	86
Lectronix Inc	18		
Litronix	22-23		
Matrox Electronic Systems	50		
Mepco Electra	56		
Micro Communications Corp	122		
Mid-Continent Communications Co	154		
Mini-Circuits Laboratory	3, 41		

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

Crossed signals

Dear Editor:

As a busy EE, although I find EDN invaluable, I do not have the time to read it all the way through. Therefore, it would be a great service to your readers if you would supply them with special glasses that would make the essential points stand out in red, the medium-interest passages appear yellow and the non-essential lines disappear altogether.

Sincerely,
J R Vague
JRV Associates
Blue Forks, MI

Organic memory is a slice of life

HAL Corp has announced that scientists at its de'Hormel research facility in Paramus, NJ, have succeeded in storing up to 40 bytes of unformatted data on a single 5-1/4-in. slice of bologna. Dubbed a "really-floppy disc" by its developer, Dr Otto Oikenheimer, the pork platter attains its outrageous storage capacity by whirling around and around and around at 33-1/3 rpm until little grease specs fly off. Each spec represents one bit of digital data.

The port sports a 4-port EIE I/O bus on rye. Mustard is optional; kosher versions will soon be announced.—**BP**


TWD International's part premiers

In a bold move sure to send shock waves through the electronics industry, TWD International has an-

nounced its fourth significant revolutionary breakthrough of the year—the Termodigitrator (Mark I).

Industry sources say the new component is bigger than a breadbox, faster than a speeding bullet, the key to peace in our time and the potential savior of all life as we know it on earth.

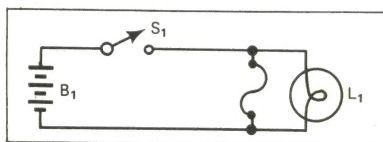TWD International (formerly Teeny Weeny Devices Inc) is a 7-yr-old firm specializing in the manufacture of high-noise op amps, lenient voltage regulators and 10%-tolerance timer chips.—**JB**



Fuse tester for all seasons

Need a simple, portable fuse tester that doesn't require extensive operator training? The one shown provides a complete test—if the light comes on, the fuse is bad. The circuit suits all types of fuses, both metric and English; color-coded units work with it, too.—**ET**

To Vote For This Design

Circle No 6-7/8

Check out this disposable μ P

Model 80808080 sports many features that make it suitable for no applications whatsoever. Fabricated with ECSST (English-Channel silicone semiconscious technology) water gates, the device implements systems which would have cost \$40G, filled Grand Central Station

and consumed all the power it took to run North America just 20 yrs ago. To permit the ruggedized, glass-passivated chip to handle power in the kilowatt region, a RIP (rarely in-line package) contains space for seven standard MIL-TFD-41S ice cubes. For specialized applications, an output-fuss-free RIP leadless package permits greater packing density (Model 80808080 RIP-OFF). Chip versions are also available. Price: High. Delivery: How long can you tread water? National Texsil Interolachild Hemiconductor Inc, 2¹⁶⁻¹ E Rte 2⁸⁻¹, Revlon-on-Avon, Taxachusetts 31415.—**DR**


Circle No π

When you hate to remember

This versatile, super-volatile Model 20/140 random-access forgetter (RAF) enables you to forget the things you wish you never knew (and goes OFF even when the lights stay ON). The names of friends you wish you never had, the time of appointments you never wanted to keep and the sum of the tax bill you never intended to run up, once entered into this device, disappear forever. With an infinite access time and infinite capacity, the unit comes in special expanded-capability Presidential (-PFIB), Senatorial (-SFIB) and Special Advisor (-SAFIB) Models for testimony before congressional committees. **Anacreon Memory Co**, 1023 Morpheus St, Last Chance, SN.—**JV**

Circle No 3.3333

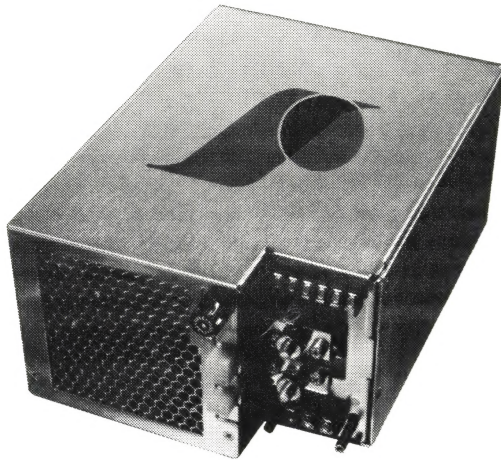For 21 years we've quietly built Switchers.



Now it's time to let the World in on it.

Back in 1958, Pioneer Magnetics built its first switching power supply. We've been quietly pioneering the design of switching supplies ever since.

Today we offer the system designer a complete family of standard models providing output voltages ranging from 2 to 48 VDC with output power to 2000 Watts. Single and multiple output configurations with a wide range of options are available.

FEATURES:

A.C. Input: 92 to 138 or 184 to 250V single phase 47 to 63 Hz.

D.C. Input: 24, 48, 120 or 240 VDC standard.

Brownoutproof: Supplies ignore most line variations and continue to supply specified regulated outputs at full load if input voltage drops as low as 80 or 140 VAC.

Total Error Band: Output deviations will not exceed $\pm 2\%$ due to line changes, static and dynamic load changes, ripple and noise spikes, temperature variations and drift.

Power Loss Holdup: Output will remain within regulation 30 msec after loss of AC input at full load and nominal line.

Safety Standards: Standard models are recognized to UL478.

SINGLE OUTPUT SUPPLIES

AC INPUT MODEL DC INPUT MODEL		PM2496A PM2721	PM2497A PM2722	PM2498B ---	PM2499 ---
OUTPUT VOLTAGE	TYPE NUMBERS (Add Amps in Blanks)		OUTPUT CURRENT	OUTPUT CURRENT	OUTPUT CURRENT
	AC MODELS	DC MODELS	CURRENT	CURRENT	CURRENT
2	20	2F	100	200	400
3	30	3F	60	100	200
5	50	5F	50	100	200
5	50	5F	60	120	---
5	50	5F	---	150	300
12	120	12F	25	60	120
15	150	15F	25	50	100
18	180	18F	22	45	90
21	210	21F	18	36	72
24	240	24F	16	33	66
28	280	28F	13	27	54
48	480	48F	8	16	32
SIZE (INCHES) (CENTIMETERS)		5x8x11 12.7x20.3x27.9	5x8x11 12.7x20.3x27.9	5x18x11 12.7x40.6x27.9	5x8x15 12.7x20.3x38.1
WEIGHT (POUNDS) (KILOGRAMS)		16 7.3	18 8.2	35 15.9	25 11.4

MULTIPLE OUTPUT SUPPLIES

AC INPUT MODEL DC INPUT MODEL		PM2675A PM2775	PM2676A PM2776	PM2677A	PM2678A			
MAX. TOTAL OUTPUT POWER IN WATTS		375W	600W	750W	850W			
MAIN CHANNEL	OUTPUT VOLTAGES AVAILABLE	2, 3, 5, 12, 15, 18, 21, 24, 28, 48						
	MAX. POWER IN WATTS	250W	500W	600W	750W			
SECOND CHANNEL	OUTPUT VOLTAGE	5	12	15	18	21	24	28
	OUTPUT CURRENT MAX. (see note 1)	7	7	7	CHECK FACTORY			
THIRD CHANNEL	OUTPUT VOLTAGE	5	12	15	18	21	24	28
	OUTPUT CURRENT MAX. (see note 1)	10	10	10	CHECK FACTORY			
FOURTH CHANNEL	OUTPUT VOLTAGE	5	12	15	18	21	24	28
	OUTPUT CURRENT MAX.	4	4	4	4	3	3	
SIZE (INCHES) (CENTIMETERS)		5 x 8 x 11 12.7 x 20.3 x 27.9 (see note 2)						
WEIGHT (POUNDS) (KILOGRAMS)		26 9						

Note 1: Higher currents available to 30 Amperes.

Note 2: Add 1 9/16" (4 cm.) for external fan on Models PM2677A, PM2678A.

For more information, Circle No 111

The Pioneers in Switching Supplies



**Pioneer
Magnetics**

Pioneer Magnetics, Inc. • 1745 Berkeley Street, Santa Monica, California 90404 • Telephone: 213/829-6751 • TWX 910-343-6249

New CMOS microprocessor kit: You get the terminal, power supply plus all this from RCA for only \$325.

Why is RCA offering such a terrific bargain?

Answer: To demonstrate the low power consumption and easy programming of our CMOS microprocessors.

For just \$325 (optional with distributors), you get everything you need to build a microprocessor evaluation system: CPU, RAM's,

ROM's, I/O's, passive components, p.c. board, hardware, even a micro-terminal. And we're throwing in the power supply free.

With the kit, you can discover how the RCA COSMAC architecture and a repertoire of 91 easy to use instructions give maximum performance with minimal memory.

You can also use the kit to learn
For more information, Circle No 113

about basic system design, hardware interfacing, and programming. Or for breadboarding and prototyping your own COSMAC Evaluation System (CDP 18S025).

For more information, contact your local RCA Solid State distributor.

Or contact RCA Solid State headquarters in Somerville, New Jersey. Brussels, Belgium. Tokyo, Japan.

